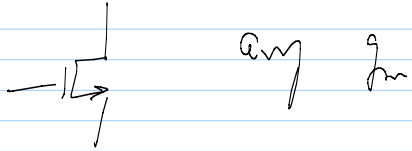




18/9/14

lec 24

Controlled sources using MOSFETs  
(Incremental)



1) VCVS

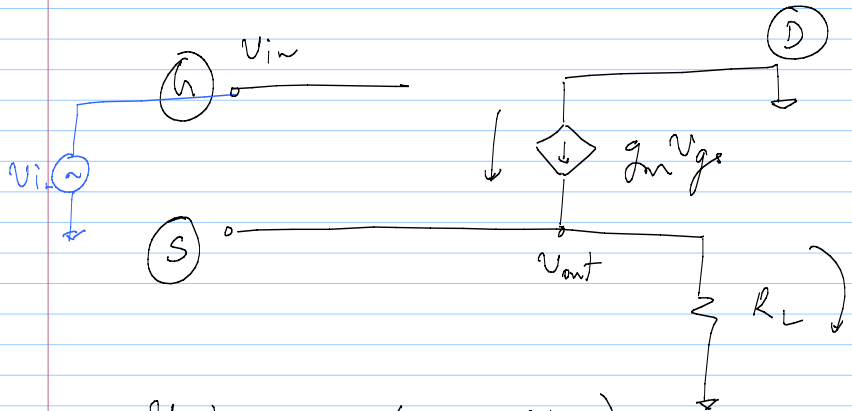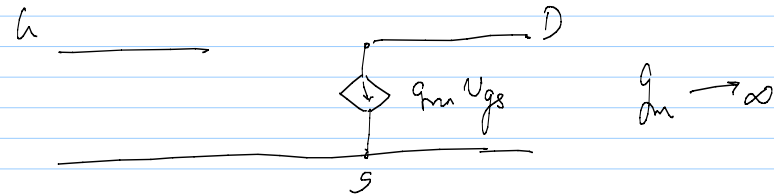


$$\frac{V_{out}}{R_L} = g_m (V_{in} - V_{out})$$


$$V_{in} \approx V_{out} \Rightarrow g_m \rightarrow \infty$$

$V_{CVS} = 1 \Rightarrow V_{out} = V_{in}; Z_{in} = \infty; Z_{out} = 0$

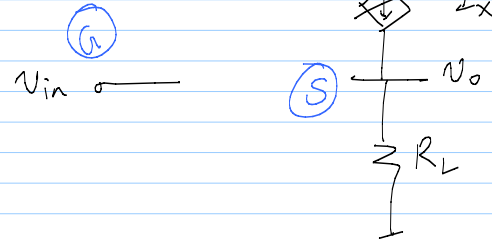- \* Measure  $V_{in}, V_{out}$
- \* change  $V_{out}$  s.t.  $V_{in} = V_{out}$
- \* vary  $I_x$  till  $V_o = V_{in}$





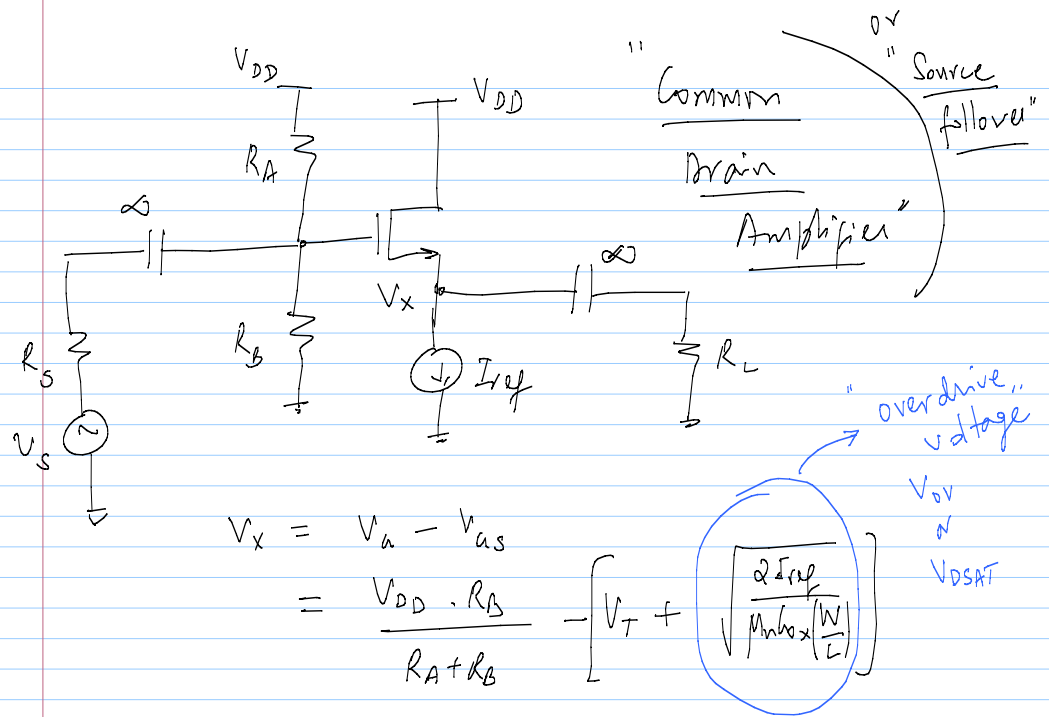- \* If  $V_{out} > V_{in} \Rightarrow \downarrow I_x$
- \* If  $V_{out} < V_{in} \Rightarrow \uparrow I_x$




$$V_x = V_a - V_{as} = \frac{V_{DD} \cdot R_B}{R_A + R_B} - \left[ V_T + \sqrt{\frac{2 I_{ref}}{\mu_n C_{ox} \left( \frac{W}{L} \right)}} \right]$$

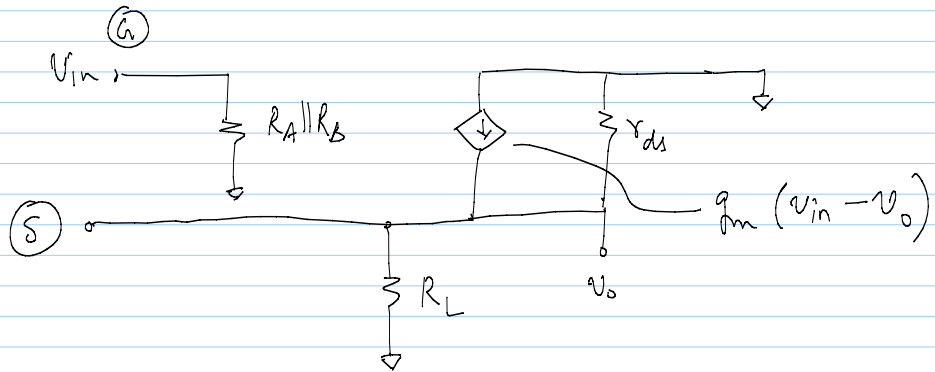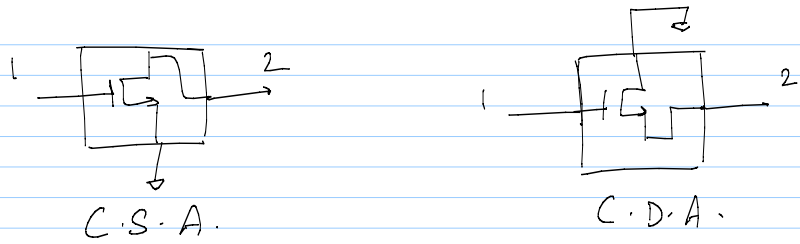"overdrive" voltage  $V_{ov} \approx V_{DSAT}$



$$Z_{in} = R_A || R_B \Rightarrow \text{choose } R_A, R_B = \text{large}$$

$$Z_{out} = ?$$

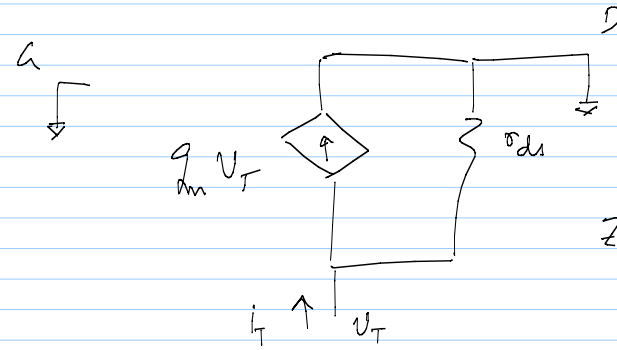


$$Z_{out} = r_{ds} || 1/g_m$$

$$= \frac{r_{ds}}{1 + g_m r_{ds}}$$

$$= \frac{1}{g_m} \frac{g_m r_{ds}}{1 + g_m r_{ds}}$$

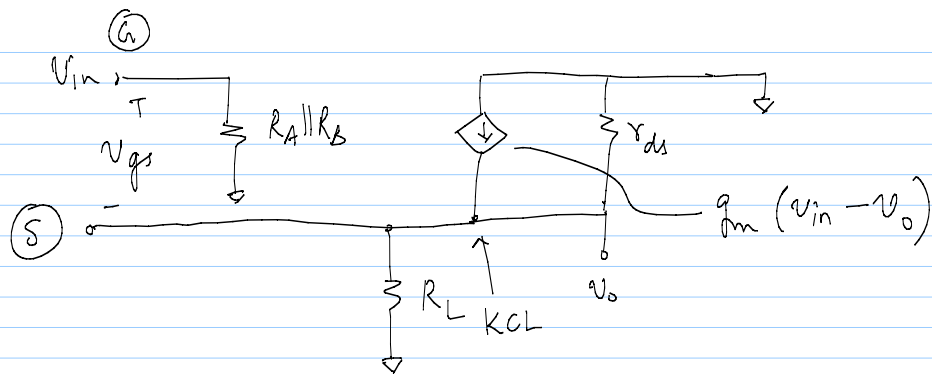
as  $g_m \rightarrow \infty$  &  $r_{ds} \rightarrow \infty$   
 $Z_{out} \rightarrow 0$



$$V_{out} [g_L + g_{ds}] = g_m V_{in} - g_m V_{out}$$

$$\frac{V_{out}}{V_{in}} = \frac{g_m}{g_m + g_{ds} + g_L} < 1$$

$= 1$  if  $g_m \rightarrow \infty$

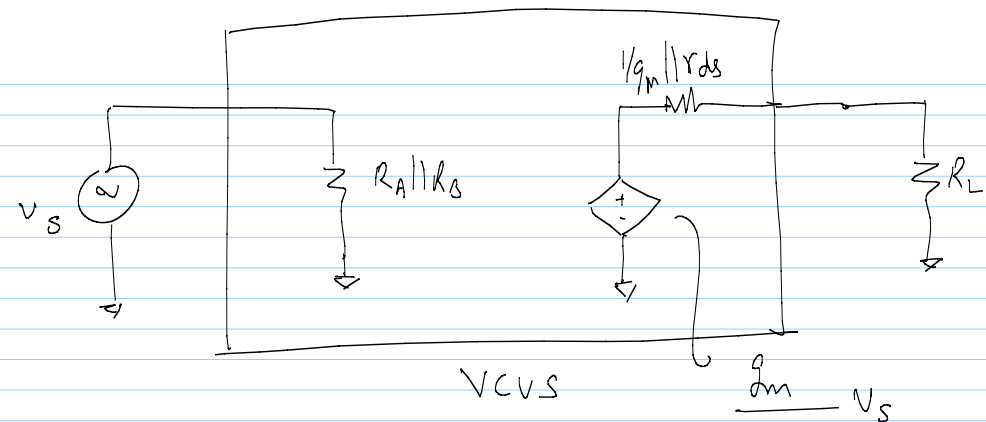

- \* Choose large  $R_A || R_B$
  - \* As  $g_m \rightarrow \infty$ ,  $g_{in} \rightarrow 1$ ;  $Z_{out} \rightarrow 0$
  - \* If  $r_{ds} = \infty$ ,  $\frac{V_o}{V_s} = \frac{g_m}{g_m + g_L} = \frac{g_m R_L}{1 + g_m R_L}$
- $\Rightarrow g_m R_L \gg 1 \approx g_m \gg \frac{1}{R_L}$