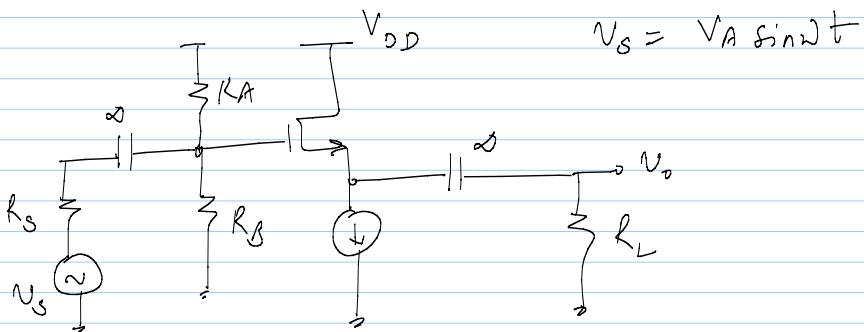


24/01/14

lec 25

Swing limits of CDA



Triode limit

$$V_D = V_u - V_T$$

$$\Rightarrow V_{DD} = V_{DD} \cdot \frac{R_B}{R_A + R_B} + V_{A_1} \sin \omega t - V_T$$

$$V_{A_1} = \boxed{\frac{V_{DD} \cdot R_A}{R_A + R_B} + V_T}$$

Cutoff limit $I_D = 0$

$$I_D = I_Q + i_d$$

$$I_Q = I_{ref}$$

$$i_d = \frac{V_o}{R_L} = \frac{g_m R_L}{1 + g_m R_L}, \quad \frac{V_{A_2} \sin \omega t}{R_L}$$


$$I_D = 0$$

$$\Rightarrow I_{ref} = \frac{g_m R_L}{1 + g_m R_L} \cdot \frac{V_{A_2}}{R_L}$$

$$V_{A_2} = I_{ref} R_L \left[1 + \frac{1}{g_m R_L} \right]$$

Incremental VCS

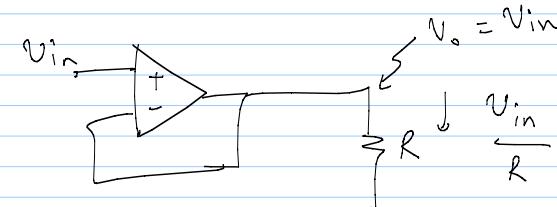
$$i_{out} = \frac{v_{in}}{R}; \quad Z_{in} = \infty; \quad Z_{out} = \infty$$



$$V_{in} \rightarrow \boxed{R} \downarrow i_{int} = \frac{g_m}{1+g_m R} \cdot V_{in}$$

$$\boxed{R} \downarrow v_o = \frac{g_m R}{1+g_m R} \cdot V_{in}$$
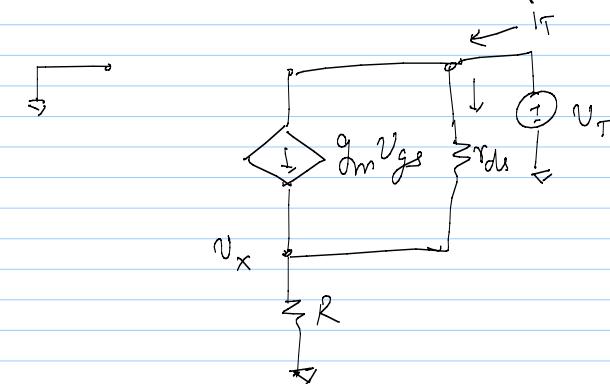
$$V_{in} \rightarrow \boxed{R} \downarrow \leftarrow Z_{out}$$



$$\frac{(V_T - V_x)}{R_{ds}} - g_m V_n = \frac{V_n}{R}$$

$$V_n = R i_T$$

$$(V_T - i_T \cdot R) g_{ds} - g_m R i_T = i_T$$


$$V_T \cdot g_{ds} = i_T [1 + g_m R + g_{ds} R]$$


$$Z_{out} = \frac{V_T}{i_T} = \frac{1 + g_m R + g_{ds} R}{g_{ds}}$$

$$= r_{ds} + (g_m r_{ds}) R + R$$

$$\approx (g_m r_{ds}) R$$

$$= r_{ds} + R (1 + g_m r_{ds})$$

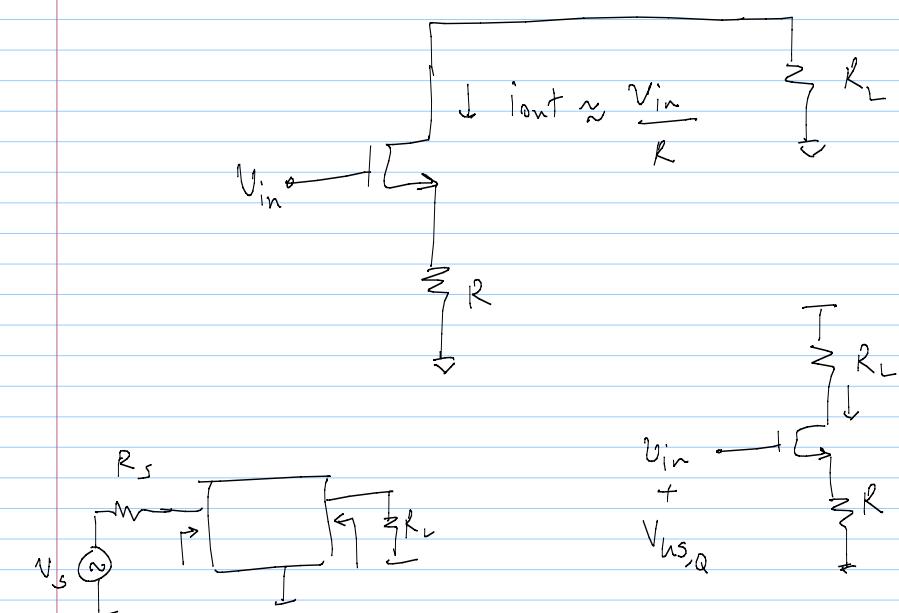

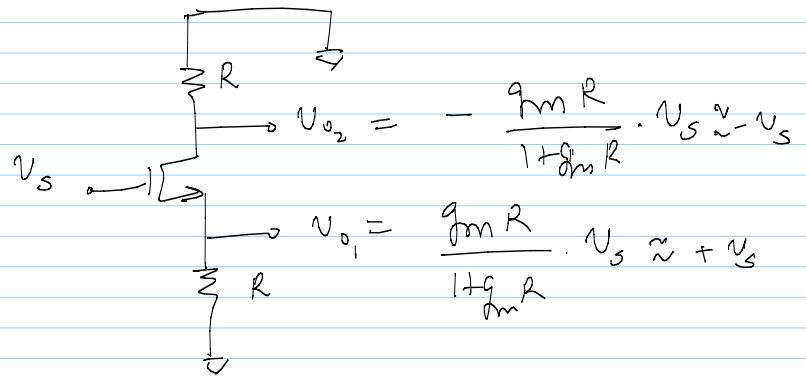

Phase Splitter Circuit