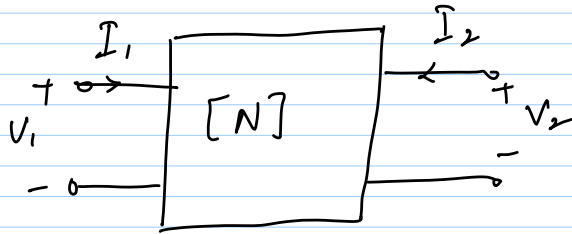


1/8/14

# lec 3

01-08-2014


- \* Review of inl ckts
- \* 2-ports w/ NL elements



$$[I] = [Y][V]$$

$$[i] = [y][v]$$
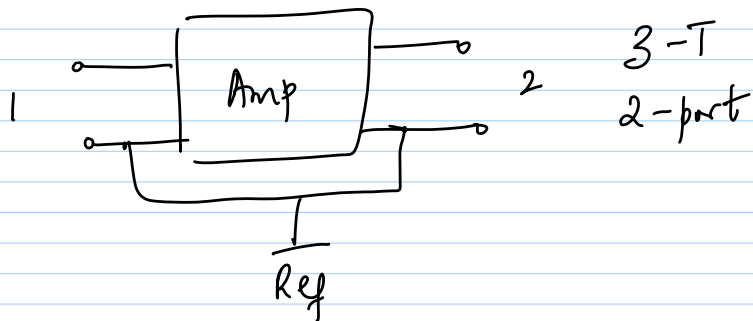
$$\begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix}$$




$$\left. \begin{aligned} I_1 &= f_1(v_1, v_2) \\ I_2 &= f_2(v_1, v_2) \end{aligned} \right\} \text{Use a 2-D Taylor Series}$$

$$I_1 + i_1 = I_1 + \frac{\partial f_1}{\partial v_1} \cdot v_1 + \frac{\partial f_1}{\partial v_2} \cdot v_2$$


$$I_2 + i_2 = I_2 + \frac{\partial f_2}{\partial v_1} \cdot v_1 + \frac{\partial f_2}{\partial v_2} \cdot v_2$$
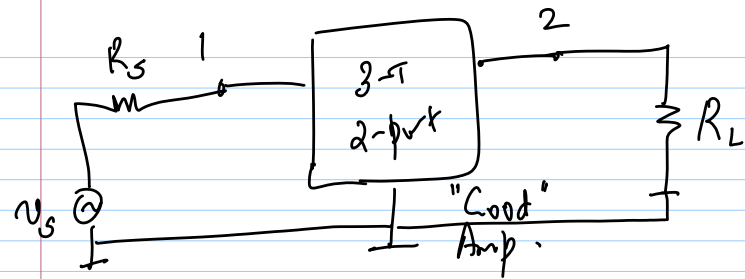
$$\begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \underbrace{\begin{bmatrix} \partial f_1 / \partial v_1 & \partial f_1 / \partial v_2 \\ \partial f_2 / \partial v_1 & \partial f_2 / \partial v_2 \end{bmatrix}} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix}$$





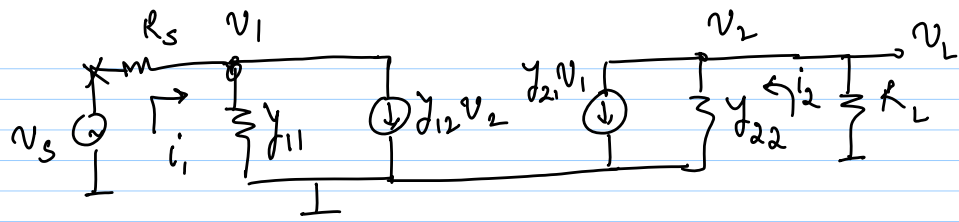- 1) Gain should not depend on  $R_s$
- 2) " " " " "  $R_L$
- 3) High gain

$$\rightarrow \text{Implications on } [y] = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix}$$



$$\frac{v_L}{v_s} = ?$$

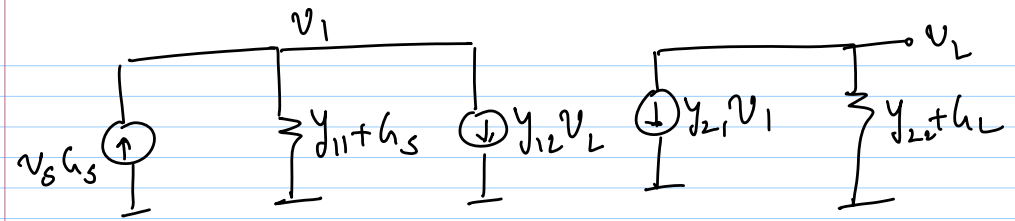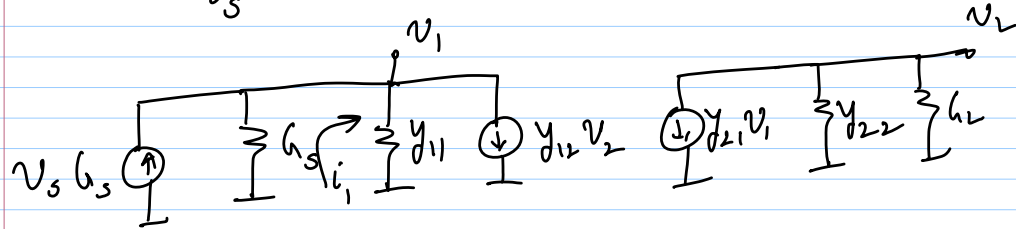

KCL @ input:

$$v_s \cdot g_s = v_1 (y_{11} + g_s) + y_{12} v_L$$

KCL @ output:

$$v_L \cdot [y_{22} + g_L] + y_{21} v_1 = 0$$

$$v_1 = \frac{v_s g_s - y_{12} v_L}{y_{11} + g_s}$$

$$\frac{v_L}{v_s} = ?$$

$$v_L [y_{22} + g_L] + \frac{y_{21} (v_s g_s - y_{12} v_L)}{y_{11} + g_s} = 0$$