


15/10/14

lec 34

I_f $V_{Tn} = V_{Tp}$

$$\frac{(W/L)_p}{(W/L)_n} = \frac{\mu_n}{\mu_p}$$

$\Rightarrow V_B = \frac{V_{DD}}{2}$

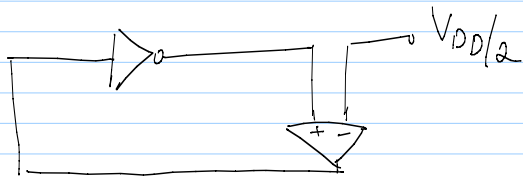

V_x

$$V_{Dp} - V_{a_p} = V_{Tp}$$


$$V_x - V_B = V_{Tp}$$

$$V_x = V_B + V_{Tp}$$




V_y


$$V_{Dn} = V_{a_n} - V_{Tn}$$

$$V_y = V_B - V_{Tn}$$

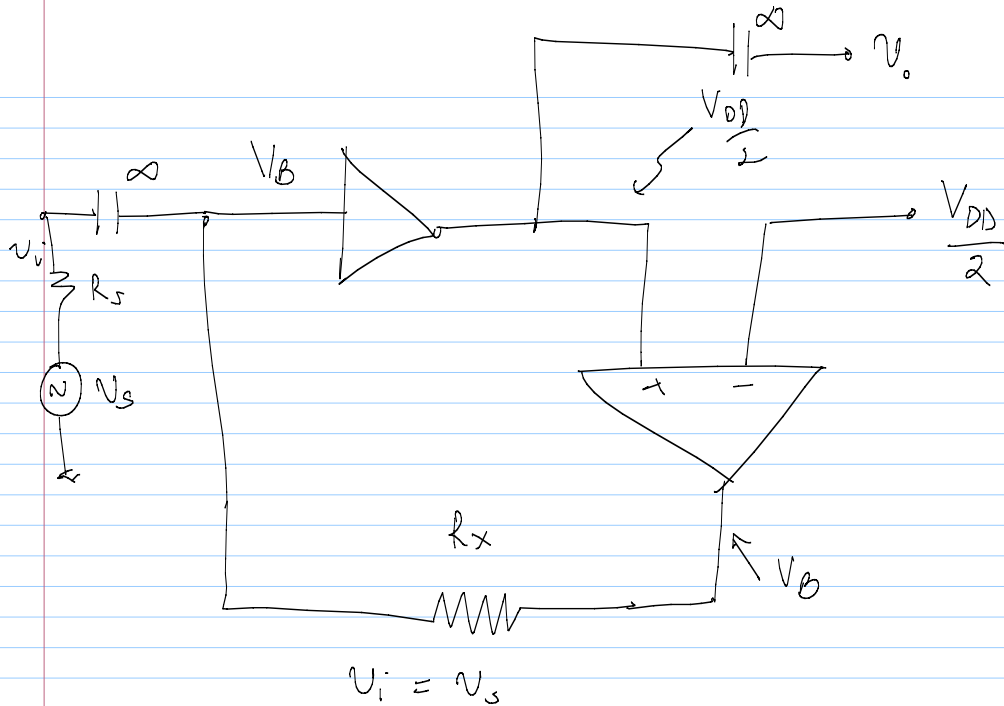

Differential Amplifiers

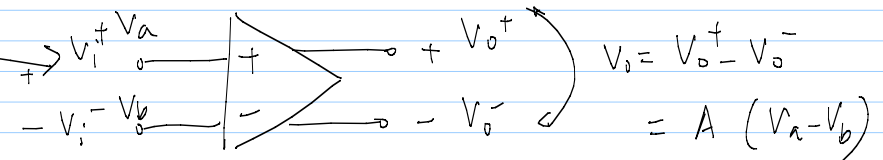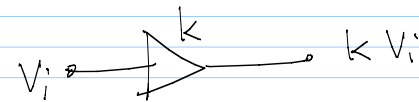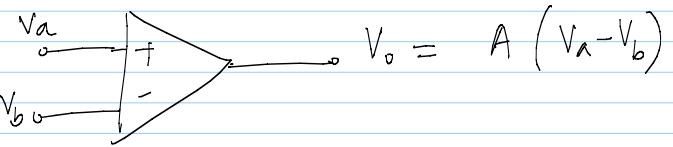

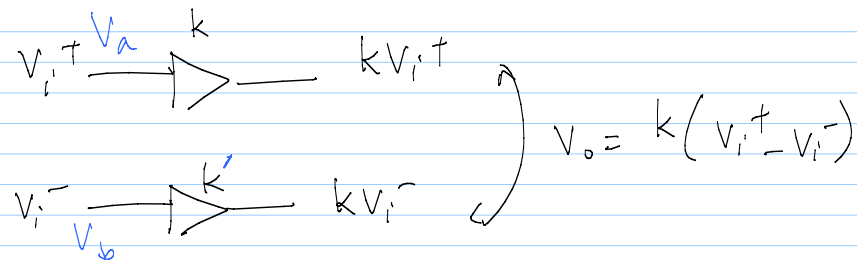

$$V_o = kV_a - k'V_b$$

$$= k(V_a - V_b) + (k - k')V_b$$

$$V_a = \frac{V_a - V_b}{2} + \frac{(V_a + V_b)}{2}$$

$$V_b = -\left[\frac{V_a - V_b}{2}\right] + \frac{(V_a + V_b)}{2}$$

$$\frac{V_a - V_b}{2} = V_{dm} \quad \text{differential mode voltage}$$

$$\frac{V_a + V_b}{2} = V_{cm} \quad \text{common-mode voltage}$$

$$V_a = V_{cm} + V_{dm}$$

$$V_b = V_{cm} - V_{dm}$$