

7/8/14



lec 6

$$I_D = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right) [V_{GS} - V_T]^2 [1 + \lambda V_{DS}]$$

* $\lambda = V^{-1} \rightarrow A/V^2$

* λ should be small
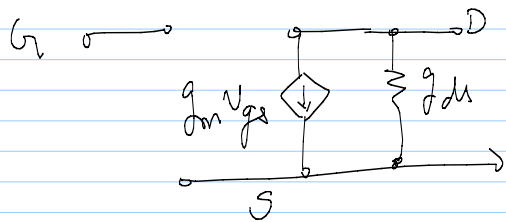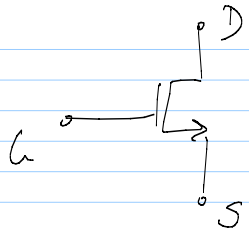
$$g_m \left(= \frac{\partial I_D}{\partial V_{GS}}\right) = \frac{\partial I_D}{\partial V_{GS}} = \mu_n C_{ox} \left(\frac{W}{L}\right) (V_{GS} - V_T) (1 + \lambda V_{DS})$$
$$\approx \mu_n C_{ox} \left(\frac{W}{L}\right) (V_{GS} - V_T)$$



Small signal equivalent ckt of MOSFET



$$y_{22} = \frac{\partial I_D}{\partial V_{DS}}$$

$$= \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right) (V_{GS} - V_T)^2 \cdot \lambda$$


$\approx I_D$

$$g_{ds} = y_{22} = \lambda I_D$$


$$r_{ds} = 1/g_{ds}$$

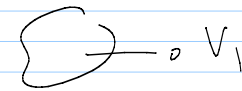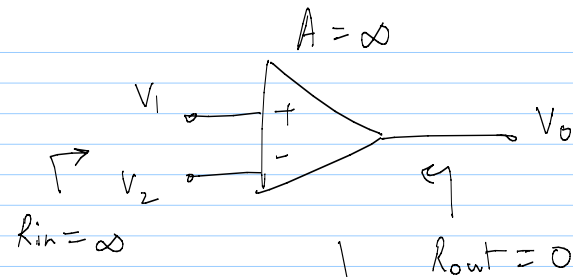

Build using MOSFETs

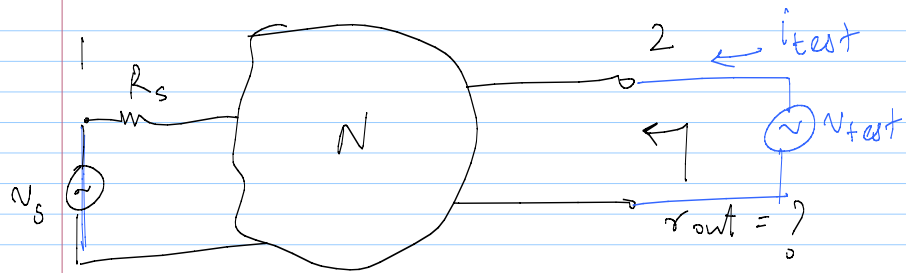

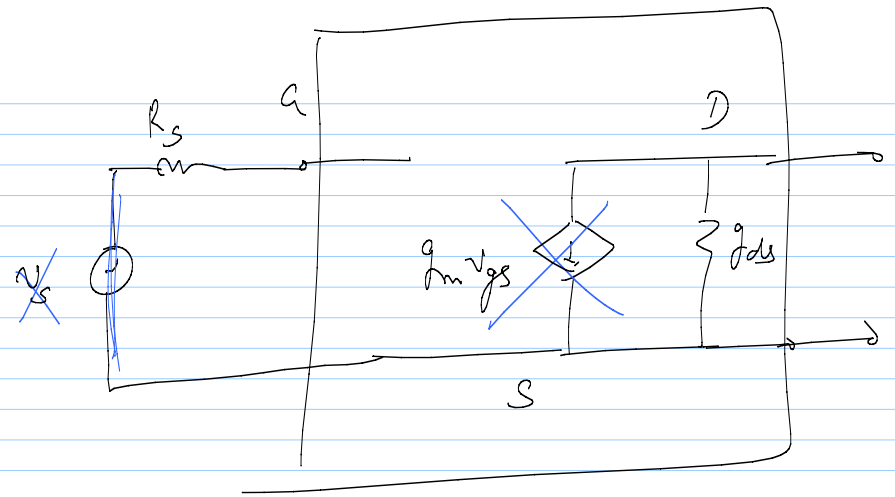- * Short V_s (indep. voltage source)
- * apply V_{test} @ port 2
- * find out i_{test} drawn from V_{test}
- * $r_{out} = \frac{V_{test}}{i_{test}}$



$$r_{out} = r_{ds} = \text{large}$$

