


Adder Inputs : A, B, C<sub>in</sub>

FA.

$$S(A, B, C_{in}) = A \oplus B \oplus C_{in}$$

$$C_{out}(A, B, C_{in}) = AB + BC_{in} + AC_{in}$$

Complementary CMOS implementation.

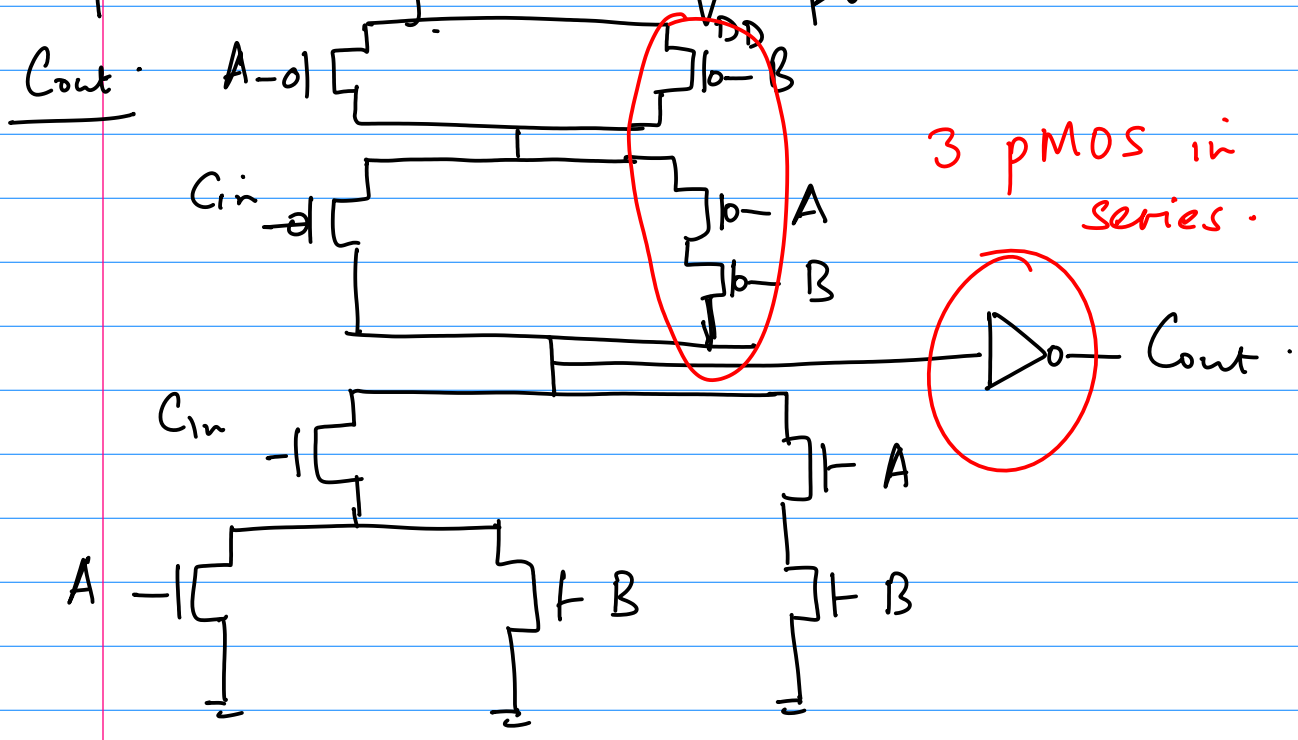

3 pMOS in series.

Sum:  $A \oplus B \oplus C_{in} = \bar{A} \bar{B} C_{in} + \dots$

$$= \Sigma(1, 2, 4, 7)$$

3 transistors in series

4 pMOS transistors in series in the PUN.

24 transistors for sum & Cout.

12     "     "     "

1. Minimise no of transistors
2. Reduce the number of PMOS transistors in series in the PUN. X

## Boolean expressions

$$S(A, B, C_{in}) = \sum(1, 2, 4, 7)$$

$$\bar{S}(A, B, C_{in}) = \sum(0, 3, 5, 6)$$


$$C_{out}(A, B, C_{in}) = \sum(3, 5, 6, 7)$$

$$\bar{C}_{out}(A, B, C_{in}) = \sum(0, 1, 2, 4)$$

$$S(A, B, C_{in}) = \bar{C}_{out}(A + B + C_{in}) + ABC_{in}$$

14 + 2 transistors:

Series transistors in PUN.

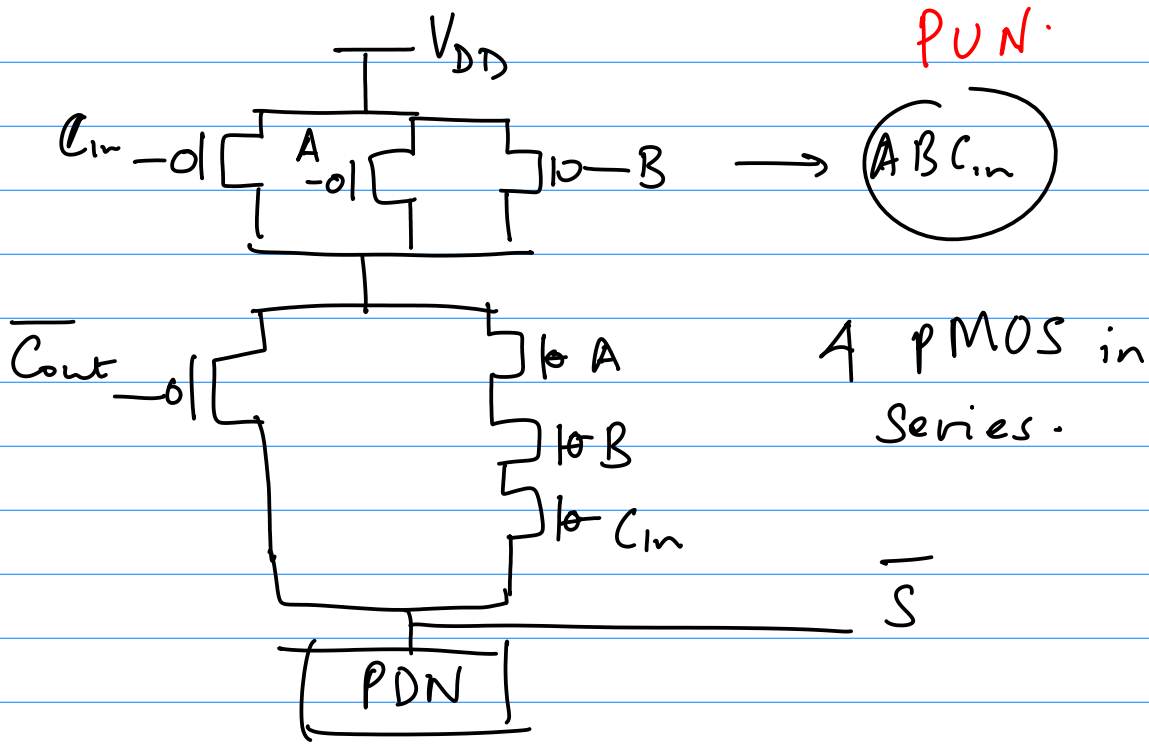

$$S(A, B, C_{in}) = \sum(1, 2, 4, 7)$$

$$\bar{S}(A, B, C_{in}) = \sum(0, 3, 5, 6)$$

$$= S(\bar{A}, \bar{B}, \bar{C}_{in})$$

$$\bar{C}_{out}(A, B, C_{in}) = C_{out}(\bar{A}, \bar{B}, \bar{C}_{in})$$

$$\overline{AB + BC_{in} + AC_{in}} = \bar{A}\bar{B} + \bar{B}\bar{C}_{in} + \bar{A}\bar{C}_{in}$$

2 input NAND ·  $F = \overline{AB} \rightarrow$  PDN  
 $= \overline{\bar{A} + \bar{B}}$  PUN

$\bar{C}_{out}$  ·  $\overline{AB + BC_{in} + AC_{in}} \rightarrow$  PDN

3 pMOS  
transistors  
in series

$$\left( \bar{A} + \bar{B} \right) \left( \bar{B} + \bar{C}_{in} \right) \left( \bar{A} + \bar{C}_{in} \right) \rightarrow$$

$$= \bar{A}\bar{B} + \bar{B}\bar{C}_{in} + \bar{A}\bar{C}_{in}$$


4  
2 pMOS transistors  
in series.

Mirror symmetric implementation.

Do the same for the Sum.

$\bar{S}$  — Do —


$\bar{C}_{out}$  — Do —  $C_{out}$

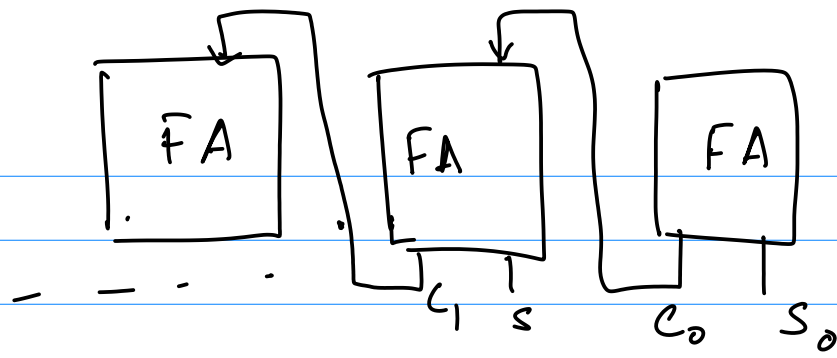

Ripple carry adder

carry path is the critical path.  
 'N' bit adder,  $t_D = (N-1)t_{carry} + t_{sum}$ .

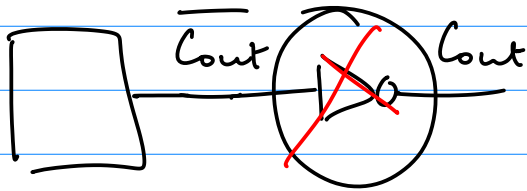Optimise carry path to  
 maximise speed.



$$S(A, B, C_{in}) = AB C_{in} + \overline{C_{out}}(A+B+C_{in})$$

$$\overline{S}(A, B, C_{in}) = \overline{A} \overline{B} \overline{C_{in}} + C_{out} (\overline{A} + \overline{B} + \overline{C_{in}})$$

$$C_{out}(A, B, C_{in}) = AB + B C_{in} + A C_{in}$$

$$\overline{C_{out}}(A, B, C_{in}) = \overline{A} \overline{B} + \overline{B} \overline{C_{in}}$$

