

## Lecture 13: Natural Frequency and Bode Plot


Lecturer: Dr. Vinita Vasudevan

Scribe: Shashank Shekhar

## Natural Frequencies

- \* No. of natural frequencies = # of independent initial conditions that can be assigned  $\equiv$  order of the circuit.
- \* can be obtained by solving for roots of the polynomial obtained by determinant of the node/mesh based network matrix.
- \*  $n$  natural frequencies  $k_1 e^{s_1 t} + k_2 e^{s_2 t} + \dots + k_n e^{s_n t}$  but it may happen that a frequency have multiplicity more than one.  
e.g.  $\frac{1}{(s+a)^2} \rightarrow k t e^{-at}$
- \* System is stable, poles in LHP/simple poles in  $j\omega$  axis; transient will die out or you get solution of form  $\cos\omega_0 t, \sin\omega_0 t, u(t)$

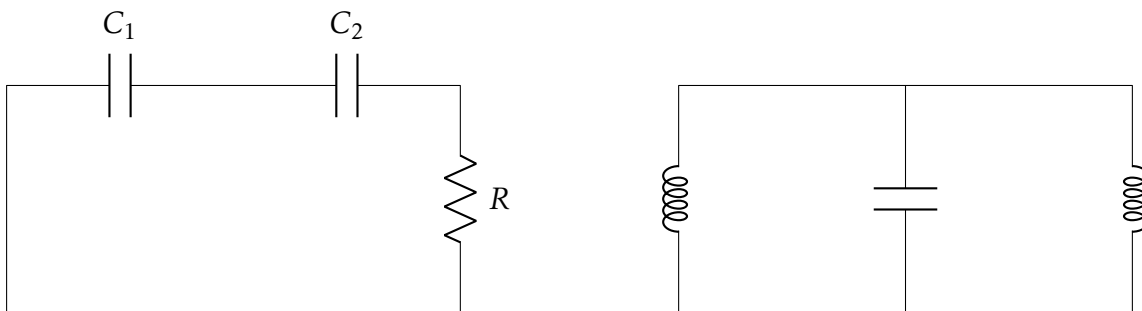
**Exercise - Find the natural frequencies of the following circuits**



**Hint:** There could be additional poles at zero.

**Laplace/Time domain analysis with loops of voltage sources and capacitors**

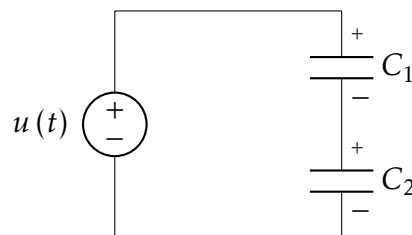**Example 1 :** Assume capacitors are initially uncharged.



To satisfy KVL, capacitors voltages must also be of the form  $Ku(t) \Rightarrow$  Impulsive current that charge both the capacitors.

In the Laplace domain,

$$I(s) \left( \frac{1}{sC_1} + \frac{1}{sC_2} \right) = \frac{1}{s}$$


$$I(s) = \frac{C_1 C_2}{C_1 + C_2} \leftrightarrow i(t) = \frac{C_1 C_2}{C_1 + C_2} \delta(t)$$

$$V_{C_1}(s) = \frac{1}{sC_1} \frac{C_1 C_2}{C_1 + C_2} = \frac{1}{s} \frac{C_2}{C_1 + C_2}$$

$$v_{C_1}(t) = \frac{C_2}{C_1 + C_2} u(t)$$

$$v_{C_2}(t) = \frac{C_1}{C_1 + C_2} u(t)$$

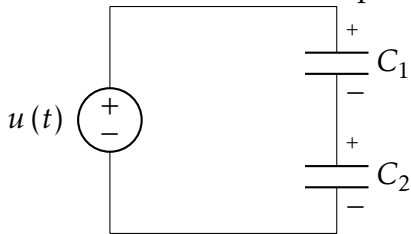We can also solve this problem in the time domain using capacitor charge equation




$$C_1 V_1 = C_2 V_2$$

$$V_1 + V_2 = 1$$
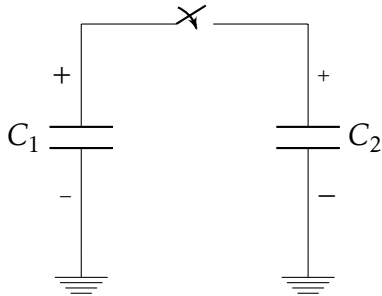
### Switch capacitor circuits

Assume initial voltage across  $C_1$  is  $V_{C_1}$  and  $C_2$  is initially uncharged. Final voltage is  $V_f$ .



when switch is closed the charge in  $C_1$  will be redistributed so that final voltage is the same.

$$\text{Initial voltage across } C_1 \text{ is } V_{C_1}(0)$$

$$Q = C_1 V_{C_1}(0) = V_f (C_1 + C_2)$$

### Bode Plots

\* circuits is stable ( $j\omega$  axis is in the ROC)

$\Rightarrow$  Given  $H(s)$ , can find  $H(j\omega)$  Plot response to  $e^{j\omega t}$  (Eigenfunction). Plot magnitude and phase response.

$$e^{j\omega t} \rightarrow \underbrace{H(j\omega)}_{|H(j\omega)| \ \& \ \angle H(j\omega)} e^{j\omega t}$$

**Example 1:**  $H(s) = 1 + s/a$

$$H(j\omega) = 1 + j\omega/a$$

$$|H(j\omega)| = \sqrt{1 + \frac{\omega^2}{a^2}}, \quad \angle H(j\omega) = \arctan(\omega/a)$$

$$H_{dB} = 20 \log_{10} |H(j\omega)| \quad \text{decibel}$$

$$= 10 \log_{10} |H(j\omega)|^2$$

$$|H(j\omega_2)| = 10 |H(j\omega_1)|$$

$$H_{1dB} - H_{2dB} = 20 \log_{10} \frac{|H(j\omega_2)|}{|H(j\omega_1)|}$$

$$= 20dB$$


$$|H(j\omega_2)| = 2|H(j\omega_1)| \Rightarrow 6dB \text{ change}$$

$$|H(j\omega)|^2 = 1 + \frac{\omega^2}{a^2}$$

$$H_{dB} = 10 \log_{10} \left( 1 + \frac{\omega^2}{a^2} \right)$$

$$H_{dB} \approx 10 \log_{10} 1 = 0 \quad \omega \ll a;$$
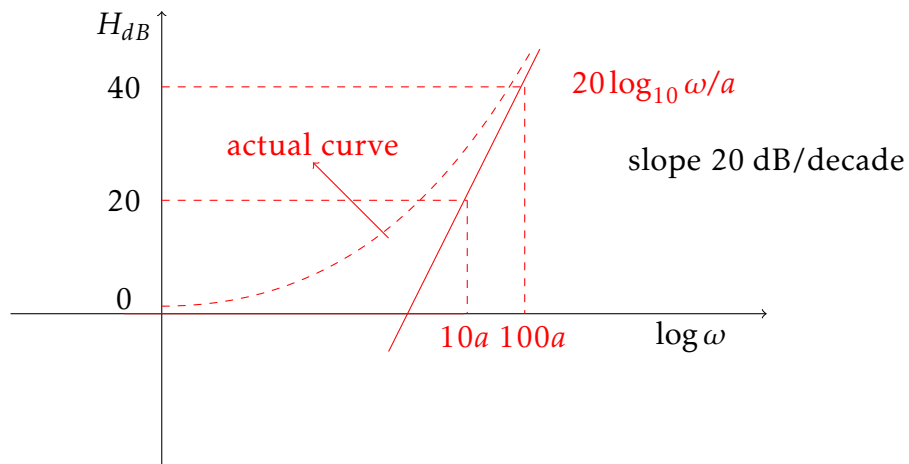
$$H_{dB} \approx 20 \log_{10} \omega/a \quad \omega \gg a$$




$$\angle H(j\omega) = \arctan(\omega/a)$$

$$\omega \ll a \quad \rightarrow \quad \angle H(j\omega) \approx 0$$

$$\omega = a \quad \rightarrow \quad \angle H(j\omega) = \pi/4$$


$$\omega \gg a \quad \rightarrow \quad \angle H(j\omega) \approx \pi/2$$

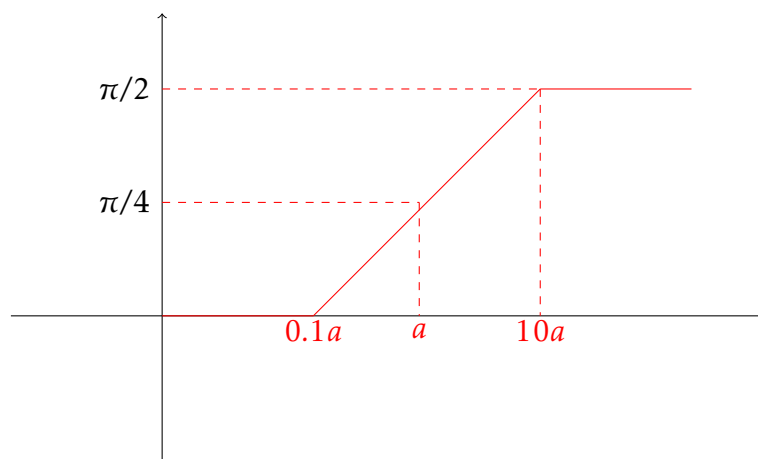

**Example 2:**  $H(s) = \frac{1}{1 + s/a}$


$$|H(j\omega)| = \frac{1}{\sqrt{1 + \frac{\omega^2}{a^2}}}, \quad \angle H(j\omega) = -\arctan(\omega/a)$$

$$H_{dB} = -10 \log_{10} \left( 1 + \frac{\omega^2}{a^2} \right)$$

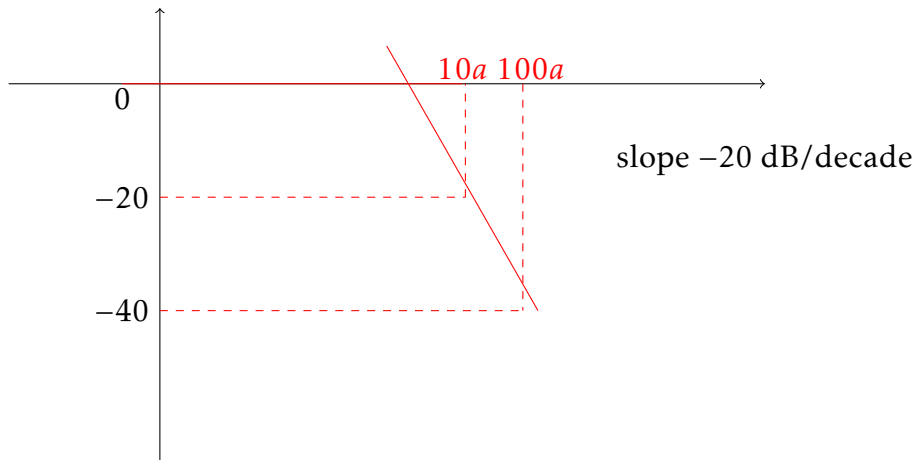

**Example 3:**  $H(s) = s$

$$|H(j\omega)| = \omega, \quad \angle H(j\omega) = \pi/2$$

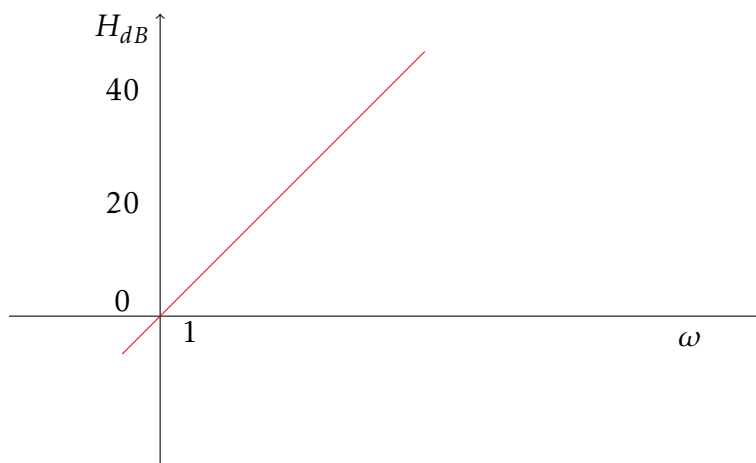

**Exercise**  $H(s) = \frac{1}{(1 + s/10)(1 + s/100)}$

$$|H(j\omega)| = \frac{1}{\sqrt{1 + \omega^2/100} \cdot \sqrt{1 + \omega^2/10^6}}$$