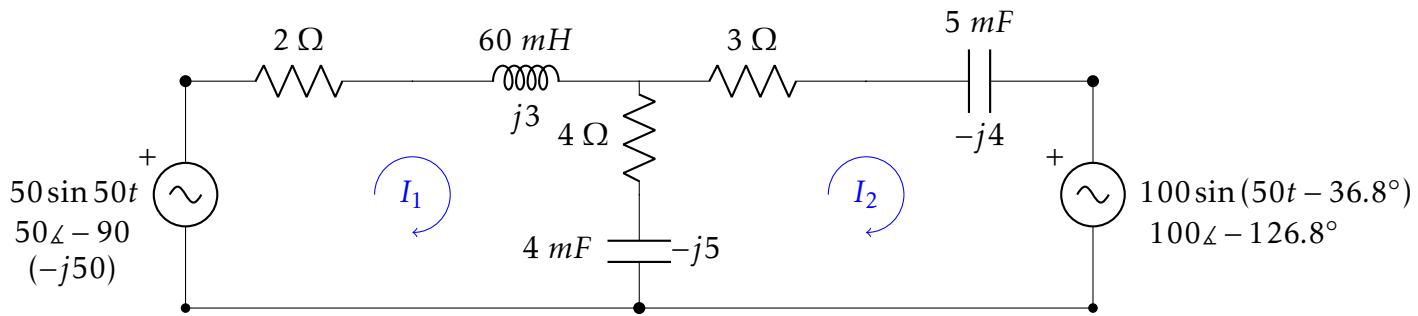


## Lecture 27: Sinusoidal Steady State (Contd...)

Lecturer: Dr. Vinita Vasudevan

Scribe: Shashank Shekhar



### Example 1 : Superposition




$$\begin{bmatrix} 6-j2 & -4+j5 \\ -4+j5 & 7-j9 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} -j50 \\ -100\angle -126.8 \end{bmatrix}$$

$$= \begin{bmatrix} -j50 \\ 0 \end{bmatrix} + \begin{bmatrix} 0 \\ -100\angle -126.8 \end{bmatrix}$$

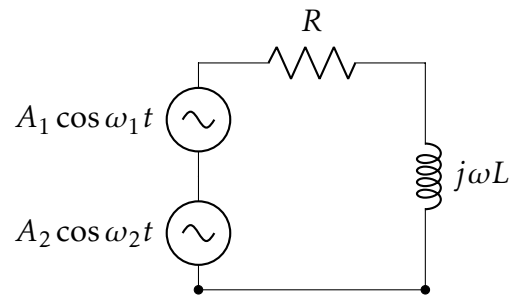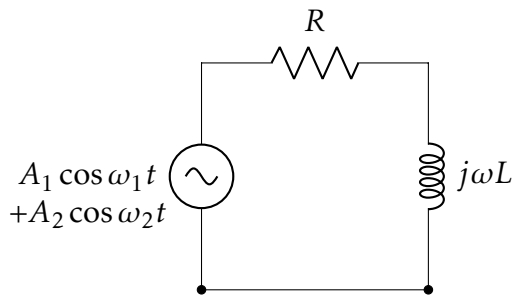
⇒ Superposition can be used to solve for the system response. Especially useful if you have sources with different frequencies.



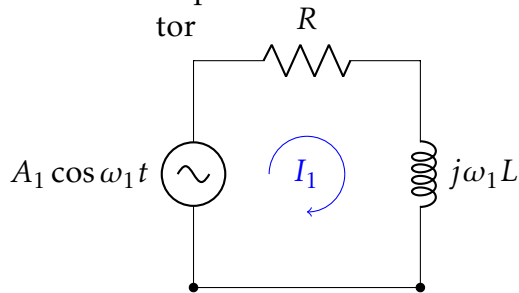Here the question is which  $\omega$  value should we use for impedance of inductor



$$I_1 = \frac{A_1}{R + j\omega_1 L}$$

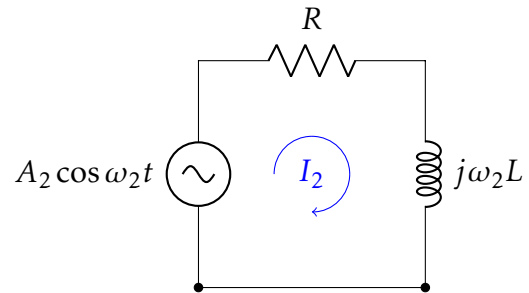

$$I_2 = \frac{A_2}{R + j\omega_2 L}$$

**Same frequency :**

$$B_1 e^{j\omega t} + B_2 e^{j\omega t} = (B_1 + B_2) e^{j\omega t}$$

Adding the two signals is the same as adding the phasors and then multiplying by  $e^{j\omega t}$

**Different frequency :**




$$B_1 e^{j\omega_1 t} + B_2 e^{j\omega_2 t} \rightarrow \text{Cannot add the phasors.}$$

Add signals in time domain after multiplying by  $e^{j\omega t}$

$$\text{Total response : } \frac{A_1}{R + j\omega_1 L} e^{j\omega_1 t} + \frac{A_2}{R + j\omega_2 L} e^{j\omega_2 t}$$

$$\text{Actual response : } \text{Re}\{I_1 e^{j\omega_1 t} + I_2 e^{j\omega_2 t}\}$$


**Periodic signal as Input**

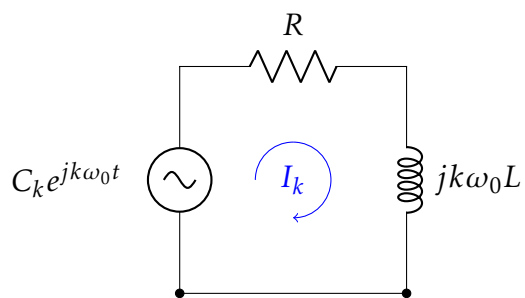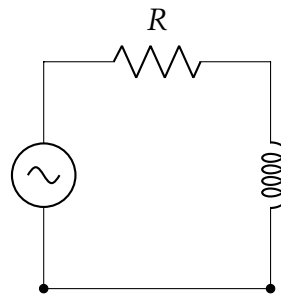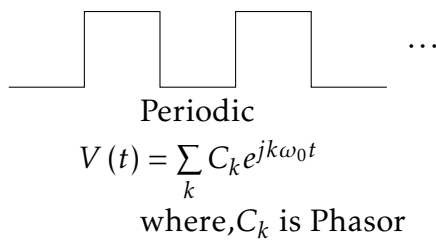


$$I_k = \frac{C_k}{R + jk\omega_0 L}$$

$$I(t) = \sum_k \frac{C_k}{R + jk\omega_0 L} e^{jk\omega_0 t}$$

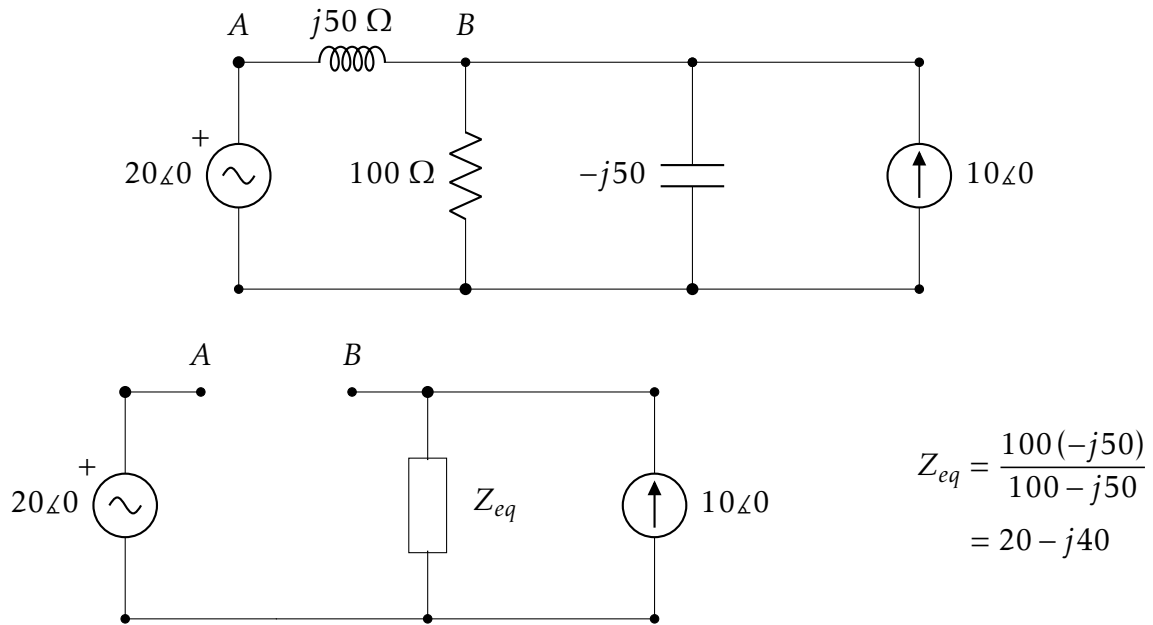**Example 2 :** Find Thevenin's equivalent circuit as seen by inductor. **Note :** Proof of Thevenin's theorem depends only on substitution and superposition theorem; both of which can be used with phasors.



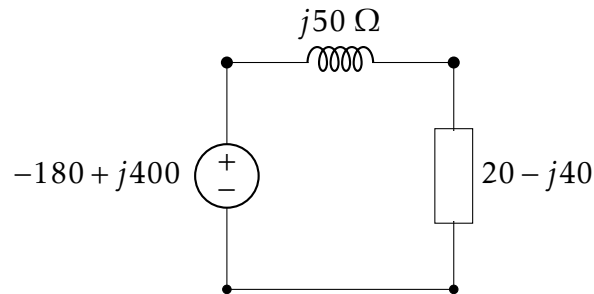
$$V_{AB} = V_{oc} = 20\angle 0 - 10\angle 0(Z_{eq}) = -180 + j400$$



$$\tan^{-1}\left(\frac{400}{-180}\right) = -65.77 + 180$$

### Driving point impedance

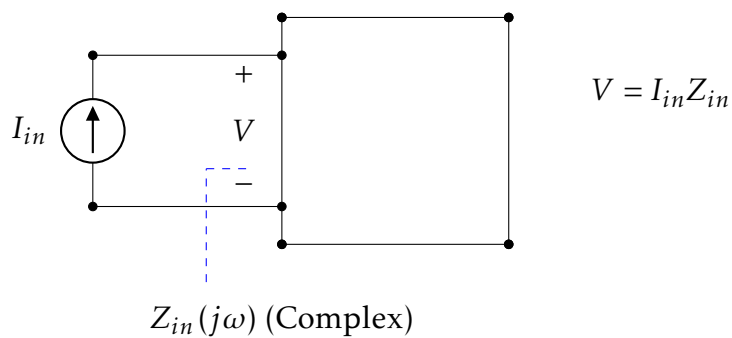

Connect  $I_{in}e^{j\omega t}$ ; response is  $Ve^{j\omega t}$


$$Ve^{j\omega t} = I_{in}Ze^{j\omega t}$$

$Z_{in} = \frac{V}{I_{in}}$  where  $V, I_{in}$  are phasors.

$Z$  is complex and  $Z = \frac{|V|}{|I_{in}|}e^{j(\theta_V - \theta_I)}$
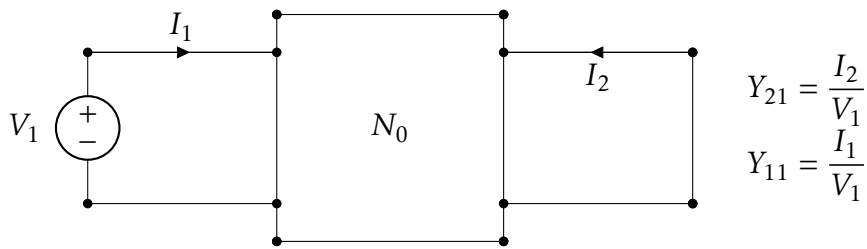
### Two port networks

For analysis in sinusoidal steady state, use phasors.



$$Y_{21} = \frac{I_2}{V_1}$$
$$Y_{11} = \frac{I_1}{V_1}$$

$V_1, I_1$  and  $I_2$  are phasors.