


## Lecture 5: Power and Energy (Cont'd...)

Lecturer: Dr. Vinita Vasudevan

Scribe: RSS Chaithanya

### Power and Energy

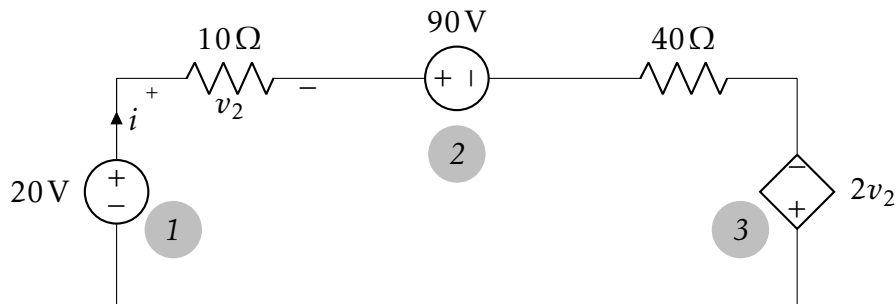**Example 1.** Consider the following circuit and calculate the power of each voltage source




$$20 - 10i - 90 - 40i - 2(10i) = 0$$

$$i = -1A$$

$p_1 = 20W$  (absorbing power),  $p_2 = -90W$  (delivering power),  $p_3 = 20W$  (absorbing power)

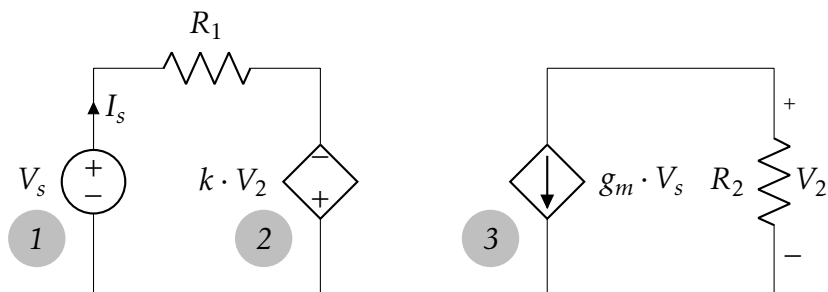**Example 2.** Consider the following circuit with  $k, g_m > 0$



$$V_s - I_s R_1 - k V_2 = 0, \quad g_m V_s R_2 = -V_2$$

$$V_s = I_s R_1 + k(-g_m V_s R_2)$$


$$I_s = \frac{V_s}{R_1} (1 + k g_m R_2)$$

$p_1$  is  $-ve$ ,  $p_2$  is  $-ve$ ,  $p_3$  is  $-ve$ . Therefore all the sources (both independent and dependent) in the above circuit deliver power.


Controlled sources can deliver power or absorb power similar to independent sources.
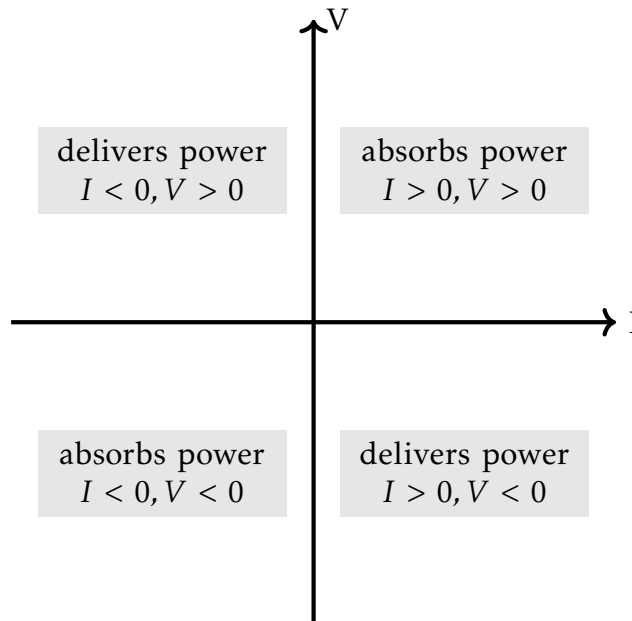
## I-V characteristics


Any generic element absorbs power if it is operating in 1<sup>st</sup> or 3<sup>rd</sup> quadrant and delivers power if it is operating in 2<sup>nd</sup> or 4<sup>th</sup> quadrant.  $V$  is the voltage drop and the reference direction for  $I$  is in the direction of the voltage drop.



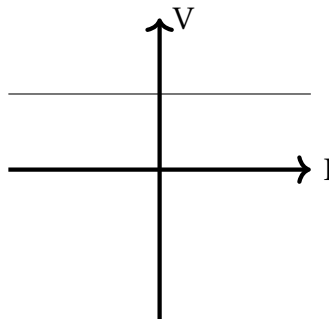
- **Ideal Voltage Source:** Ideal voltage source can deliver power or absorb power depending upon which quadrant it is operating in.




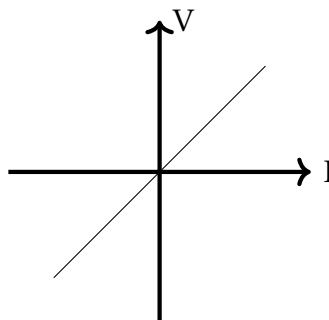
- **Resistor:** Resistor always absorbs power.



- **Ideal Current Source:** Ideal current source can deliver or absorb power depending on its operating point.

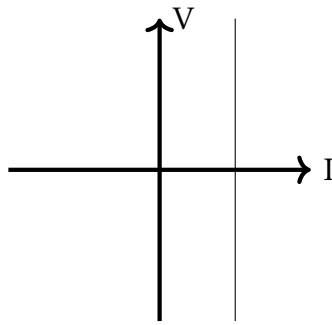

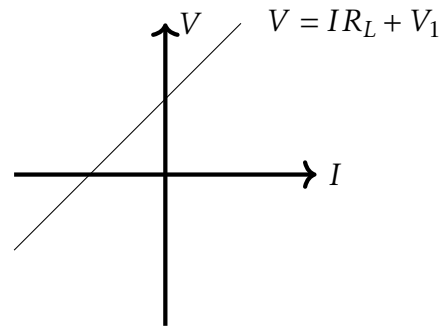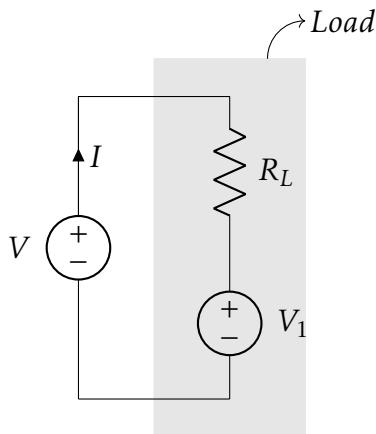**Example 3.** Consider the following circuit




*I-V characteristic of 'Load'*

In this example 'Load' can operate in three quadrants, capable of both generating and absorbing power.

I-V characteristics can be drawn for any part of circuit, considering that part as a generic 'Load' element.

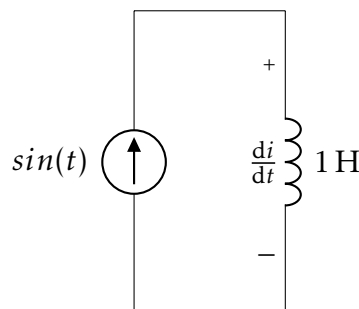**Example 4.** Consider the following circuit



Power =  $i \frac{di}{dt} = \sin(t) \cdot \cos(t) = \frac{1}{2} \sin(2t)$ . In this case, inductor oscillates between absorbing and delivering power at twice the frequency of current source.

### Unilateral Laplace transform

$$\text{Bilateral Laplace transform: } F(s) = \int_{-\infty}^{\infty} f(t)e^{-st} dt$$

$$\text{Unilateral Laplace transform: } F(s) = \int_{-\infty}^{\infty} f(t)u(t)e^{-st} dt = \int_{0^-}^{\infty} f(t)e^{-st} dt$$

Bilateral Laplace transform of  $e^{-at}u(t)$  and  $-e^{-at}u(-t)$  are same ( $\frac{1}{s+a}$ ) but with different region of convergences. For  $e^{-at}u(t)$  it is  $s > -a$  and for  $-e^{-at}u(-t)$  it is  $s < -a$ . We want the inverse transform to be causal. It is enough to do unilateral Laplace transform (referred as just Laplace transform) since its inverse gives unique causal signal.