


Lecture 8: Mesh Analysis

Lecturer: Dr. Vinita Vasudevan


Scribe: Shashank Shekhar

Nodal Analysis (cont...)

Example 1: Given $v_C(0^-) = 2V$

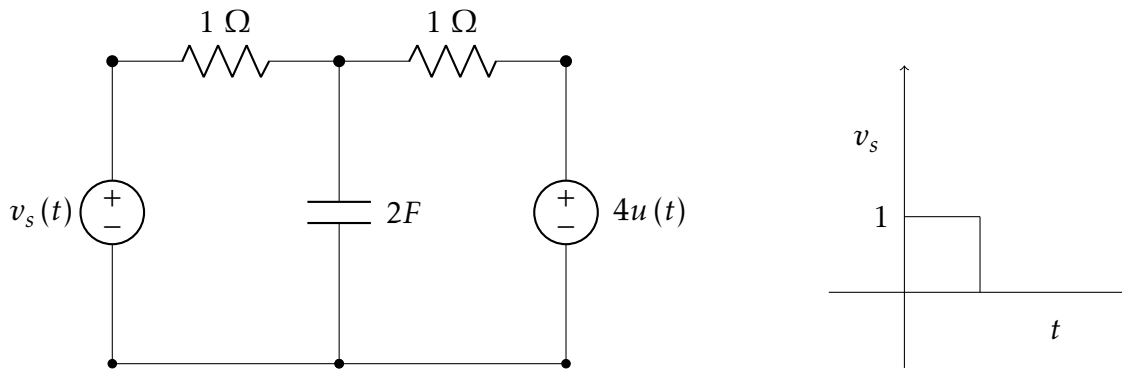

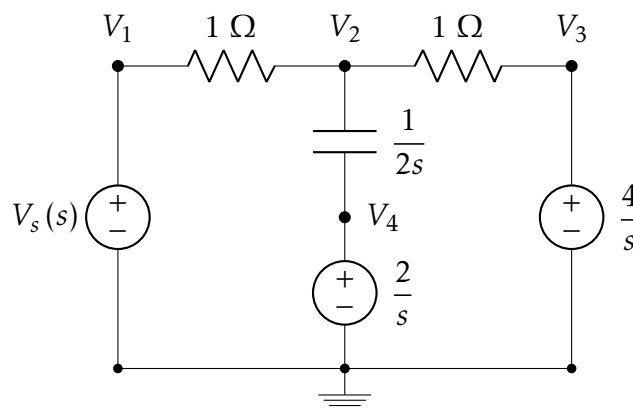
Using laplace transform the above circuit will be as follows:



Given $v_s(t) = u(t) - u(t-1)$. So, $V_s(s) = \frac{1 - e^{-s}}{s}$

As we can observe, V_1, V_4, V_3 along with reference node form a supernode. So, we need to write KCL only at V_2 .
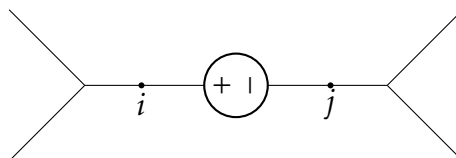
$$V_2(s)(2 + 2s) - 1 \cdot V_1(s) - 1 \cdot V_3(s) - 2sV_4(s) = 0$$



If there is a voltage source between nodes i and j , write KCL for supernode. In the above example, $V_1, V_4, & V_3$ are connected to reference node through voltage source so the supernodes are $[(1)-(R)], [(4)-(R)]$ and $[(3)-(R)]$ We do not write KCL for the reference node so only

write one equation for node 2. Additional equations are

$$V_1 = \frac{1 - e^{-s}}{s} \quad (1)$$

$$V_3 = \frac{4}{s} \quad (2)$$

$$V_4 = \frac{2}{s} \quad (3)$$

$$(4)$$

Therefore,


$$V_2(s) = \frac{1 - e^{-s}}{2s(s+1)} + \frac{2}{s}$$

Find $v_2(t)$

Note: Remember that the voltage across capacitor is $V_2(s)$ not $V_2(s) - V_4(s)$

Mesh Analysis: Find loops that do not cross a branch (no loop inside the loop) → mesh. Mesh currents are unknowns (assume all mesh currents in clockwise direction)

Example 2:

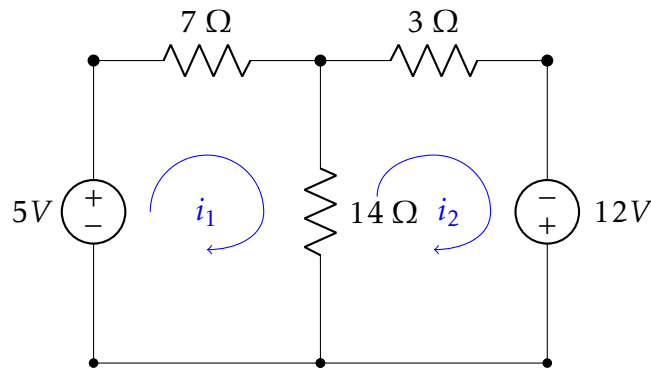

$$\text{Mesh 1: } -5 + 7i_1 + 14(i_1 - i_2) = 0$$

$$\text{Mesh 2: } -12 + 3i_2 + 14(i_2 - i_1) = 0$$

or

$$(7 + 14)i_1 - 14i_2 = 5$$


$$-14i_1 + (14 + 3)i_2 = 12$$

In the matrix form,



$$\begin{bmatrix} 21 & -14 \\ -14 & 17 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} 5 \\ 12 \end{bmatrix}$$

Invert the matrix and solve for i_1 & i_2 . Note that the diagonal entries are the sum of the impedances in the loop and the off-diagonal terms are the negative of the impedance between the two loops.

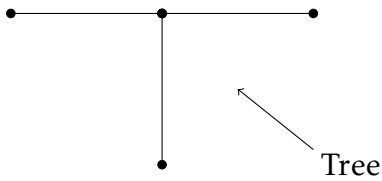If we have a circuit with N nodes, b branches then the number of meshes will be equal to $b - (N - 1)$. Explanation is given below:




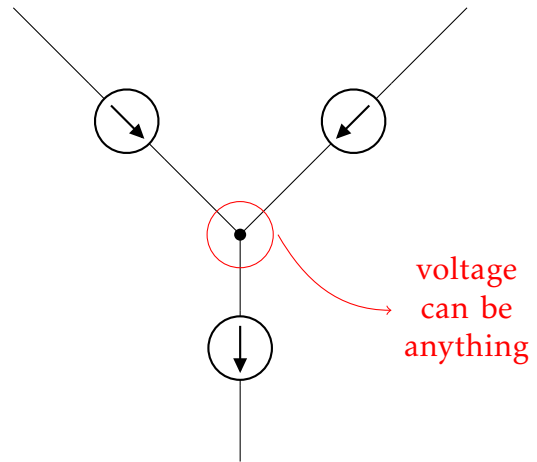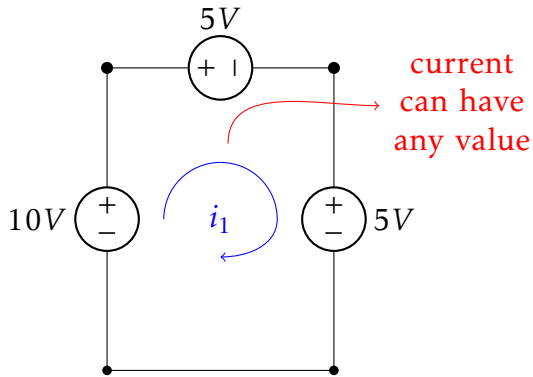with 'N' nodes you can form a tree (no loops) with $N - 1$ branches. Every additional branch you add will form a loop(mesh) with the existing tree branches. The mesh current in the additional branch is independent of the currents in all other branches; Therefore, the equations are independent



In practice you should never do this.

Example 3:

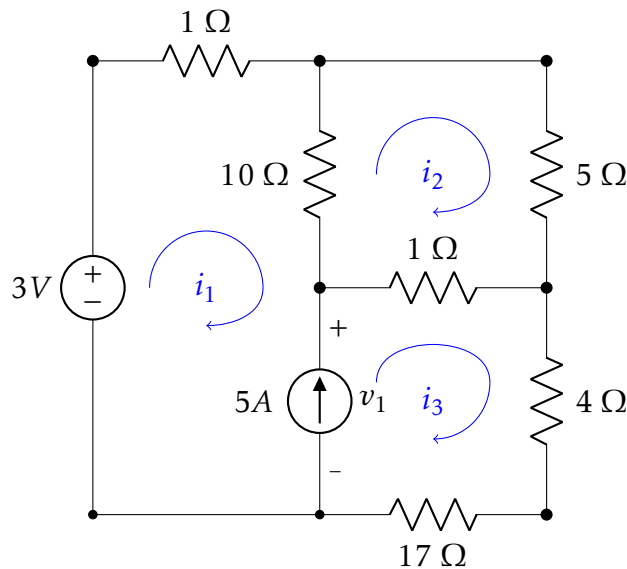

If there is a current source, form a super mesh by adding the equations for two meshes. Assume voltage across the current source is v_1 . The equations for mesh 1 and 3 can be written as

$$\begin{aligned} -3 + 10(i_1 - i_2) + v_1 &= 0 \\ 1(i_3 - i_2) + 4i_3 + 17i_3 - v_1 &= 0 \end{aligned}$$

The equation for supermesh is the sum of the above two equations.

$$10(i_2 - i_1) + 5i_2 + 1(i_2 - i_3) = 0$$

The additional equation needed can be obtained by writing the current source current as the difference of two mesh currents.

$$i_3 - i_1 = 5A$$

So we have,

$$\begin{aligned}10i_1 - (10 + 1)i_2 + (17 + 4)i_3 &= 3 \\ -10i_1 + (10 + 5 + 1)i_2 - i_3 &= 0 \\ i_1 - i_3 &= -5\end{aligned}$$

or,

$$\begin{aligned}10i_1 - (11)i_2 + (21)i_3 &= 3 \\ -10i_1 + (16)i_2 - i_3 &= 0 \\ i_1 - i_3 &= -5\end{aligned}$$

we can write above equations in matrix form

$$\begin{bmatrix} 10 & -11 & 21 \\ -10 & 16 & -1 \\ 1 & 0 & -1 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 3 \\ 0 \\ -5 \end{bmatrix}$$

Solve these equations for i_1, i_2 & i_3 .