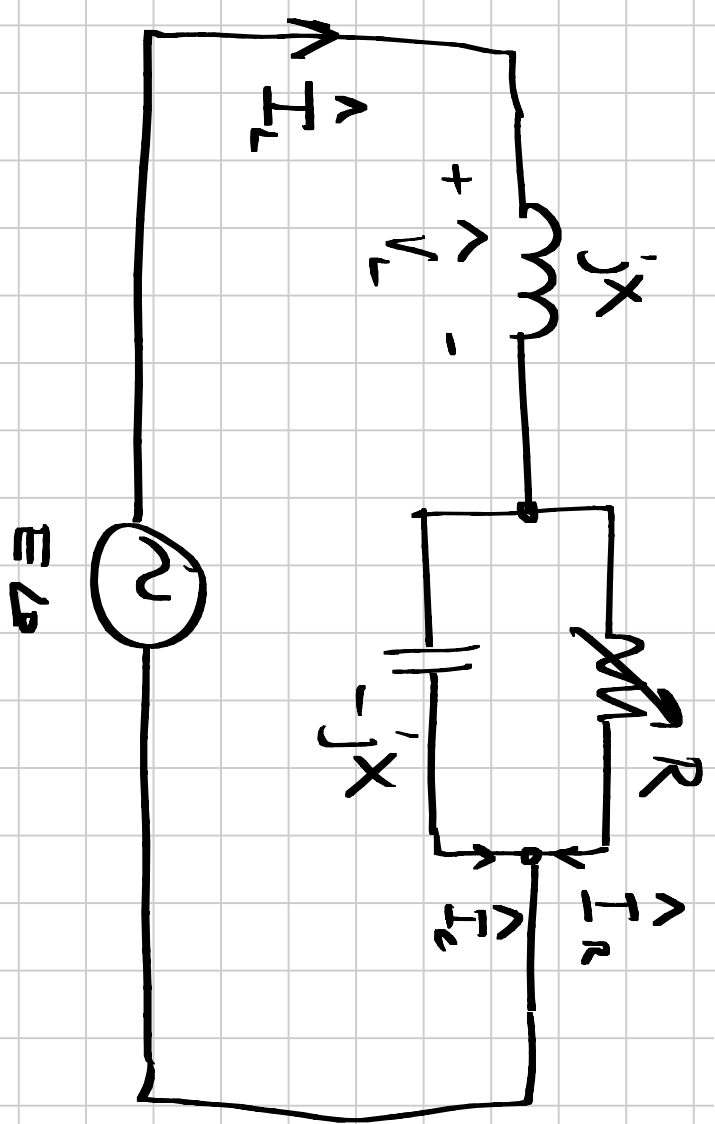


Problem 1 :



The inductor and capacitor have the same reactance at the


frequency of excitation.

(a) Calculate I_R , the current through the resistor, in terms of E , X & R .

(b) Draw a phasor diagram indicating the current through and voltage across R , L , C and the source.


(c) Draw the loci of i_1 , V_c , i_2 , I_c , i_3 , I_L and V_L as R is varied from 0 to ∞ .

Problem 2

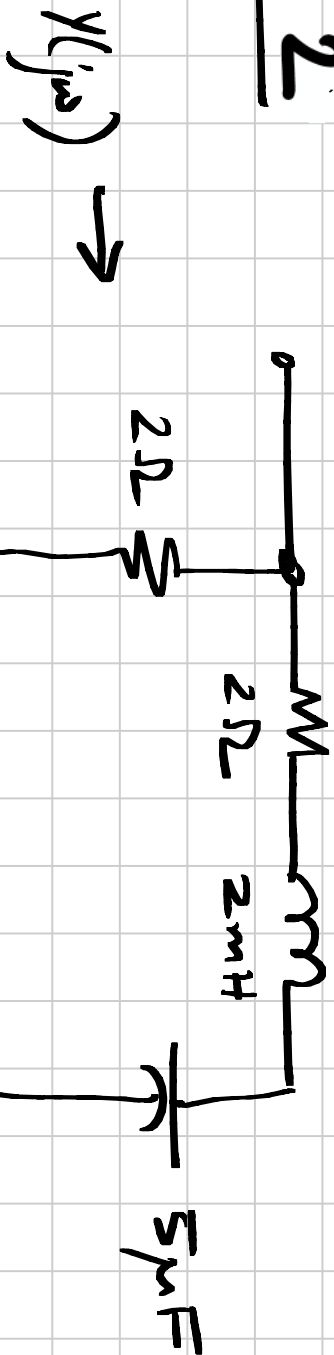


Compute $Y(j\omega)$ and draw its locus as ω varies from 0 to ∞ .

Problem 3

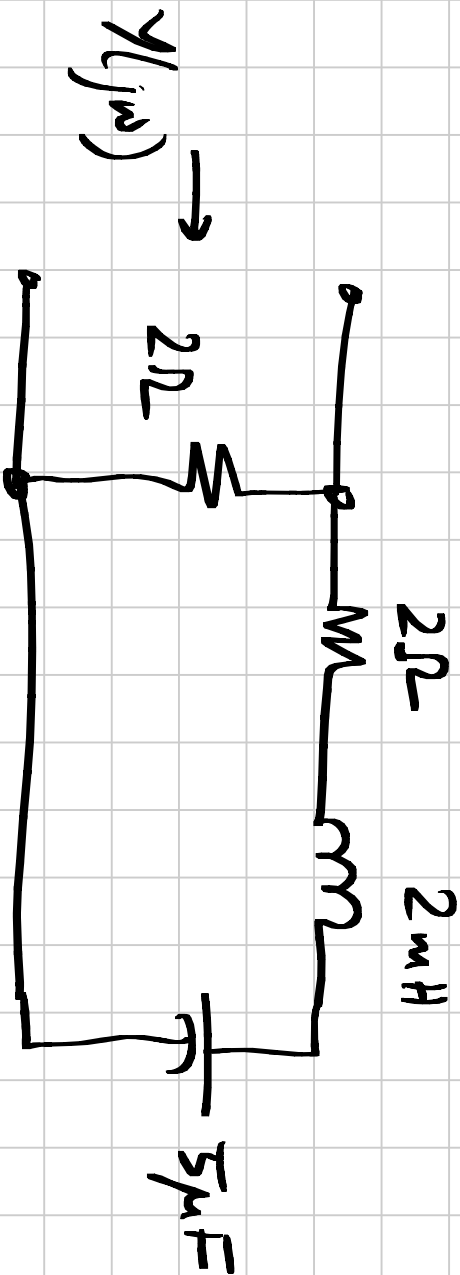


Draw the locus of $Y(j\omega)$ as ω varies from 0 to ∞ .

Problem 4

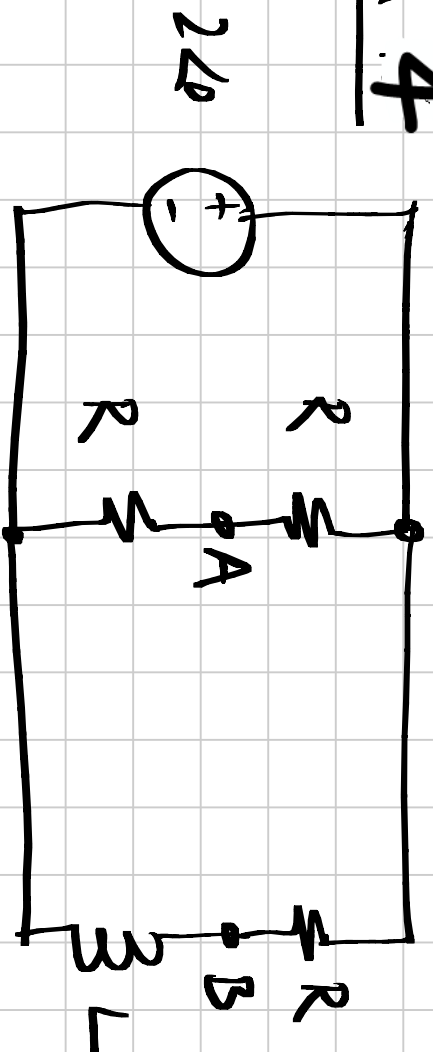


Use a locus diagram to show that the magnitude of V_B does not change with frequency.

Problem 5

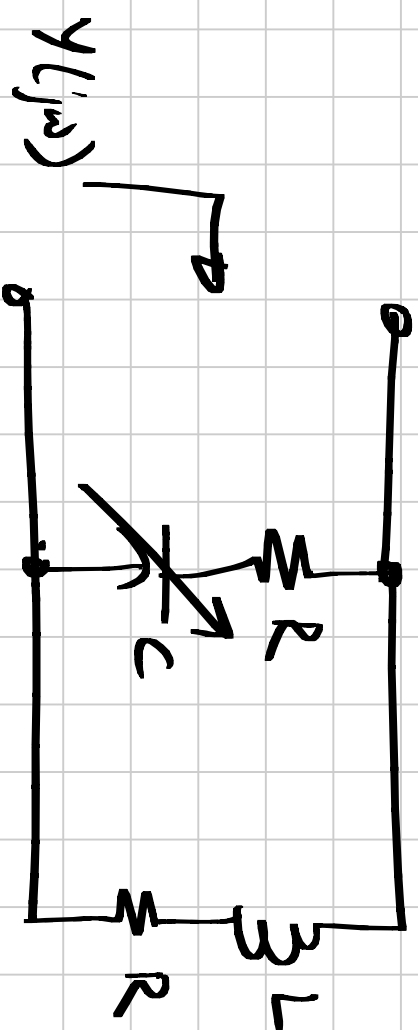

Plot the admittance locus of Y as C is varied, for some fixed ω .

(6)

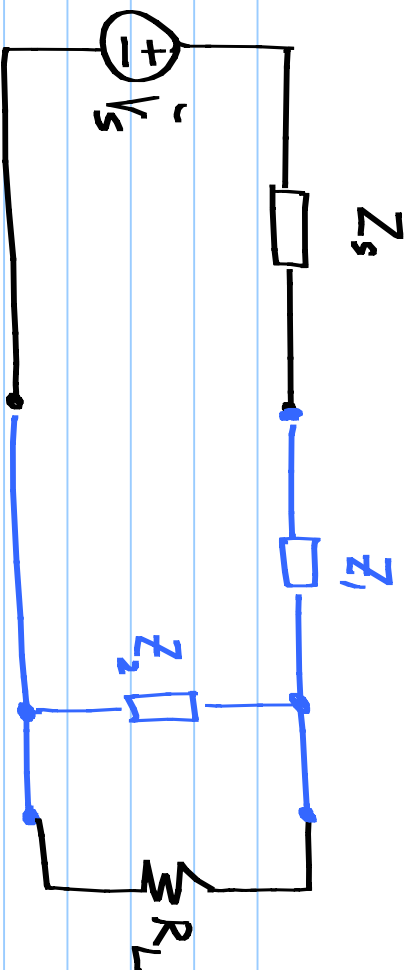


\tilde{V}_s, Z_s is a source with a complex impedance.

The matching network, shown in blue consists of only lossless components (obviously, to avoid wasting any power).

It should be such that R_L draws the maximum available power from the source

Draw neat locus diagrams for all 4 possible choices for Z_1 & Z_2 and two possibilities for Z_3 (positive & negative imaginary parts.)

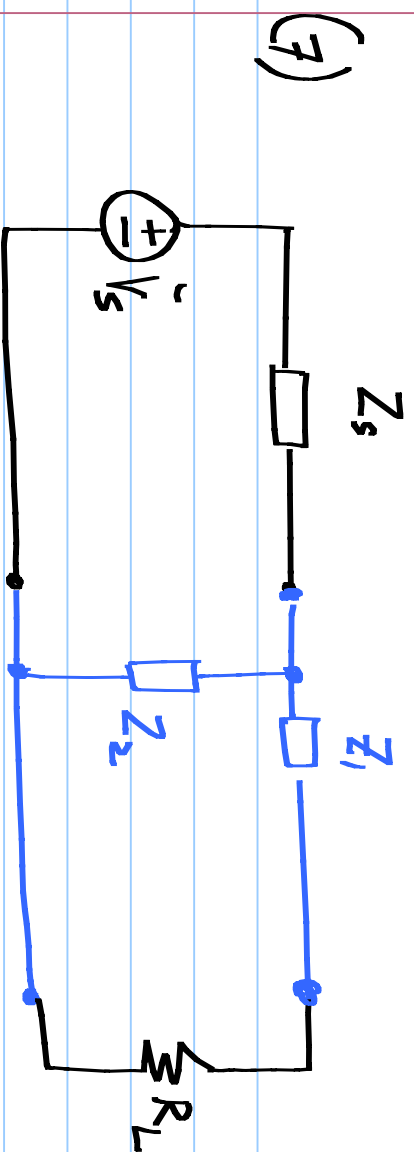Comment on values of R_L which can be matched and the type of elements in the matching network which give the most freedom to match



\tilde{V}_s, Z_s is a source with a complex impedance.


The matching network, shown in blue consists of only lossless components (obviously, to avoid wasting any power).

It should be such that Z_L draws the maximum available power from the source

Draw neat locus diagrams for all 4 possible choices for Z_1 & Z_2 and two possibilities for Z_3 (positive & negative imaginary parts.)

Comment on values of R_L which can be matched and the type of elements in the matching network which give the most freedom to match

(8)

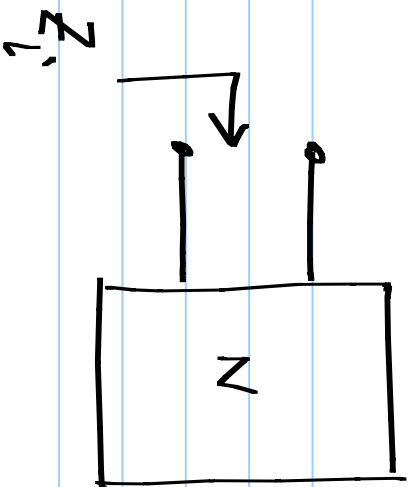

N consists of an arbitrary interconnection of passive elements (R, L, C). What can you say about the resistive part of Z_L ?

(Reason out clearly)