

# EE2019–Analog Systems and Lab: Tutorial 5

Nagendra Krishnapura, Shanthi Pavan

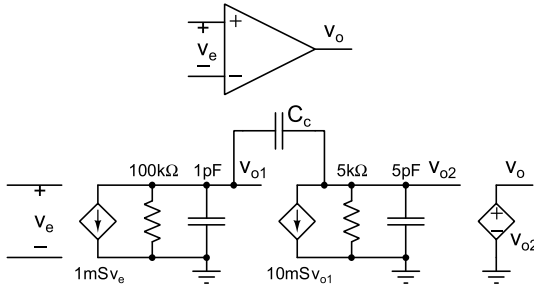


Figure 1: Circuit for problem 1

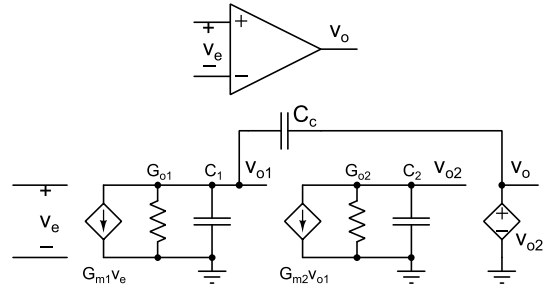


Figure 2: Circuit for problem 2

- Fig. 1 shows the internal schematic of a Miller-compensated opamp. This opamp is used to realize a unity gain, non-inverting amplifier.
  - What is the phase margin?
  - Determine  $C_c$  so that the phase margin is  $60^\circ$ .
  - If the same opamp is used without any change to realize an inverting amplifier of gain  $-4$ , what are the phase margin and the closed loop bandwidth?
  - Re-design the opamp (value of  $C_c$ ) so that when an inverting amplifier of gain  $-4$  is realized using it, the phase margin is  $60^\circ$ . Compare the three cases wrt the following aspects: (a) Closed loop bandwidth, (b) phase margin, (c) phase lag contributed by the right-half-plane zero at the unity loop gain frequency.
  - Compare the bandwidths you obtain to the ones in the previous tutorial in which you simply increased  $C_1$ .
- Determine the transfer function of the opamp in Fig. 2. How does it differ from the conventional Miller compensated opamp in the previous problem?
- It is common to approximate the unity loop gain frequency as  $\omega_{u,loop} \approx L_0 p_1$  where  $L_0$  is the dc loop gain and  $p_1$  is the dominant pole. If the loop gain is a second order function  $L(s) = L_0 / (1 + s/p_1)(1 + s/p_2)$ , determine the exact unity loop gain frequency and the phase margin for the following cases: (a)  $p_2 = 4L_0 p_1$ , (b)  $p_2 = 2L_0 p_1$ , and (c)  $p_2 = L_0 p_1$ . Compare them to the values obtained using the approximation above.  $L_0 \gg 1$ .  
(This approximation is very commonly used for hand calculations, but you should know how much error you end up with while doing so.)
- Analyze the circuit of Problem 1 in LTSpice and verify your answers with simulation.

While determining the unity loop gain frequency, phase margin, and  $C_c$ , do the calculations with and without the approximation  $C_c \gg C_{1,2}$ .