

EE2019 Analog Systems and Lab: Problem Set 6

Problem-1

 


Figure 1: Circuit for Problem-1

Figure 1 shows a linear regulator. Assuming op-amp OA is ideal:

- Determine the polarity of input terminals 1 & 2 of the op-amp for negative feedback operation.
- Find the output voltage V_{out} .
- Find the minimum and maximum value of V_c if I_{LOAD} varies from 1mA to 10mA.

Problem-2

 


Figure 2: Circuit for Problem-2

Figure 2 shows the linear regulator of Figure 1 with a real 2-stage compensated op-amp having transfer function:

$$A(s) = \frac{100}{(1 + 5 \times 10^{-6}s)(1 + 5 \times 10^{-8}s)}$$

- Assuming op-amp pole as dominant, find the maximum value of the load capacitor, C_{LOAD} to maintain the phase margin $> 45^\circ$. Support your answer with bode magnitude and phase plot.
- Is it possible to use C_{LOAD} larger than the value found in (a) and still achieve a phase margin $> 45^\circ$? Support your answer with bode magnitude and phase plot.
- Determine the value of C_{LOAD} for which phase margin becomes 0° .
- Find the steady error in V_{out} due to finite dc loop gain.

Problem-3

Simulate the circuit of Figure 2 in LTSpice and compare the result found in Problem-2 with your simulated results. Comment on differences, if there are any. For Problem 2 (b), perform transient analysis with initial condition $V_{out}=0$, observe the magnitude and frequency of oscillations at V_{out} and relate the same with your loop gain analysis.

Problem-4

In class, we saw that the response of a “slow” linear time-invariant system to a rapidly varying input like v_i in Figure 4 is approximately the same as that due to \hat{v}_i . In this problem, we will convince ourselves of this by working a specific example on LTSpice simulation.

Assume that v_i has a frequency of 1 MHz, and a duty cycle of 10%. $RC = 1$ mS. On the same graph, plot $v_o(t)$ when the input is $v_i(t)$, and when it is $\hat{v}_i(t)$.

 


Figure 4: Circuit for Problem-4

Problem-5

 


Figure 5: Circuit for Problem-5

Figure 5 shows a buck converter. The battery voltage V_{bat} is 5V. ϕ and $\bar{\phi}$ are complementary switch drive signals. The duty cycle of ϕ is denoted by D . The switching frequency is 1.5 MHz. $L = 2.2 \mu\text{H}$ and $C = 22 \mu\text{F}$. The load resistor $R = 10\Omega$.

- Determine D needed to achieve $V_{out} = 3.3\text{V}$.
- Determine the transfer function from v_x to V_{out} .
- Using the observation that the pole frequency of the LC filter is much lower than the switching frequency, determine the ripple in the inductor current and output voltage.
- Sketch the current waveforms in the inductor and capacitor in steady state.
- Sketch the voltage waveform V_{out} in steady state.

Problem-6

As usual, the switching period T_s is much smaller than the time-constant of the LC network. S1 and S2 are controlled by complementary waveforms, and the waveform controlling S1 is shown in the figure. Determine the average output voltage v_o , and the average current drawn from the source. Draw the steady state current and voltage waveforms through/across the inductor and capacitor.

 


Figure 6: Circuit for Problem-6

Problem-7

Figure 7 shows the circuit diagram of a type-I (integral) compensated buck converter with output voltage, V_{out} regulated at 2.5V for input supply, $V_{DD}=5\text{V}$ and load current, $I_{LOAD}=1\text{A}$. Assuming switches S_P and S_N are ideal.

- Model the buck converter in continuous time domain and find the small signal loop gain transfer function.
- Determine the value of capacitor C_1 to achieve the gain margin of $> 20\text{dB}$ and draw the bode magnitude and phase plot.
- Find the value of control voltage, V_{CTRL} and duty cycle, D to regulate the output voltage at 2.5V.
- Find the value of peak to peak inductor ripple current and peak-to-peak output ripple voltage.
- Draw the steady state waveforms for PWM voltage (V_{PWM}), switch currents (I_P and I_N), inductor current (I_L) and output voltage (V_{out}).

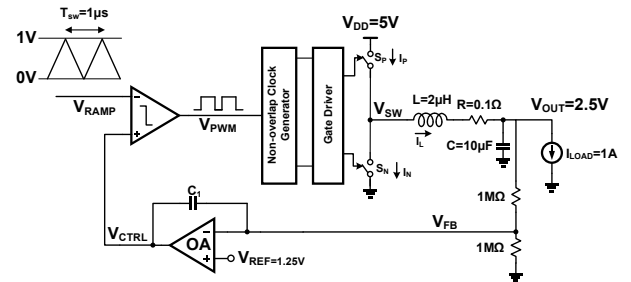


Figure 7: Circuit for Problem-7

Problem-8

Design the buck converter circuit shown in Figure 7 and its continuous time model in LTSpice.

- Perform AC analysis and plot the loop gain magnitude and phase response of the continuous time model and verify your results found in Problem-7 (b). Observe and comment on the effect of varying capacitor (C_1) value on unity gain frequency (ω_u) and gain margin. Use enough points per decade in your AC simulation to get the correct value of Q_O due to LC resonance.
- Perform transient analysis and plot waveforms V_{CTRL} and V_{OUT} of buck converter and corresponding signals in its continuous time mode on the same graph. Verify that V_{CTRL} and V_{OUT} of the buck converter have the average value as of its continuous time model. Comment on the differences if observed any. Use initial condition $V_{OUT}=0$ in your transient simulation. Verify your results found in Problem 7 (c), (d) and (e).