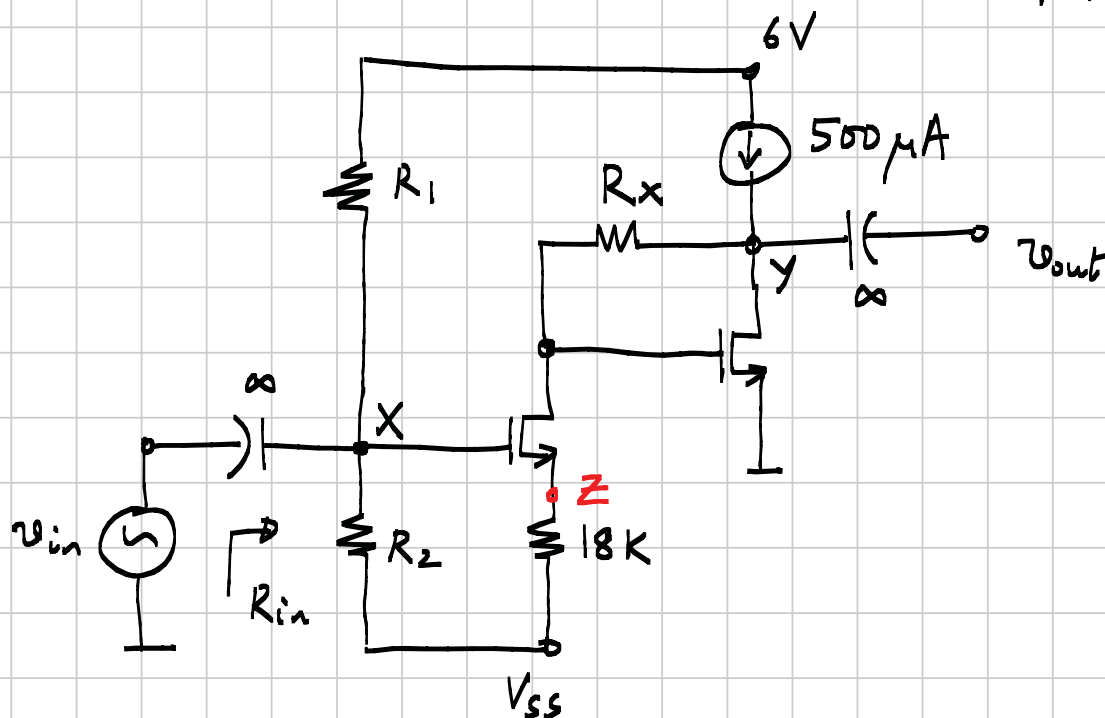


## Problem 1

\* For this problem, both transistors are identical, with  $V_T = 0.5\text{ V}$ ,  $\lambda = 0$ ,  $\mu_n C_{ox} \frac{W}{L} = 500\ \mu\text{A}/\text{V}^2$ .



The quiescent currents through both transistors are equal. Determine  $R_x$ ,  $V_{SS}$ ,  $R_1$ , &  $R_2$  so that

- $v_{in}$  can be coupled without using  $C_1$
- $R_{in} = 1\text{ M}\Omega$
- $\frac{v_{out}}{v_{in}} = 2$ , after accounting for finite  $g_m$  of the transistors


After determining the values above, find the quiescent voltage at node  $y$  and the maximum sinusoidal amplitude one can use at the input so that

the output is not distorted.

Now, an infinite capacitor is connected from node  $z$  to ground. What is  $\frac{v_{out}}{v_{in}}$  now?


## Problem 2

\*

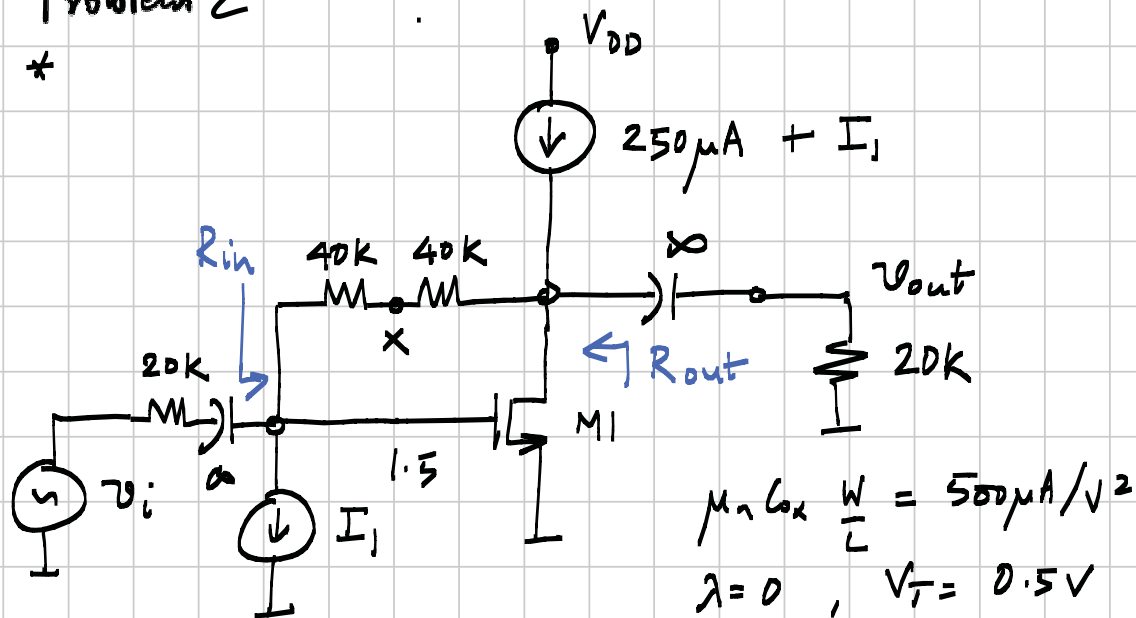

- Determine the quiescent current of  $M_1$ .
- Assuming large  $g_m$ , what gain do you expect from  $v_{in}$  to  $v_{out}$ ? What is the actual gain?
- Determine the input & output impedances  $R_{in}$  &  $R_{out}$ .
- Determine  $I_1$  so that the output sinusoid just clips at both extremes for an input amplitude of 1V. For this part, assume  $g_m$  is very large.
- An infinite capacitor is now connected between the node marked  $x$  and ground. Determine the incremental gain from  $v_i$  to  $v_{out}$ .


### \* Problem 3

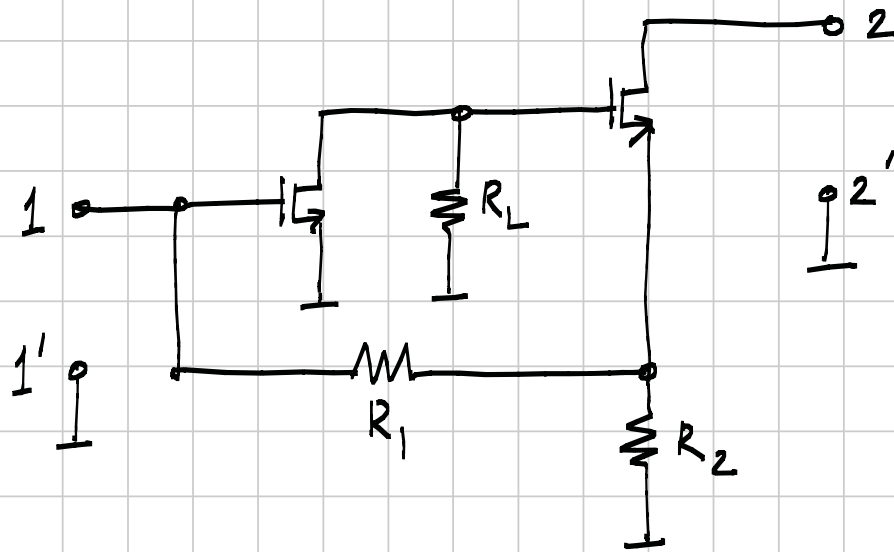

The circuit above is the incremental equivalent of an amplifier. The transistors have transconductances denoted by  $g_m$ .


- Determine the input impedance @ port 1 when port 2 is shorted.
- Determine the output impedance @ port 2 when port 1 is shorted.
- What kind of controlled source is this?
- If  $g_m \rightarrow \infty$ , determine the transfer function of the above controlled source.

\* Problem 4

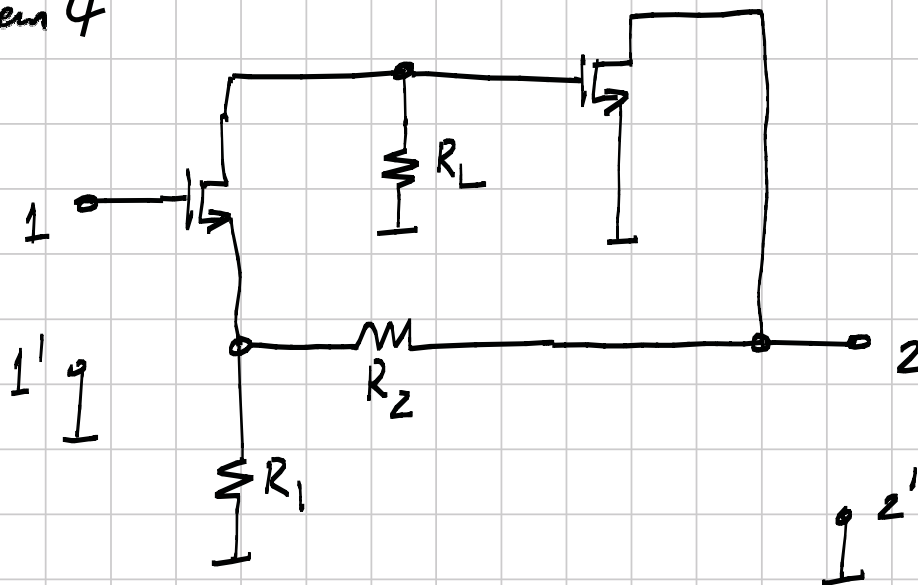

Repeat the previous problem for the incremental circuit shown above.

\* Problem 5

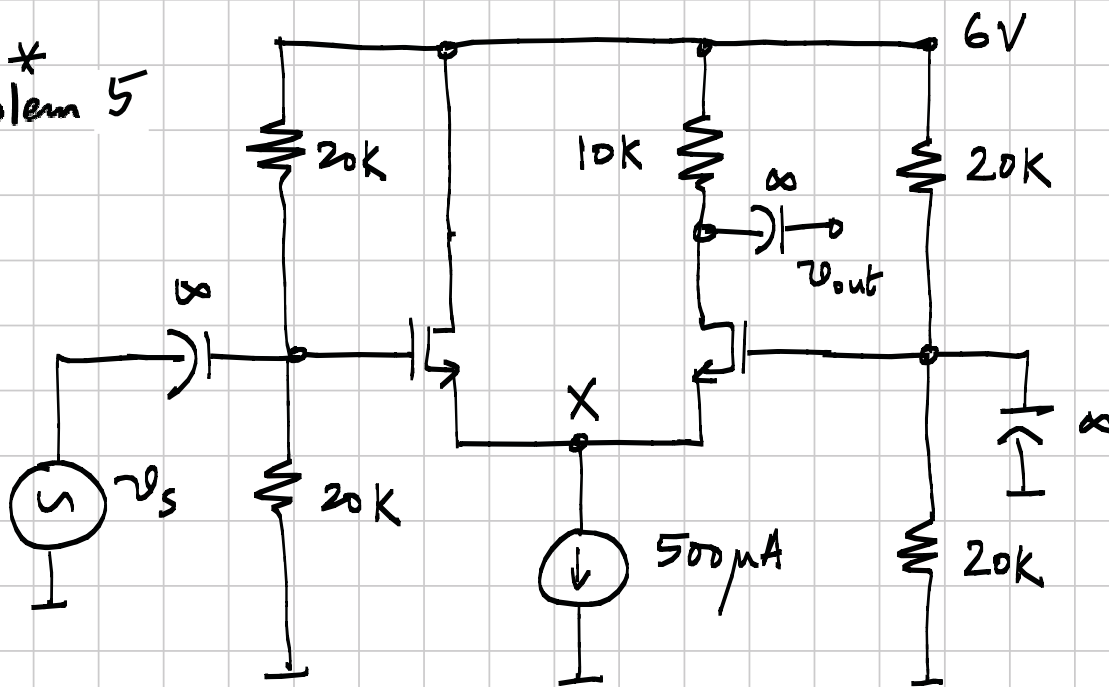

$$V_T = 0.5 \text{ V} \quad \mu_n C_{ox} \frac{W}{L} = 500 \mu\text{A}/\text{V}^2$$



$$\lambda = 0$$

In the circuit above


(a) Find the operating point.

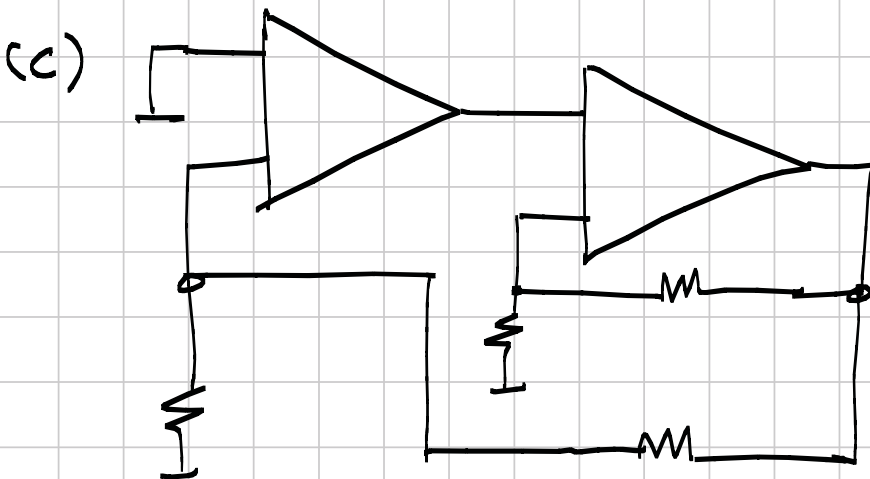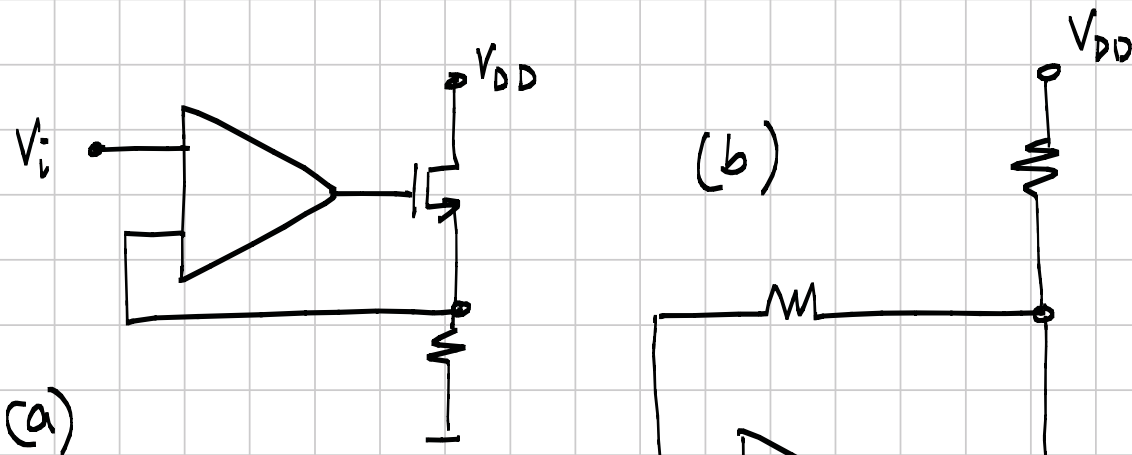(b) The incremental gain  $v_{out}/v_{in}$ .

Prob 6\* Determine the signs on the opamps for negative feedback operation.




\* Problem 7

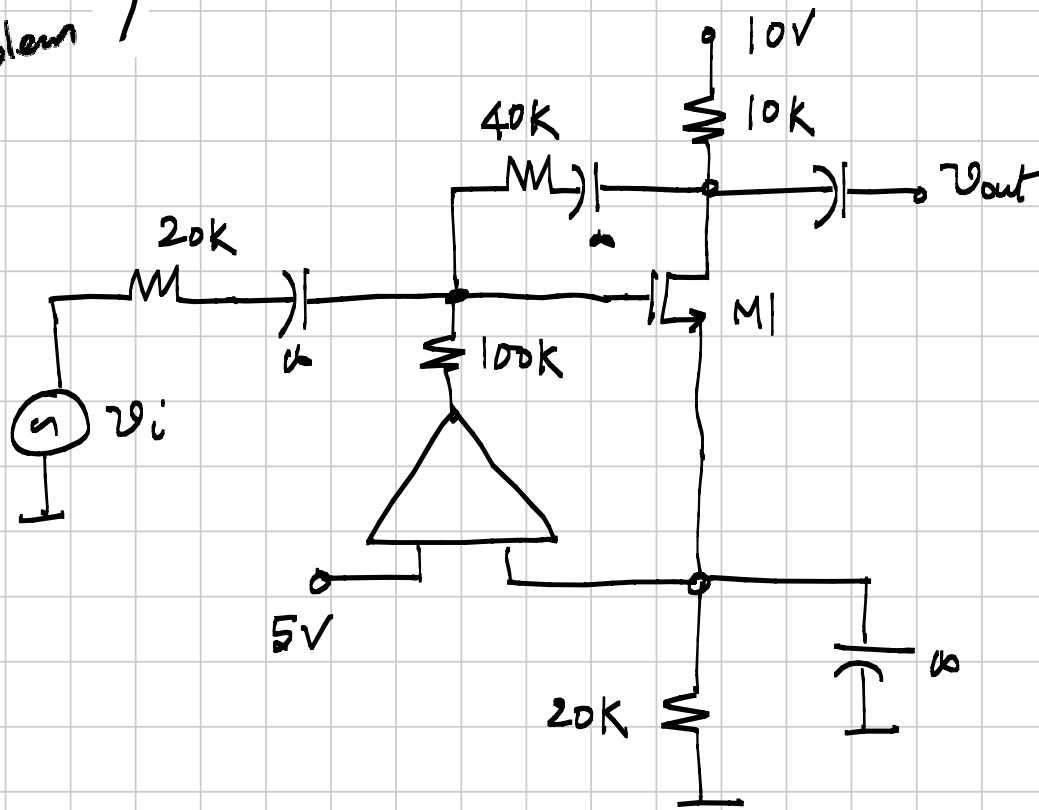


- (a) Determine the signs on the opamp for negative feedback operation
- (b) Determine the quiescent potential @ the gate of M1.
- (c) What is the incremental gain  $\frac{V_{out}}{V_i}$  ?

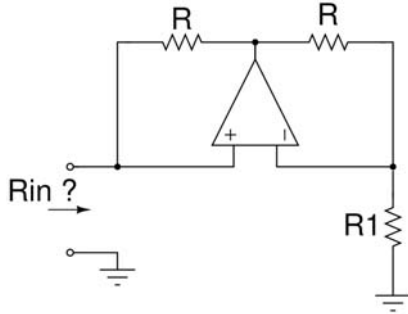8) The opamp in the circuit shown below is ideal. Determine  $R_{in}$ .




Circuit for Problem 8

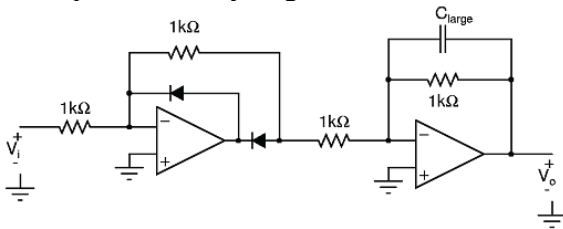9) In the circuit shown below, the input voltage  $V_i = 5V + 2\pi \cos(2\pi \cdot (1\text{kHz}) \cdot t)$ ; Determine  $V_o$ . The capacitor is very large.



Circuit for Problem 9

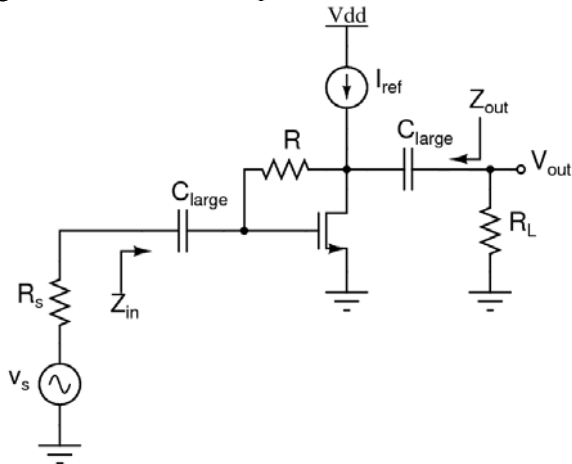10) In the circuit shown in the figure below, the capacitors ( $C_{large}$ ) may be assumed to be infinite.  
 (a) Determine the input impedance  $Z_{in}$  and the output impedance  $Z_{out}$ .  
 (b) Determine the overall small-signal voltage gain  $v_{out}/v_s$  for this amplifier.



Circuit for Problem 10