

# Analog Circuits (EE3002/EE5310) : Problem Set 8

shanthi@ee.iitm.ac.in

## Problem 1

 


Figure 1: Circuit for problem 1.

In the bandgap reference generator of Fig. 1, all transistors operate in saturation. The incremental output resistances of M1 and M2 may be assumed to be infinite. Assume that the temperature coefficient of the diode with size 1 is  $-2 \text{ mV/K}$ . The opamp is ideal. Assume that the gate-overdrive voltages of M1 and M2 are  $V_{ov}$ .

- Determine the ratio  $R2/R1$  for  $V_{ref}$  to have zero temperature coefficient (ZTC). Assume  $V_{o1}$  and  $V_{o2}$  are zero.
- Assuming that  $R2/R1$  is the value you found in part (a), determine the effect of opamp offset voltage  $V_{o1}$ , and threshold mismatch  $V_{o2}$  between M1 and M2. To simplify analysis, assume that  $V_{o1}$  and  $V_{o2}$  are small signals.

## Problem 2

In the bandgap reference generator of Fig. 2, all transistors operate in saturation. The incremental output resistances of M1 and M2

 


Figure 2: Circuit for problem 2.

may be assumed to be infinite. Assume that the temperature coefficient of the diode with size 1 is  $-2 \text{ mV/K}$ . The opamp is ideal. Determine the ratio  $R2/R1$  to achieve a  $V_{ref}$  with ZTC.

### Problem 3

For all transistors, use  $\mu_n C_{ox} = 200 \mu\text{A/V}^2$ ,  $\mu_p C_{ox} = 50 \mu\text{A/V}^2$ ,  $V_{TN} = V_{TP} = 0.1 \text{ V}$ . Use  $\lambda = 0$ . The (W/L)s of the devices are marked next to them. Assume that the voltage across the diode of size 1 is  $0.6 \text{ V}$  and  $(kT/q) \log_e 8 = 54 \text{ mV}$  at  $300\text{K}$ .

 


Figure 3: Circuit for problem 3.

Determine  $R2$  to achieve a zero TC for  $V_{ref}$ . For this  $R2$ , determine the voltage at every node in the circuit. What is the minimum  $V_{dd}$  that can be used while still allowing all transistors to operate in saturation?

### Problem 4

Repeat problem 2 for the circuit of Fig. 4.

### Problem 5

What should  $a$  be to achieve an output with ZTC? What is the reference voltage achieved? As usual, assume that all transistors are in saturation, and have infinite output resistance.

 


Figure 4: Circuit for problem 4.

 


Figure 5: Circuit for problem 5.