

# Analog Circuits (EE3002/EE5310) : Problem Set 2

shanthi@ee.iitm.ac.in

## Problem 1

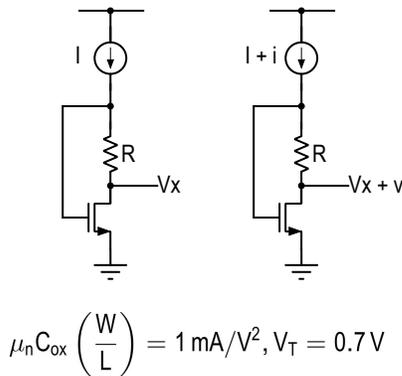


Figure 1: Circuit for problem 1.

In Fig. 1(a), determine the largest  $I$  that can be used while still maintaining the transistor in saturation.

In part(b) of the figure,  $i$  is a small signal, and  $I$  has been chosen so that the transistor is in saturation. Determine the quiescent voltage  $V_x$ , and the incremental voltage  $v$ . How will you choose  $R$  to make  $v$  independent of  $i$ ?

## Problem 2

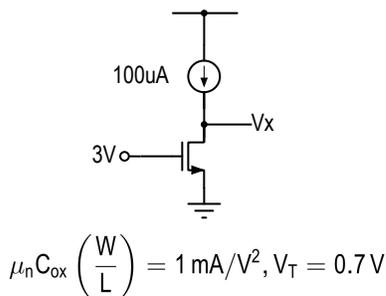


Figure 2: Circuit for problem 2.

For the circuit shown above, determine the region of operation of the transistor. Find  $V_x$ .

## Problem 3

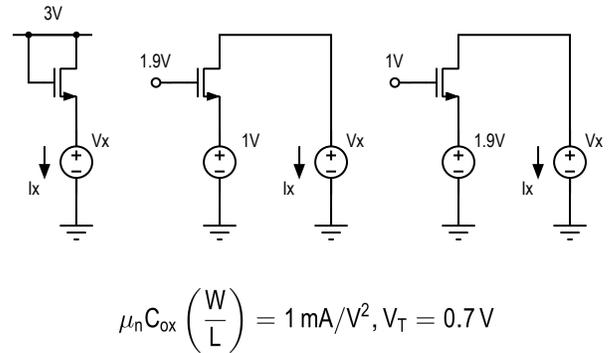


Figure 3: Circuits for problem 3.

For each of the circuits shown above, plot  $I_x$  as  $V_x$  varies from 0-3 V.

## Problem 4


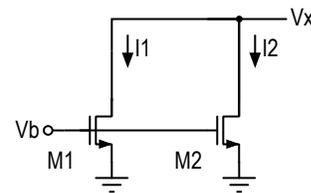


Figure 4: Circuit for problem 4.

Assume that  $V_x$  is large enough to keep M1 and M2 in saturation. Both transistors are identical. The threshold voltage of M2 is *slightly* larger than that of M1, by an amount  $\Delta V_T$ . Determine  $I_2$  in terms of  $\mu_n C_{ox} (W/L)$ ,  $V_T$  and  $V_b$ .
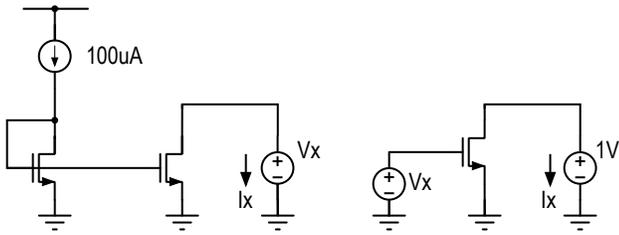
## Problem 5

For the circuits of Fig. 5, sketch  $I_x$  as  $V_x$  varies in the range 0.5-3 V.



$$\mu_n C_{ox} \left( \frac{W}{L} \right) = 1 \text{ mA/V}^2, V_T = 0.7 \text{ V}$$

Figure 5: Circuit for problem 5.

### Problem 6


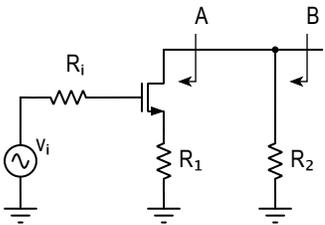


Figure 6: Circuit for problem 6.

The small signal equivalent circuit of an amplifier is shown above. The transistor is assumed to be in saturation, with transconductance  $g_m$  and output conductance  $g_o$ . Determine the Norton equivalent looking in at A, as well as the Thevenin equivalent looking in at B. What happens to these equivalents when  $g_m \rightarrow \infty$ ?

### Problem 7

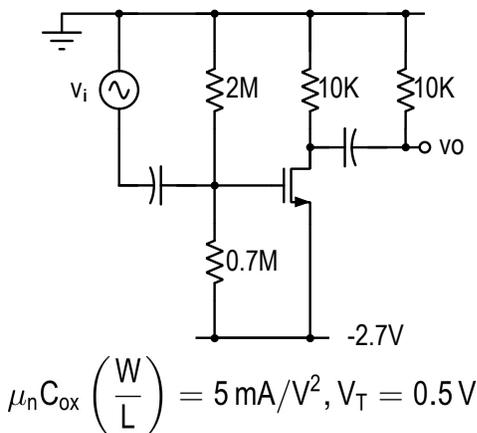


$$\mu_n C_{ox} \left( \frac{W}{L} \right) = 5 \text{ mA/V}^2, V_T = 0.5 \text{ V}$$

Figure 7: Circuit for problem 7.

Determine the quiescent operating point and small signal gain

of the amplifier of Fig. 7. What is the maximum permissible amplitude of the sinewave input so that clipping of the output is avoided?

### Problem 8

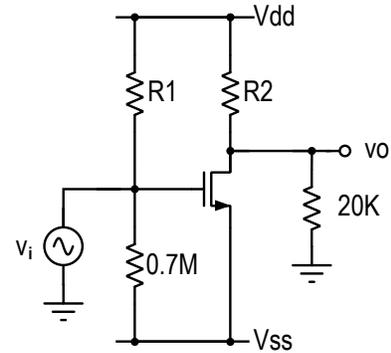

$$\mu_n C_{ox} \left( \frac{W}{L} \right) = 5 \text{ mA/V}^2, V_T = 0.5 \text{ V}$$

Figure 8: Circuit for problem 8.

The input to the amplifier shown below is a sinusoid of amplitude  $A$ . Determine  $R1$ ,  $R2$ ,  $A$ ,  $V_{dd}$  and  $V_{ss}$  in the circuit to achieve the following:

- There must be no quiescent current flowing through the 20K load, and input source.
- The incremental gain must be -4.
- The output sinewave must begin to just begin to clip at both extremes.

### Problem 9

The MOSFET in Fig. 9 has  $V_T = 0.7 \text{ V}$ , and  $\mu_n C_{ox} = 500 \mu\text{A/V}^2$ . The drain current in the device is 1 mA.

- Determine the small signal gain from  $v_i$  to  $v_o$ .
- Determine the  $(W/L)$  of the device and the quiescent  $V_{GS}$  and  $V_{DS}$ .
- The lowest frequency contained in  $v_s$  is 100 rad/s. Determine the minimum values of  $C1$ ,  $C2$  and  $C3$  required so that the natural frequencies associated with their charging/discharging is at least 10 times smaller than the smallest input frequency.

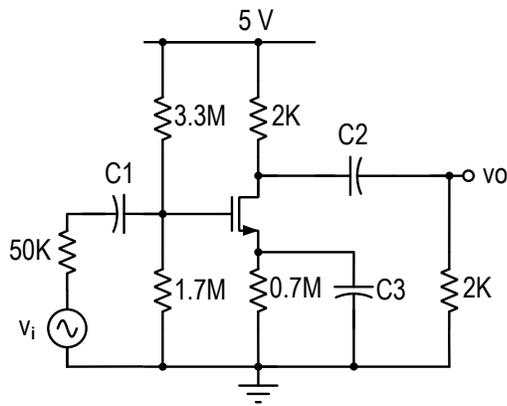


Figure 9: Circuit for problem 9.

- Determine the voltage swing limits at  $v_o$ . What is the amplitude of the largest sinusoidal input signal that can be applied before the output begins to clip ?
- The supply voltage is changed to 5.5 V. Determine the small signal gain of the amplifier.
- Due to a change in temperature,  $V_T$  increases by 100 mV. What is the new small signal gain of the amplifier ?

### Problem 10

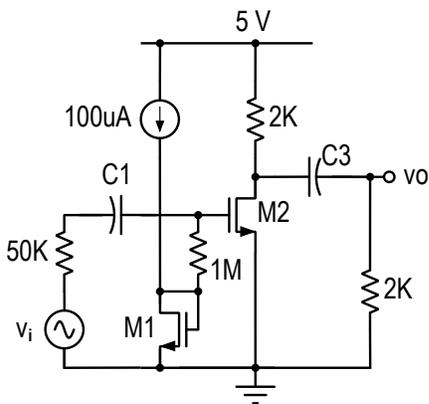


Figure 10: Circuit for problem 10.

The MOSFETs in Fig. 10 have  $V_T = 0.7 V$ , and  $\mu_n C_{ox} = 500 \mu A/V^2$ . Like in Problem 9, the drain current in M2 is 1 mA, and has the same (W/L) as in that problem.

- Determine the small signal gain from  $v_i$  to  $v_o$ .
- Determine the (W/L) of M1 and the quiescent  $V_{GS}$  and  $V_{DS}$ .

- The lowest frequency contained in  $v_i$  is 100 rad/s. Determine the minimum values of  $C_1$  and  $C_3$  required so that the natural frequencies associated with their charging/discharging is atleast 10 times smaller than the smallest input frequency.
- Determine the voltage swing limits at  $v_o$ . What is the approximate amplitude of the largest sinusoidal input signal that can be applied before the output begins to clip ?
- The supply voltage is changed to 5.5 V. Determine the small signal gain of the amplifier. How does this compare with the results of Problem 9 ? Why ?
- What is the small signal gain of the amplifier if (a)  $V_{T,M1} = 0.8 V, V_{T,M2} = 0.7 V$  (b)  $V_{T,M1} = 0.7 V, V_{T,M2} = 0.8 V$  and (c)  $V_{T,M1} = 0.8 V, V_{T,M2} = 0.8 V$  ? How does this compare with the results of Problem 9 ? Why ?

### Problem 11

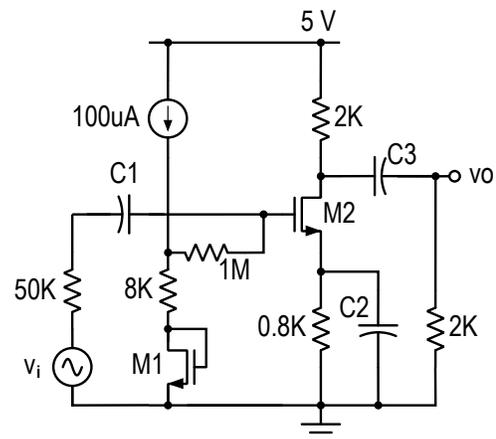


Figure 11: Circuit for problem 11.

The MOSFETs in Fig. 11 have  $V_T = 0.7 V$ , and  $\mu_n C_{ox} = 500 \mu A/V^2$ . Like in Problem 10, the drain current in M2 is 1 mA, and has the same (W/L) as in that problem.

- Determine the small signal gain from  $v_i$  to  $v_o$ .
- Determine the (W/L) of M1 and the quiescent  $V_{GS}$  and  $V_{DS}$ .
- The lowest frequency contained in  $v_i$  is 100 rad/s. Determine the minimum values of  $C_1$  and  $C_3$  required so that the natural frequencies associated with their charging/discharging is atleast 10 times smaller than the smallest input frequency.
- Determine the voltage swing limits at  $v_o$ . What is the approximate amplitude of the largest sinusoidal input signal that can be applied before the output begins to clip ?

- The supply voltage is changed to 5.5 V. Determine the small signal gain of the amplifier. How does this compare with the results of Problem 9 ? Why ?
- What is the small signal gain of the amplifier if (a)  $V_{T,M1} = 0.8 V, V_{T,M2} = 0.7 V$  (b)  $V_{T,M1} = 0.7 V, V_{T,M2} = 0.8 V$  and (c)  $V_{T,M1} = 0.8 V, V_{T,M2} = 0.8 V$  ? How does this compare with the results of Problem 9 ? Why ?