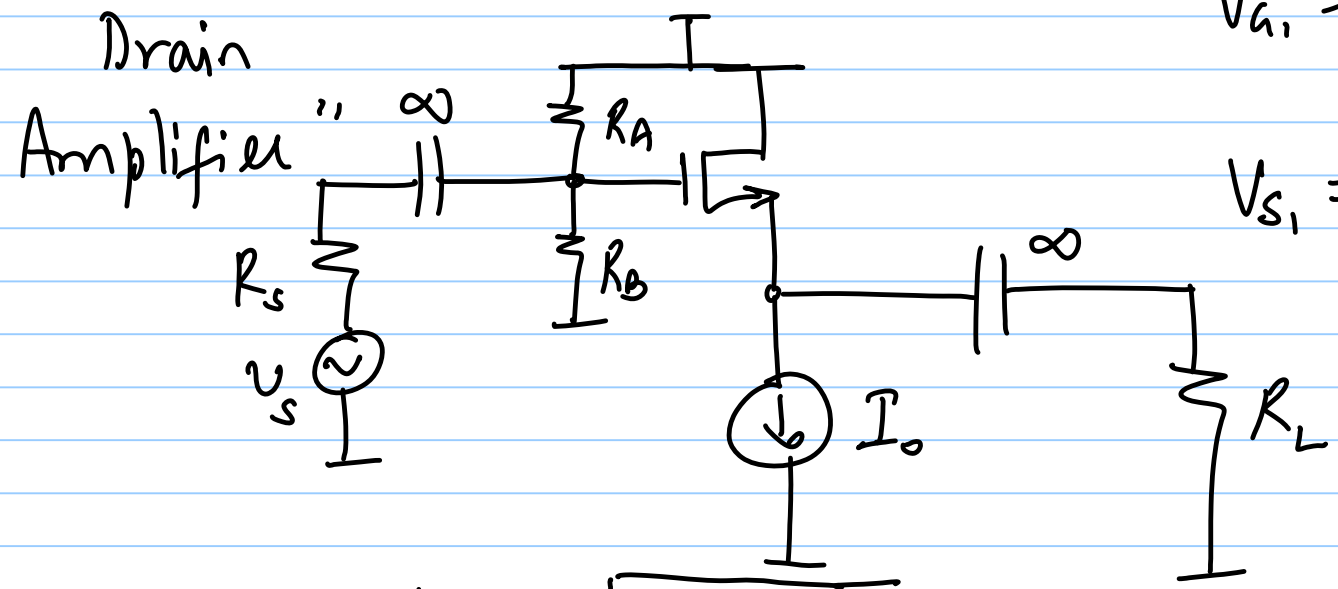


28/8/19

"Common
Drain
Amplifier"

Lec 14




$$V_{GS} = V_T + \sqrt{\frac{2I_o}{\mu_n C_{ox} \left(\frac{W}{L}\right)}}$$

$$V_{D1} = V_{DD}$$

$$V_{G1} = \frac{R_B}{R_A + R_B} \cdot V_{DD}$$

$$V_{S1} = V_{G1} - V_{GS} \Big|_{I_o}$$

$$I_D = I_o$$

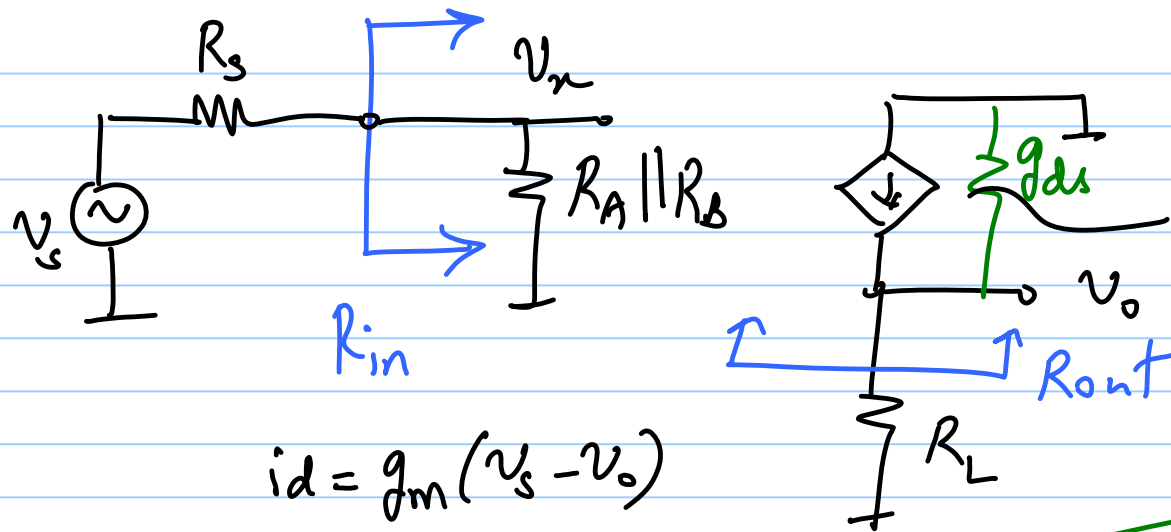




$$R_A || R_B \rightarrow R_s$$

$$v_n = \frac{R_A || R_B}{R_A || R_B + R_s} \cdot v_s$$

$$i_d = g_m(v_n - v_o)$$

$$v_o = \frac{g_m R_L}{1 + g_m R_L} \cdot v_n \approx v_s \quad \text{if } g_m \gg \frac{1}{R_L}$$

$$R_{in} = R_A || R_B ; \quad R_{out} = \frac{1}{g_m} \left\{ \frac{1}{g_m + g_{ds}} \right\}$$

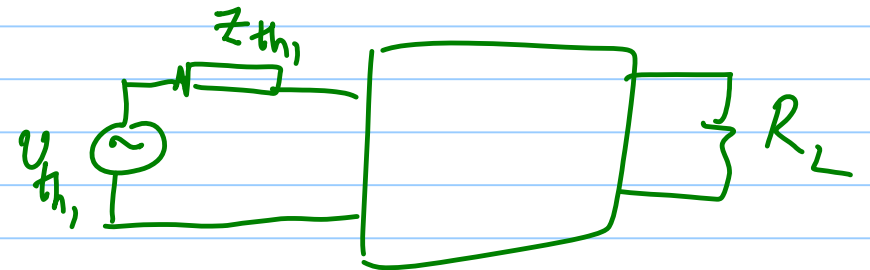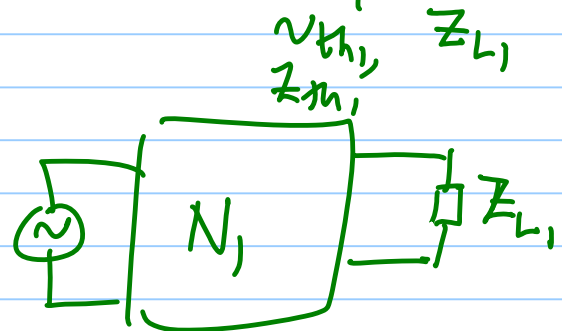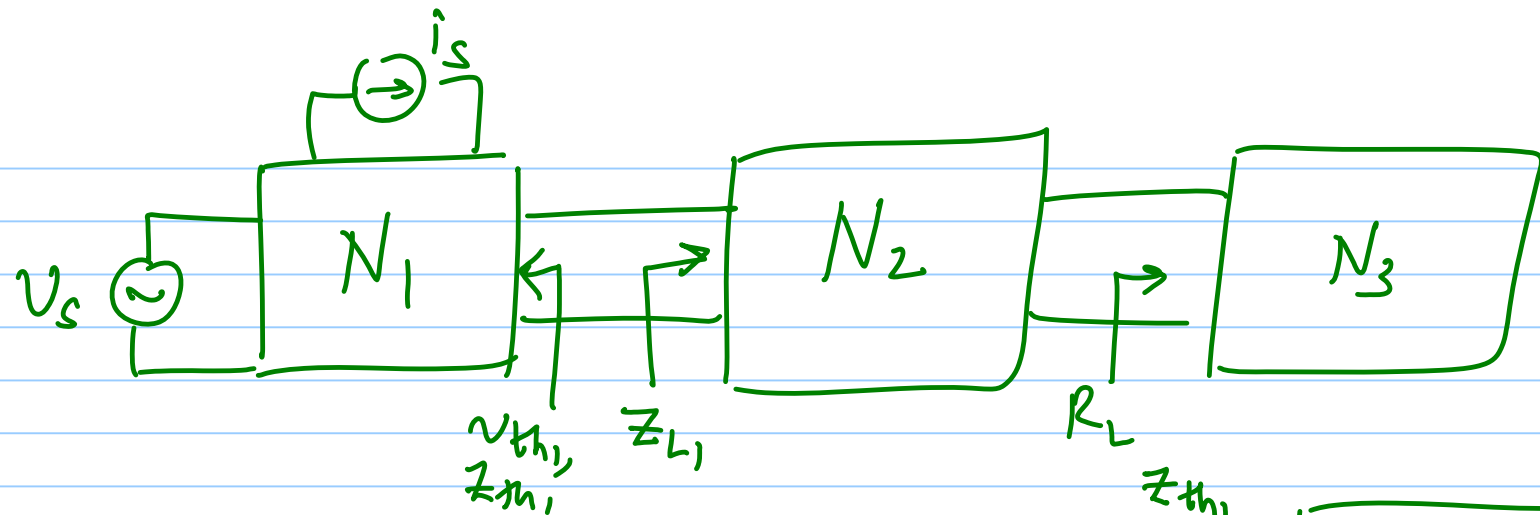

Swing limits

$$v_o = \frac{g_m R_L}{1 + g_m R_L} \cdot v_s$$

$$v_s - v_o = v_s \left[1 - \frac{g_m R_L}{1 + g_m R_L} \right]$$

$$= \frac{v_s \cdot 1}{1 + g_m R_L}$$

$$i_d = g_m (v_s - v_o) = \frac{g_m}{1 + g_m R_L} \cdot v_s$$

$$v_s = V_A \sin \omega t$$

Triode Limit : $V_{DS} = V_{GS} - V_T$

$$V_D - V_S = V_G - V_S - V_T$$

$$V_D = V_G - V_T$$

$$V_{DD} = V_{G1} + V_A \sin \omega t - V_T$$

$$\frac{V_{DD} \cdot R_B}{R_A + R_B}$$

$$V_{A1} = \frac{R_A}{R_A + R_B} \cdot V_{DD} + V_T$$

Cut off limit


$$I_D = I_Q + i_d$$


→ goes to zero

$$0 = I_Q + \frac{g_m}{1 + g_m R_L} \cdot V_{A2} \sin \omega t$$

$$V_{A2} = \frac{I_0 \cdot (1 + g_m R_L)}{g_m}$$

$$V_A = \min \{ V_{A1}, V_{A2} \}$$

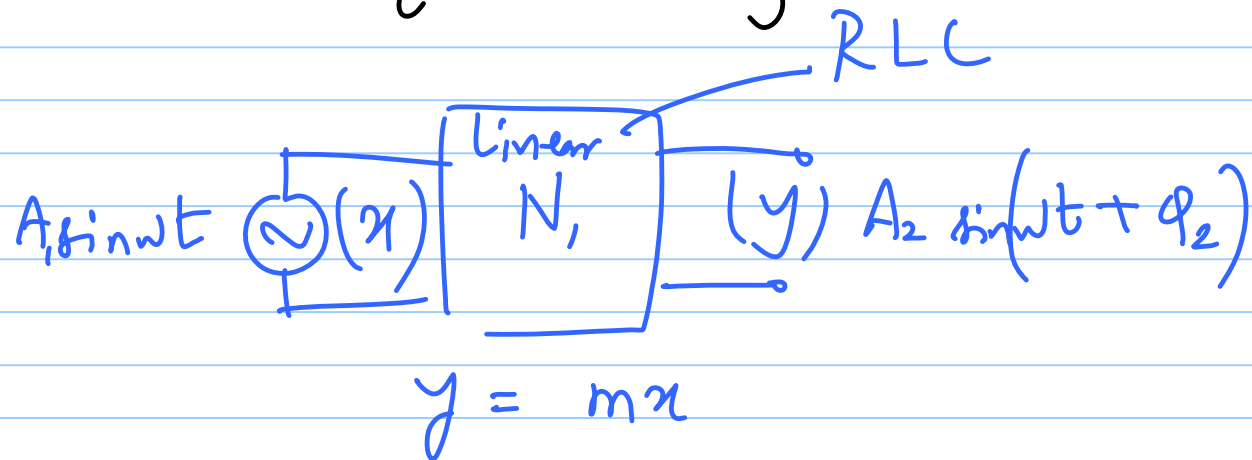

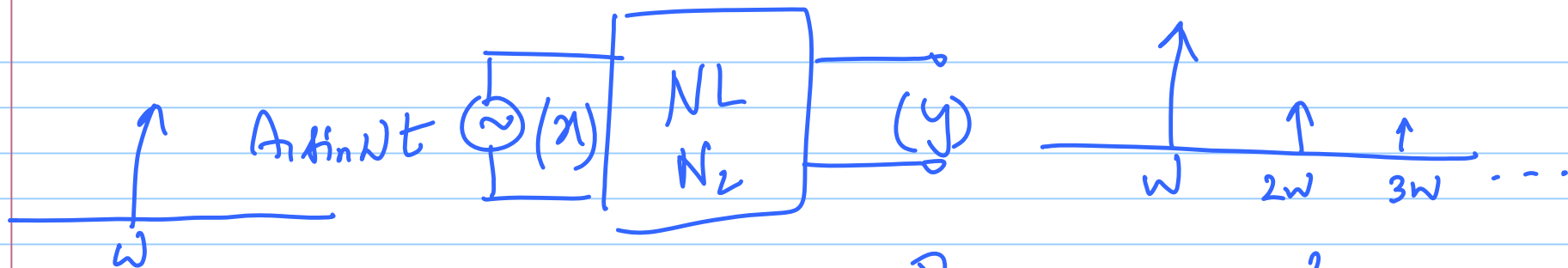

$$y = \cancel{a_0} + a_1 x + a_2 x^2 + \dots$$

incl. VCCS $i_o = \frac{v_{in}}{R}$; $R_{in} = \infty$
 $R_{out} = \infty$

