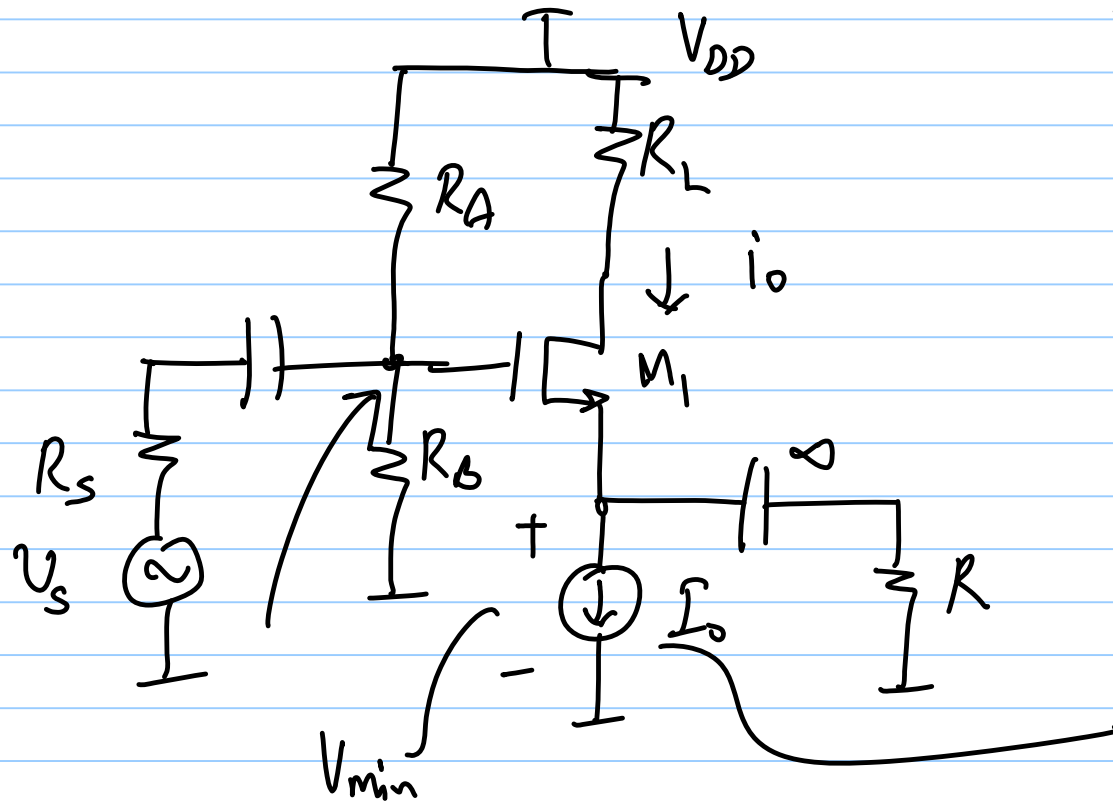


29/8/19

Lec 15




$$V_{G1} = \frac{R_B}{R_A + R_B} \cdot V_{DD}$$


$$\geq V_{min} + V_{GS}|I$$

$$V_{D1} = V_{DD} - I_o R_L$$
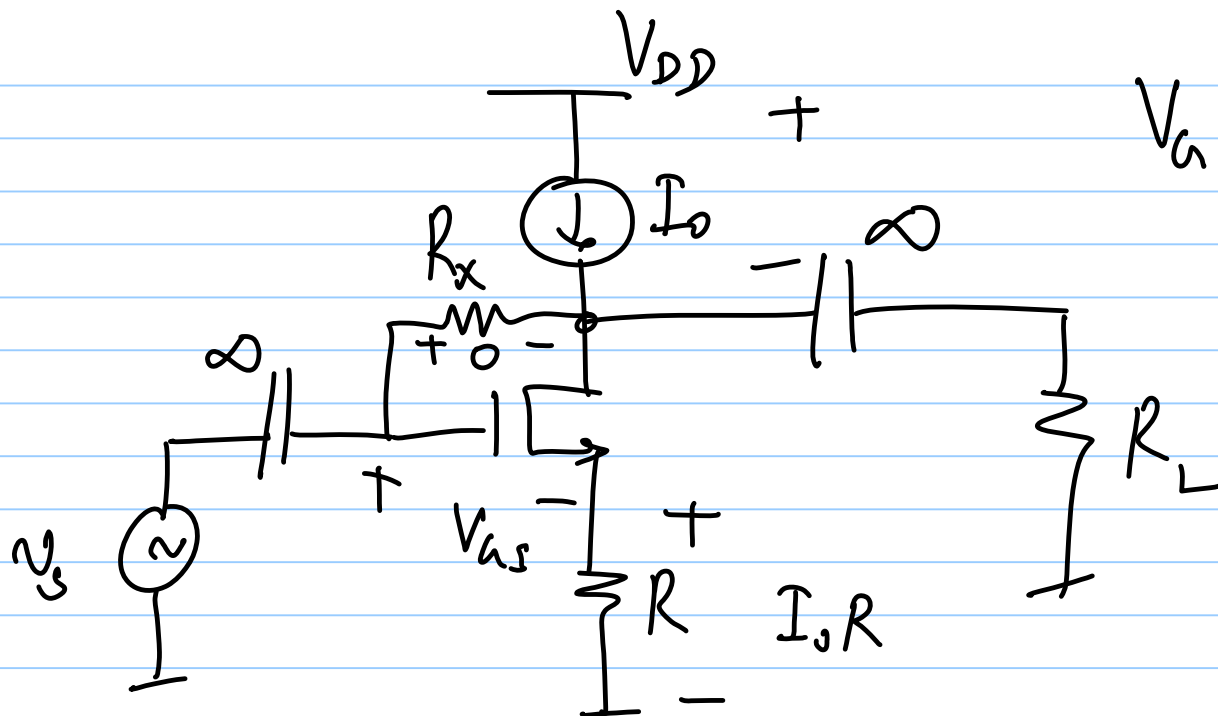
$$V_B \rightarrow \begin{matrix} \downarrow I_o \\ \uparrow M2 \end{matrix} \quad \begin{matrix} \sqrt{R_o = \infty} \\ + \\ V_{min} = V_o - V_T \\ - \end{matrix}$$



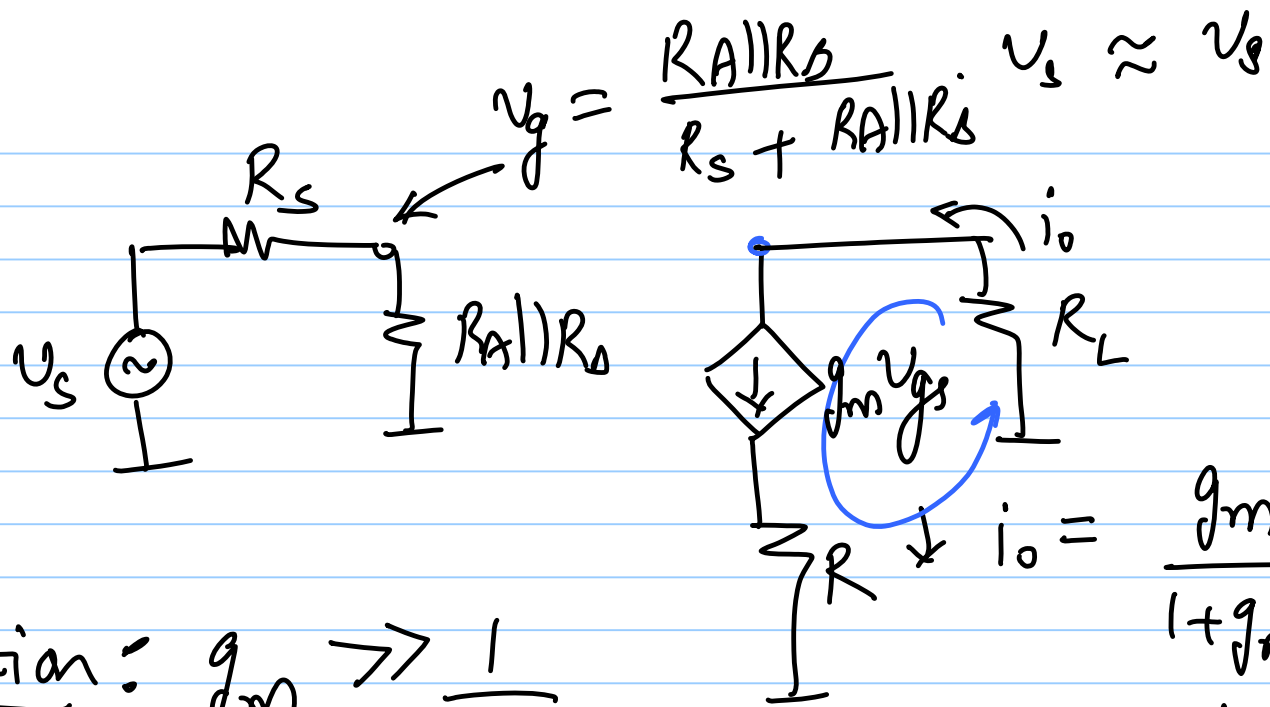
$$V_G = V_D = I_0 R + V_{gs} \quad / \quad I_0$$



Condition: $g_m \gg \frac{1}{R}$
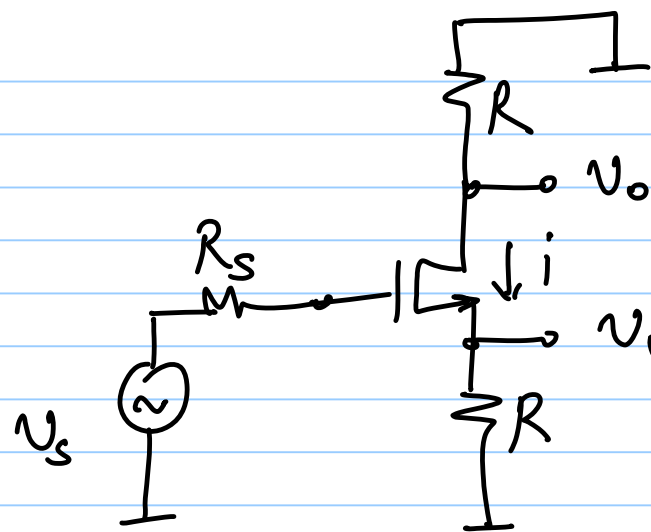
$$\begin{aligned}
 i_o &= \frac{g_m}{1 + g_m R} \cdot v_s \\
 &= \frac{v_s}{R} \cdot \frac{g_m R}{1 + g_m R}
 \end{aligned}$$



$$v_{o2} = - \frac{g_m R}{1 + g_m R} \cdot v_s \approx -v_s$$



$$v_{o1} = \frac{g_m R}{1 + g_m R} \cdot v_s \approx v_s$$


$$i = \frac{g_m}{1 + g_m R} \cdot v_s$$

"Phase splitter"
Circuit

incremental CCCS , $gain = 1$, $R_{in} = 0$

$R_{out} = \infty$

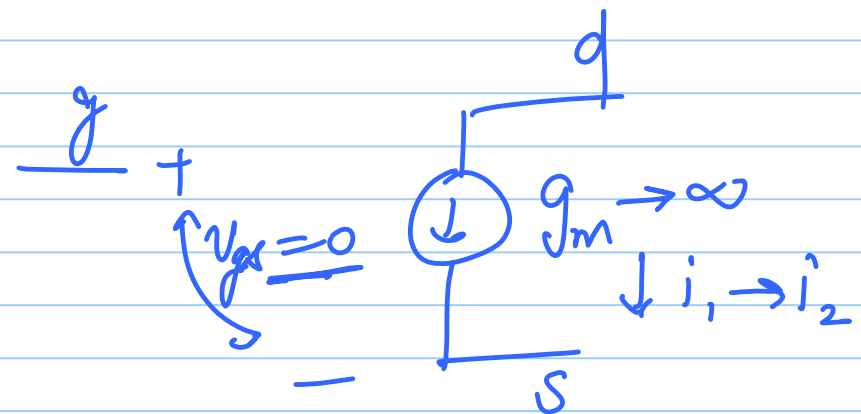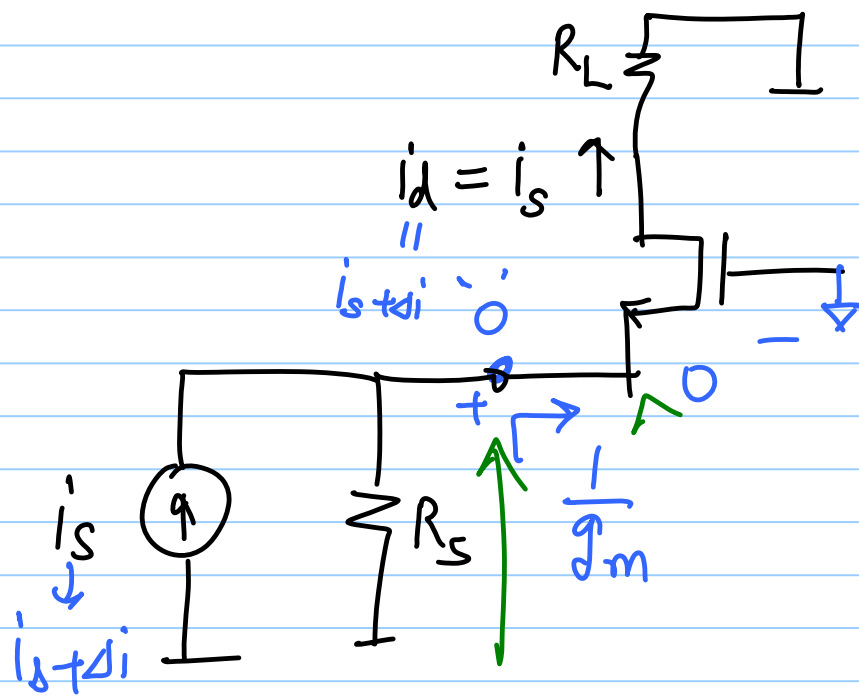

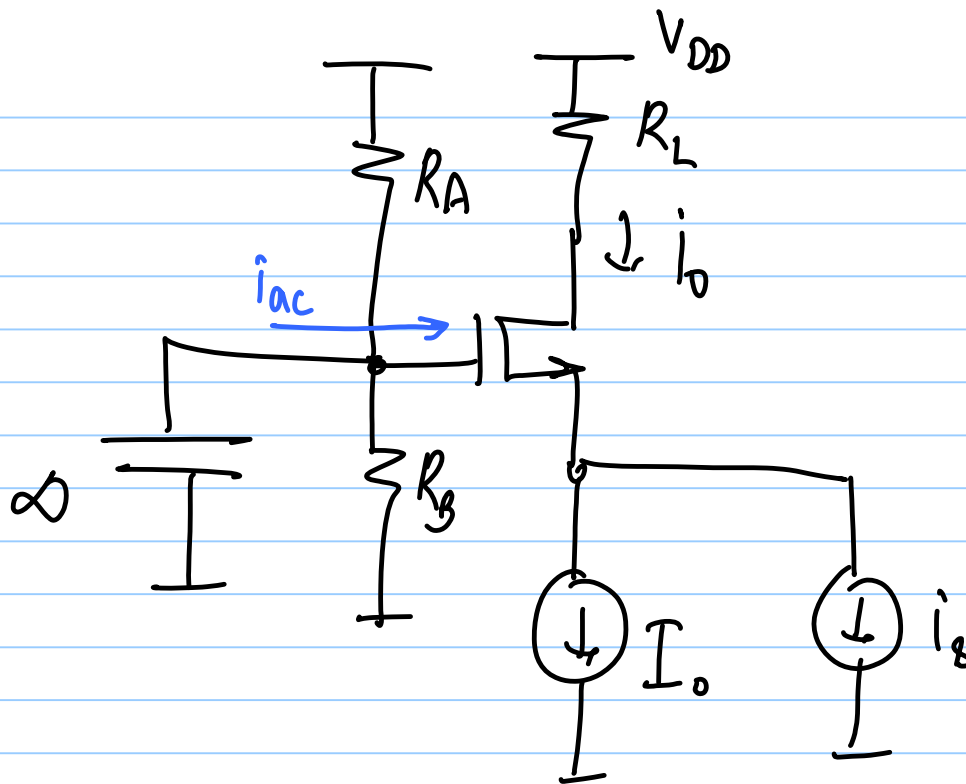

"Common - Gate
Amplifier"