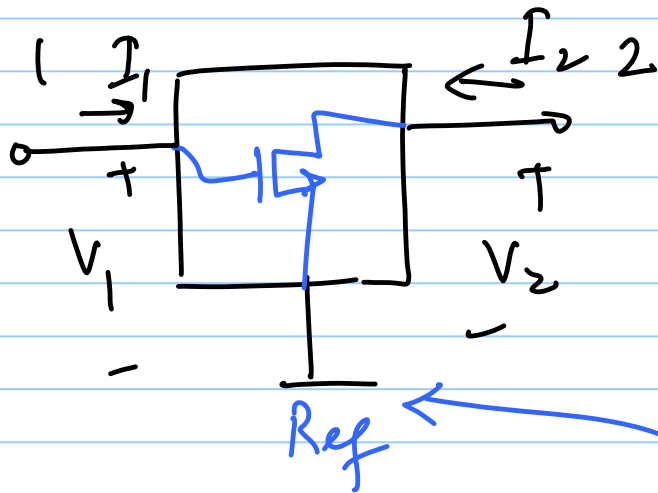



4/9/19



Lec 17




$$I_1 = \text{constant}$$

$$I_2 = f(V_1) \text{ only}$$

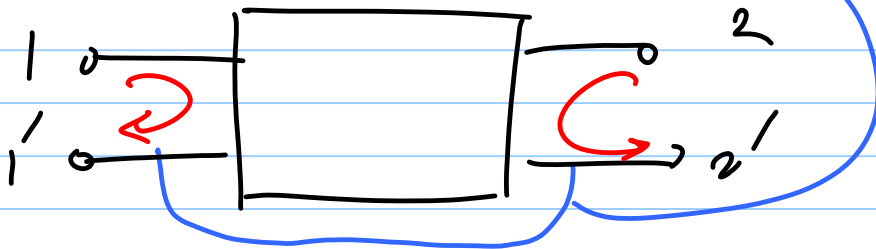


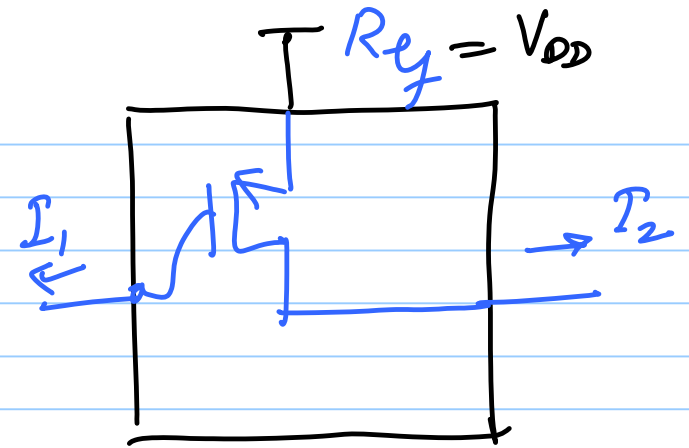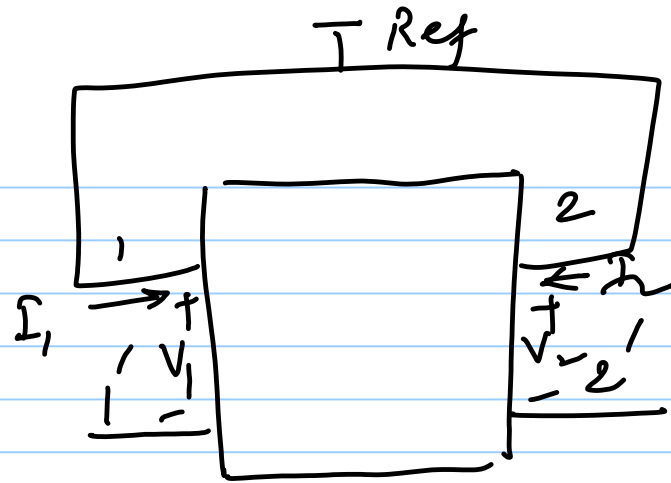

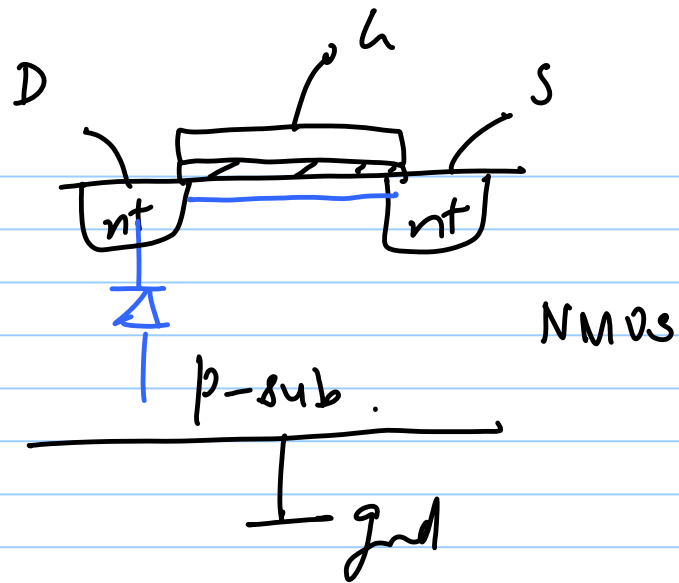
"PMOS" transistor,
p-channel MOSFET, pMOSFET



$$V_G = V_{DD} - V_{Tp}$$

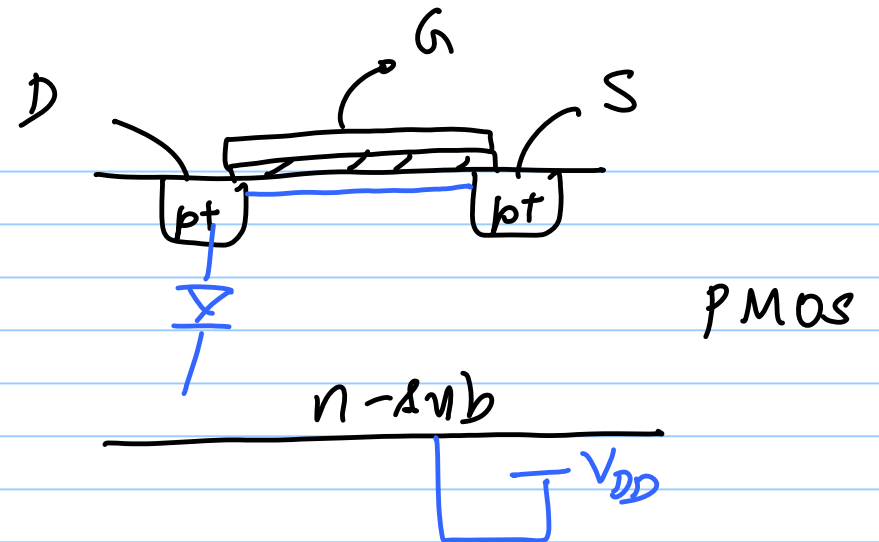

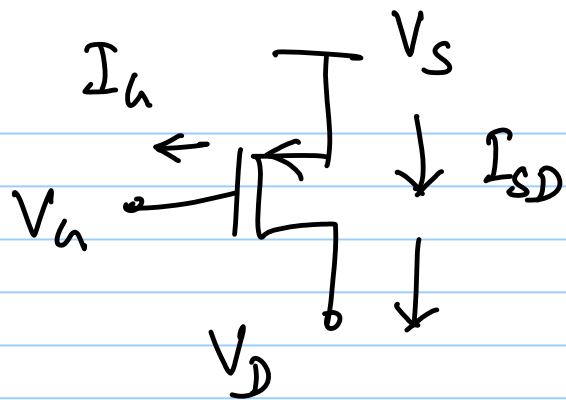Cut off: $V_{sa} \leq V_{Tp} \therefore I_{sd} = 0$



$$I_G = 0$$

$$I_S = I_D$$

V_{TP} is positive

Sat: $V_{SD} \geq V_{SG} - V_{TP}$

or
 $V_D \leq V_G + V_{TP}$

$$V_{SG} \leq V_{TP} : I_{SD} = 0 \Rightarrow \text{Cutoff}$$

$$V_{SG} \geq V_{TP} : I_{SD} = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L} \right) (V_{SG} - V_{TP})^2 (1 + \lambda_p V_{SD})$$

(saturation)

$$'' : I_{SD} = \mu_p C_{ox} \left(\frac{W}{L} \right) \left[(V_{SG} - V_{TP}) \cdot V_{SD} - \frac{V_{SD}^2}{2} \right] \text{ (triode)}$$