

6/9/19

Lec 18

NMOSFET

- * I_D flows into (D)
- * Sat: $V_D \gg V_S$
- * Tri limit: $V_D = V_G - V_{Tn}$
- * $V_{GS} \geq V_{Tn}$ for $I_D \geq 0$
- * $V_{Tn} > 0$ for enh. mode

PMOS transistor


- * I_D flows out of (D)
- * Sat: $V_D \ll V_S$
- * Tri limit: $V_D = V_G + V_{Tp}$
- * $V_{SG} \geq V_{Tp}$ for $I_D \geq 0$
- * $V_{Tp} > 0$ for enh. mode

$V_{Tn}, V_{Tp} > 0$: enhancement mode MOSFETs

$V_{Tn}, V_{Tp} < 0$: depletion mode MOSFETs

Small-signal :
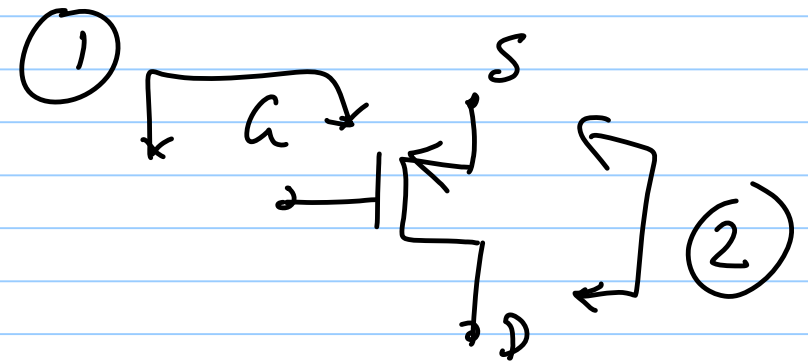
$$[y] = \begin{bmatrix} 0 & 0 \\ g_m & g_{ds} \end{bmatrix}$$





$$y_{21} = g_{mp} = \mu_p C_{ox} \left(\frac{W}{L}\right)_p (V_{sgp} - V_{Tp}) = \frac{\partial I_{SD}}{\partial V_{sg}} = \frac{\partial I_{DS}}{\partial V_{gs}}$$



$$y_{22} = g_{dsp} = \lambda_p I_D$$


$$\text{intrinsic gain} = \frac{g_{mp}}{g_{dsp}}$$

same as that
for NMOS

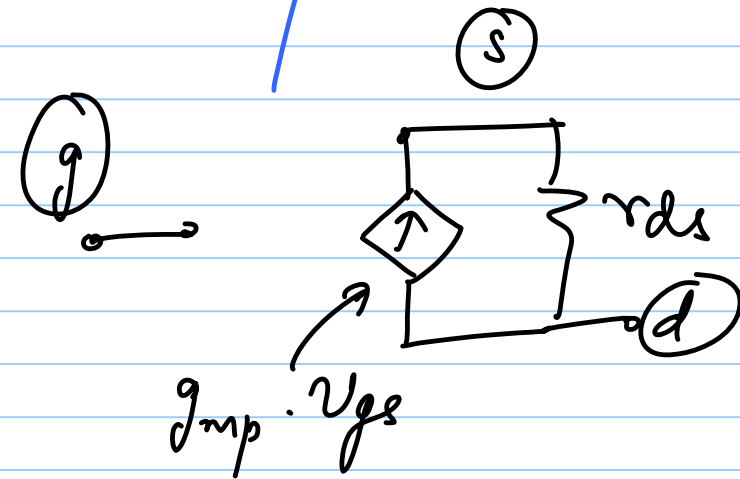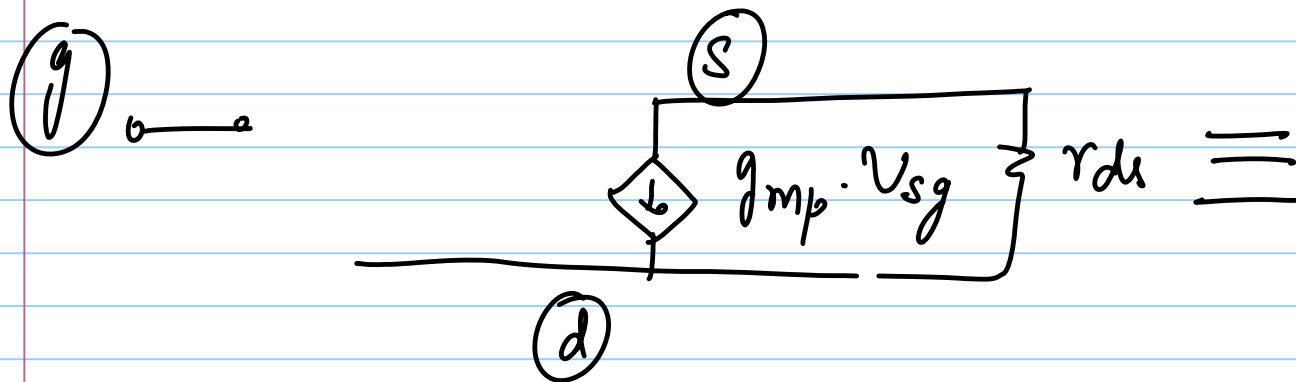

PMOS CSA

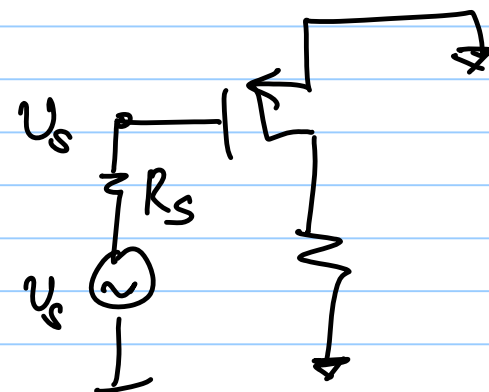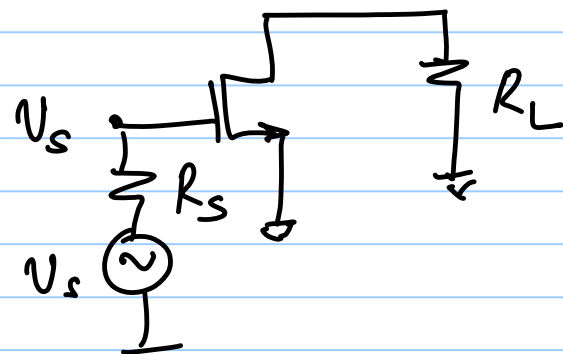

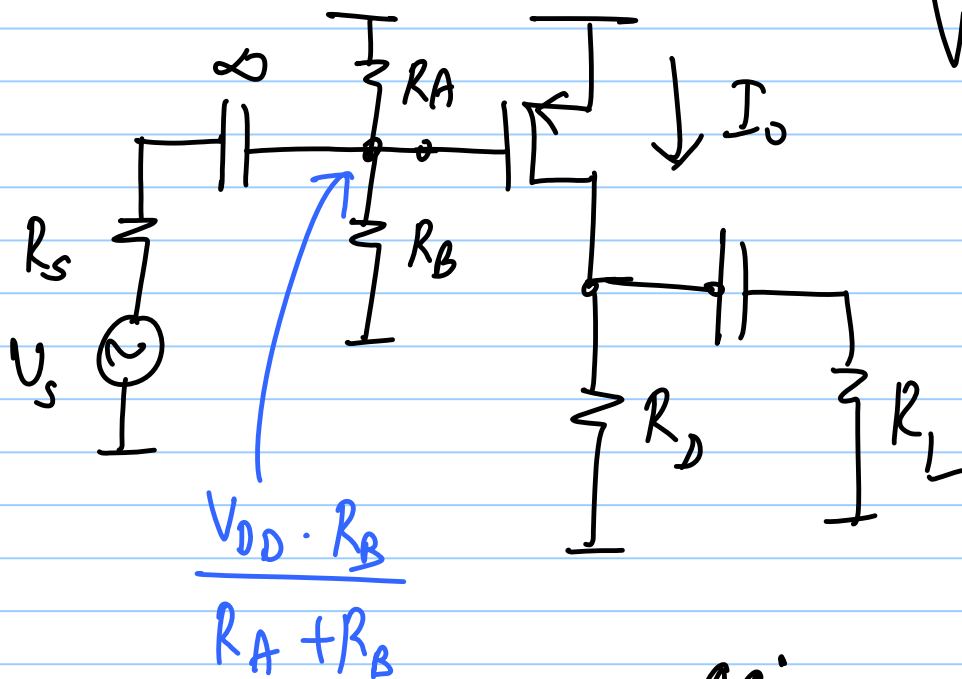

$$V_{SG} = \frac{V_{DD} \cdot R_A}{R_A + R_B} \Rightarrow I_O$$

$$R_A || R_B \rightarrow R_S$$

$$V_D = I_O \cdot R_D$$

$$\text{gain} = -g_{m_p} (R_D || R_L || r_{ds_p})$$

HW: swing limits

