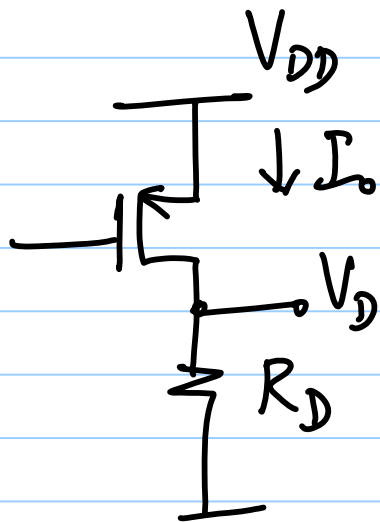


13/9/19

Lec 20




$$\text{incr. gain} = -g_{m_p} \cdot R_D$$

↑ gain

① $\uparrow R_D \Rightarrow V_D \uparrow \Rightarrow \text{PMOS goes towards triode}$

② $\uparrow I_D \Rightarrow V_D \uparrow \dots$

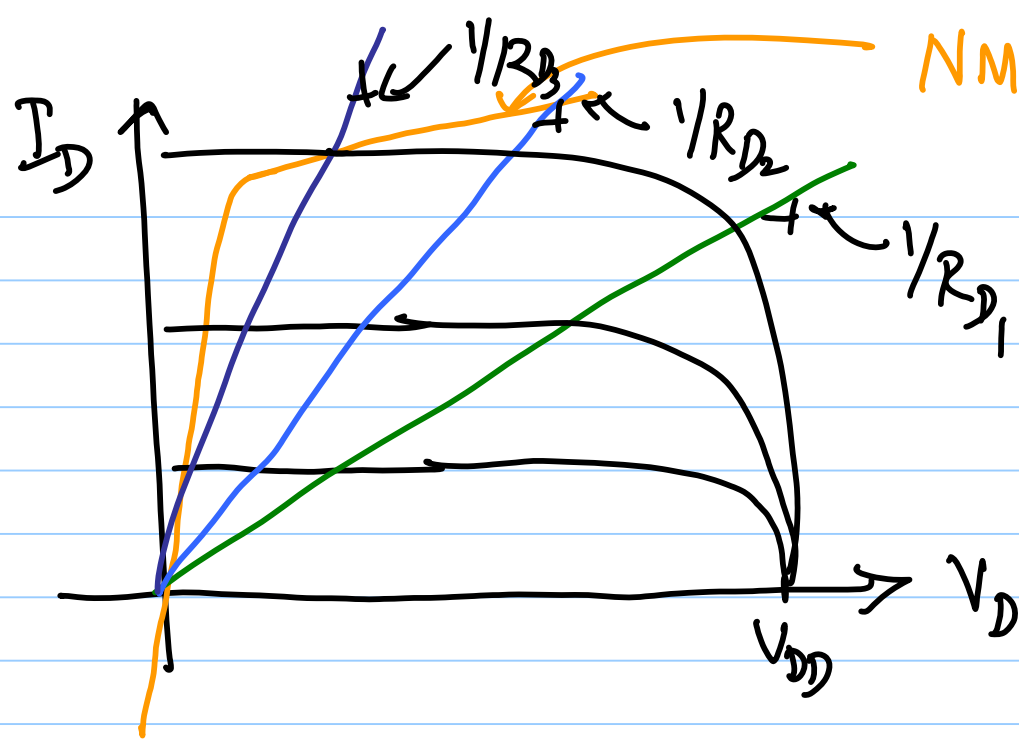
③ $\uparrow \left(\frac{W}{L}\right) \Rightarrow (V_{as} - V_T) \downarrow \Rightarrow \text{PMOS moves away from square law; slower circuit}$




NMOS device char.

$$V_D = I_D \cdot R_D$$


$$R_{D1} > R_{D2} > R_{D3}$$

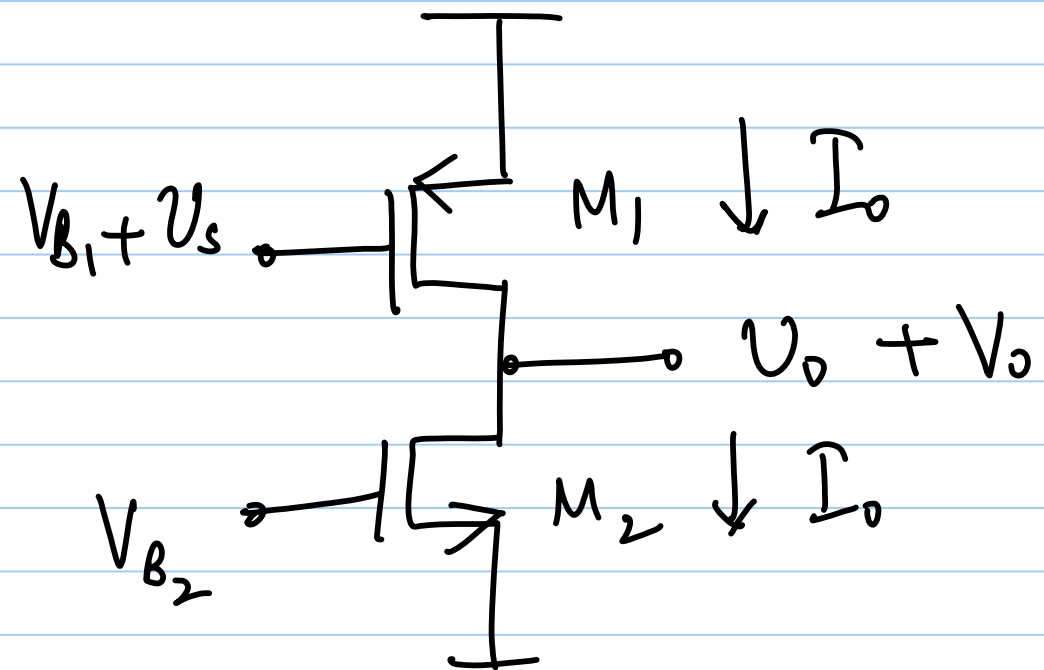


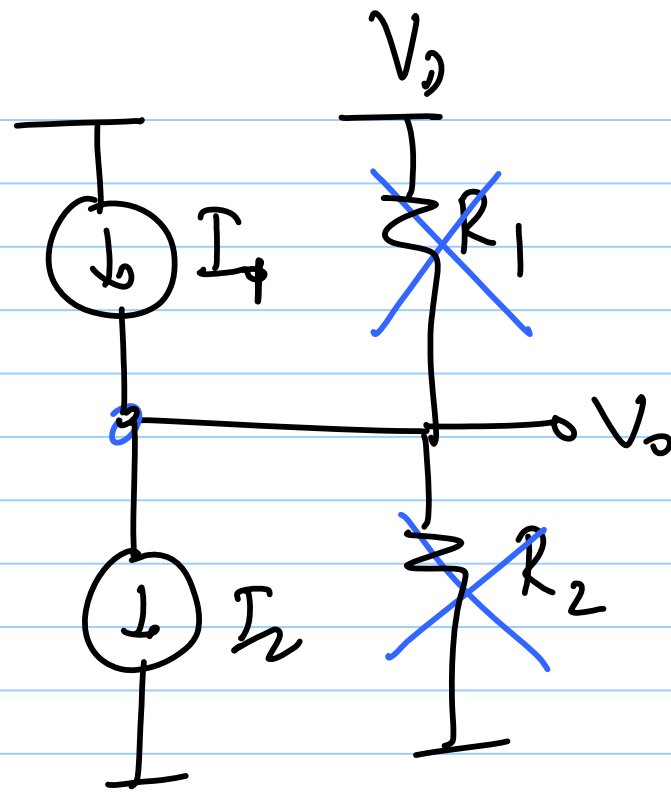



~~$$I_1 = m_1 \cdot V_0 + C_1$$~~


~~$$I_2 = m_2 V_0 + C_2$$~~

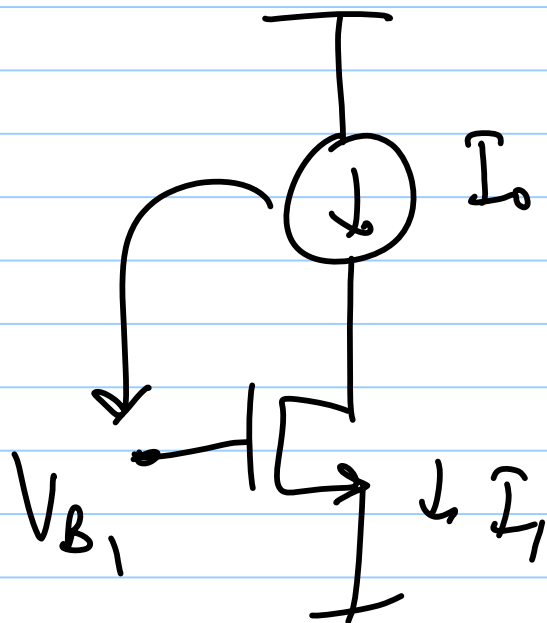

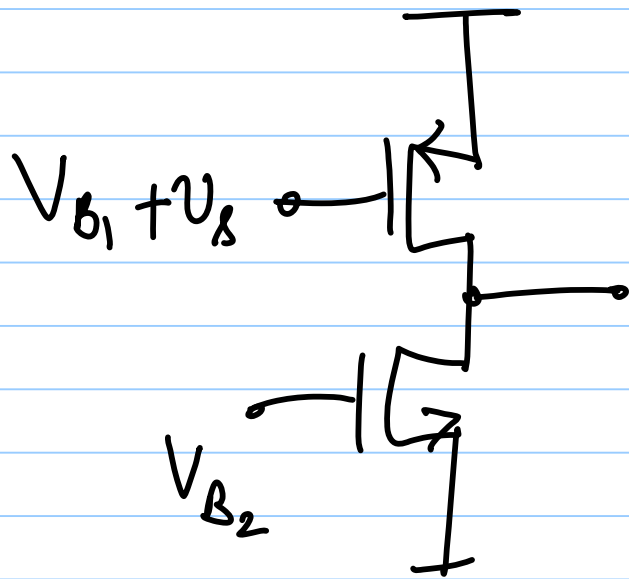

$$\frac{v_o}{v_s} = -g_{mp}(r_{ds_p} || r_{ds_n})$$

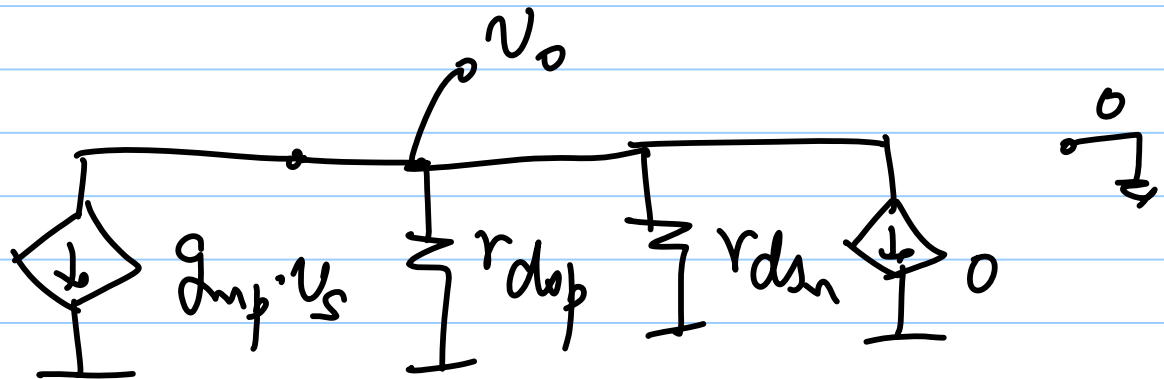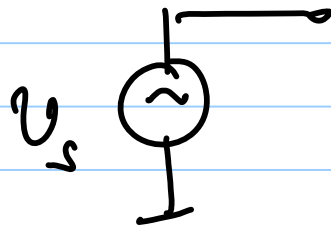

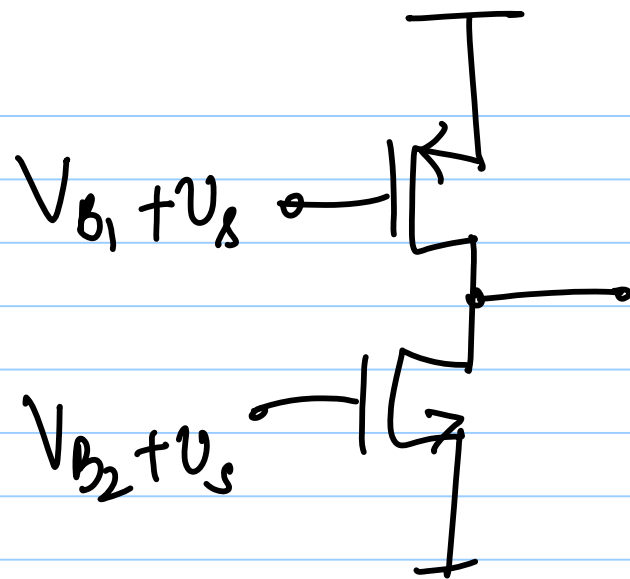

$$\frac{v_o}{v_s} = -(g_{m_n} + g_{m_p}) \cdot (r_{ds_n} \parallel r_{ds_p})$$

