
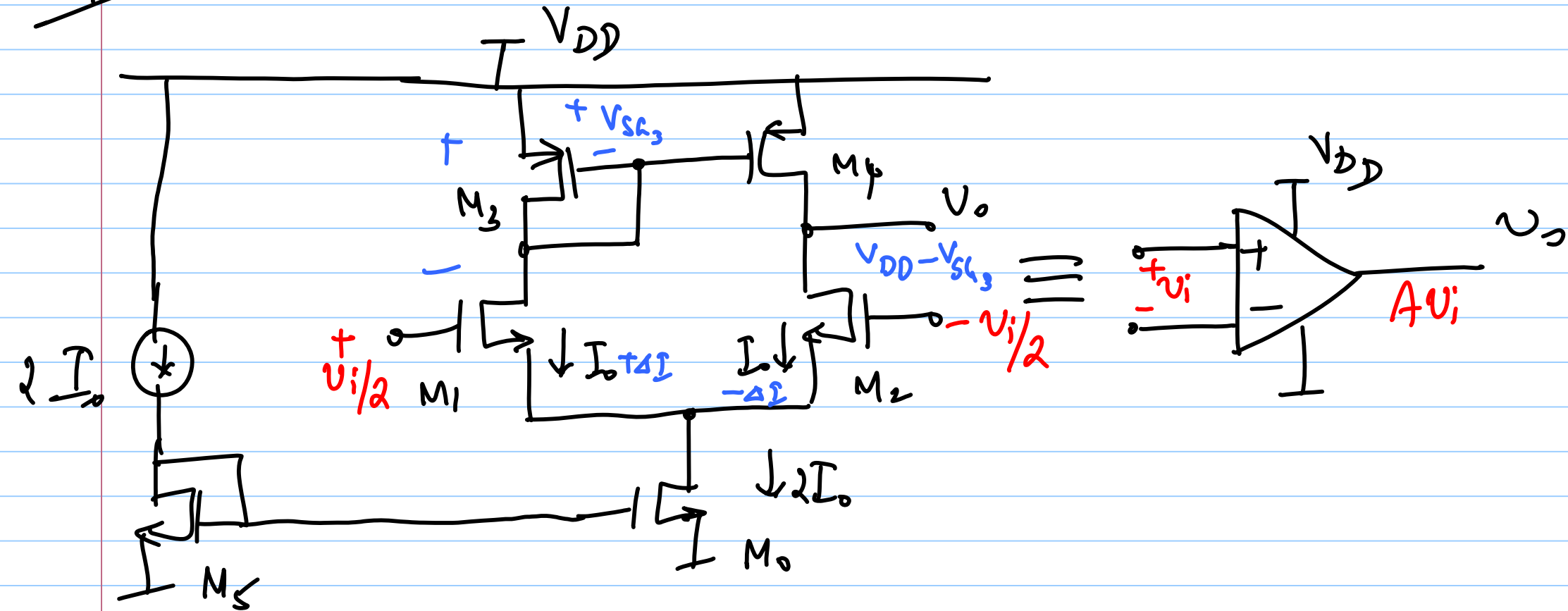


Note Title

Lec 24

21-Sep-19

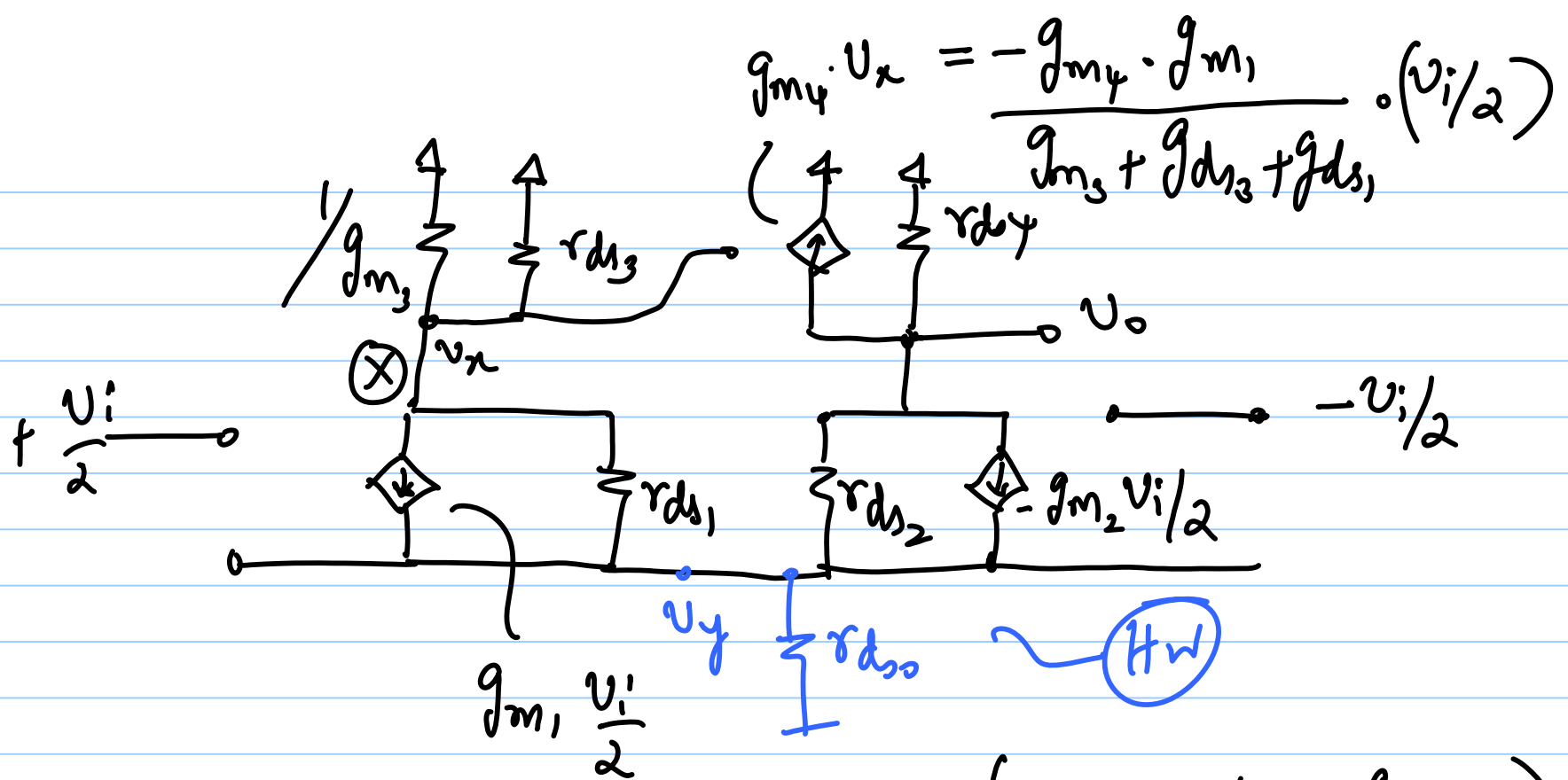






$$g_{m4} \cdot v_x = \frac{-g_{m4} \cdot g_{m1}}{g_{m3} + g_{ds3} + g_{ds1}} \cdot (v_i/2)$$

$$v_x = \frac{-g_{m1} \cdot (v_i/2)}{g_{m3} + g_{ds3} + g_{ds1}}$$

$$v_o = \frac{(+g_{m2}v_i/2 - g_{m4}v_x)}{g_{ds2} + g_{ds4}}$$

$$v_o = \frac{v_i}{2} \cdot \frac{1}{(g_{ds2} + g_{ds4})} \cdot \left\{ g_{m2} + \frac{g_{m4} \cdot g_{m1}}{g_{m3} + g_{ds3} + g_{ds1}} \right\}$$
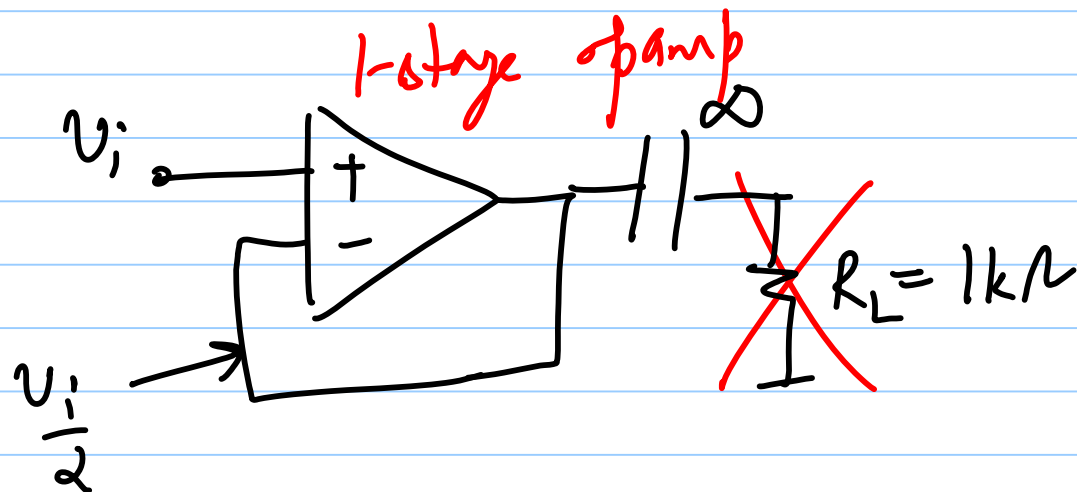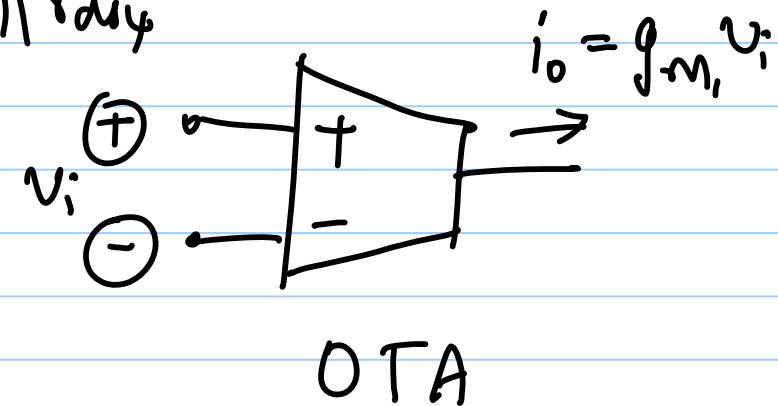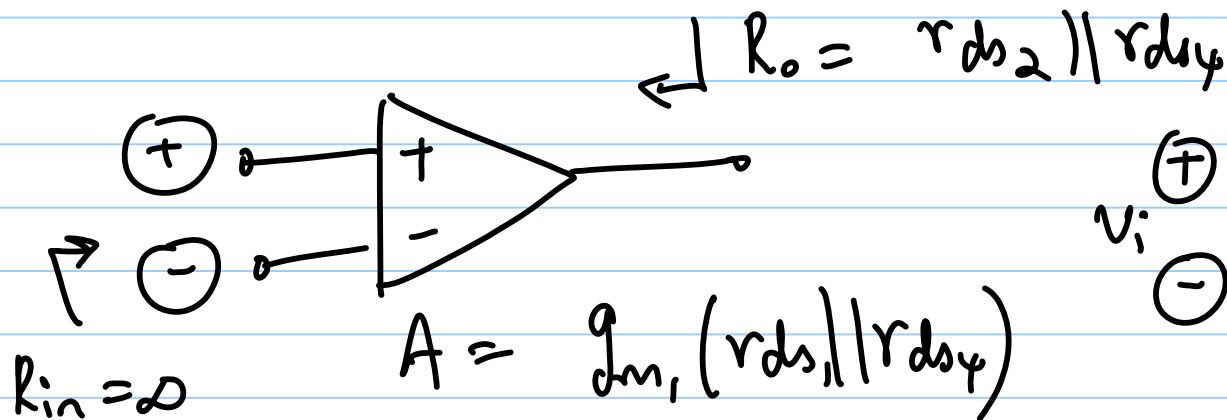
$$\frac{v_o}{v_i} \approx \frac{g_{m1}}{g_{ds2} + g_{ds4}} \approx g_{m1} (r_{ds2} \parallel r_{ds4})$$




$$r_{ds2} \parallel r_{ds4} = 100k\Omega$$

$$g_{m1} = 1mS$$

$$A = 100$$

$$\hookrightarrow A \rightarrow 1$$

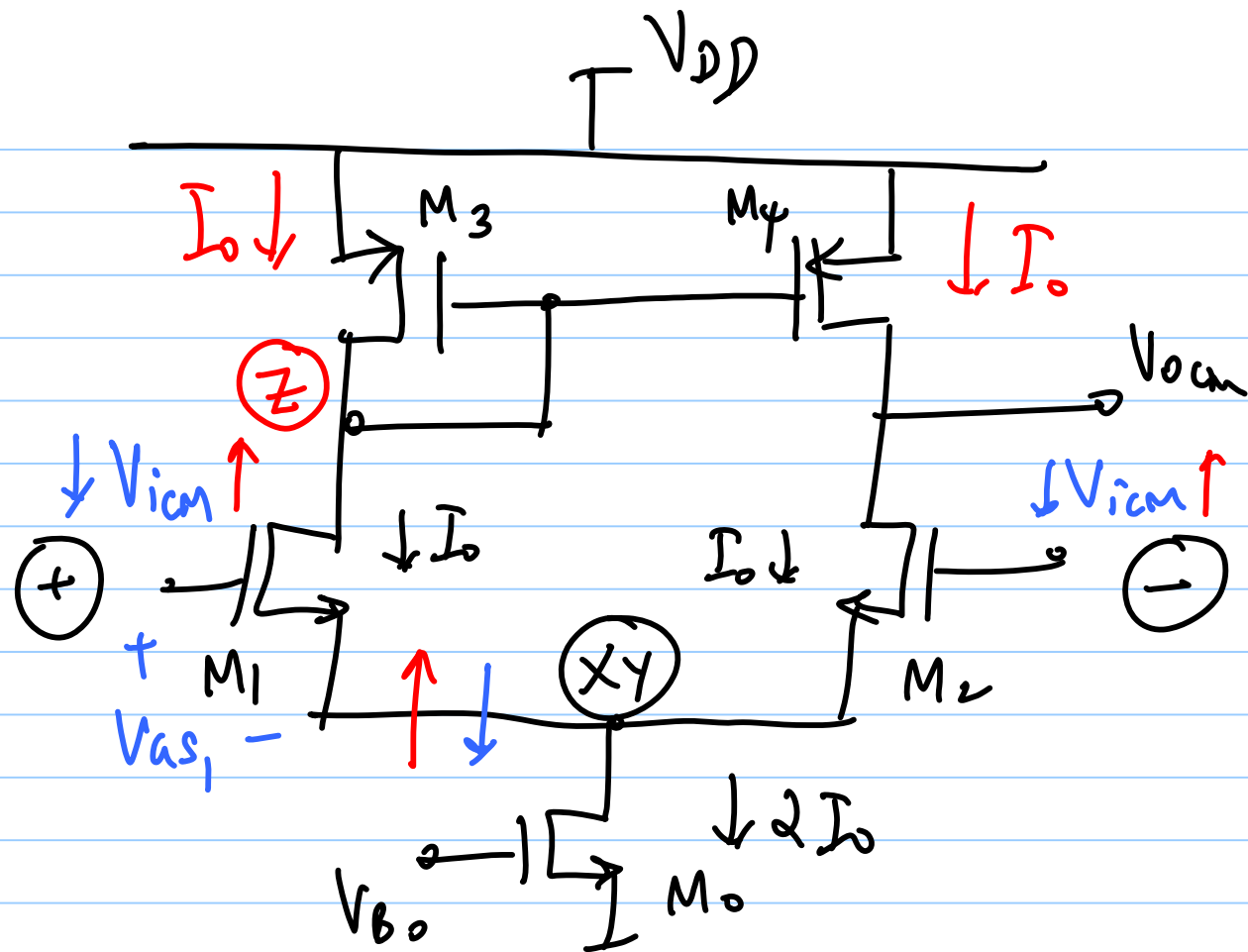

@ $V_{xy} = V_{DD} - V_{T0}$,
 M_0 goes into
 triode

$V_{as,2}$ — stays the same as long as M_0 is in sat.

V_{xy} — follows V_{icm}

$$V_{xy} = V_{icm} - V_{as,1}$$

@ edge of M_0 triode:

$$\text{min. } V_{icm} = V_{as,1} + V_{Dsat,0}$$

I_0 $2I_0$

$V_{Dsat} = V_{as} - V_T$

$$V_Z = V_{DD} - V_{S_{G_3}} \Big|_{I_0}$$

as $V_{icm} \uparrow \Rightarrow M_1$ goes closer to triode

$V_{icm \max}$:

$$V_{DS} = V_{GS} - V_T$$

$$\cancel{V_D} - \cancel{V_S} = \cancel{V_G} - \cancel{V_S} - V_T$$


$$V_{D_1} = V_{G_1} - V_{T_1}$$


$$V_{DD} - V_{S_{G_3}} \Big|_{I_0} = V_{icm} - V_{T_1}$$


$$\max V_{icm} = V_{DD} - V_{S_{G_3}} \Big|_{I_0} + V_{T_1}$$


$$ICMR = \{ V_{icm_{min}}, V_{icm_{max}} \}$$


input common-mode range

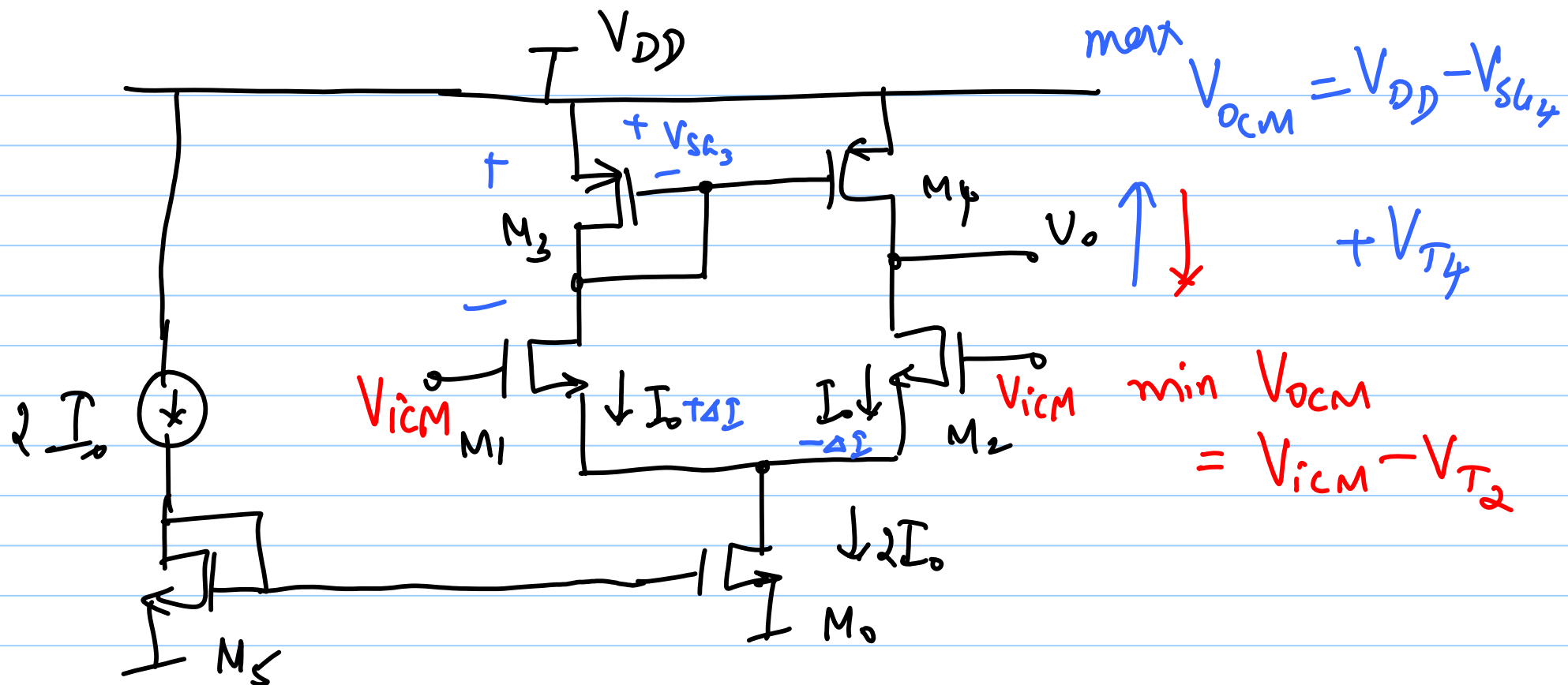

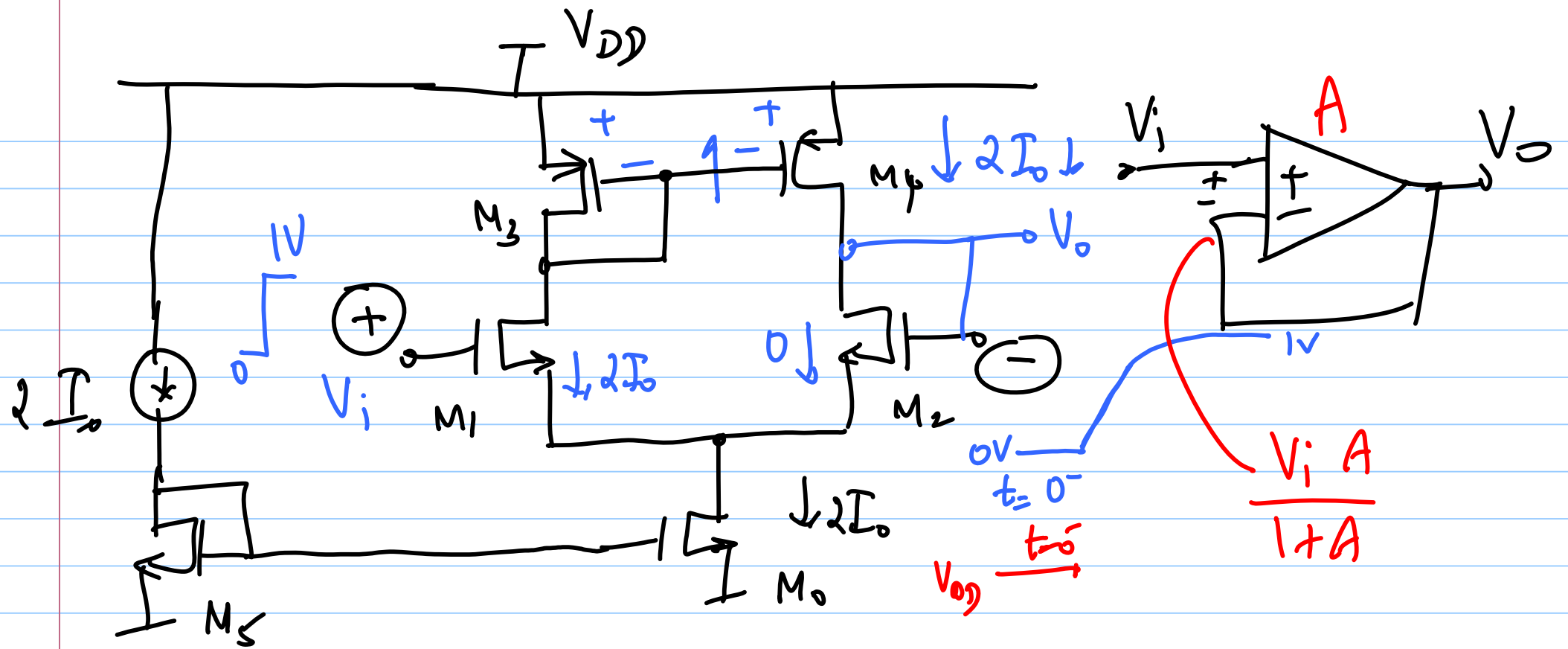

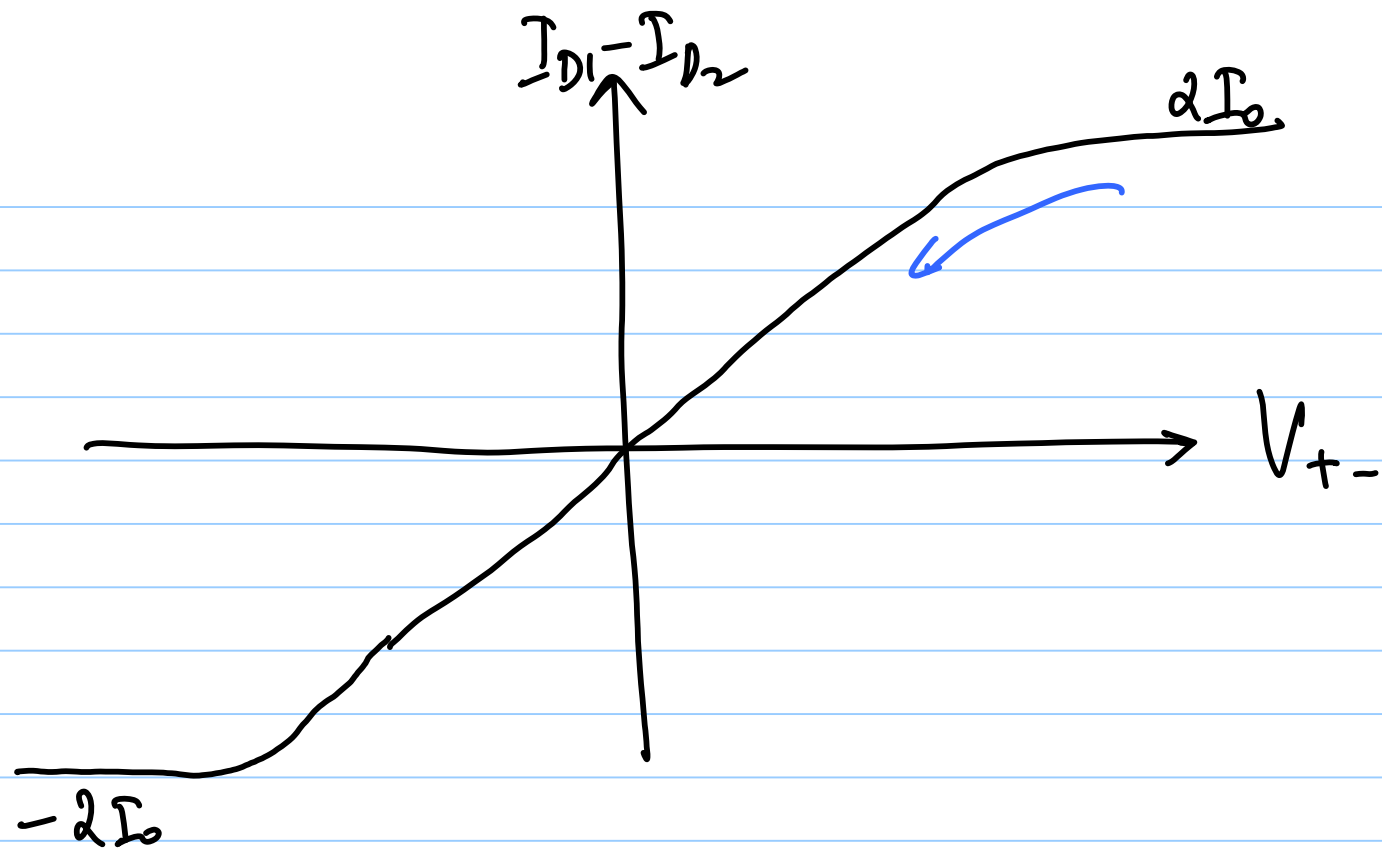

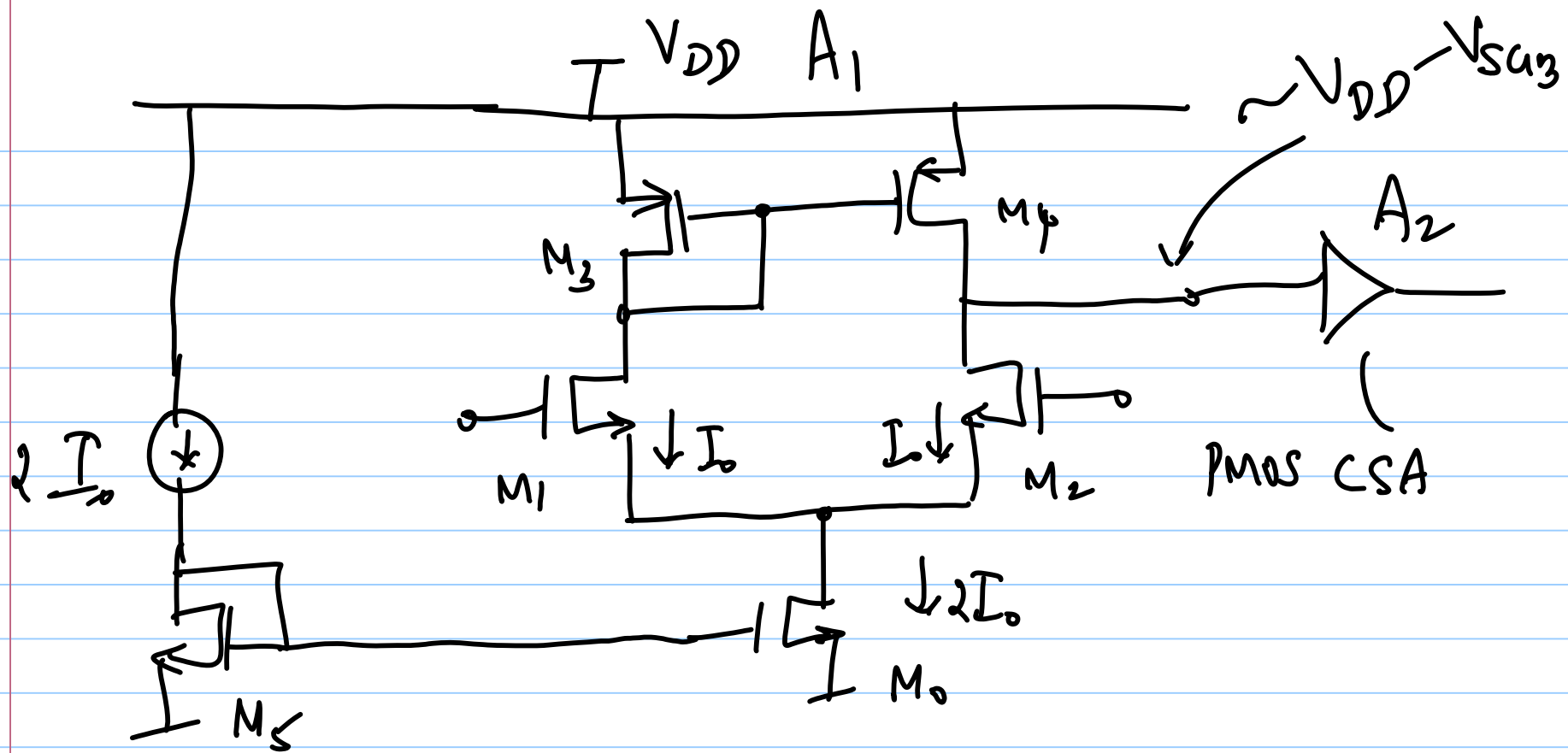

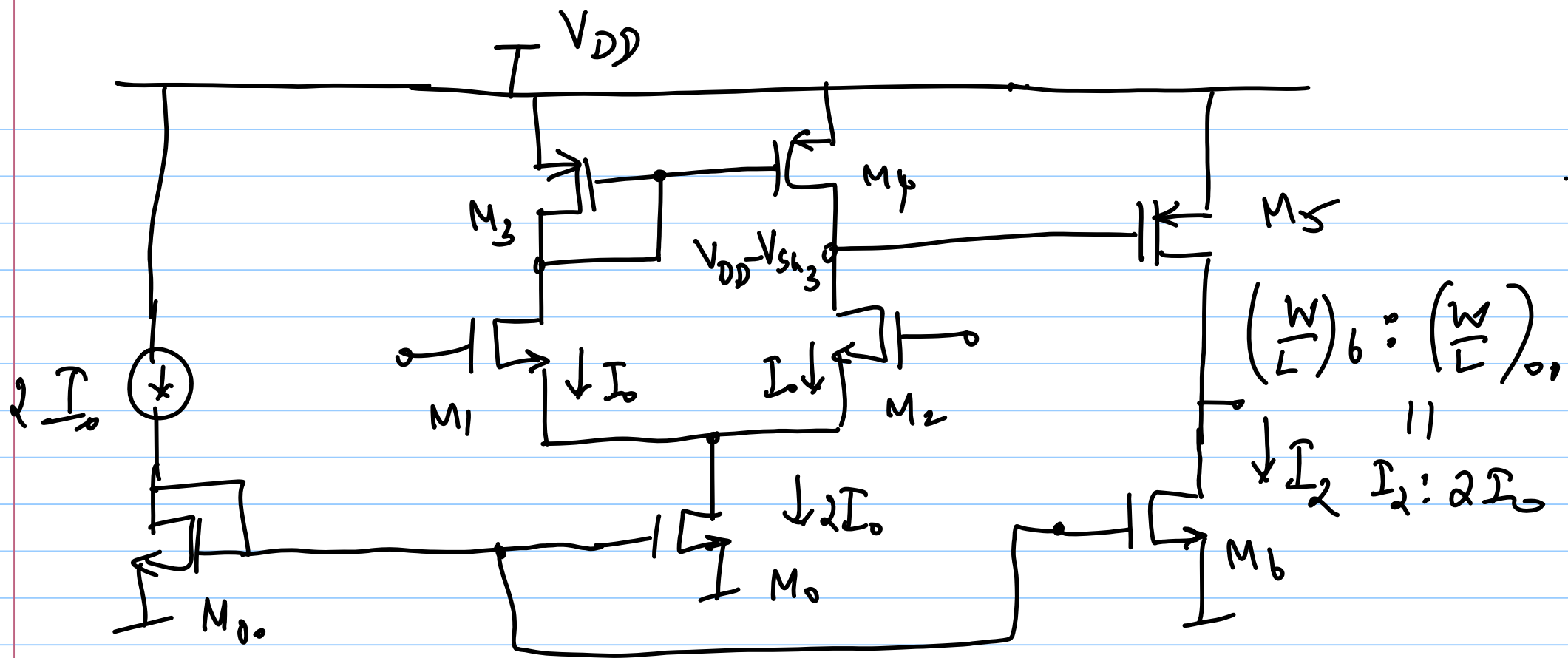

"Two stage opamp"

$$V_{DD} - V_{SG_3} \Big|_{I_0} \equiv V_{DD} - V_{SG_5} \Big|_{I_2}$$

$$V_{SG_3} \Big|_{I_0} = V_{SG_5} \Big|_{I_2}$$

$$\boxed{\frac{I_0}{(W/L)_3} = \frac{I_2}{(W/L)_5}}$$

M_3, M_4, M_5
have same
"current densities"