
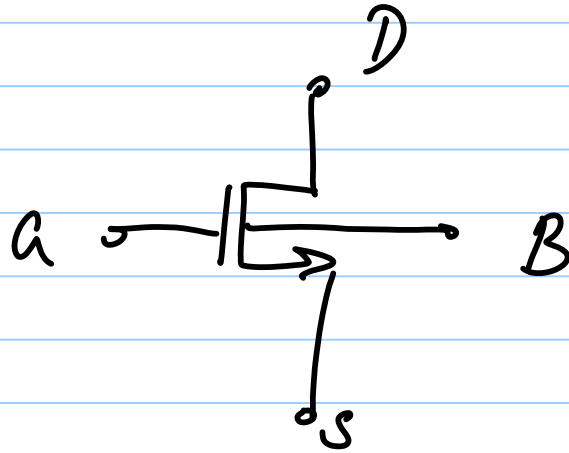



25/9/19

Lec 26

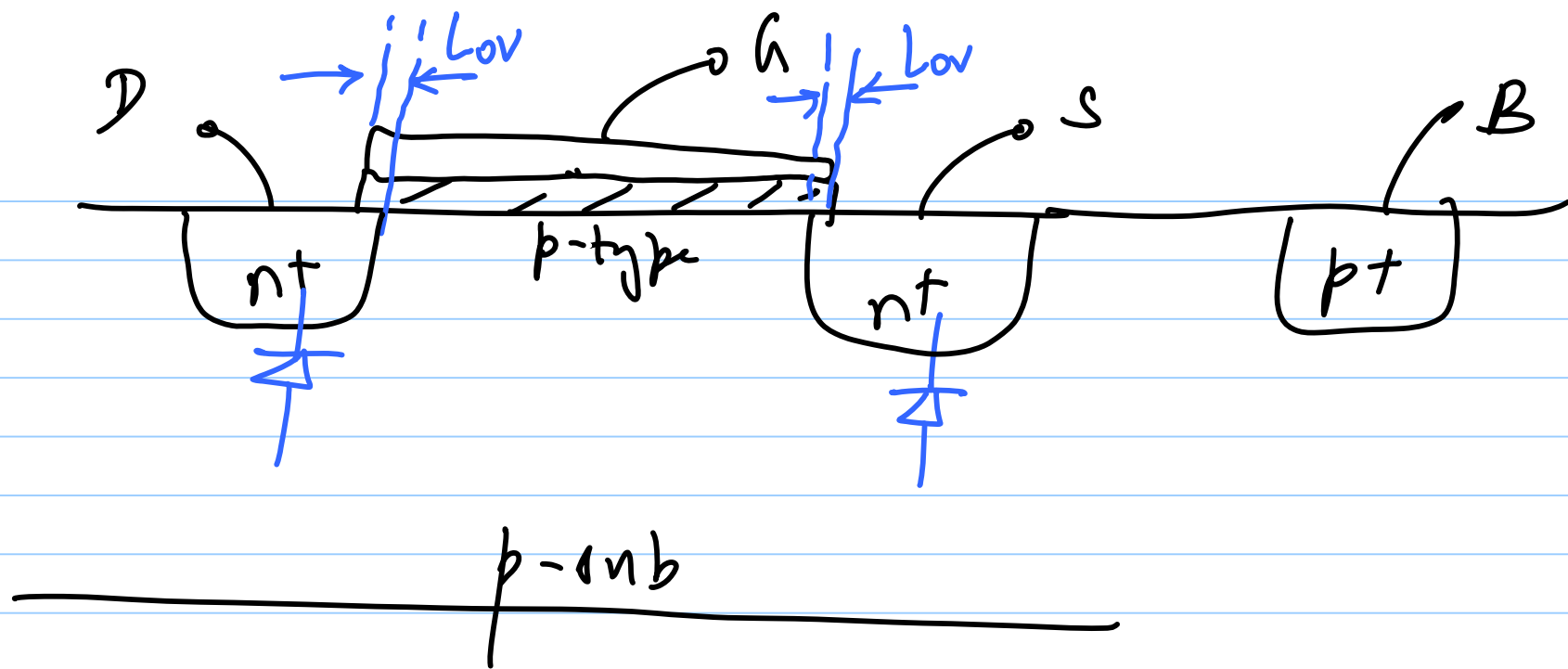


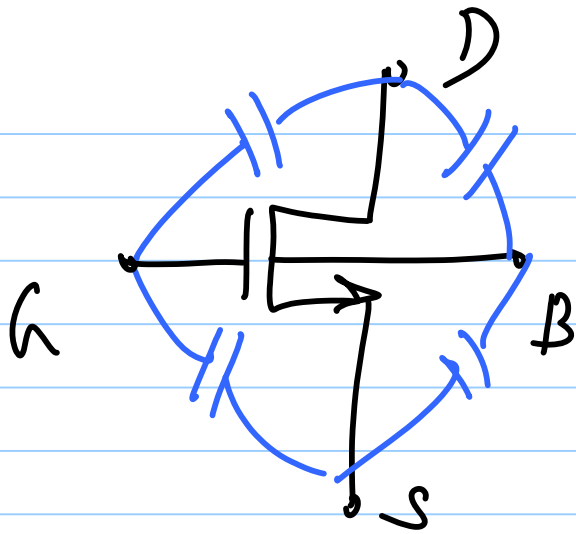C_{gs} , C_{gd} , C_{gb}
 C_{db} , C_{sb}







Triode
caps

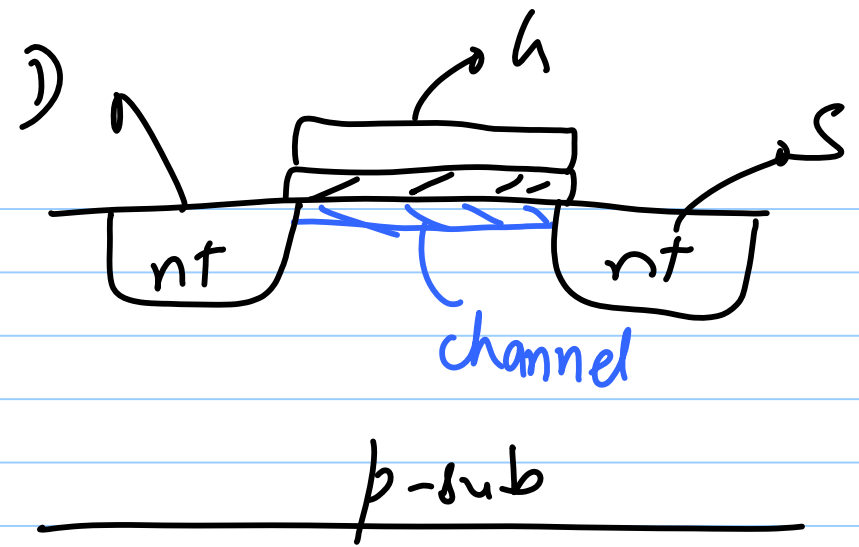

$$C_{gd} = C_{gs} = \frac{1}{2} W \cdot L \cdot C_{ox} = \frac{1}{2} C_{gch}$$



C_{db}, C_{sb}

Saturation region cap.

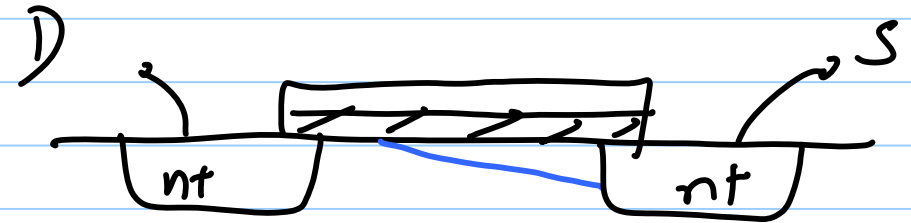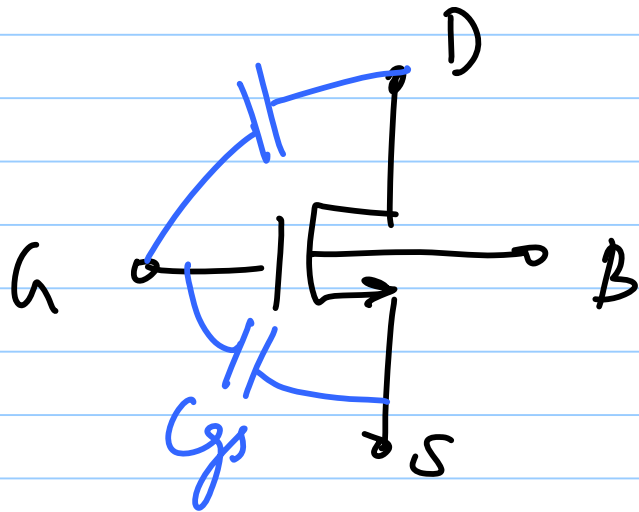

$$C_{gs} = \frac{2}{3} W L \epsilon_{ox} ; C_{gd} = W L_{ov} \epsilon_{ox} ; C_{db}, C_{sb}$$

$$R_A \parallel R_B \gg R_S$$

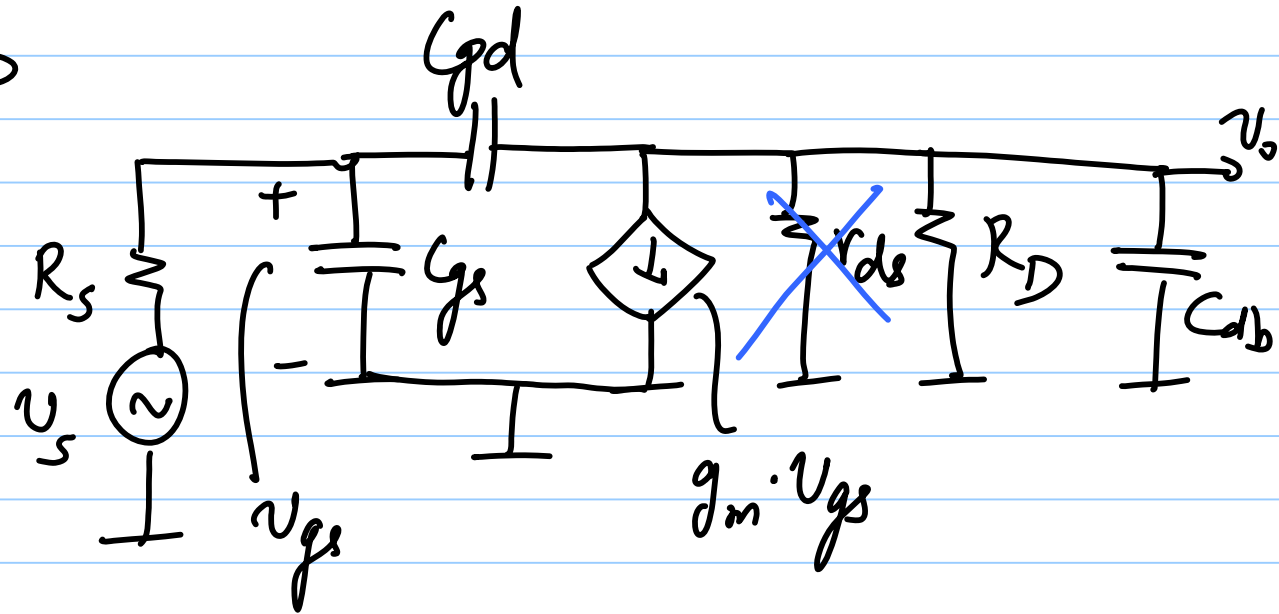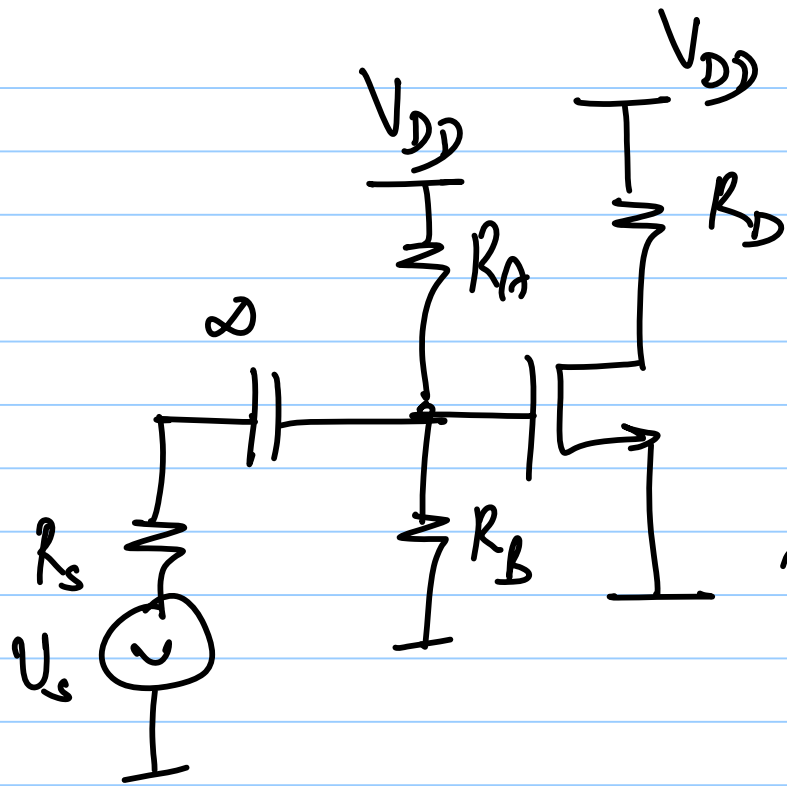


$$\frac{v_o}{v_s} = \frac{(sC_{gd} - g_m)}{\frac{1}{R_D} + s \left[C_{db} + \frac{R_s}{R_D} (C_{gs} + C_{gd}) + C_{gd} + R_s g_m C_{gd} \right] + s^2 \left[(C_{gs} + C_{gd})(C_{db} + C_{gd}) - C_{gd}^2 \right] \cdot R_s}$$

Low freq. gain = $-g_m R_D$

$$\frac{v_o}{v_s} = \left(\text{DC gain} \right) \frac{(1 + s/\omega_z)}{\left(1 + \frac{s}{\omega_{p1}} \right) \left(1 + \frac{s}{\omega_{p2}} \right)}$$

HW

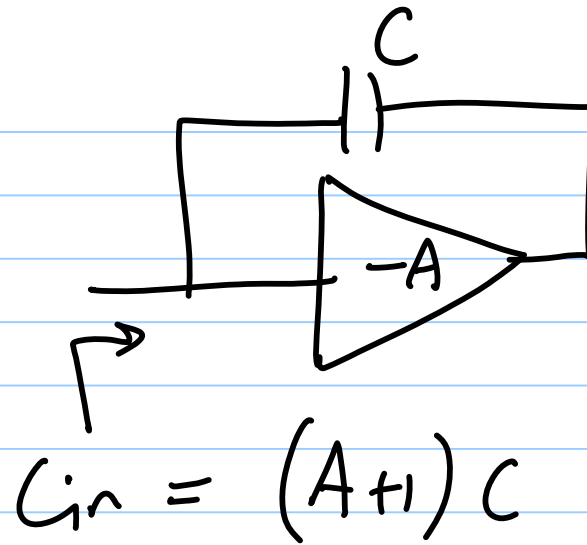

here $A = g_m R_D$
 $C = C_{gd}$