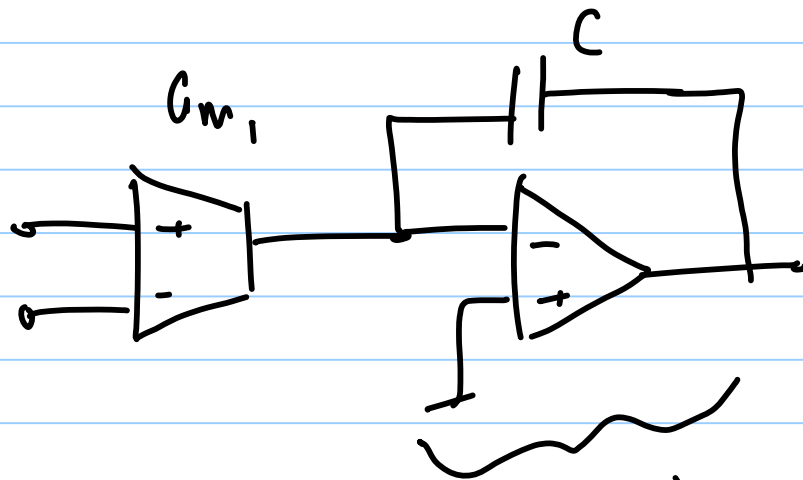



22/10/19

Lec 32.

3. stage opamp: $A_o = \frac{G_{m1} G_{m2} G_{m3}}{G_{o1} G_{o2} G_{o3}}$




2-stage of amp

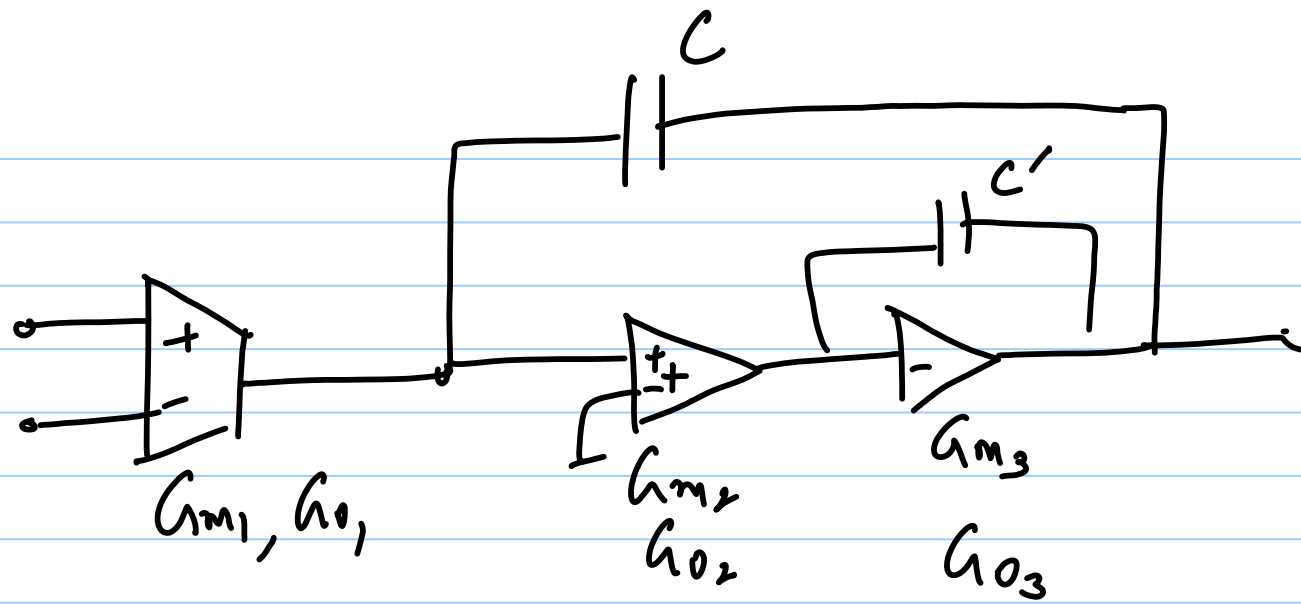

Nested
Miller
Compensation

Bandgap References

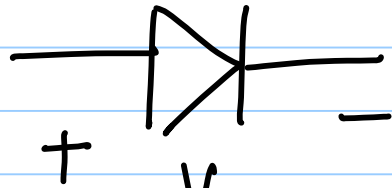


$$V_{BE} \approx 0.75V$$

$$V_{BE} = V_T \ln\left(\frac{I_0}{I_s}\right)$$

$\nearrow f(T) \qquad \qquad \qquad \searrow f(T)$
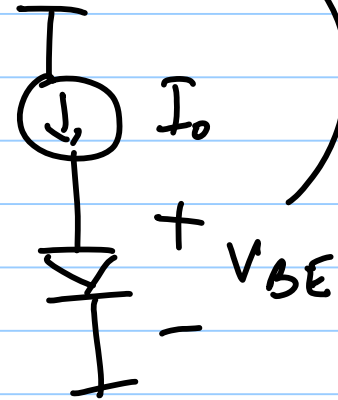
$$\frac{\partial V_{BE}}{\partial T} \approx -1.5 \text{ mV/K} @ RT$$




$$V_{ref} = \alpha_1 V_1 + \alpha_2 V_2$$

/
\

-ve T.C
+ve T.C

$$\left. \frac{\partial V_{ref}}{\partial T} \right|_{RT} = 0$$

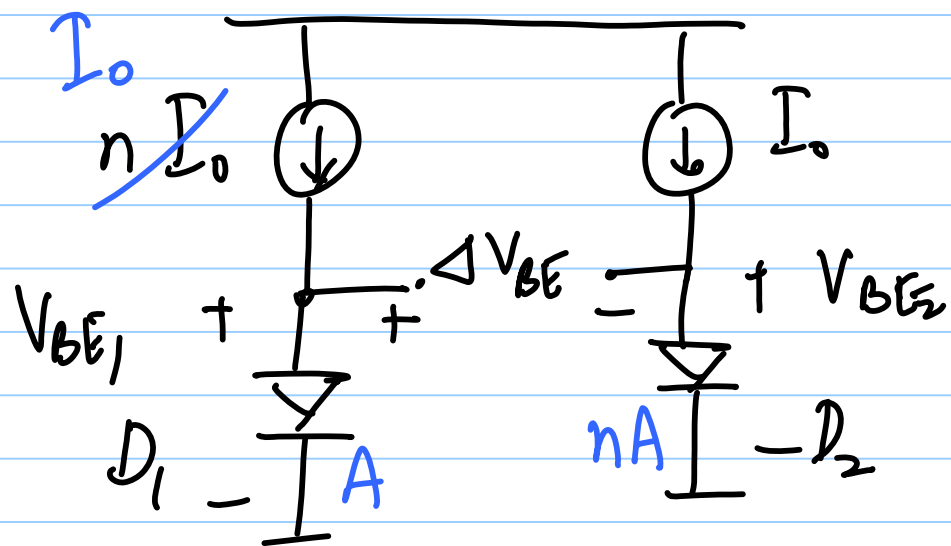


exact value of I_0 does not matter

$$\Delta V_{BE} = V_{BE1} - V_{BE2}$$

$$= V_T \ln\left(\frac{nI_0}{I_s}\right) - V_T \ln\left(\frac{I_0}{I_s}\right)$$

$$= \frac{V_T \ln(n)}{1}$$
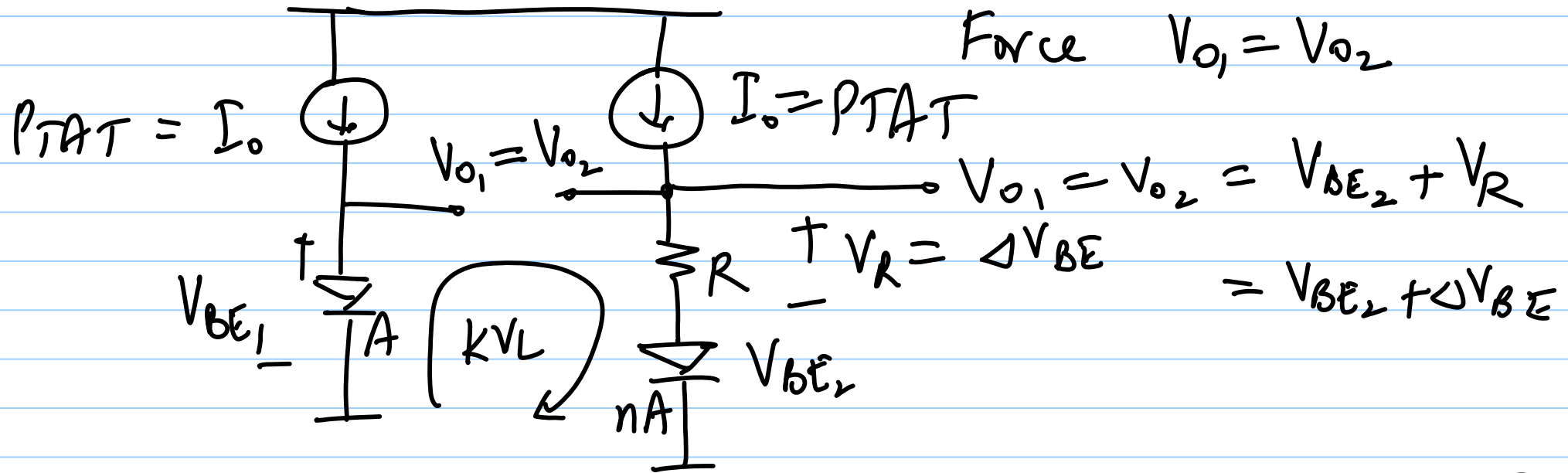
$$= \frac{kT}{q} \ln(n) \xrightarrow{\propto T, \text{ +ve } T-\text{co}} \text{"PTAT"}$$



$$V_{ref} = V_{o2} = V_{BE2} + V_T \ln(n) \leftarrow \text{Set } T.C. = 0 @ \frac{RT}{T}$$

$$\left. \frac{\partial V_{\text{mg}}}{\partial T} \right|_{300\text{K}} = 0 \Rightarrow \text{Calculate } n$$

$$\ln(n) = 17.2$$