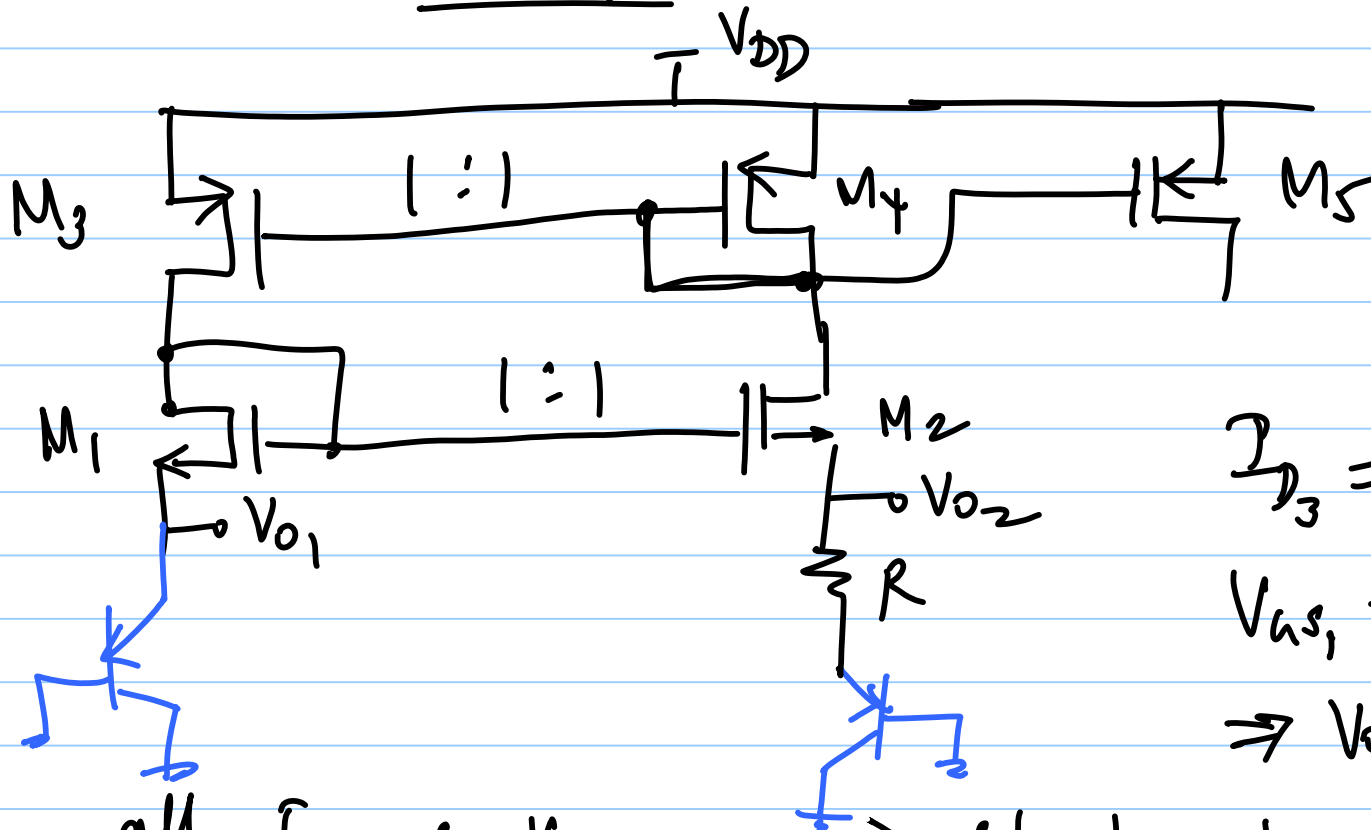


24/10/19

Lec 34






$$I_{D3} = I_{D4} = I_{D1} = I_{D2}$$

$$V_{GS1} = V_{GS2}$$


$$\Rightarrow V_{O1} = V_{O2} = V_{ref}$$

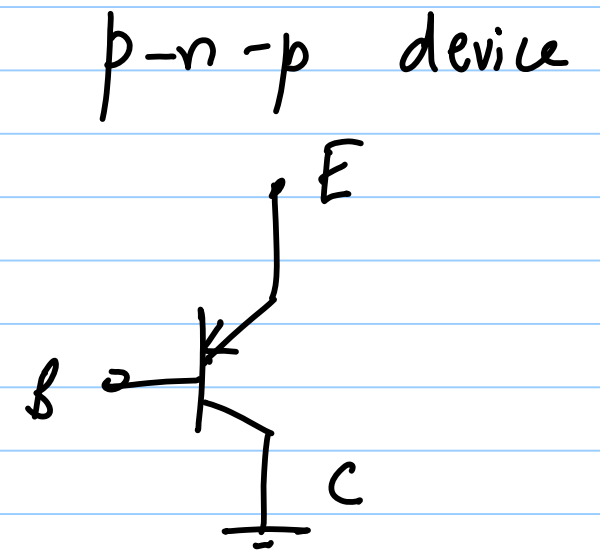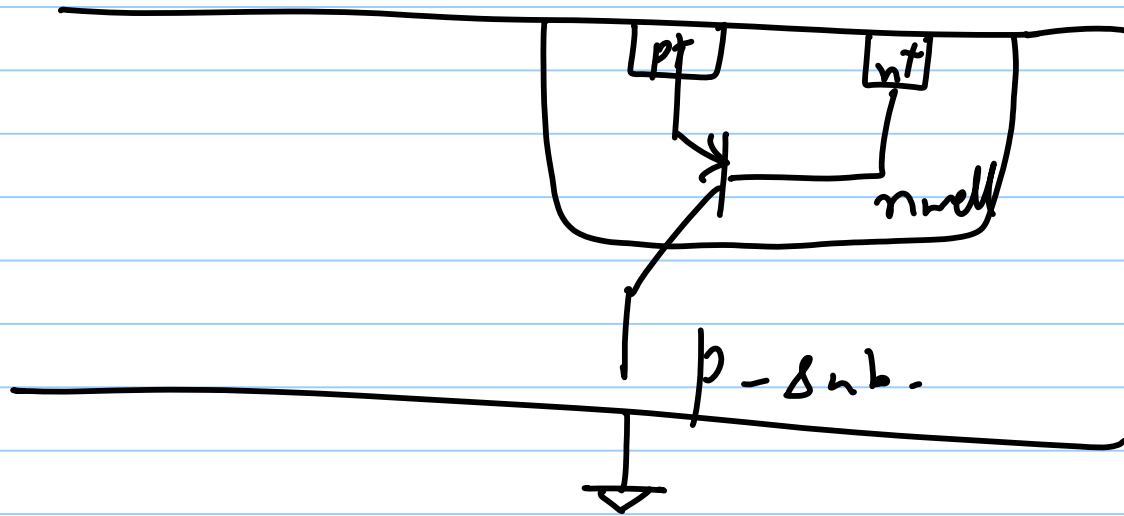all I_{Ds} & $V_{GSs} = 0 \Rightarrow$ startup circuit required



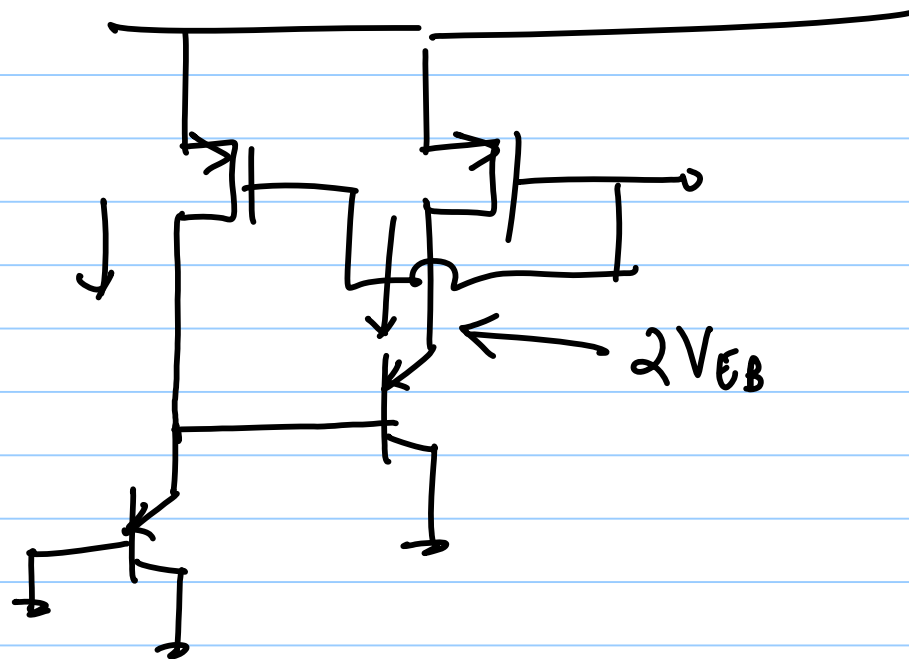


Miller Compensation


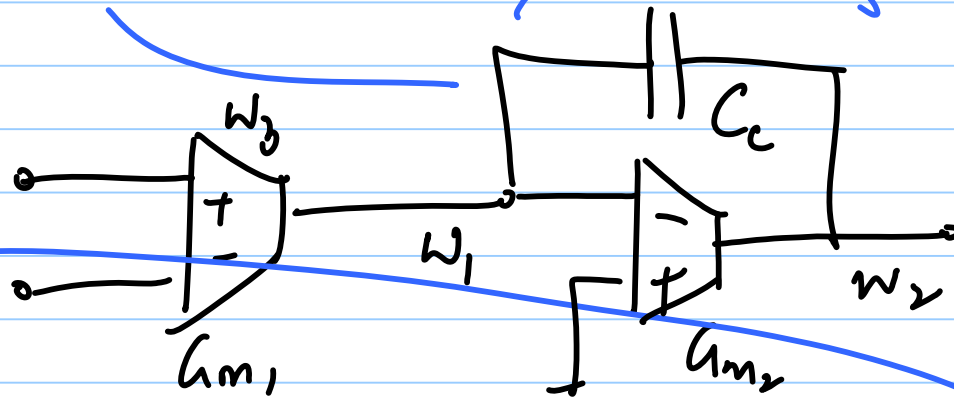


R_c C_c
 w_4 pole-zero cancellation

$A_o = 40\text{dB}$

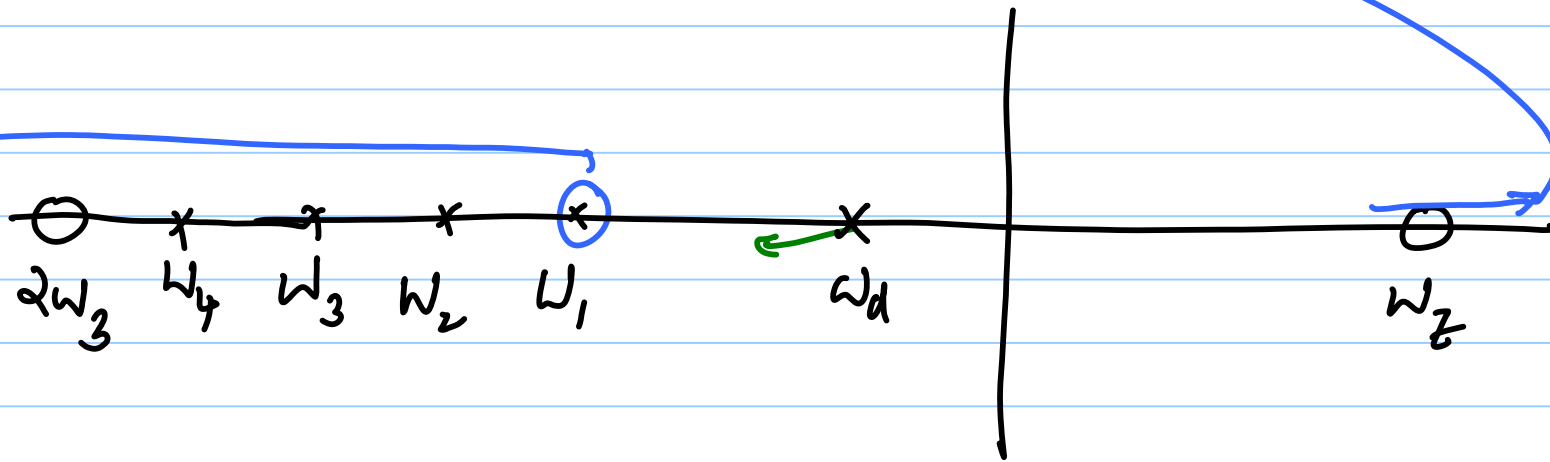

Bipolar Junction Transistor


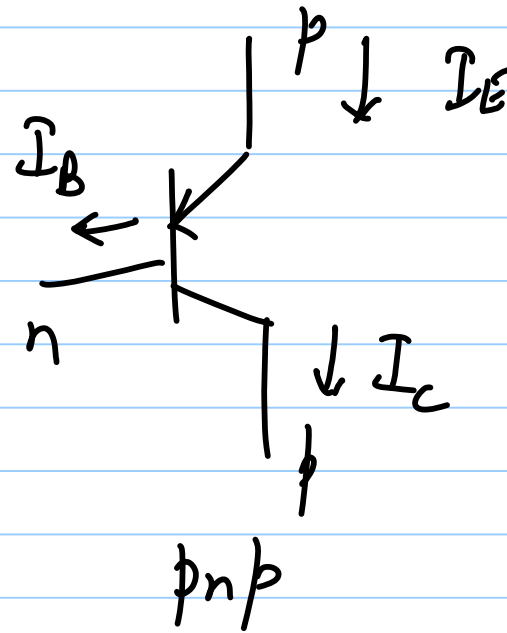
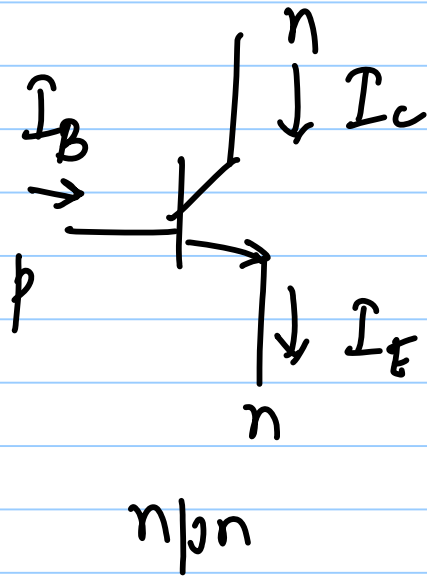


$$I_E = I_B + I_C$$

$$I_C = \beta \cdot I_B$$

$$I_C = I_S \exp\left[\frac{V_{BE}}{V_T}\right]$$

$$V_T = kT/q$$

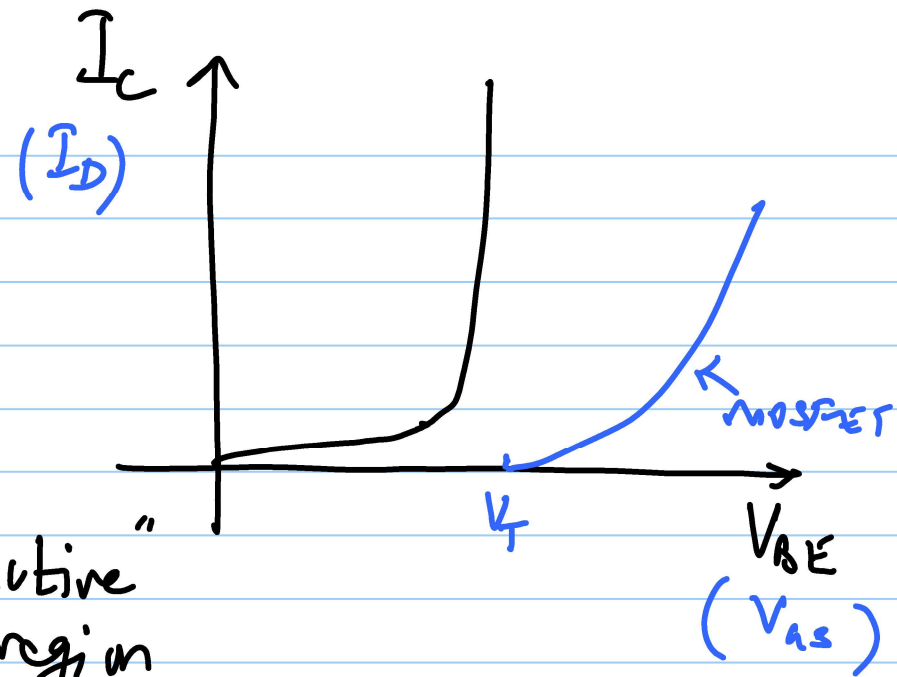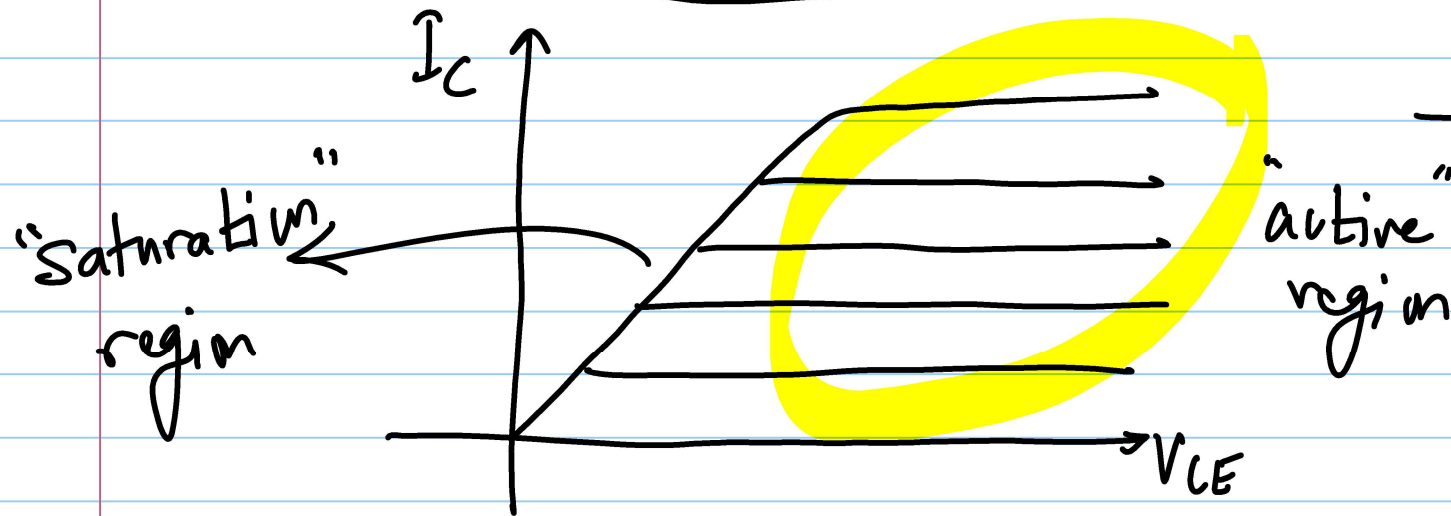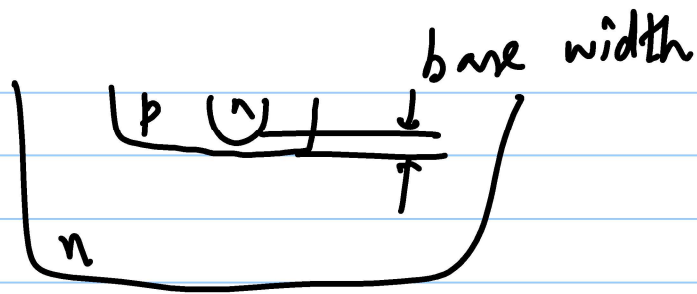

$$V_{CEsat} \approx 0.2V$$

$$y_{12} = y_{22} = 0$$

$$g_m = y_{21} = \frac{\partial I_C}{\partial V_{BE}} = \frac{1}{V_T} I_S \exp\left(\frac{V_{BE}}{V_T}\right) = \frac{I_C}{V_T}$$

$$y_{11} = \frac{\partial I_B}{\partial V_{BE}} = \frac{1}{\beta} \cdot \frac{\partial I_C}{\partial V_{BE}} = \frac{g_m}{\beta} = \frac{1}{r_\pi}$$

