

30/10/19


Lec 35

$$g_m = y_{21} = \frac{\partial I_c}{\partial V_{BE}} = \frac{I_c}{V_T}$$

$$y_{11} = \frac{\partial I_B}{\partial V_{BE}} = \frac{1}{\beta} \frac{\partial I_c}{\partial V_{BE}} = \frac{g_m}{\beta}$$

$$r_{11} = \frac{1}{y_{11}} = \beta / g_m$$



$$y_{12} = 0 \quad ; \quad y_{22} = ?$$


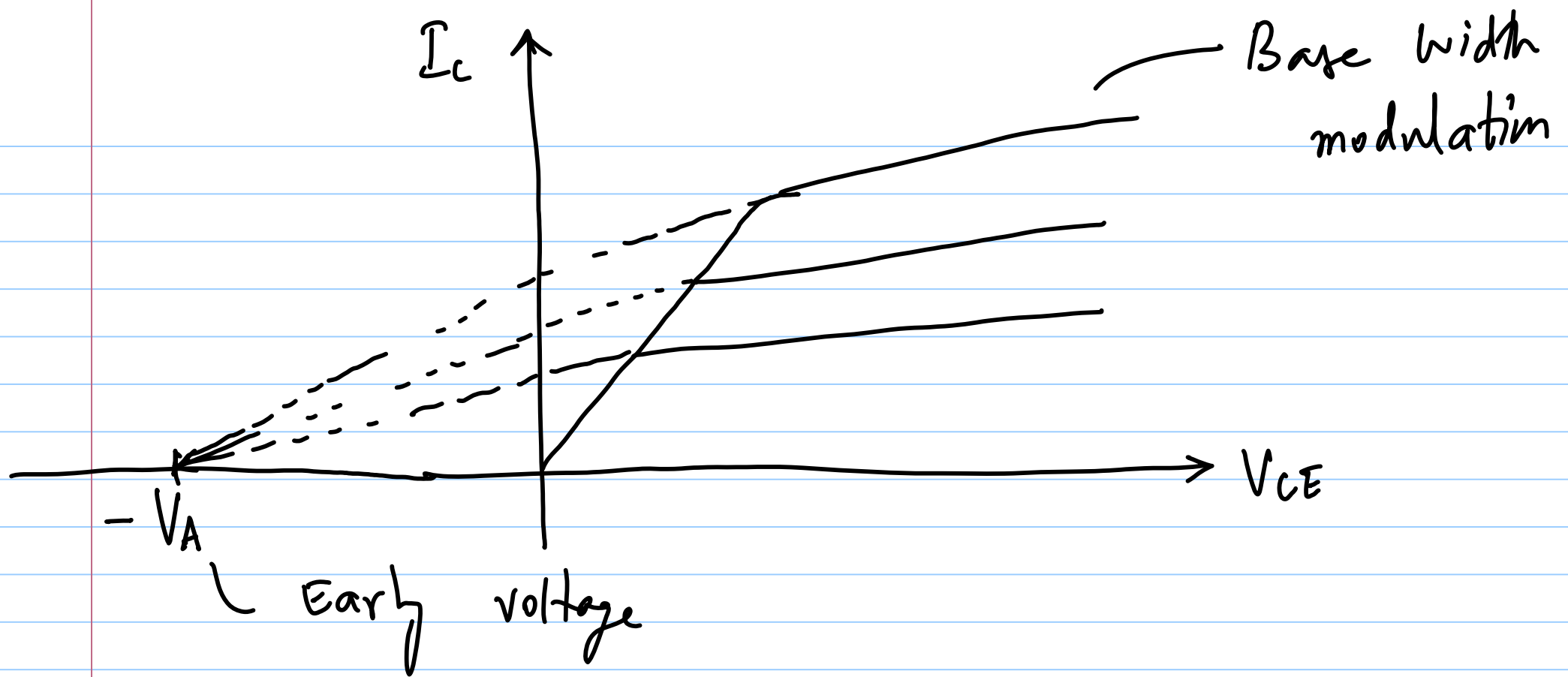



$$I_C = \left[ I_s \exp\left(\frac{V_{BE}}{V_t}\right) \right] \left[ 1 + \frac{V_{CE}}{V_A} \right]$$

$$y_{22} = \frac{\partial I_C}{\partial V_{CE}} = \frac{I_C}{V_A}$$



# Small signal model of BJT

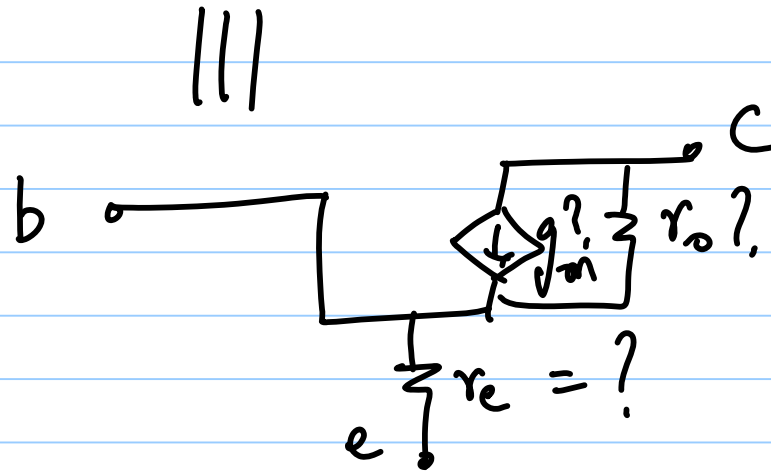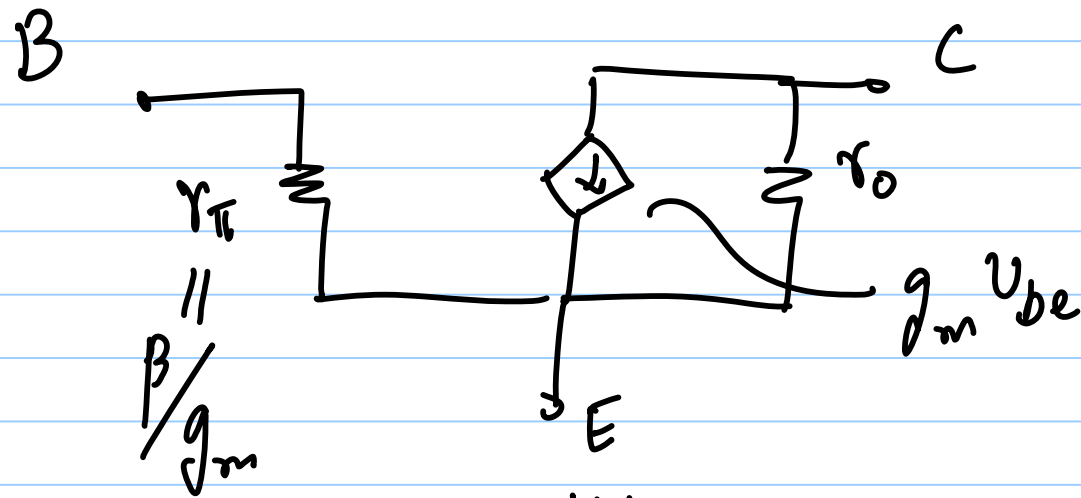


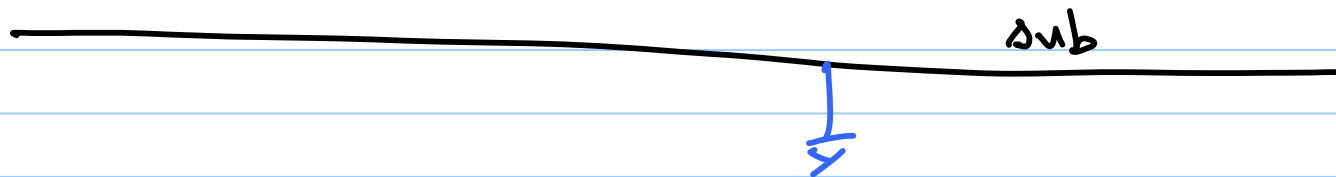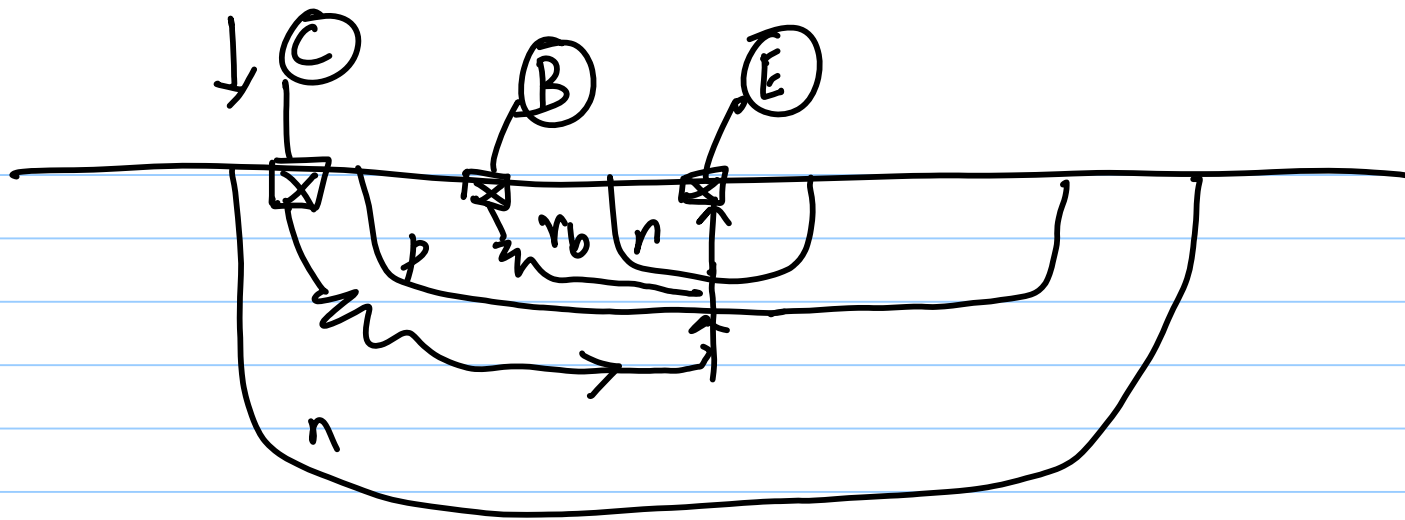

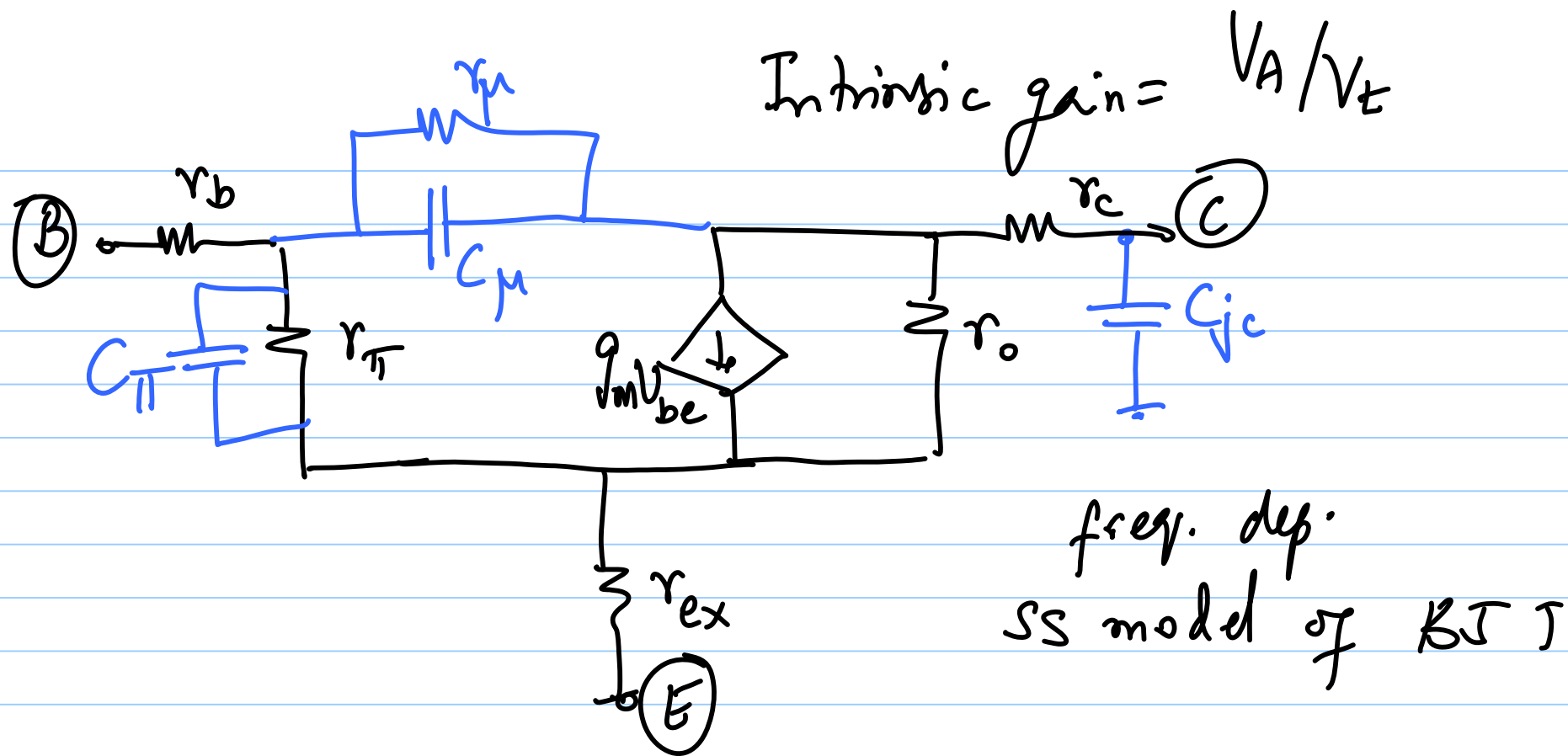


# Common Emitter Amplifier

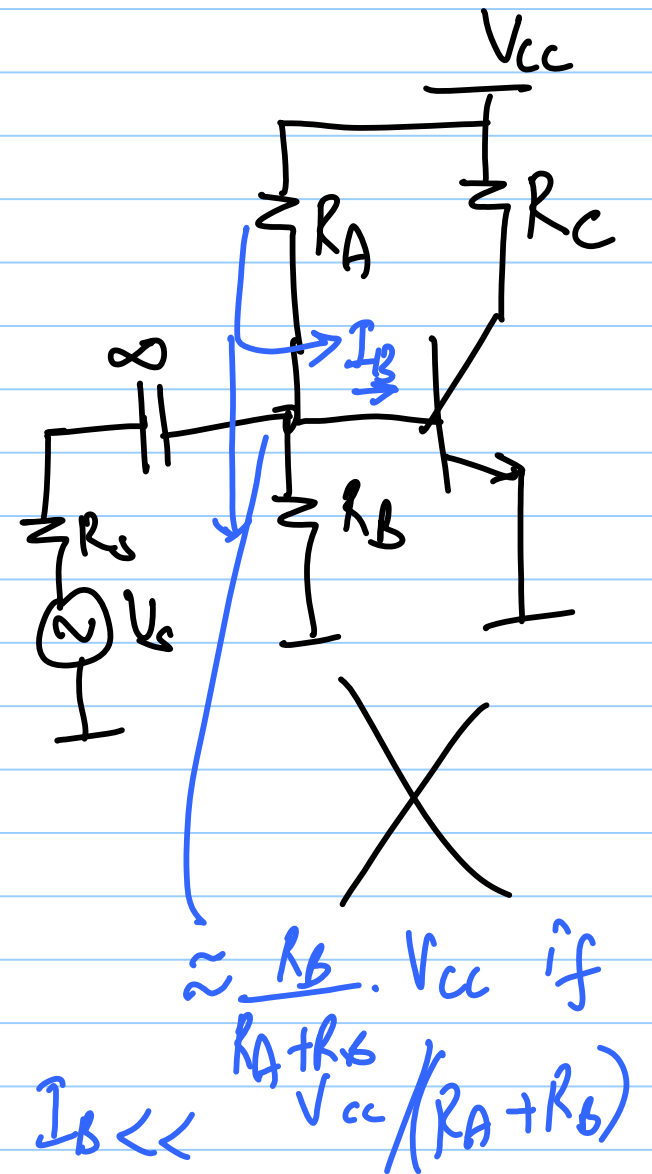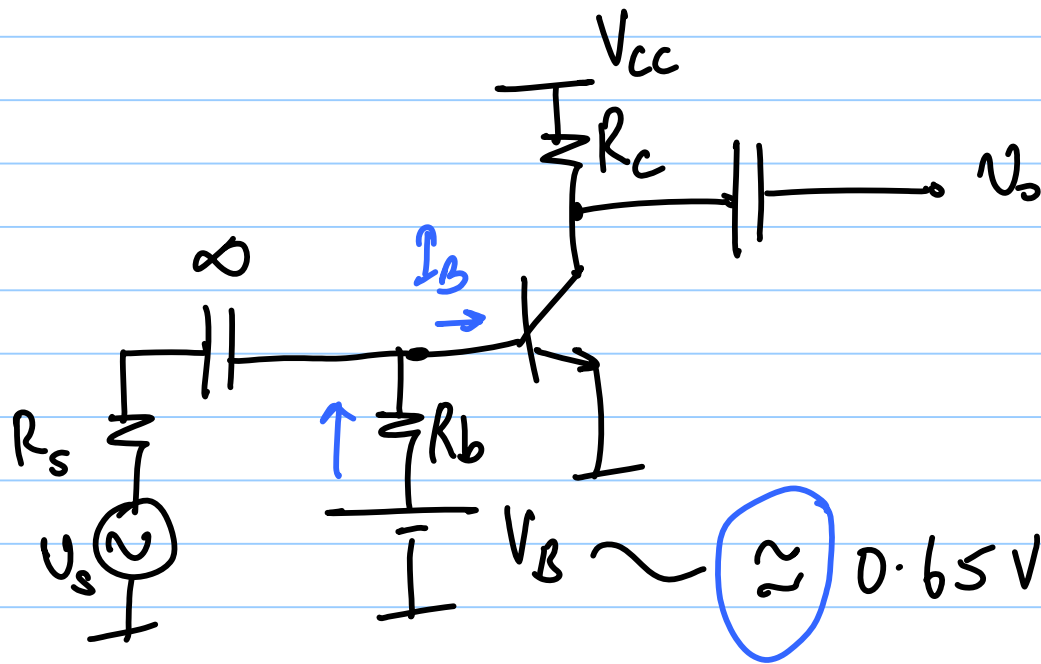

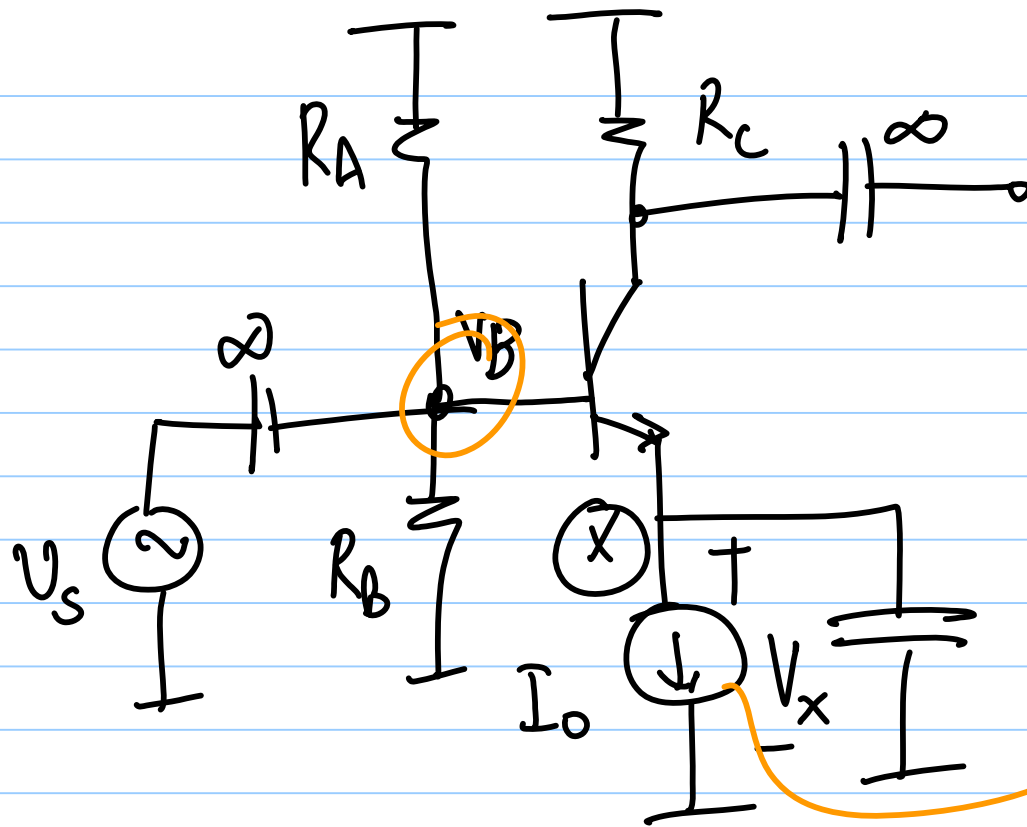

$$V_B = V_x + \underline{\underline{V_{BE}}} \rightarrow I_E = I_0$$


Current mirror

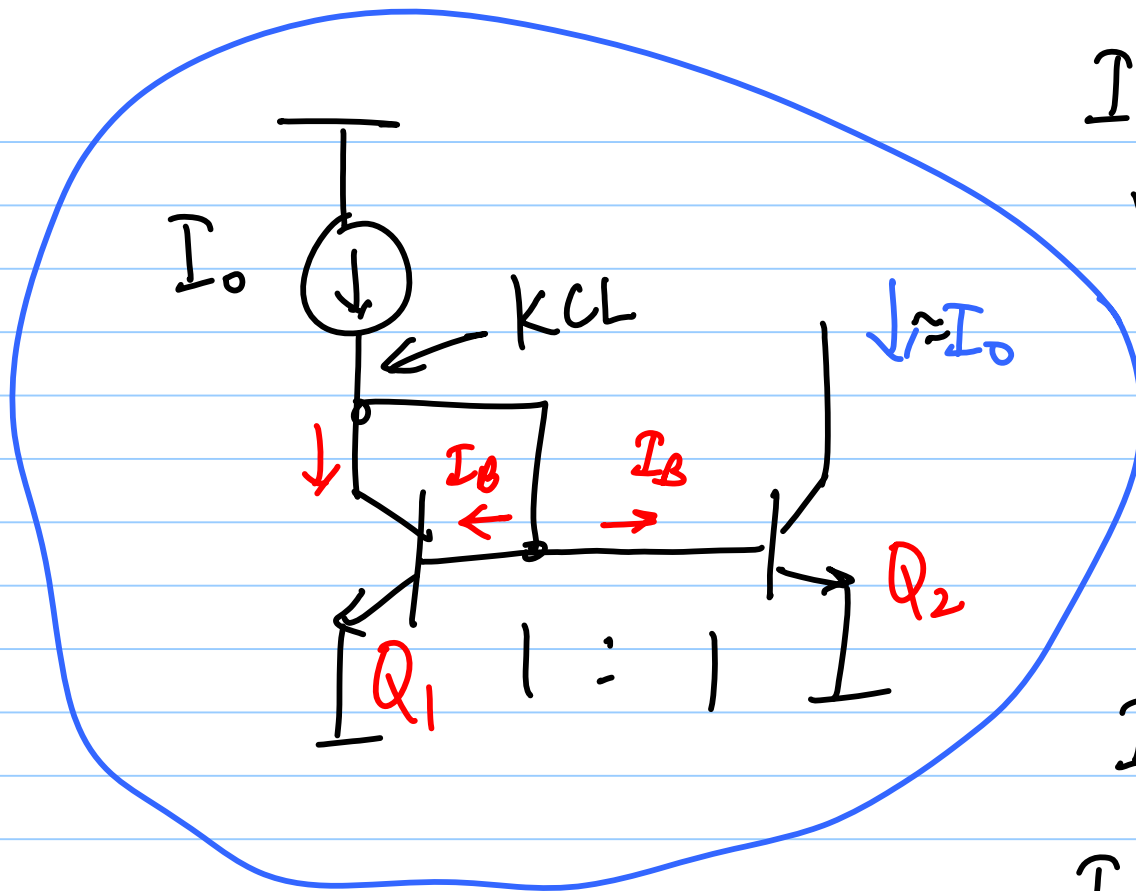

$$I_{C1} = I_o - 2I_B$$

$$V_{BE1} = V_{BE2}$$

$\equiv$

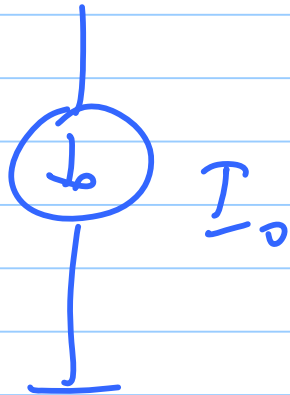

$$I_{C1} = I_{C2}$$

$$I_{C2} = I_o - 2I_B$$


$$= I_o - \frac{2I_{C2}}{\beta}$$

$$\frac{I_o \cdot \beta}{\beta + 2} \approx I_o \text{ if } \beta \text{ is large}$$

$$I_{C2} = \frac{I_o}{1 + 2/\beta} \approx$$




typical  $\beta > 100$

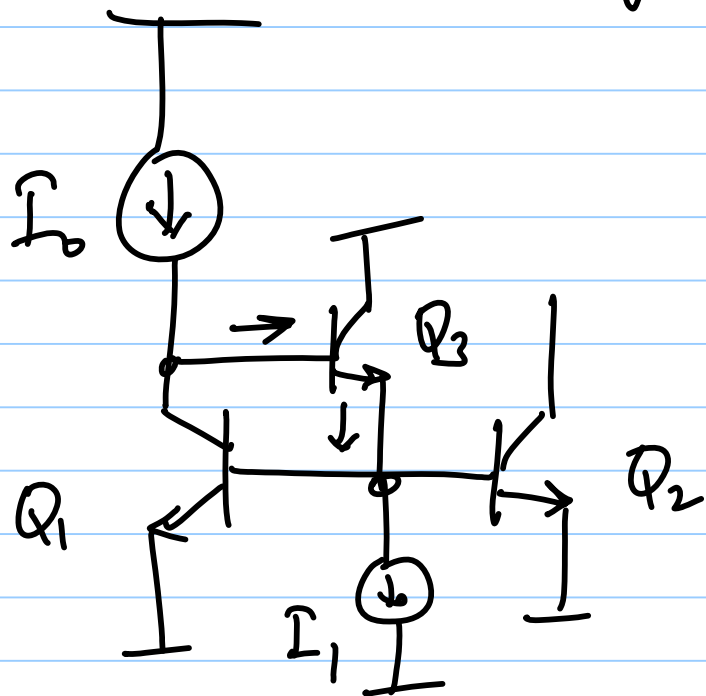

$$I_{E3} = I_{B1} + I_{B2} + I_1$$

$$I_{B3} = \frac{1}{(\beta+1)} \cdot I_{E3}$$

$$I_{C1} = I_o - I_{B3}$$

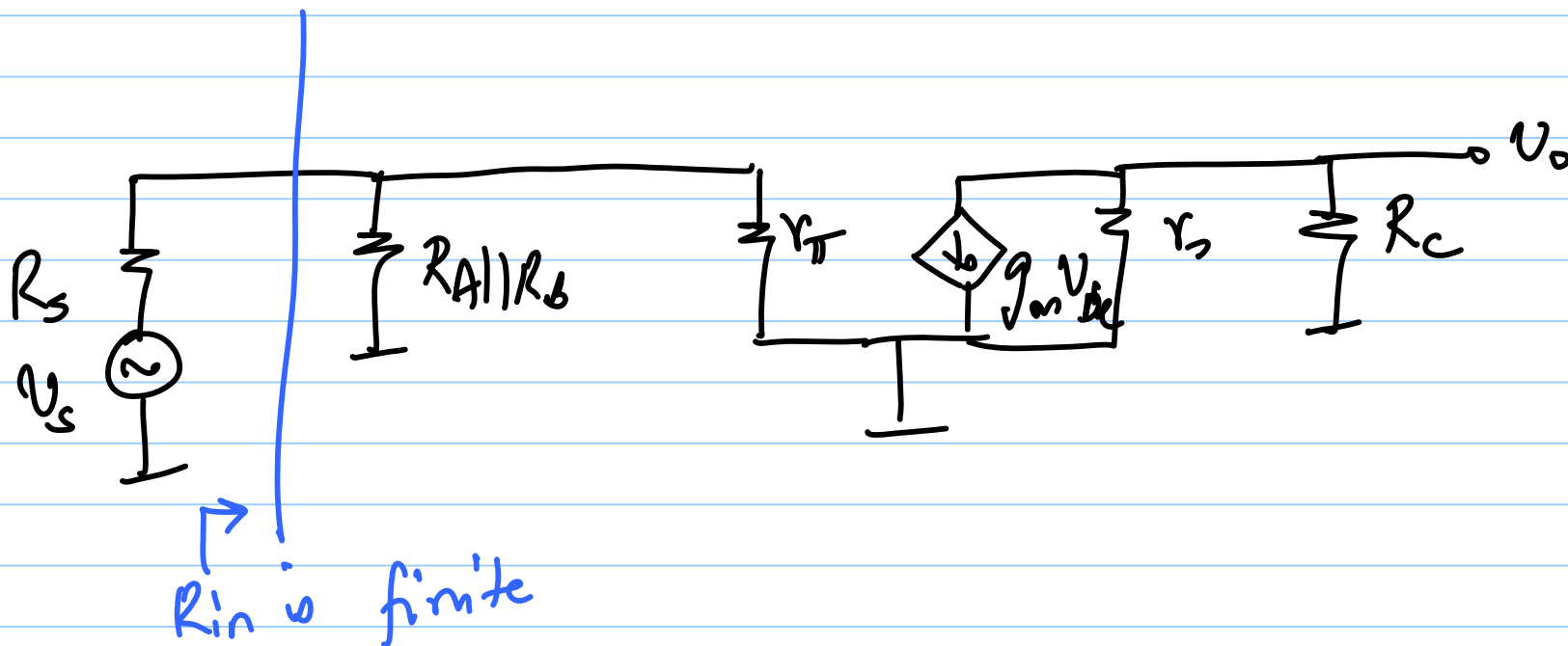

BJT

$$g_m = \frac{I_c}{V_t}$$

gives more  $g_m$  for a given current

MOS

$$g_m = \frac{I_D}{(V_{GS} - V_T)/2}$$