
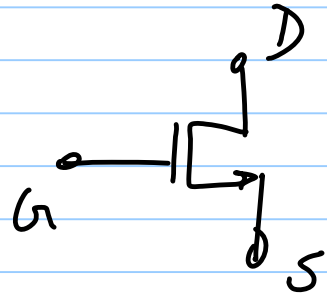


6/8/19

Note title

## Lec 6

06-Aug-19

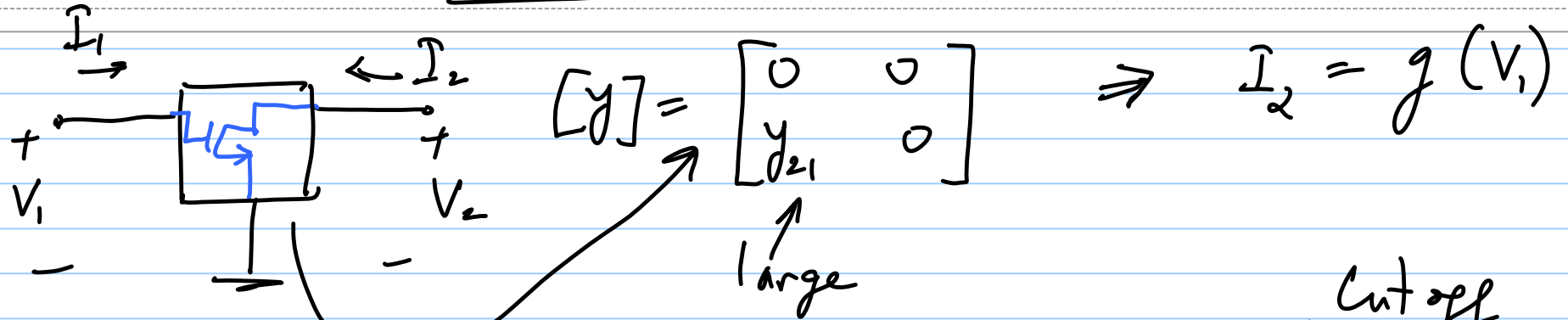

$I_D = 0$  if  $V_{GS} < V_T$  — Cutoff

$I_D = \mu_n C_{ox} \left( \frac{W}{L} \right) \left[ (V_{GS} - V_T) \cdot V_{DS} - \frac{V_{DS}^2}{2} \right]$


if  $V_{GS} \geq V_T$  and  $V_{DS} < V_{GS} - V_T$


Triode
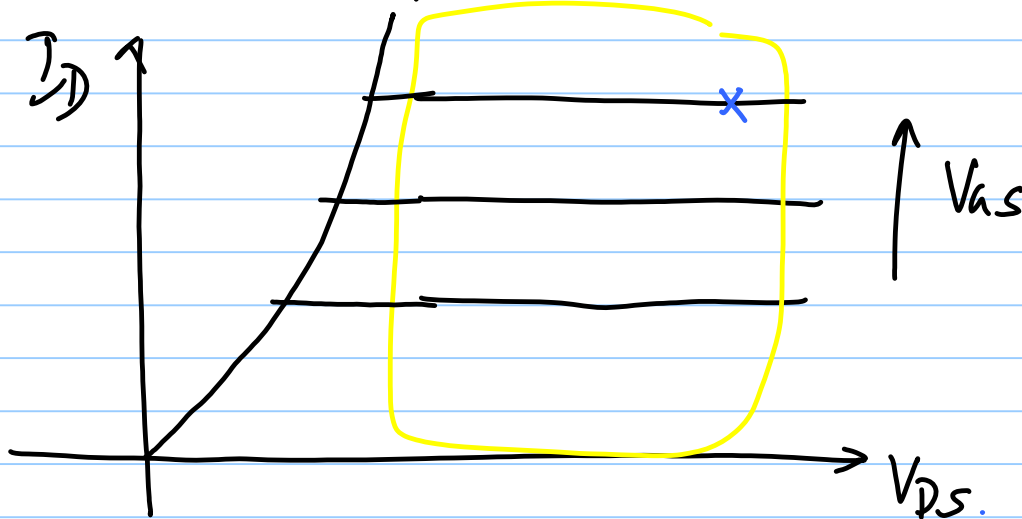
## Saturation

$$I_D = \frac{1}{2} \mu_n C_{ox} \left( \frac{W}{L} \right) (V_{as} - V_T)^2$$

if  $V_{as} \geq V_T$   
and  
 $V_{ds} \geq V_{as} - V_T$




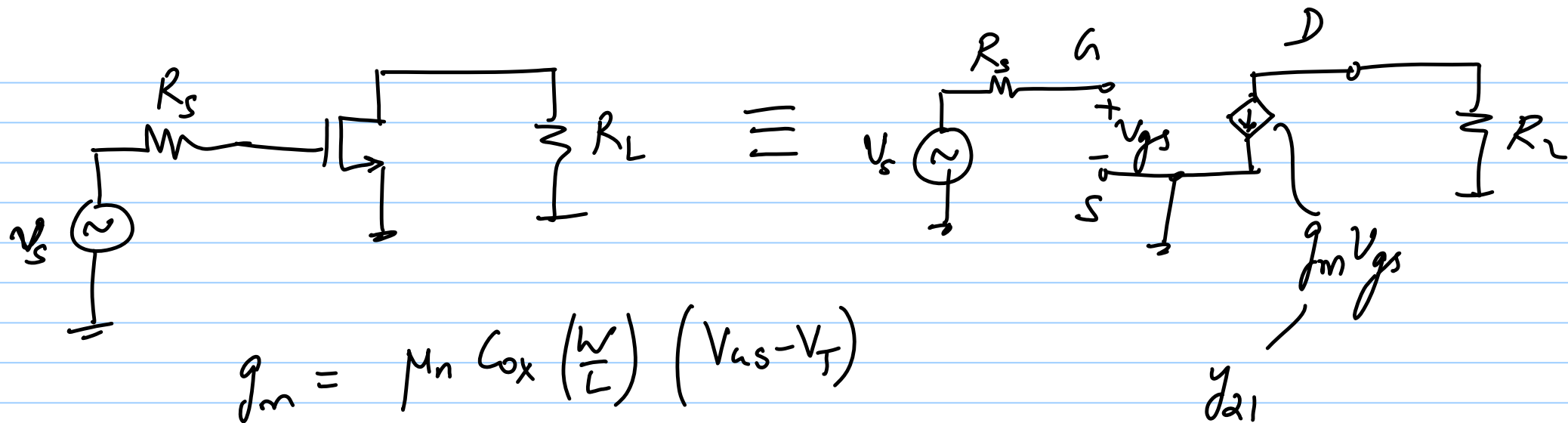


$$g_m = \mu_n C_{ox} \left( \frac{W}{L} \right) (V_{as} - V_T)$$

$$= \frac{2 I_D}{V_{as} - V_T}$$
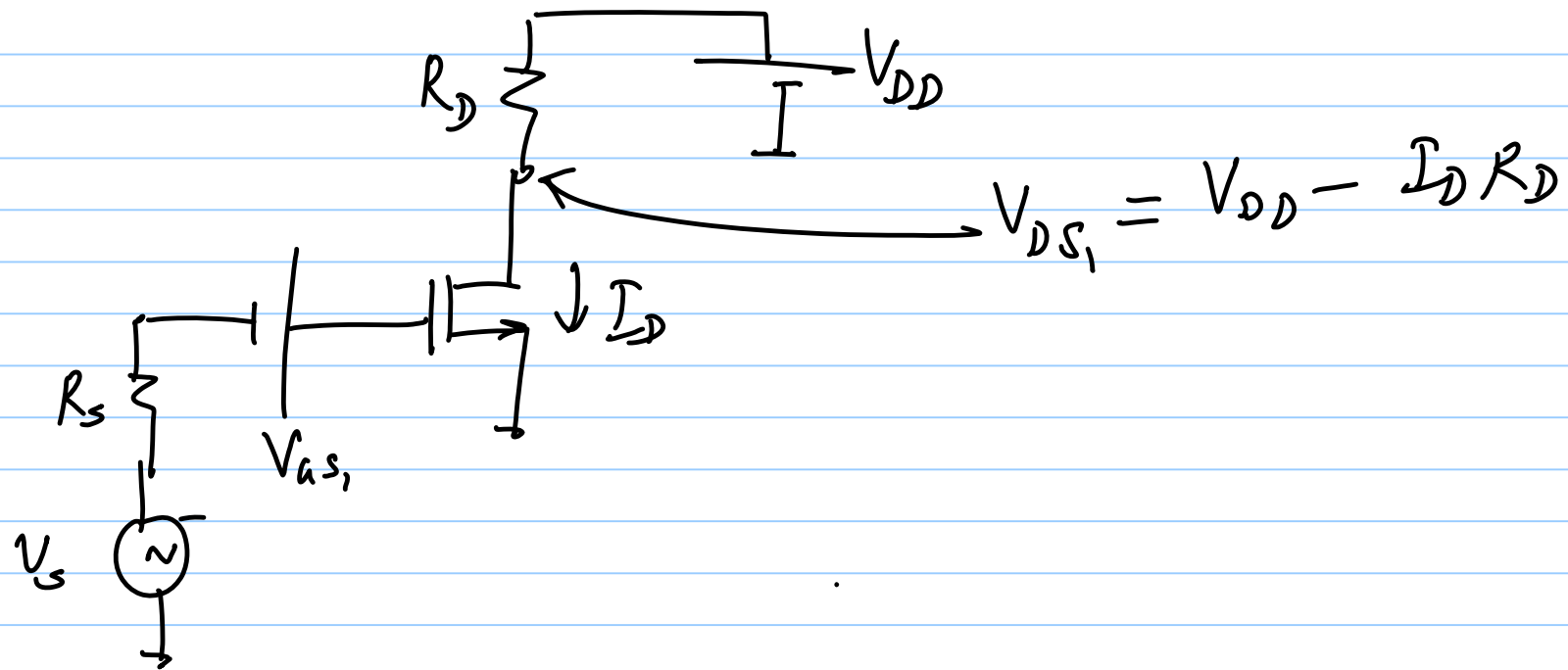
$$= \sqrt{2 \mu_n C_{ox} \left( \frac{W}{L} \right) I_D}$$




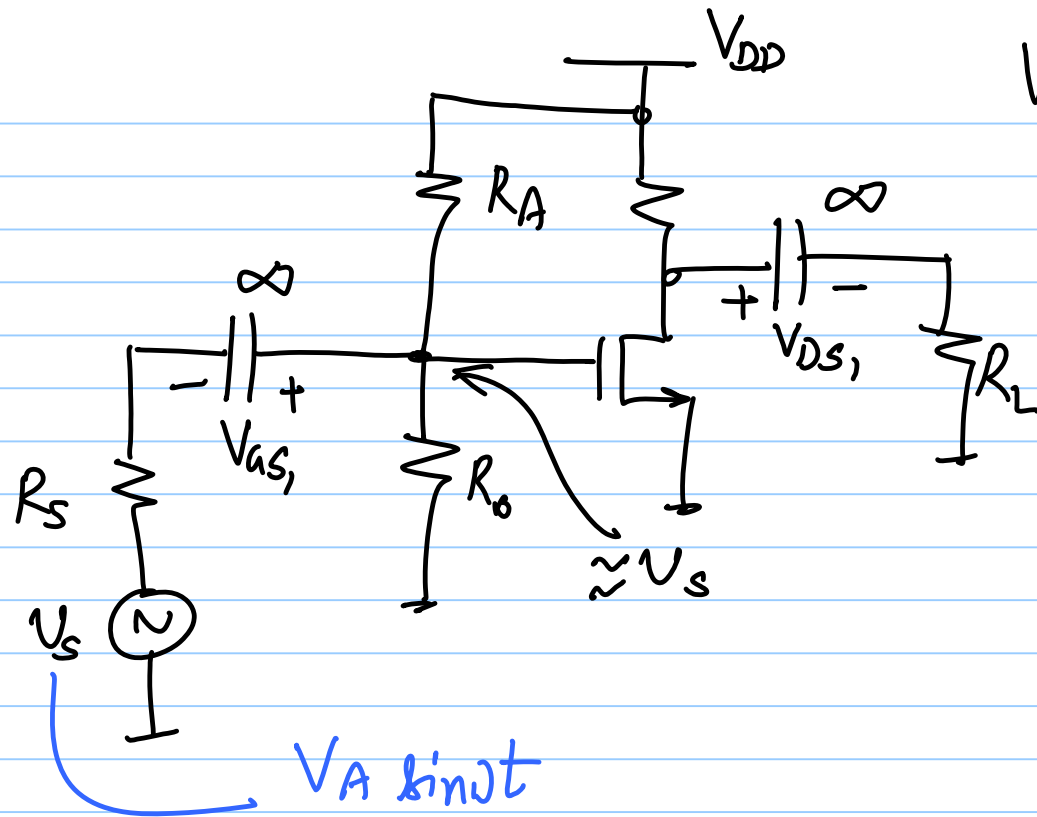

$$V_{GS1} = \frac{R_B}{R_A + R_B} \cdot V_{DD}$$


$$R_A || R_B \gg R_s$$

$$\text{Gain} \approx -g_m (R_D || R_L)$$

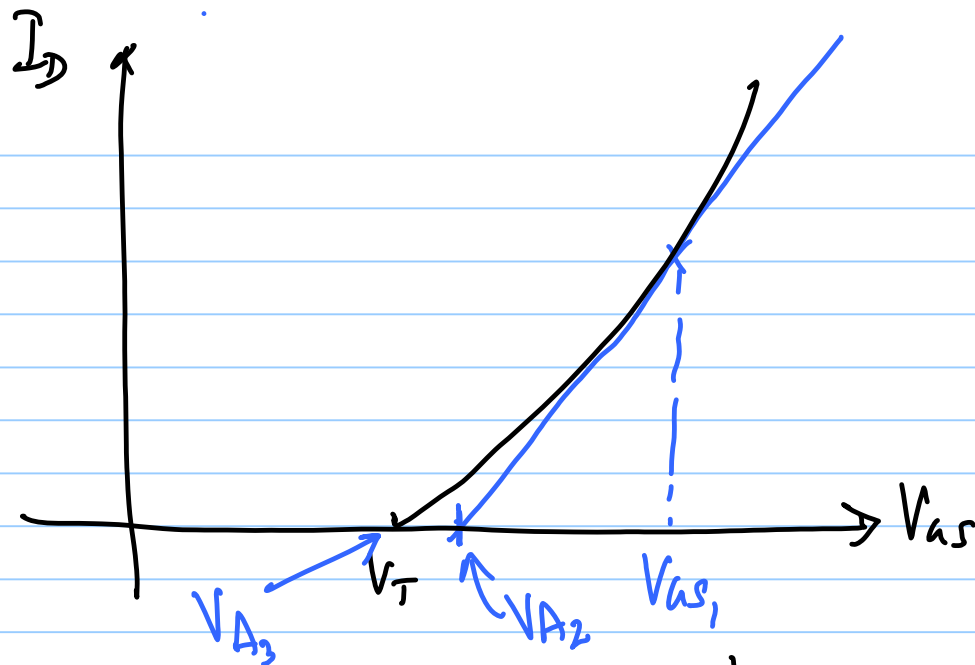

$$I_D = I_{D1} + g_m V_A \sin \omega t$$
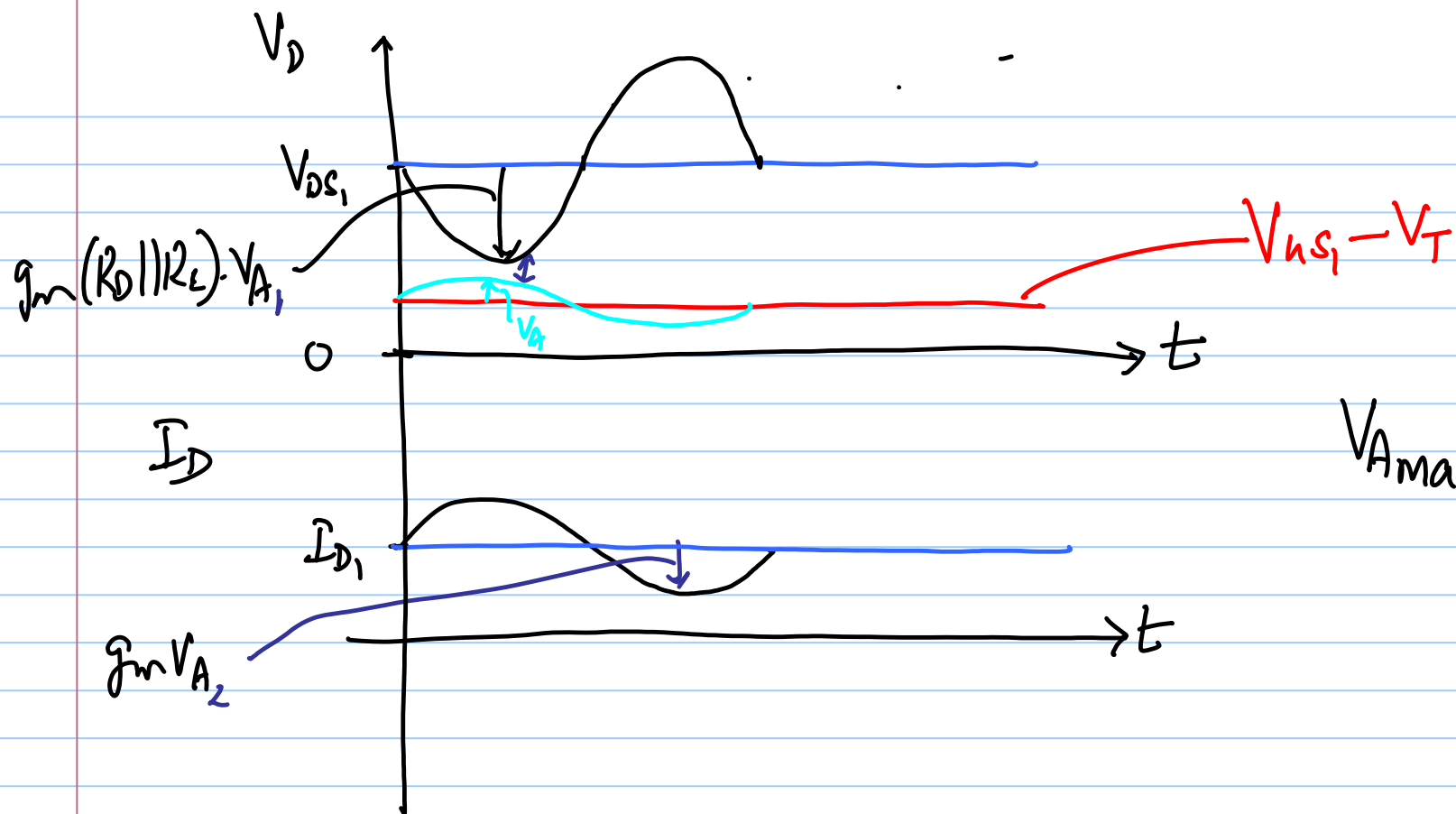
$$V_D = V_{DS1} - g_m (R_D \parallel R_L) \cdot V_A \sin \omega t$$



$$V_{Amax} = \min\{V_{A1}, V_{A2}\}$$

∴

### Triode limit

$$V_D = V_{as} - V_T \quad @ \quad \begin{array}{l} \text{minimum drain voltage} \\ \text{in 1st half cycle} \end{array}$$

$$V_{Ds,1} - g_m (R_D || R_L) \cdot V_{A,1} = V_{as,1} + V_{A,1} - V_T$$

$$V_{A,1} = \frac{V_{Ds,1} - (V_{as,1} - V_T)}{1 + g_m (R_D || R_L)}$$

Cut off limit

$$I_D = I_{D1} + g_m V_A \sin \omega t$$

$$0 = I_{D1} - g_m V_{A2}$$

$$V_{A2} = \frac{I_{D1}}{g_m}$$

$$V_{A_{max}} = \min(V_{A_1}, V_{A_2})$$

Gate limit

$$V_{as} = V_T \quad @ \quad \text{utoff limit}$$

→  $V_{as_1} + V_{A_{inwt}}$

$$V_{as_1} - V_{A_3} = V_T \Rightarrow V_{A_3} = V_{as_1} - V_T$$