
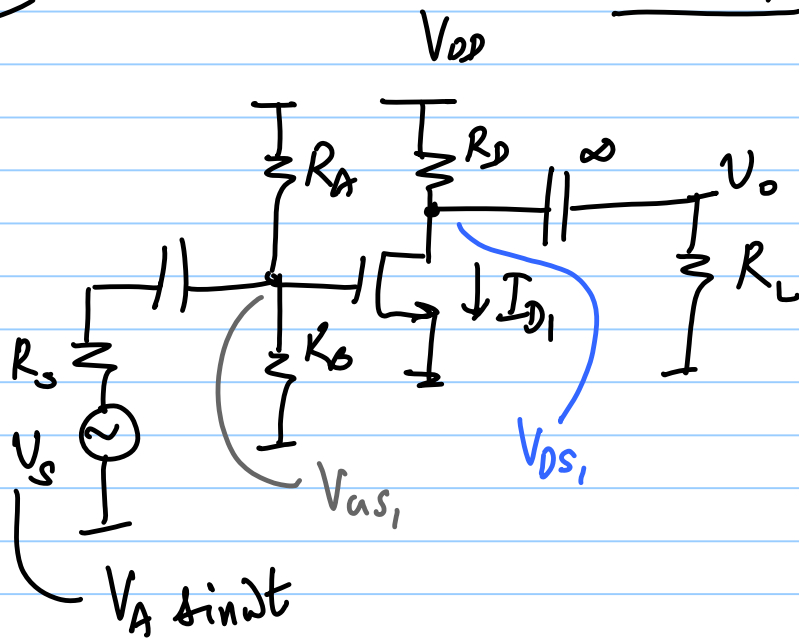


1/8/19

Lec 7

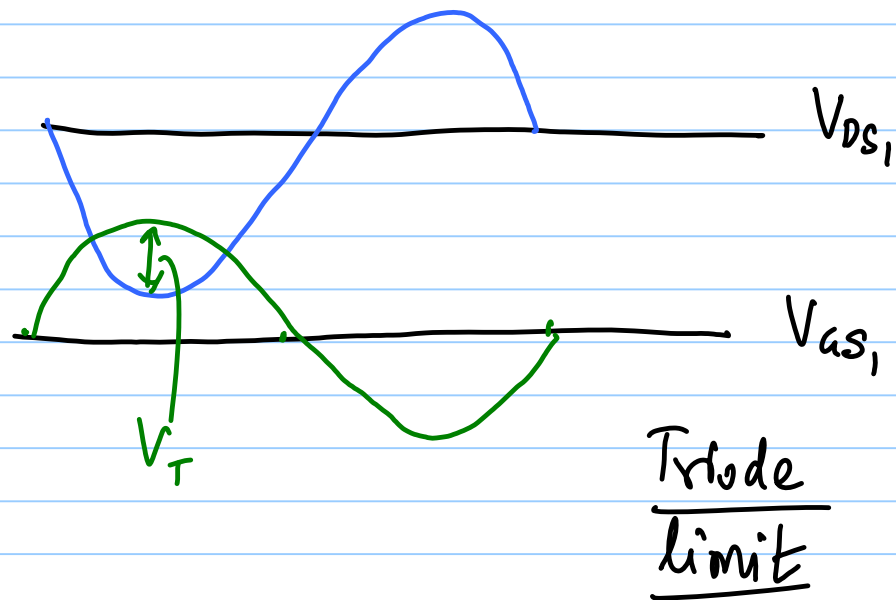




$$V_{DS} = V_{DS1} - g_m (R_D \parallel R_L) \cdot V_A \sin \omega t$$

$$V_{GS} = V_{GS1} + V_A \sin \omega t$$
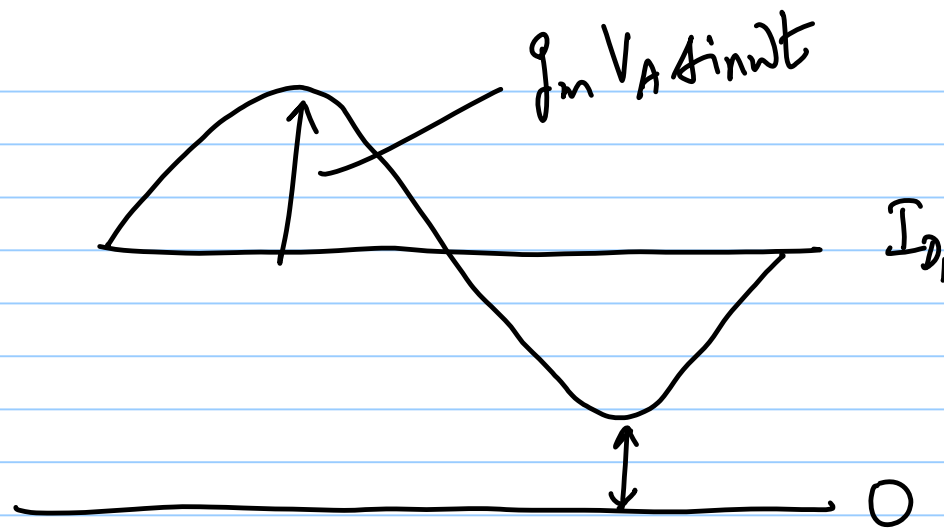
$$V_{A_i} = \frac{V_{DS1} - (V_{GS1} - V_T)}{1 + g_m (R_D \parallel R_L)}$$



$$I_{D1} + g_m V_A \sin \omega t = 0$$

@ negative peak


$$\text{Cut-off limit } V_{A2} = \frac{I_{D1}}{g_m}$$

Example

$$V_{GS1} = 1.5V$$

$$I_{D1} = \frac{1}{2} \times (100 \mu A/V^2) \times 10 \times (0.5V)^2$$
$$= 125 \mu A$$
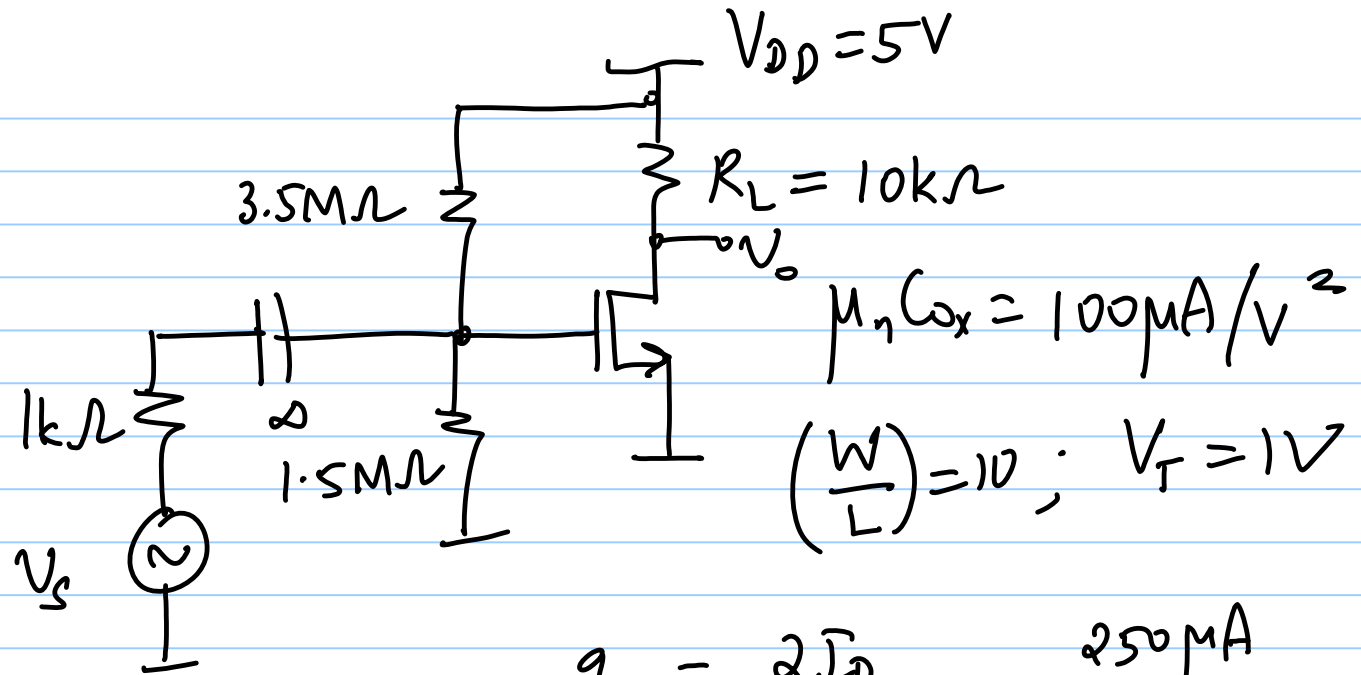
$$V_{DS1} = 5V - 125 \mu A \times 10k\Omega$$
$$= 3.75V$$



$$g_m = \frac{2I_D}{V_{GS} - V_T} = \frac{250 \mu A}{0.5V}$$
$$= 0.5mS$$

small
-signal
gain

$$\frac{v_o}{v_s} = -g_m R_L = -5 \text{ V/V}$$

Swing limits

Triode limit

$$V_G = 1.5 \text{ V} + V_A \sin \omega t$$

$$V_D = 3.75 - 5 V_A \sin \omega t$$

$$V_D = V_G - V_T$$

$$3.75 - 5 V_{A1} = 1.5 + V_A - 1$$

$$V_{A1} = \frac{3.25}{6} \approx 542 \text{ mV}$$

Cut off limit

$$I_D = 0$$

$$125 \mu A + 0.5 mS \cdot V_{A2} \sin \omega t = 0$$

$$V_{A2} = \frac{125 \mu A}{0.5 mS} = 250 mV$$

max V_A for linear operation : $\min\{V_{A1}, V_{A2}\} = 250 mV$

$$\underline{V_A = V_T} : V_{A_1} - V_{A_3} = V_T$$

$$V_{A_3} = V_{A_{S_1}} - V_T = 0.5V$$

$$I_D = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right) (V_{gs} - V_T)^2$$

$$I_D = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right) (V_{gs} - V_T)^2$$

$$I_D = f(V_{gs}, V_{ds})$$

$$I_{D1} + \frac{\partial I_D}{\partial V_{gs}} \cdot V_{gs} + \frac{\partial I_D}{\partial V_{ds}} \cdot V_{ds}$$

$$+ \frac{1}{2} \frac{\partial^2 I_D}{\partial V_{gs}^2} \cdot V_{gs}^2 + \frac{1}{2} \frac{\partial^2 I_D}{\partial V_{ds}^2} \cdot V_{ds}^2$$

+ ...

$$II \ll I$$

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right) \cdot v_{gs}^2 \ll \mu_n C_{ox} \left(\frac{W}{L} \right) (V_{ds} - V_T) \cdot v_{gs}$$

$$v_{gs} \ll 2(V_{ds} - V_T)$$