
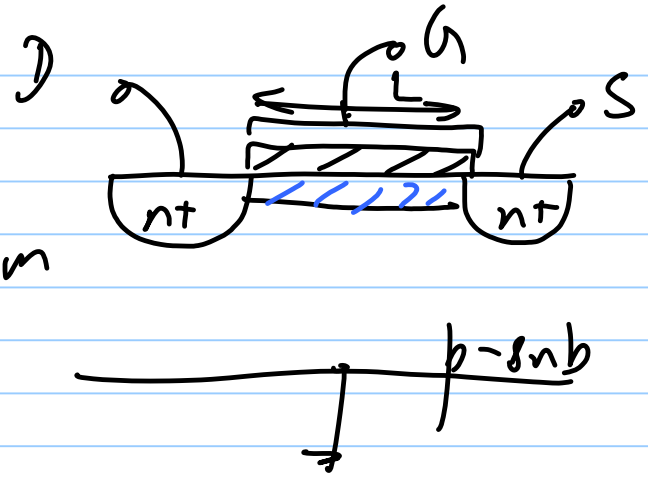


8/8/11

Lec 8

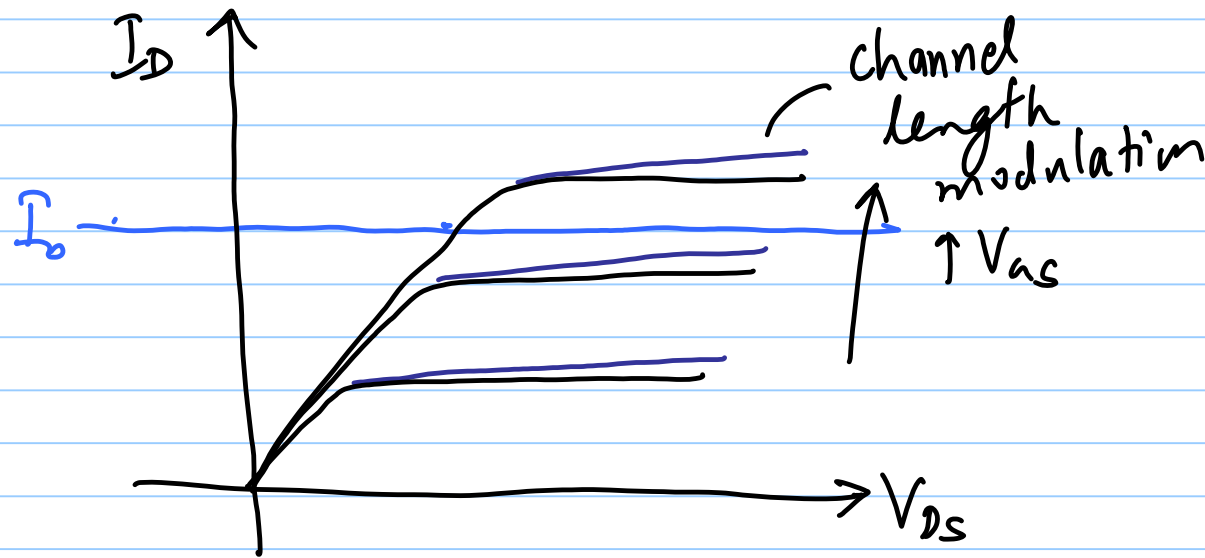

pinch off on D or S side? why?

$\frac{I_n}{sat.}$


$$I_D = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right) (V_{GS} - V_T)^2 (1 + \lambda V_{DS})$$


λ is small



1) Assume $\lambda = 0$ for operating point calculations

$$2) y_{22} = \left. \frac{\partial \bar{I}_D}{\partial V_{DS}} \right|_{\text{bias point}} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right) (V_{DS} - V_T)^2 (\lambda)$$
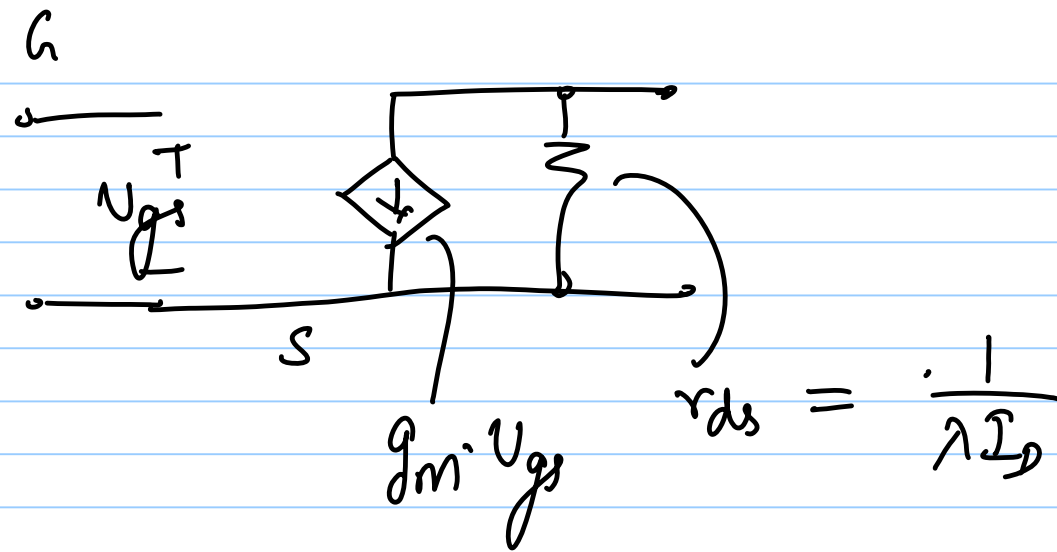
$$g_{ds} = \frac{1}{r_{ds}} \approx \lambda \bar{I}_D \quad \text{bias current}$$



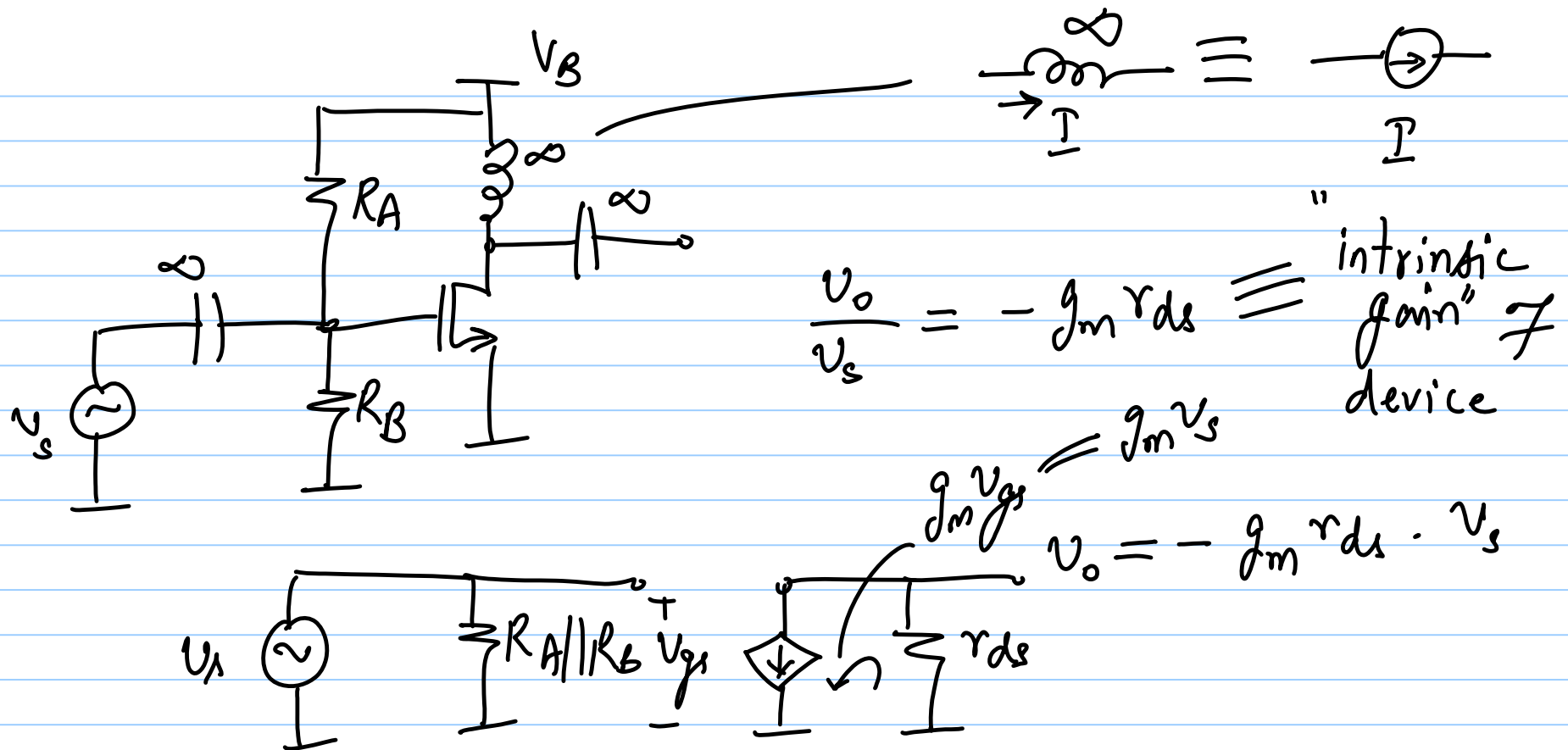


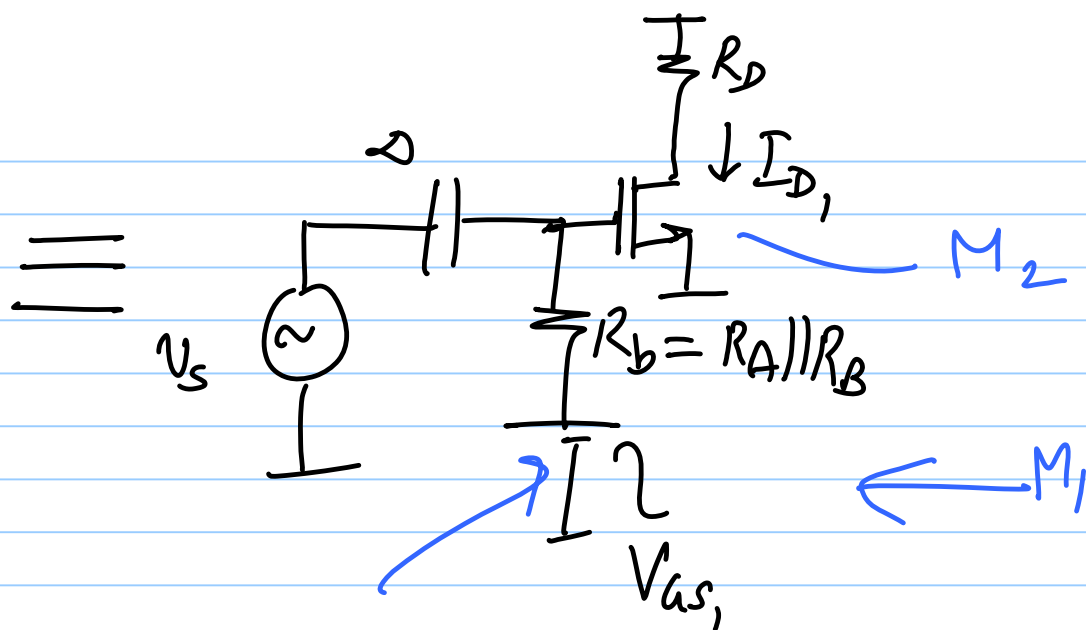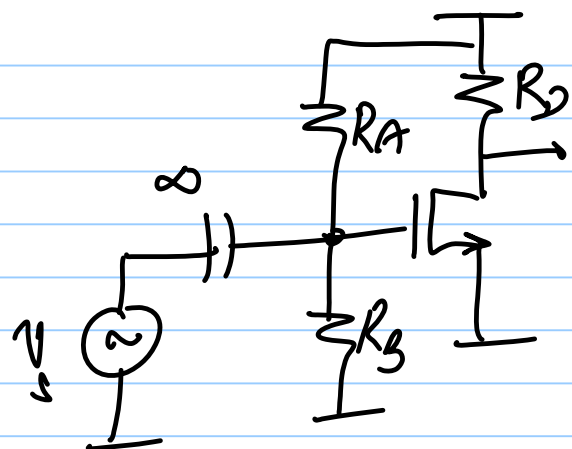

$\mu_n, C_{ox}, V_T \rightarrow$ vary from device to device

Bias @ constant I_D


Set V_{GS} so that $I_x = I_0$

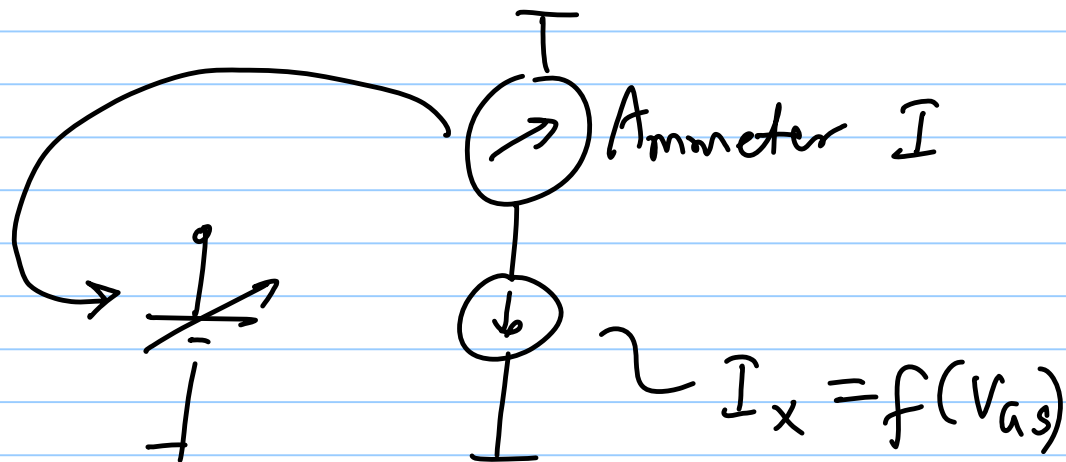

* Measure I_x

* Compare with I_0

* Set V_{GS} so that $I_x = I_0$

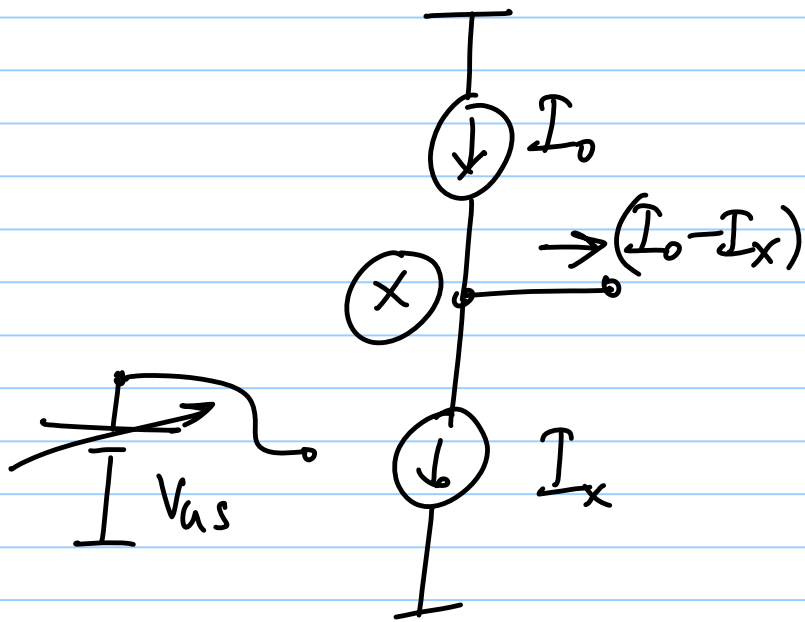


MOSFET

If $I_o > I_x$, $V_x \uparrow$
(we want to $\uparrow V_{gs}$)


If $I_o < I_x$, $V_x \downarrow$
(we want to $\downarrow V_{gs}$)

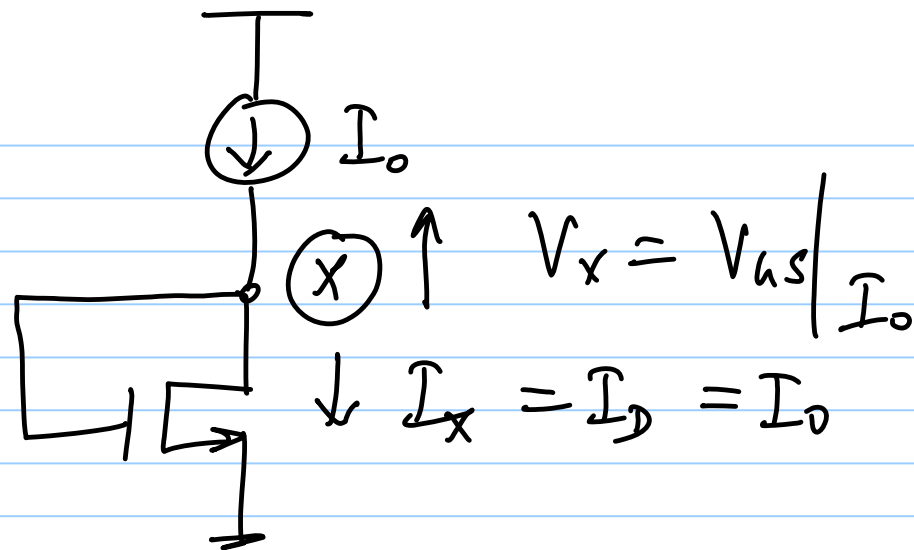If $I_o = I_x$, V_x constant
(we want constant V_{gs})



Negative feedback circuit that sets V_{gs} so that $I_D = I_o$

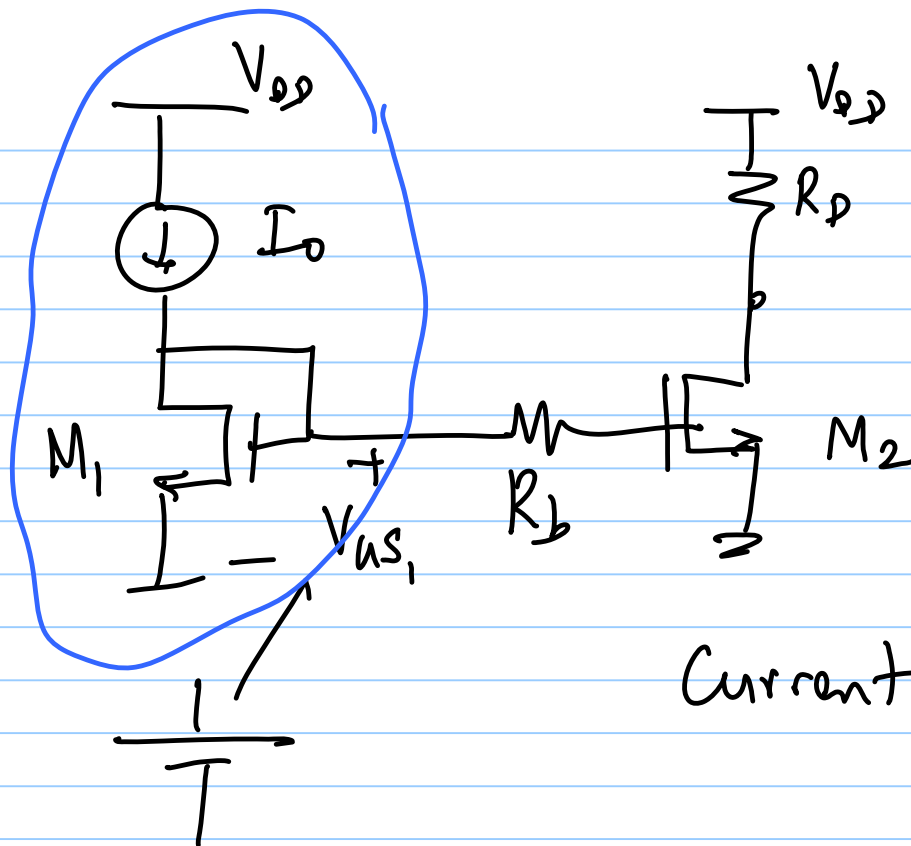$V_{DS} = V_{GS} = V_{GS}$, Device is in saturation



Current Mirror