
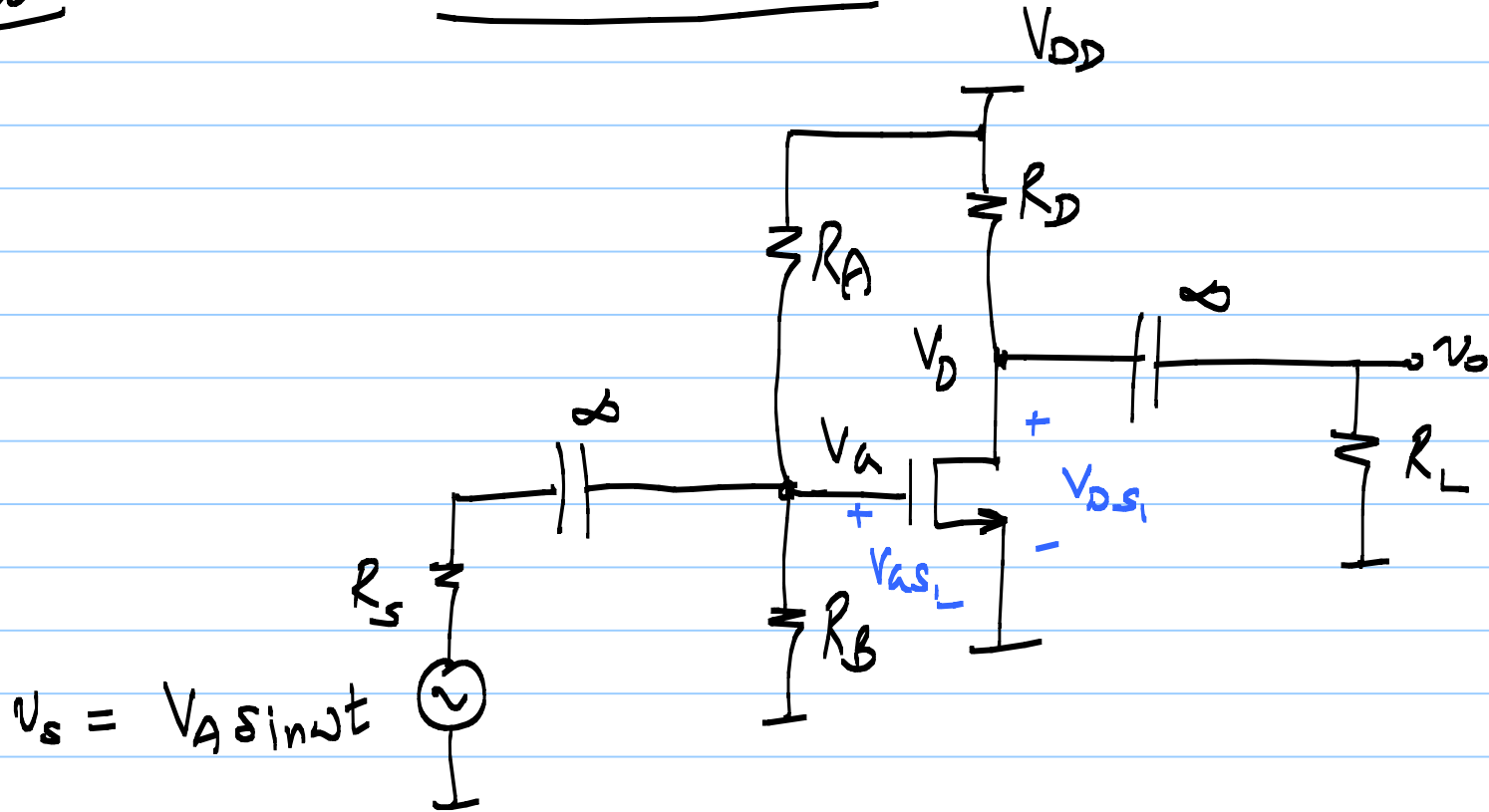


20/8/2020

Lecture 10

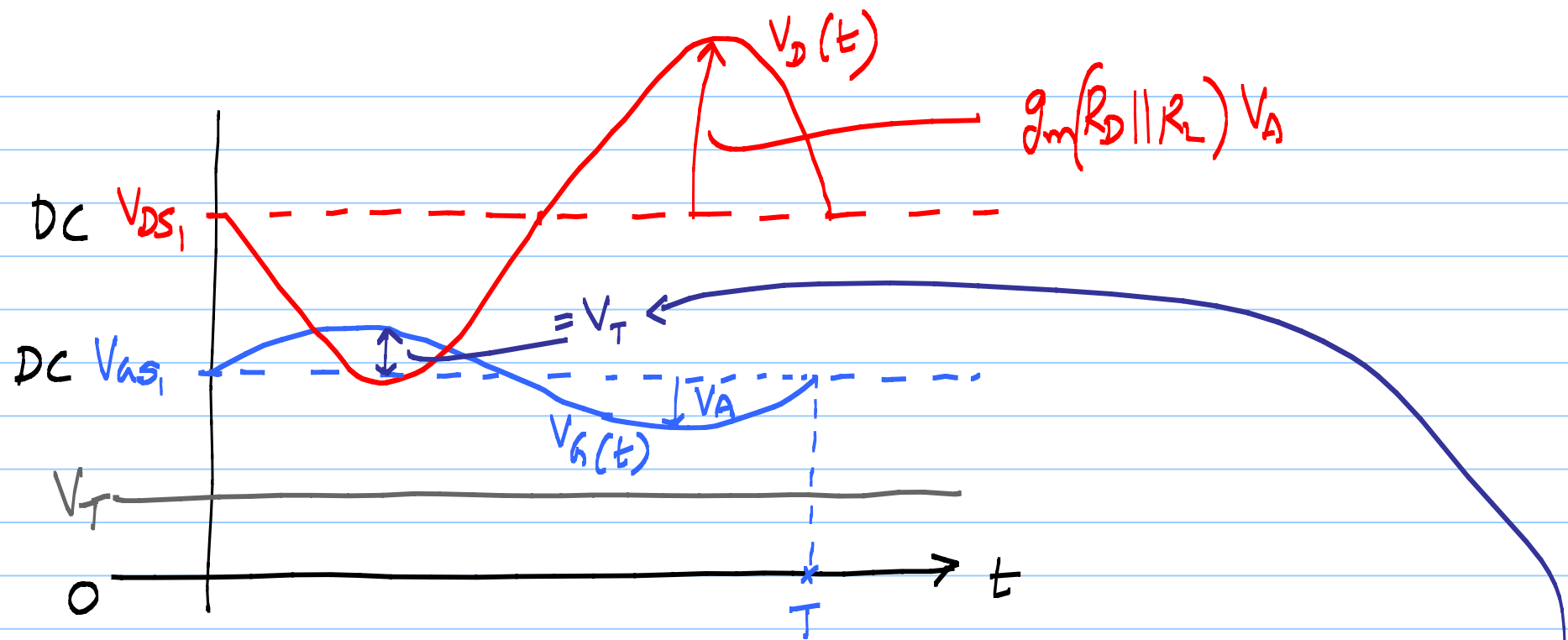


* $v_{DS}(t) > v_{GS}(t) - V_T$ at all times in the period
so that device is in saturation.



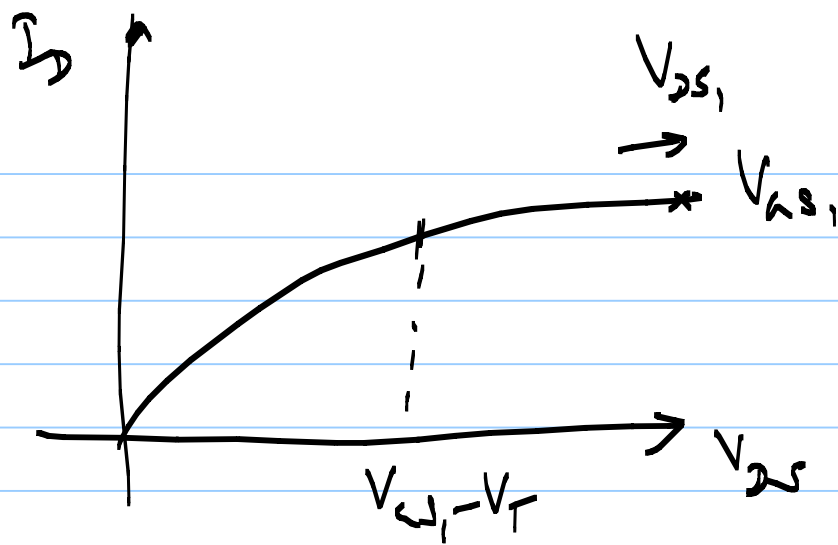1) Limit of V_A : instantaneous $V_{DS}(t) = V_{as}(t) - V_T$

$$(N) \quad V_D(t) = V_{gs}(t) - V_T$$


$V_{A_{max}}$ = maximum value of V_A that keeps M_1 from going into triode (+ve Half Cycle of input sinusoid)



larger V_{DS}
 = larger V_{Amax}

$$V_{DS,sat} - g_m (R_D || R_L) \cdot V_{Amax} = V_{GS} + V_{Amax} - V_T$$

$$V_{Amax} = \frac{V_{DS,sat} - V_{GS} + V_T}{1 + g_m (R_D || R_L)}$$

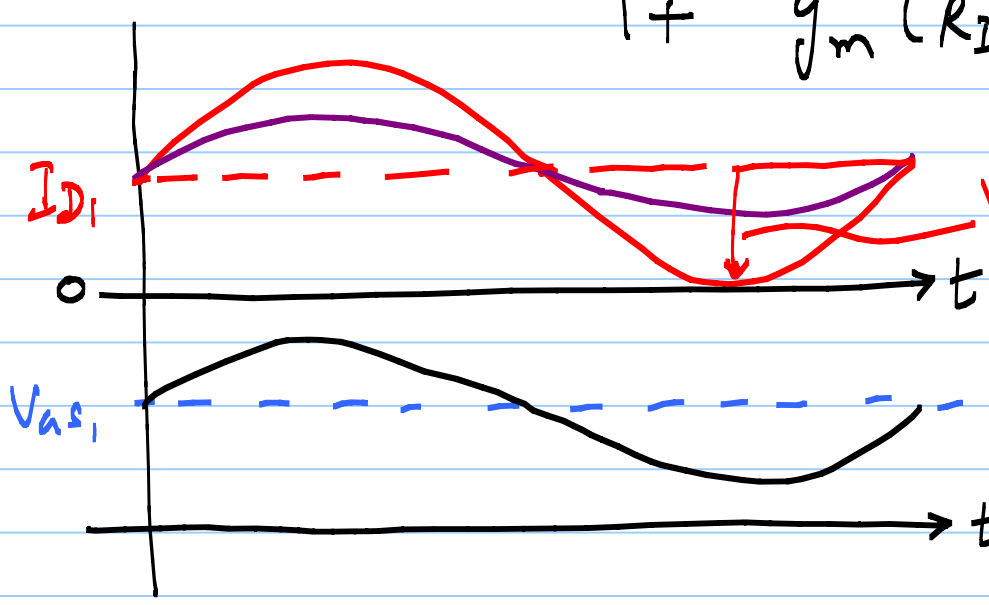

$$I_D = I_{D1} + i_d$$

$$I_D(t) = I_{D1} + g_m V_A \sin \omega t$$

@ $V_A = V_{Amax2}$
 $I_D(t) = 0$ @ neg. peak.


Device M_1 just cuts off. @ V_{Amax_2}

Any further increase in $V_A \rightarrow$ clipped sinusoid (current)

Set $I_D(t) = 0$ @ -ve peak

$$I_{D1} - g_m V_{Amax_2} = 0 \Rightarrow V_{Amax_2} = \frac{I_{D1}}{g_m}$$

What is $V_{D0}(t)$ when $I_D(t) = 0$?

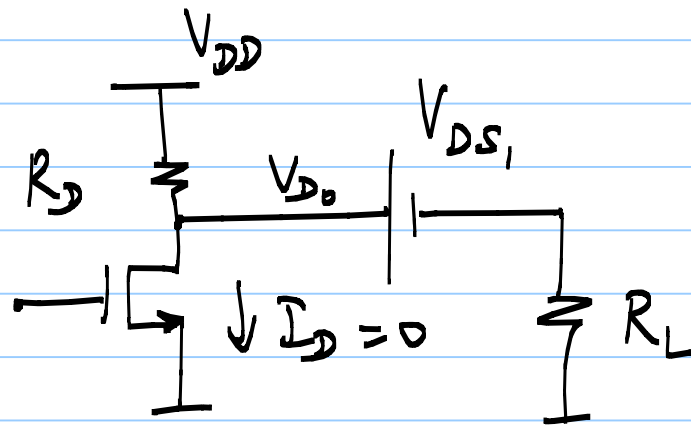

* $I_D = 0$

* KCL @ drain

$$\frac{V_{DD} - V_{D0}}{R_D} = \frac{V_{D0} - V_{DS1}}{R_L}$$

$$V_{D0} = \frac{R_L V_{DD} + R_D V_{DS1}}{R_L + R_D}$$

Swing limits of CSA


* In general, $V_{A_{max,1}} \neq V_{A_{max,2}}$

* swing limit = $\min\{V_{A_{max,1}}, V_{A_{max,2}}\}$

* good design: choose $V_{A_{max,1}} = V_{A_{max,2}}$

choose $(I_{D,1}, V_{DS,1})$ $\left\{ \begin{array}{l} \text{a) +ve H.C. peak, } M_1 \text{ just enters triode} \\ \text{b) -ve H.C. peak, } M_1 \text{ just cuts off} \end{array} \right.$

Example:

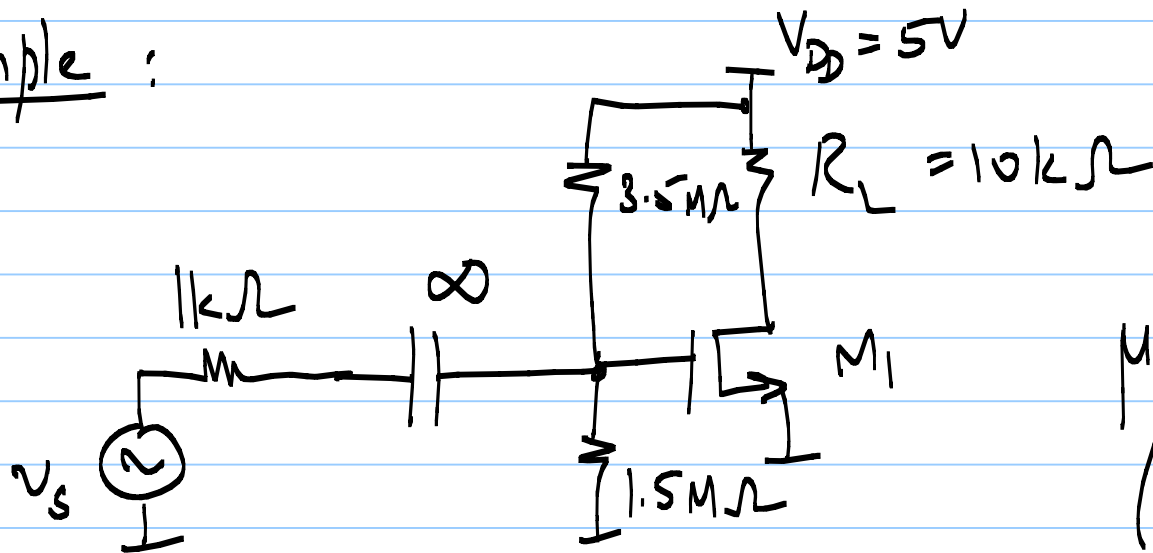

$$V_T = 1V$$

$$\mu_n C_{ox} = 100 \mu A/V^2$$

$$\left(\frac{W}{L}\right) = 10$$

$$V_{as_1} = 1.5V$$

$$I_{D_1} = \frac{1}{2} 100 \times 10^{-6} \times 10 \times (0.5)^2 = 125 \mu A$$

$$V_{DS_1} = V_{DD} - I_{D_1} \cdot R_L = 5 - (125 \times 10^{-6}) (10 \times 10^3) \\ = 3.75V$$

$$g_{m_1} = \frac{2I_{D_1}}{V_{as_1} - V_T} = \frac{0.25mA}{0.5} = 0.5 mS$$

inc. gain

$$G = -g_{m_1} R_L = -5$$

Triode limit (true HC)

$$V_a = 1.5V + V_A \sin \omega t$$

$$V_D = 3.75V - 5V_A \sin \omega t$$

$$V_D = V_L - V_T$$

$$3.75 - 5V_{A_1} = 1.5 + V_{A_1} - 1$$

$$V_{A_1} = \frac{3.25}{6} = 541.67 \text{ mV} = V_{A_{\max 1}}$$

Cut off limit (-ve H.C.)

$$I_D = I_{D_1} + g_m V_A \sin \omega t$$

$$= 125 \mu\text{A} + (0.5 \text{ mS}) V_A \sin \omega t$$

$$V_{A_2} = \frac{I_{D_1}}{g_m} = \frac{125 \mu\text{A}}{0.5 \text{ mS}} = 250 \text{ mV} = V_{A_{\max 2}}$$

$$V_{A_{\max}} = \min. \{ V_{A_1}, V_{A_2} \} = 250 \text{ mV}$$

