
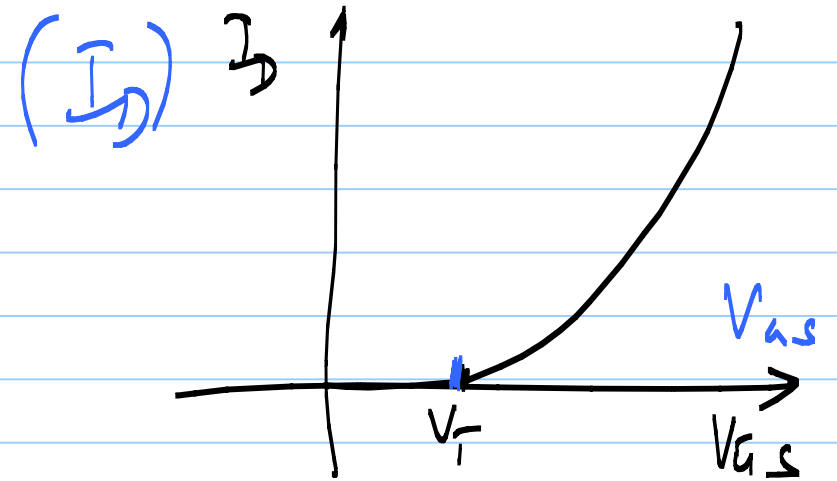
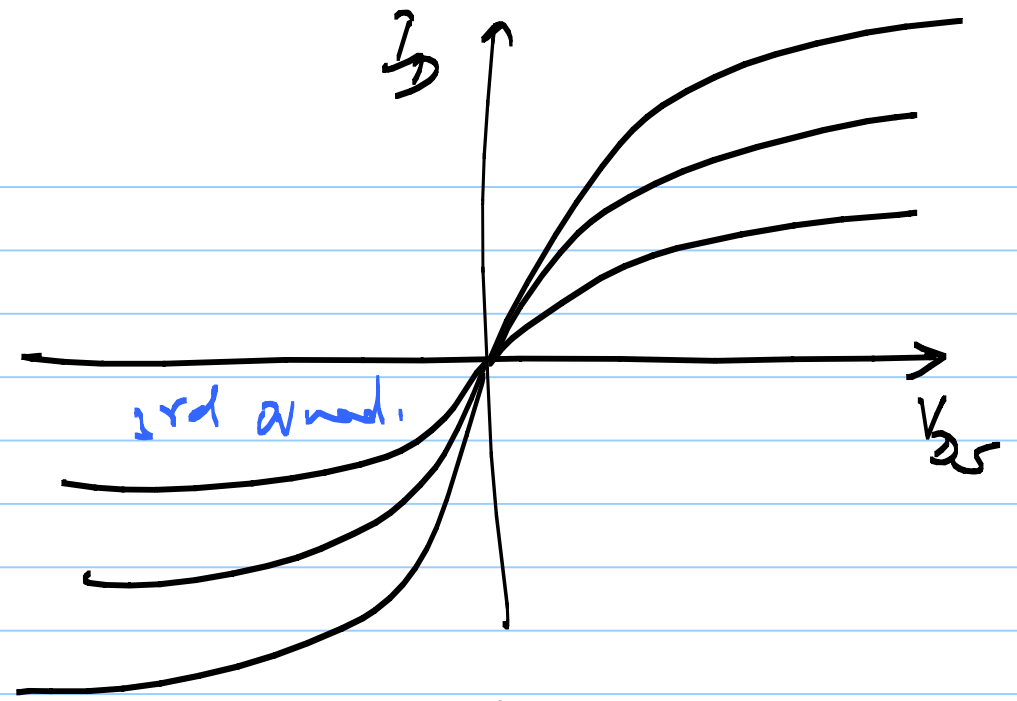


21/8/2020

Lecture 11

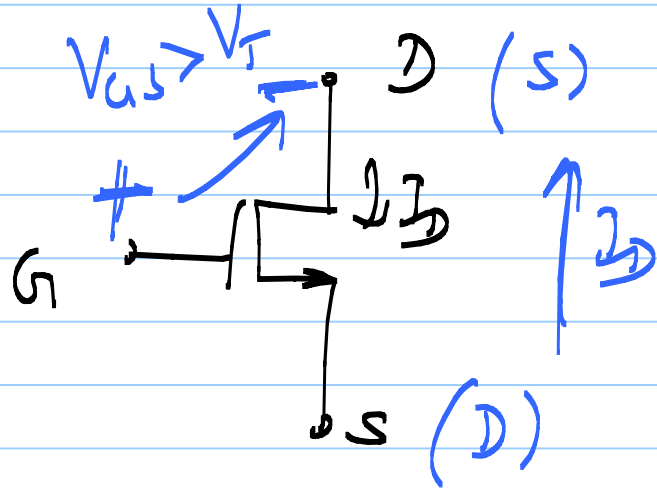


Cutoff condition @ V_{as}

$$I_D = 0 \Rightarrow V_{as} \leq V_T$$

$$V_{as} = V_T \text{ limit}$$

$$V_{as,1} + \underbrace{V_A \sin \omega t}_{-1} = V_T$$
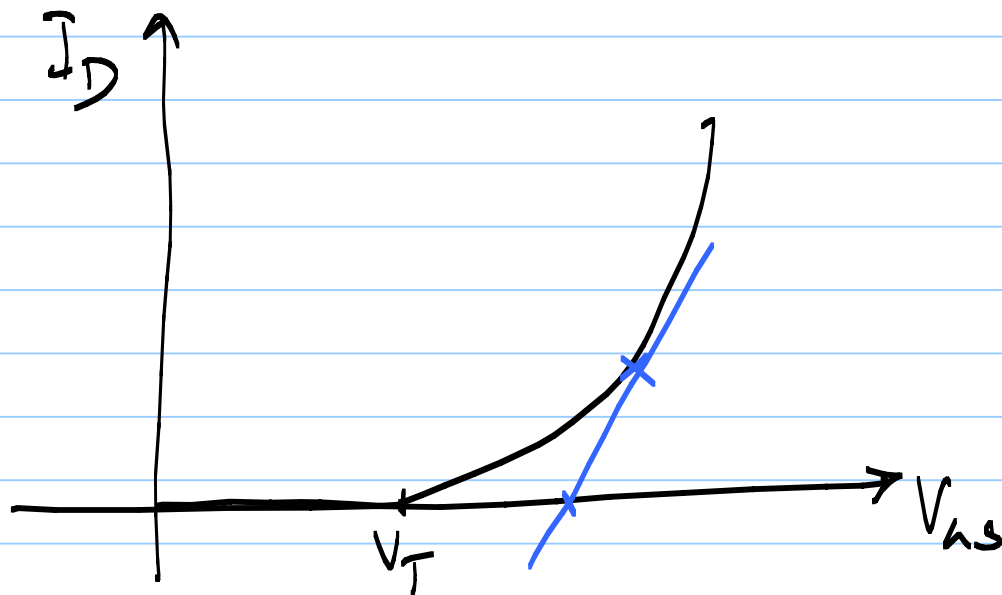
$$V_{A3} = V_{as,1} - V_T = 1.5V - 1V = 500mV$$



In sat. region

$$I_D = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right) (V_{gs} - V_T)^2$$

✓ No dep. on V_{ds}

$$I_D = f(V_{gs}, V_{ds})$$

$$I_D + i_d = f(V_{gs} + v_{gs}, V_{ds} + v_{ds})$$

$$= f(V_{gs}, V_{ds}) + \overset{\rightarrow g_m}{\frac{\partial I_D}{\partial V_{gs}}} \cdot v_{gs} + \frac{\partial I_D}{\partial V_{ds}} \cdot v_{ds}$$

$$+ \frac{1}{2} \frac{\partial^2 I_D}{\partial V_{gs}^2} \cdot v_{gs}^2 + \frac{1}{2} \frac{\partial^2 I_D}{\partial V_{ds}^2} \cdot v_{ds}^2$$

$$+ \frac{\partial^2 I_D}{\partial V_{gs} \partial V_{ds}} \cdot v_{gs} \cdot v_{ds} + \dots$$

$$\cancel{I_D} + i_d = \cancel{I_D} + \underbrace{g_m v_{gs}}_{\text{desired term (A)}} + \underbrace{\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right) \cdot v_{gs}^2}_{\text{undesired term (NL) (B)}}$$

$$(B) \ll (A)$$

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right) \cdot v_{gs}^2 \ll g_m v_{gs}$$

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right) \cdot v_{gs}^2 \ll \mu_n C_{ox} \left(\frac{W}{L}\right) (V_{as} - V_T) \cdot v_{gs}$$

$$\underline{\underline{v_{gs} \ll 2 (V_{as} - V_T)}}$$

In our example : $V_{gs} = \min \{ V_{A_1}, V_{A_2} \} = 0.25V$

$$2(V_{gs} - V_T) = 1V$$

$$\textcircled{B} \approx 25\% \text{ of } \textcircled{A}$$

{ Not small
enough }

THD : "Total Harmonic Distortion"
% age.