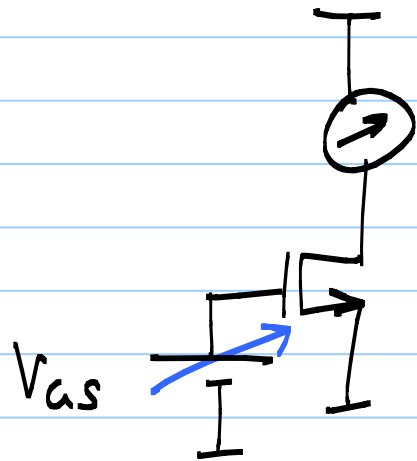


26/8/2020

## Lecture 13


### Negative feedback biasing



Ammeter =  $I_D$

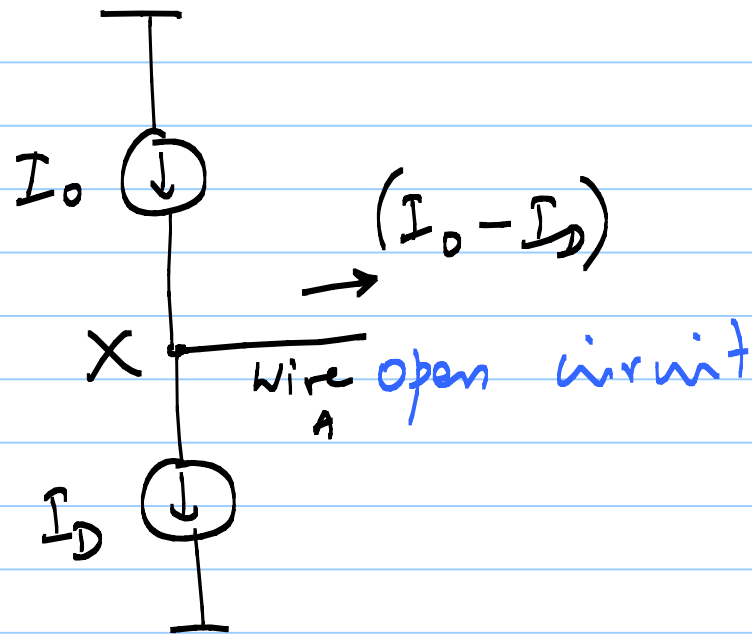- 1) Apply  $V_{as}$
- 2) Measure  $I_D$
- 3) If  $I_D > I_0$ ,  $\downarrow V_{as}$
- 4) If  $I_D < I_0$ ,  $\uparrow V_{as}$
- 5) If  $I_D = I_0$ ,  $V_{as} = \text{same as before}$

$(I_0 - I_D) \equiv$  comparing  $I_0$  with  $I_D$




In a MOSFET:  
 $V_{as}$  is cause  
 $I_D$  is effect

If wire A is open

circuited:

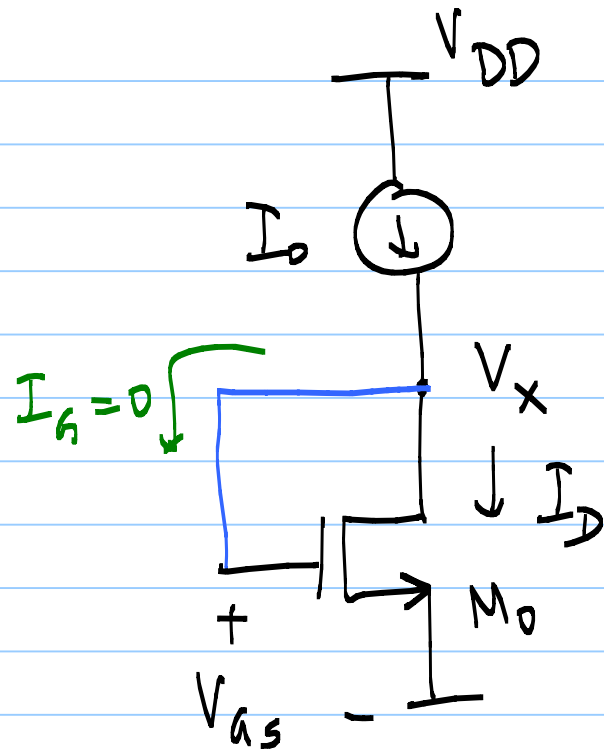- 1) If  $I_o > I_D$ :  $V_x \uparrow$   
 (need to  $\uparrow V_{as}$ )
- 2) If  $I_o < I_D$ :  $V_x \downarrow$   
 (need to  $\downarrow V_{as}$ )
- 3) If  $I_o = I_D$ :  $V_x$  stays  
 constant  
 (need to keep  $V_{as}$   
 at same value)



\* Connect X to G: Valid


\*  $I_G = 0 \Rightarrow I_D = I_0$

$$V_X = V_{GS} \quad \Bigg| \quad I_D = I_0$$

\* Verify that  $M_0$  is in saturation:

$$V_D = V_G \Rightarrow V_D > V_G - V_T$$

$M_0$  is in sat.


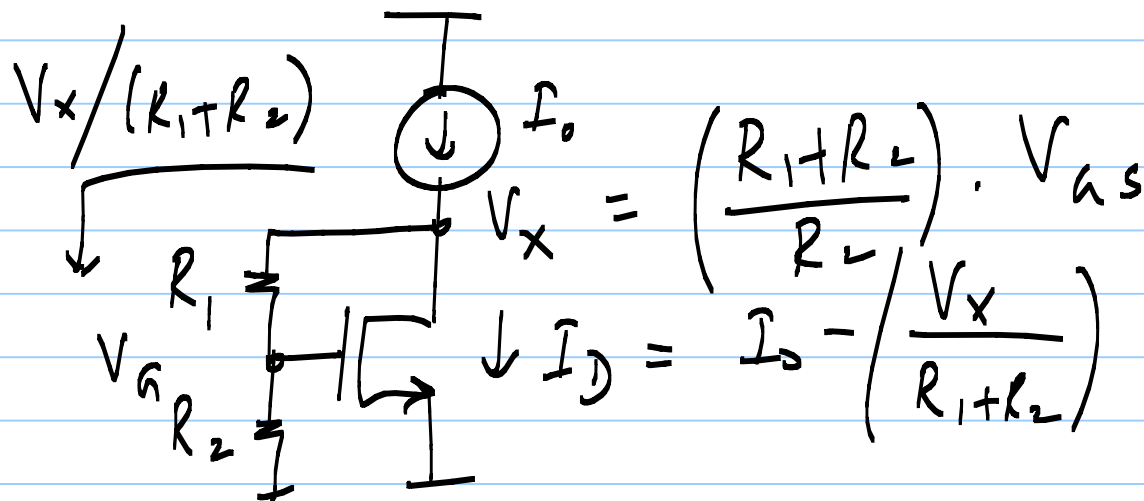


$$V_X = \left( \frac{R_1 + R_2}{R_2} \right) \cdot V_{GS}$$


$$I_D = I_0 - \left( \frac{V_X}{R_1 + R_2} \right)$$

CSA

$$R_b = R_A \parallel R_B$$

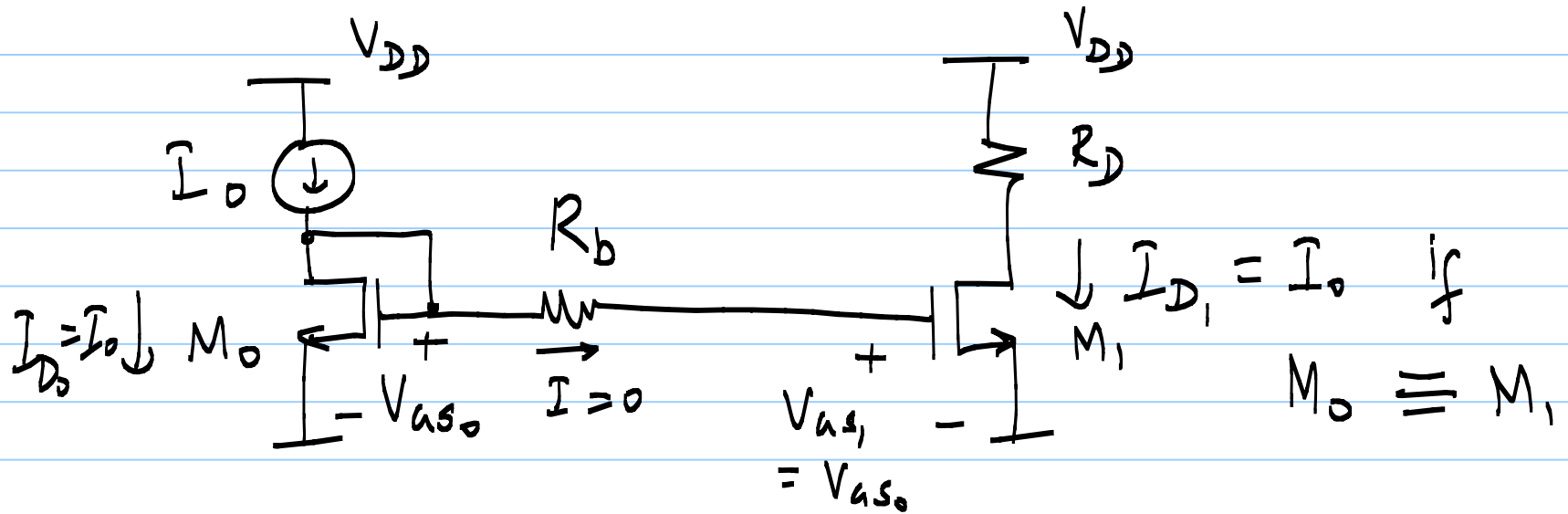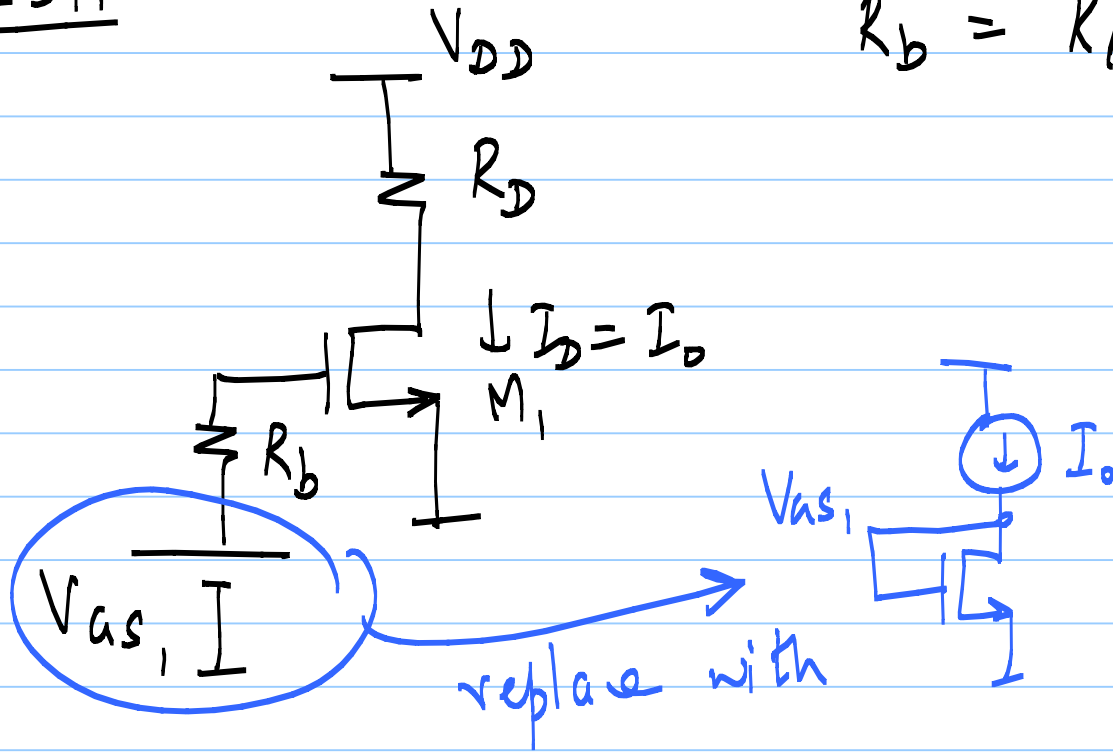

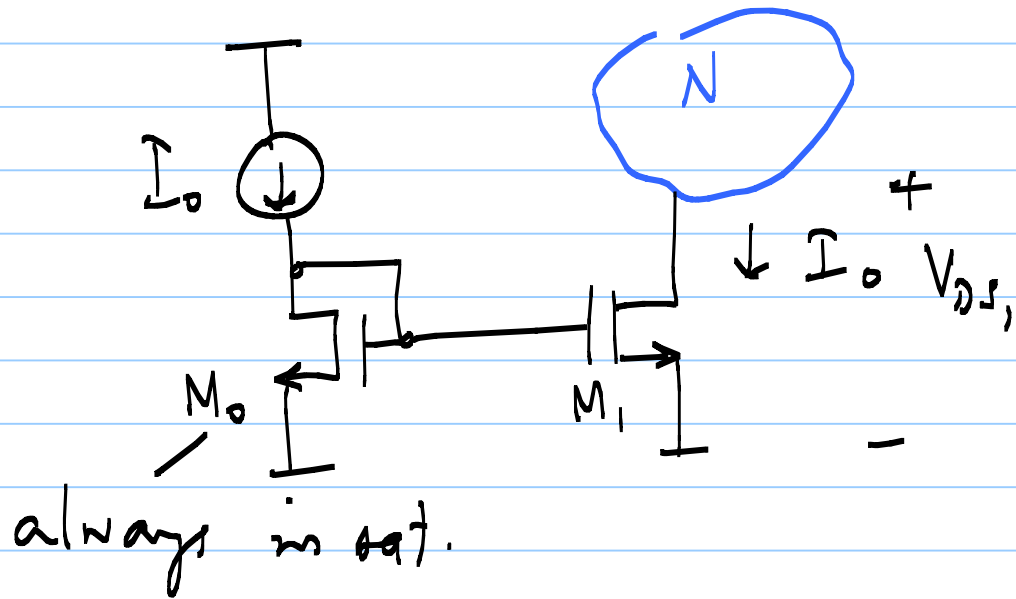$M_0 \equiv M_1$  means same  $\mu_n, C_{ox}, V_T, \left(\frac{W}{L}\right)$   
 { same W and L }



"Current Mirror"

works well as long  
 as  $V_{DS1} \geq V_{GS1} - V_T$   
 ( $M_1$  is in sat.)

