
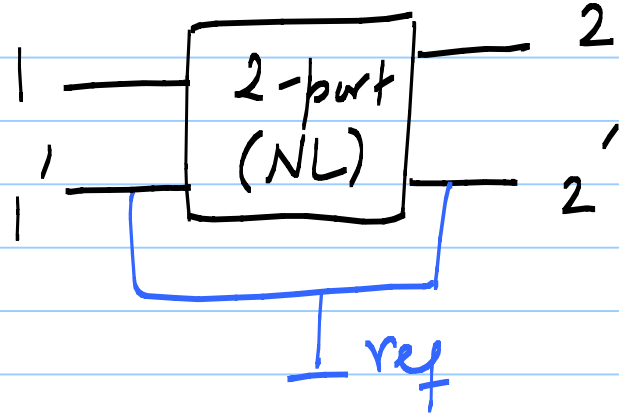


15/9/20


Lecture 24

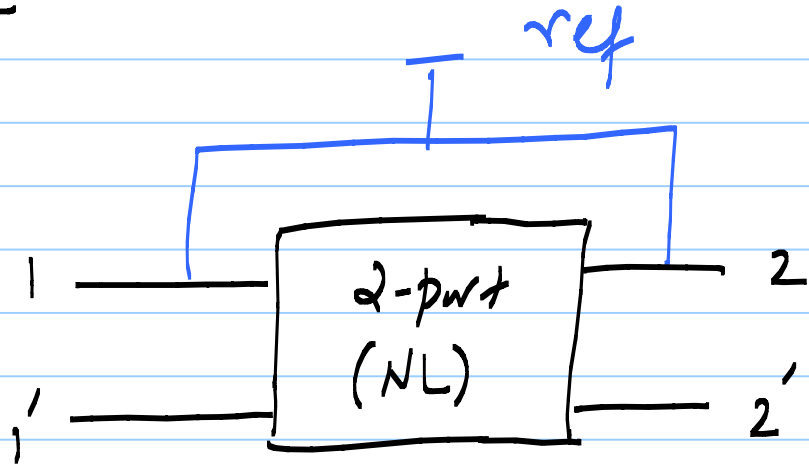


8T 2-port #1




8T 2-port #2

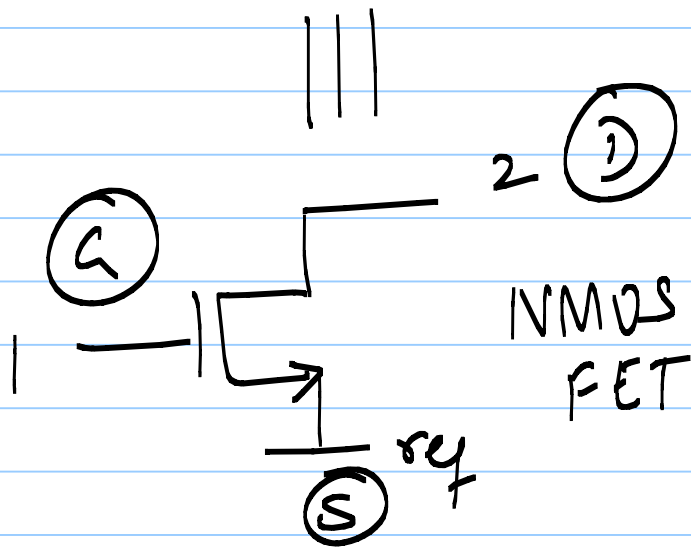



NMOS FET


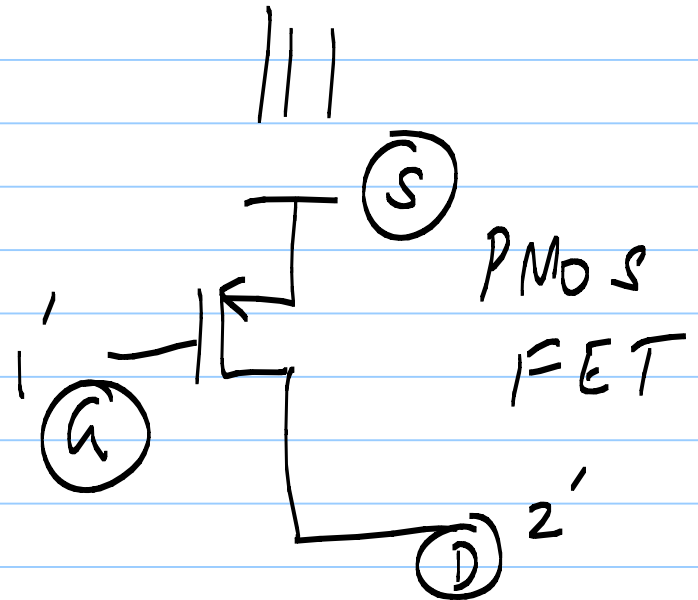


PMOS FET

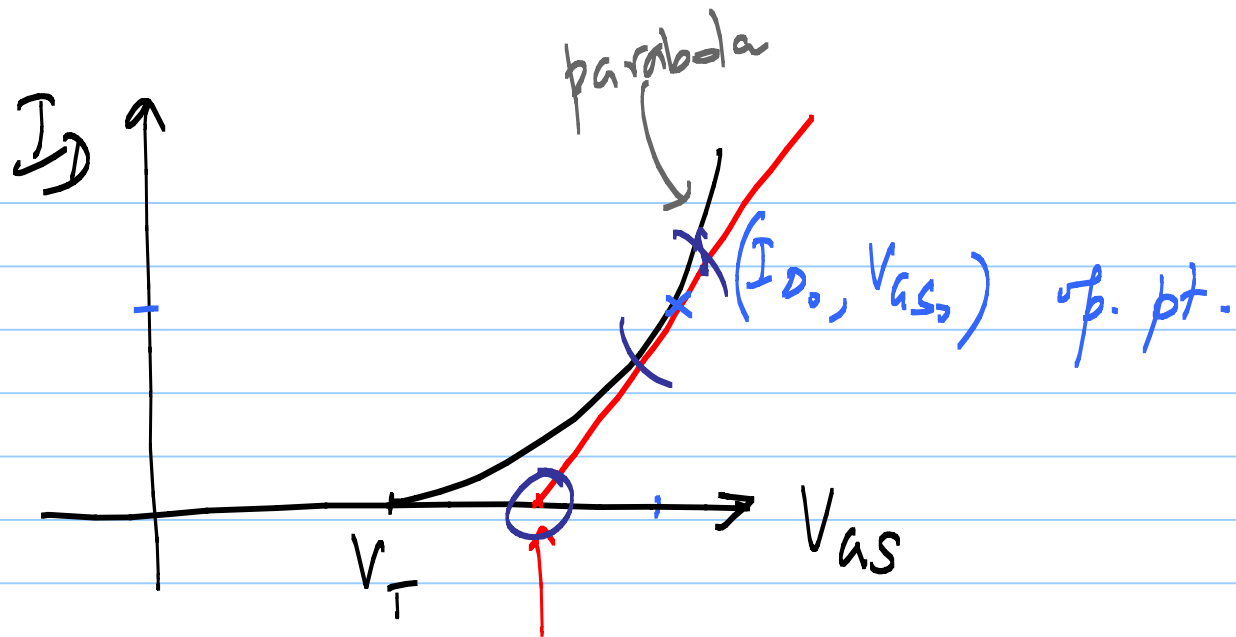

$I_D = 0$ point assuming linear approx.

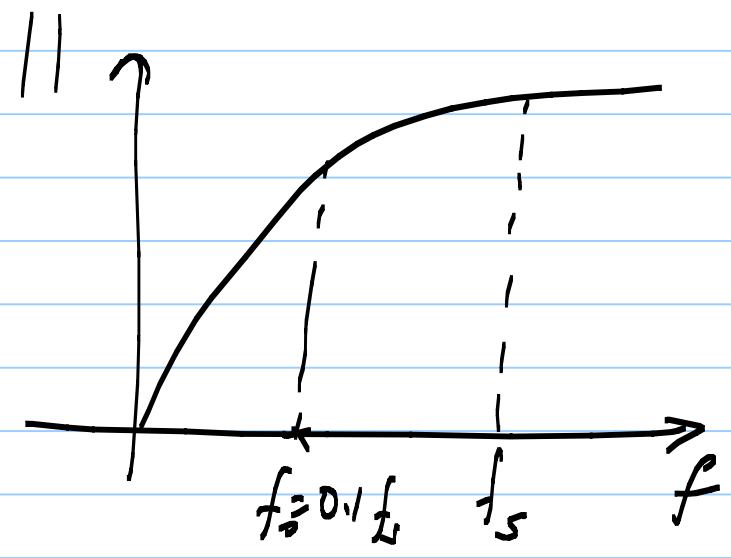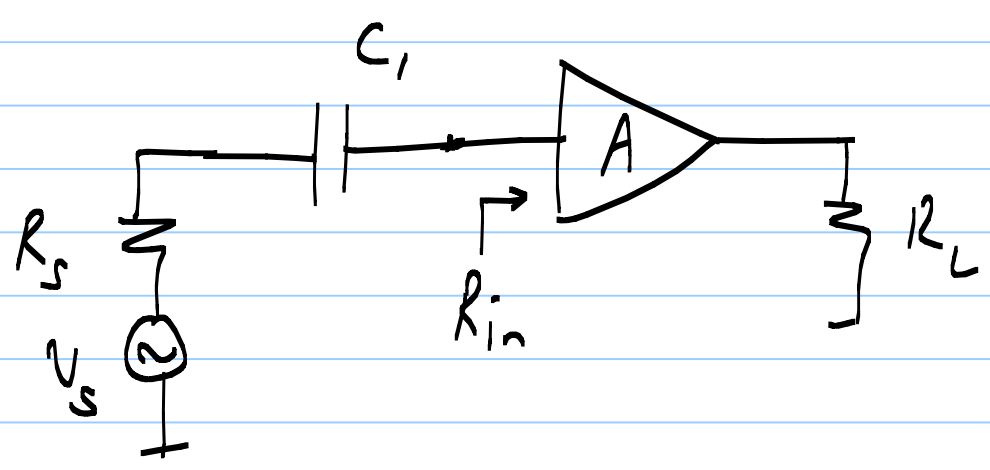

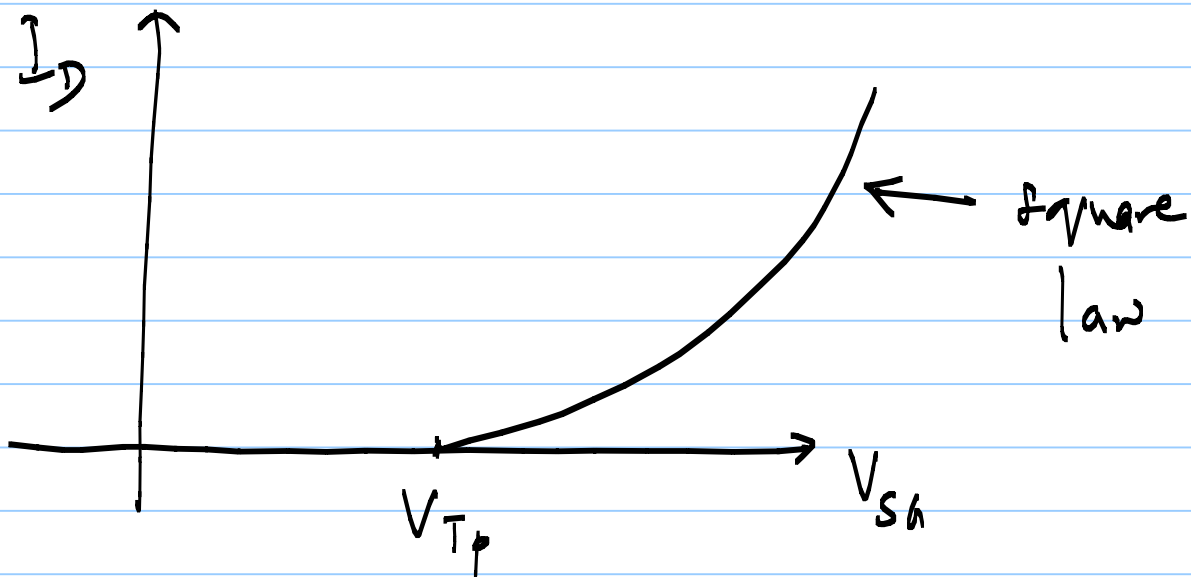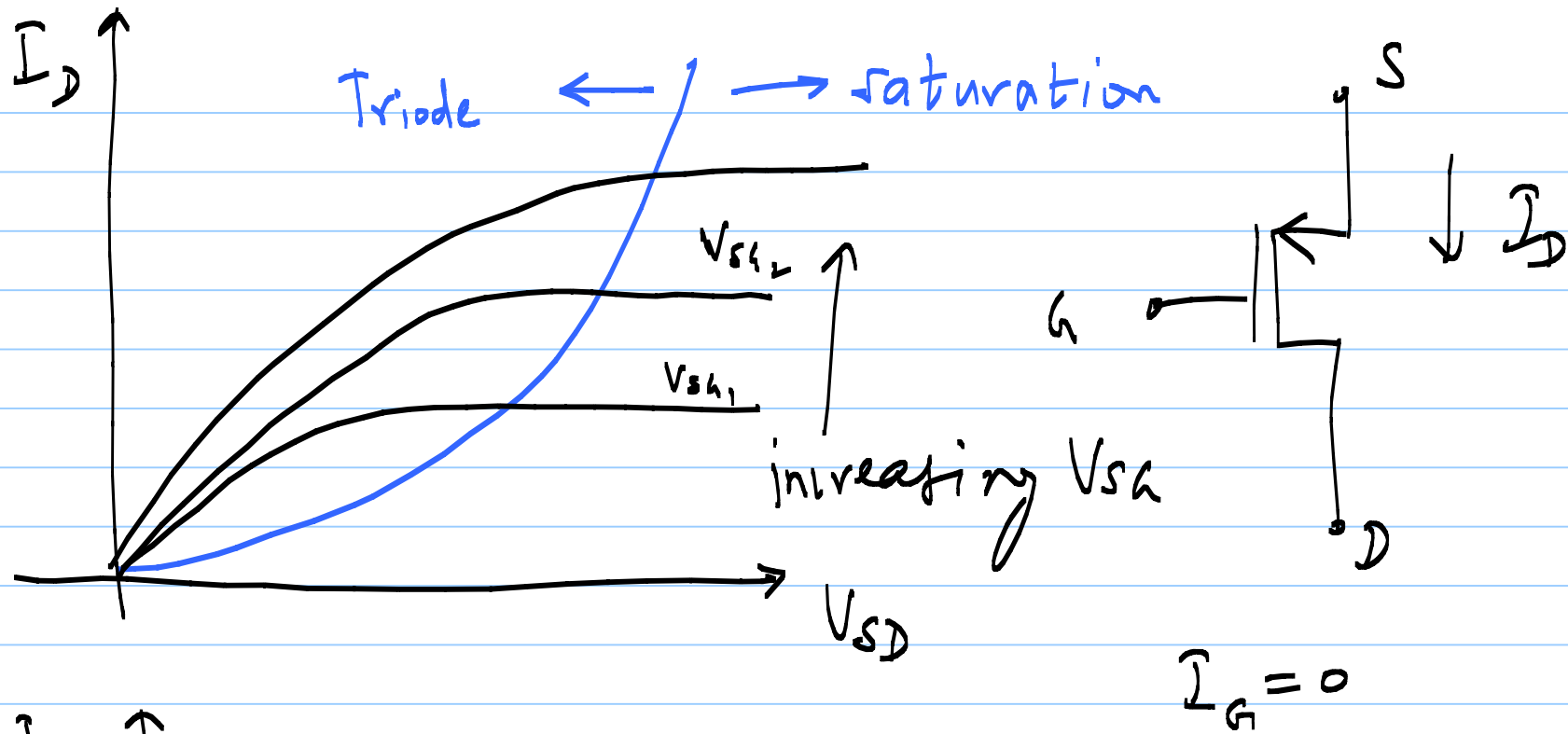

$$I_D = 0 \quad \text{if} \quad V_{GS} < V_{TP} \quad (\text{OFF})$$

$$= \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L} \right) \left[V_{GS} - V_{TP} \right]^2 \quad \text{if} \quad V_{GS} > V_{TP} \quad (\text{SAT})$$

and

$$V_{SD} \geq V_{GS} - V_{TP}$$

i.e. $V_D \leq V_G + V_{TP}$

$$= \mu_p C_{ox} \left(\frac{W}{L} \right) \left[(V_{GS} - V_{TP}) V_{SD} - \frac{V_{SD}^2}{2} \right] \quad (1 + \lambda_p V_{SD}) \quad (\text{TRIODE})$$

$$\text{if} \quad V_{GS} > V_{TP} \quad \text{and} \quad V_D > V_G + V_{TP}$$


Small-signal


$$y_{11} = 0 \quad ; \quad y_{12} = 0$$

$$Y_{21} = g_m = \mu_p C_{ox} \left(\frac{W}{L} \right) (V_{sg} - V_{TP})$$

HW 10 & other expressions for g_m
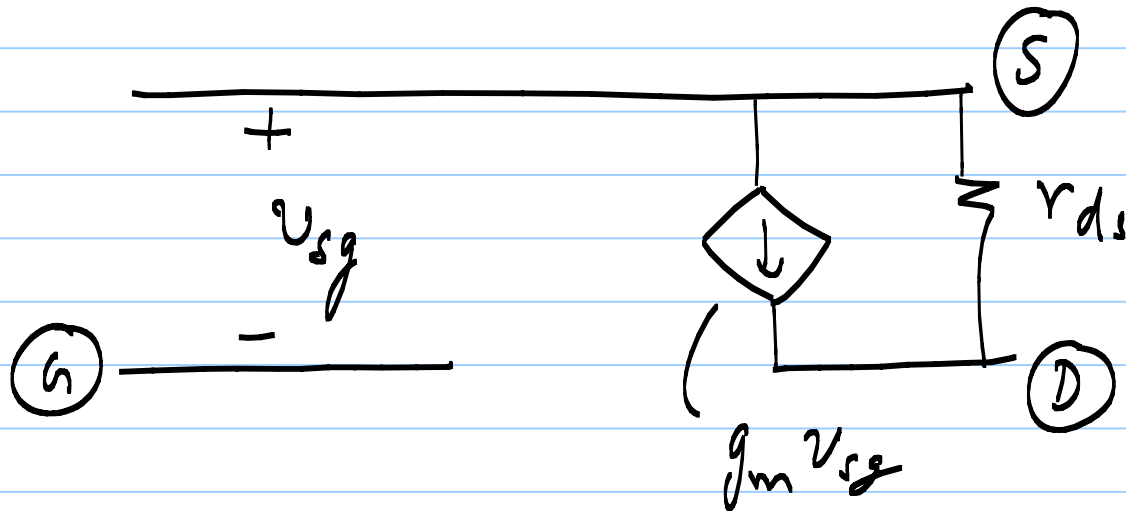
$$Y_{22} = g_{ds} = \frac{1}{r_{ds}} = \lambda_p \cdot I_D$$



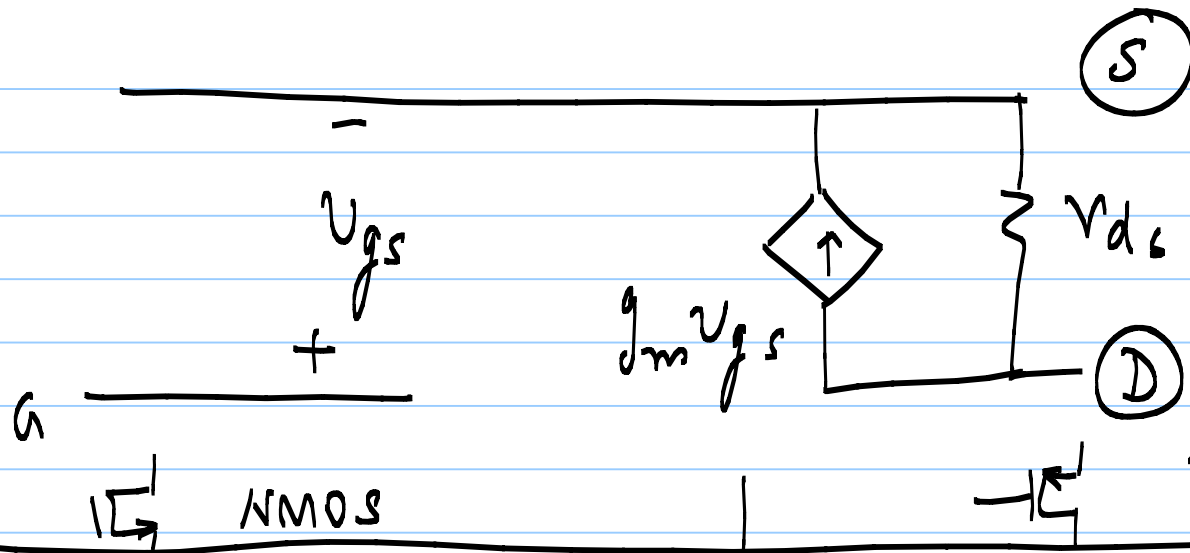

Exactly same
SS model as
for NMOS

* DC I_D flows into D

* For sat., $V_D \gg V_S$

$$V_D \geq V_G - V_{Tn}$$

* $V_{GS} \geq V_{Tn}$ for $I_D > 0$

* $V_{Tn} > 0$ for enhancement
mode device

DC I_D flows out of D

For sat. $\therefore V_D \ll V_S$


$$V_D \leq V_G + V_{Tp}$$

$V_{SG} \geq V_{Tp}$ for $I_D > 0$

$V_{Tp} > 0$ for enhancement
mode device


Common Source Amplifier

NMOS

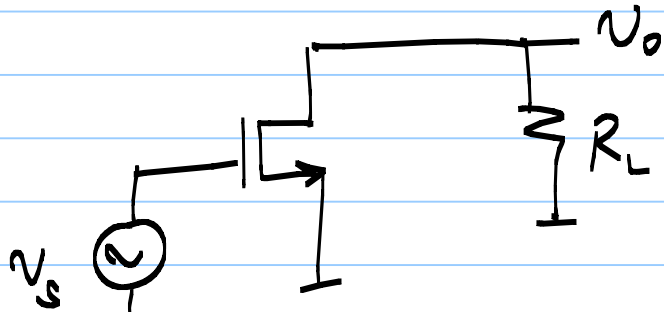


$$\frac{v_o}{v_s} = -g_{m_n} R_L$$

PMOS

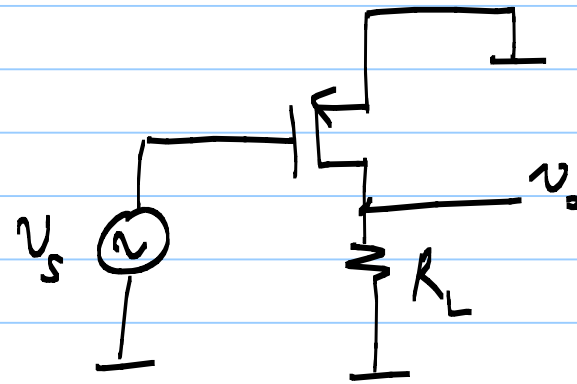


$$\frac{v_o}{v_s} = -g_{m_p} R_L$$

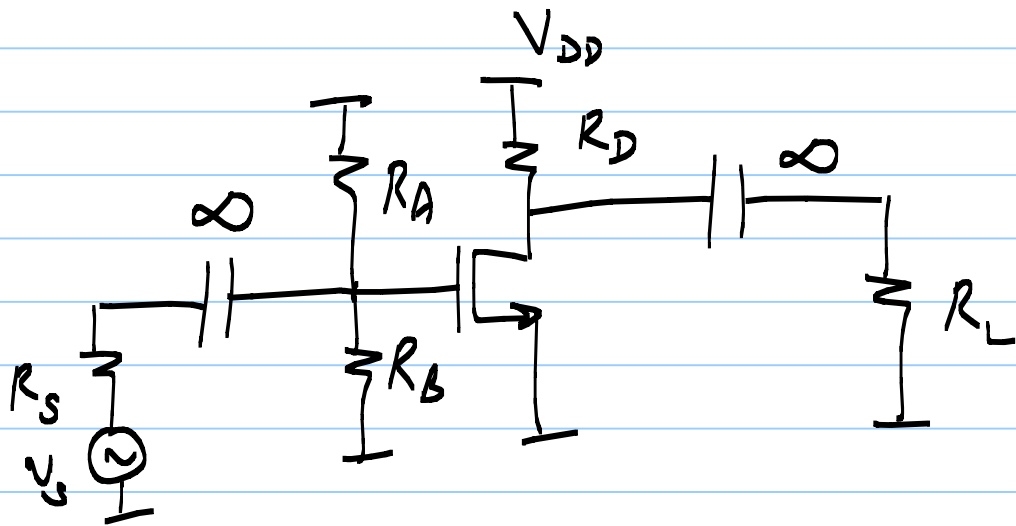

NMOS
CSA
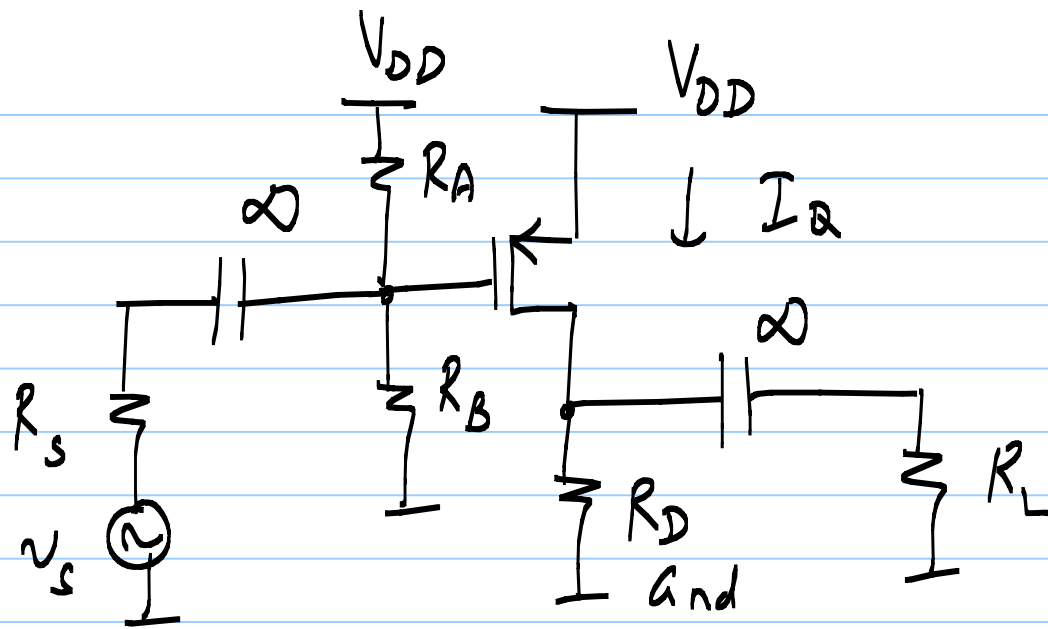
$$V_{GS_n} = \frac{R_B}{R_A + R_B} V_{DD}$$



PMOS
Common-Source
amplifier

$$I_Q = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L} \right) (V_{S_{G,Q}} - V_{T_P})^2$$

$$V_{S_{G,Q}} = \frac{R_A}{R_A + R_B} \cdot V_{DD} ; V_{S_{D,Q}} = V_{DD} - I_Q \cdot R_D$$

$$V_{S,Q} = V_{DD} ; V_{G,Q} = \frac{R_B}{R_A + R_B} \cdot V_{DD}$$

$$V_{D,Q} = I_Q \cdot R_D$$