
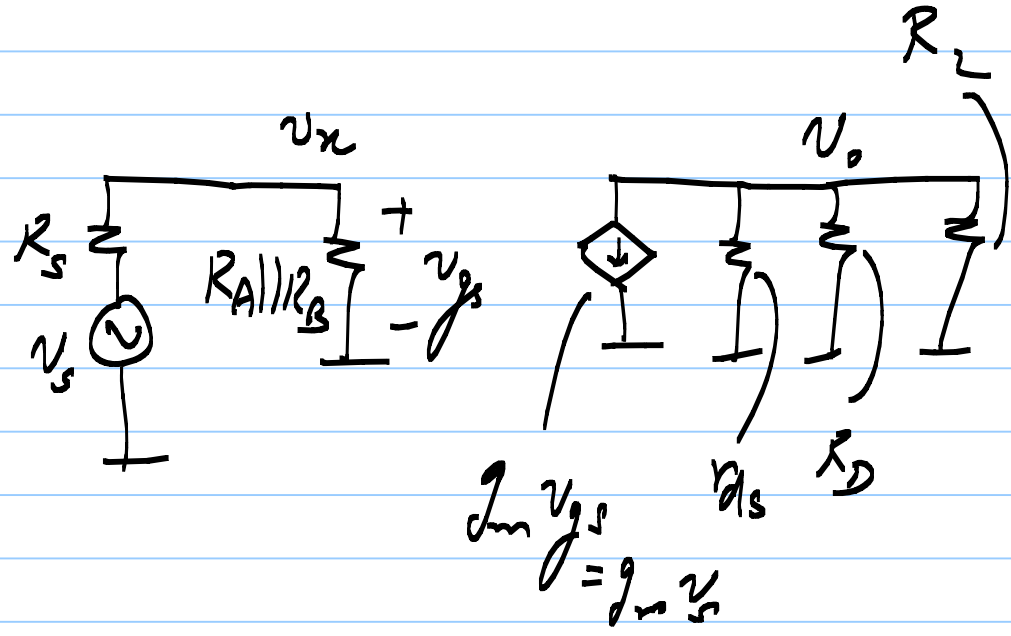


16/9/20

Lecture 25

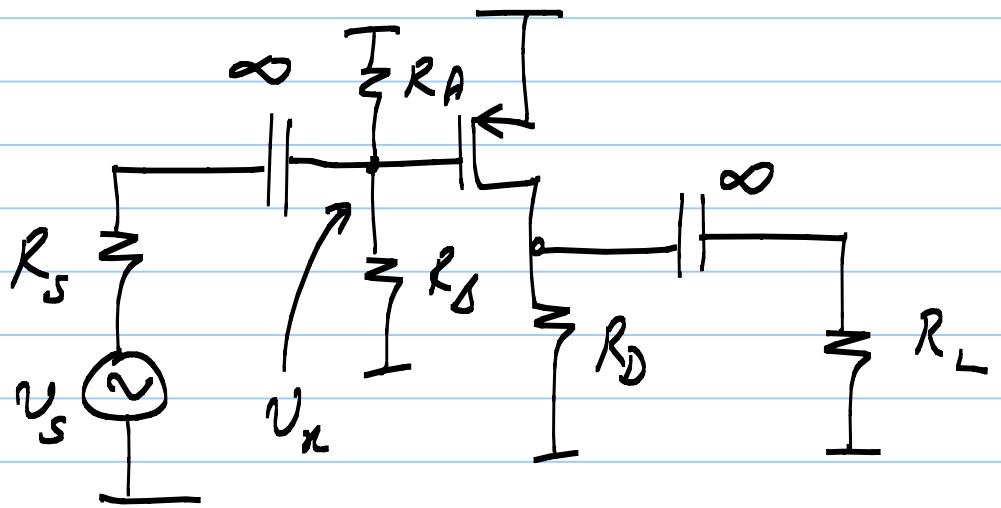

$$v_x = \frac{R_A || R_B}{R_s + R_A || R_B} \cdot v_s$$

choose  $R_A || R_B \gg R_s$   
 $\Rightarrow v_x \approx v_s$




$$v_o = -g_m (r_{ds} || R_D || R_L) \cdot v_s$$


HW 11

- Swing Limits :
- 1) Triode limit :  $V_D > V_G + V_{TP}$
  - 2) Cutoff limit :  $I_D = 0$


# Bias Stabilization

① Drain to gate f.b.

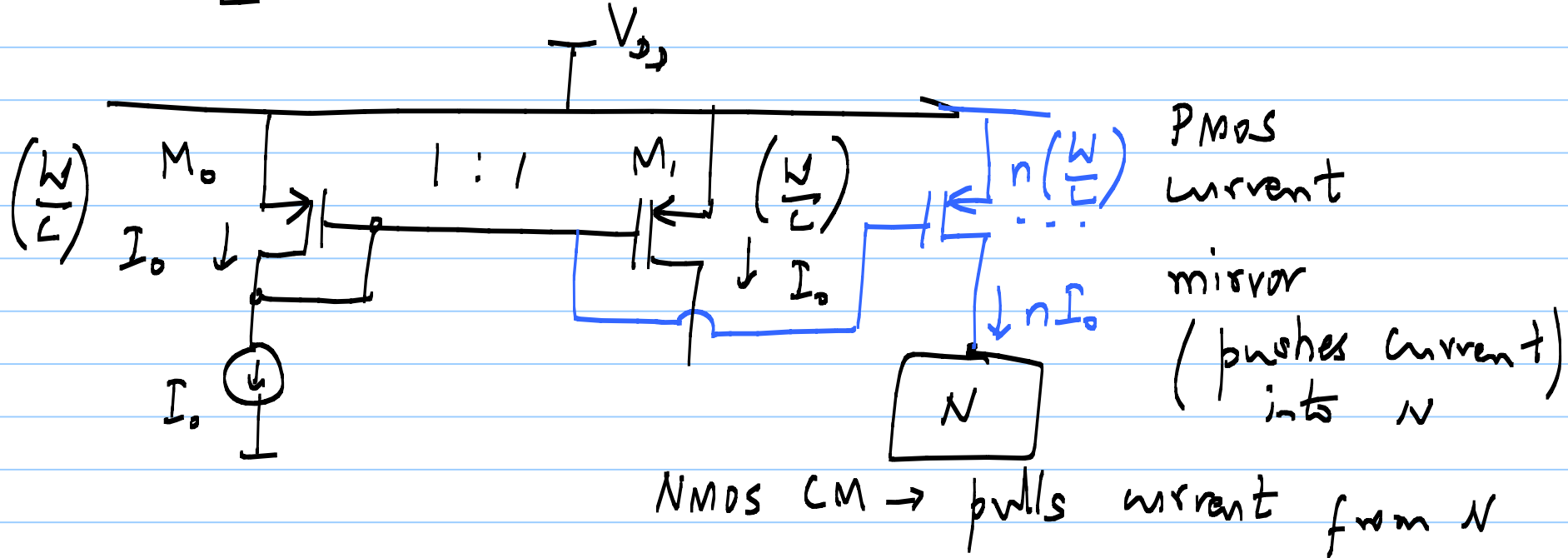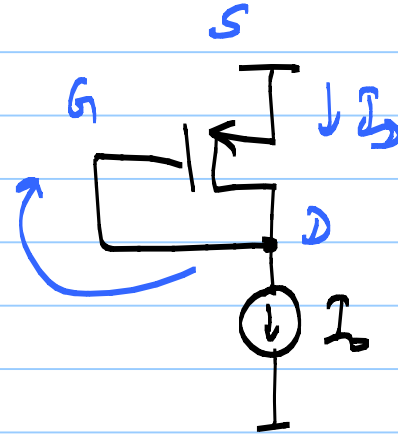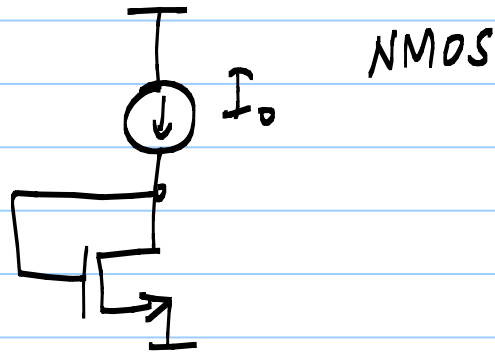

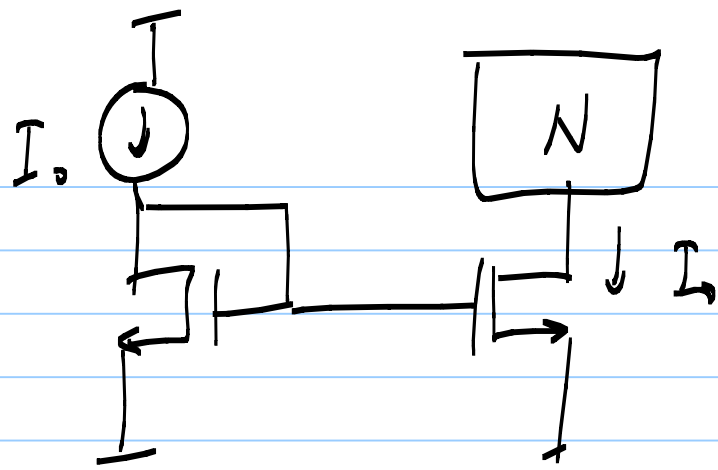


pulls current  $I_0$   
from  $N$ .

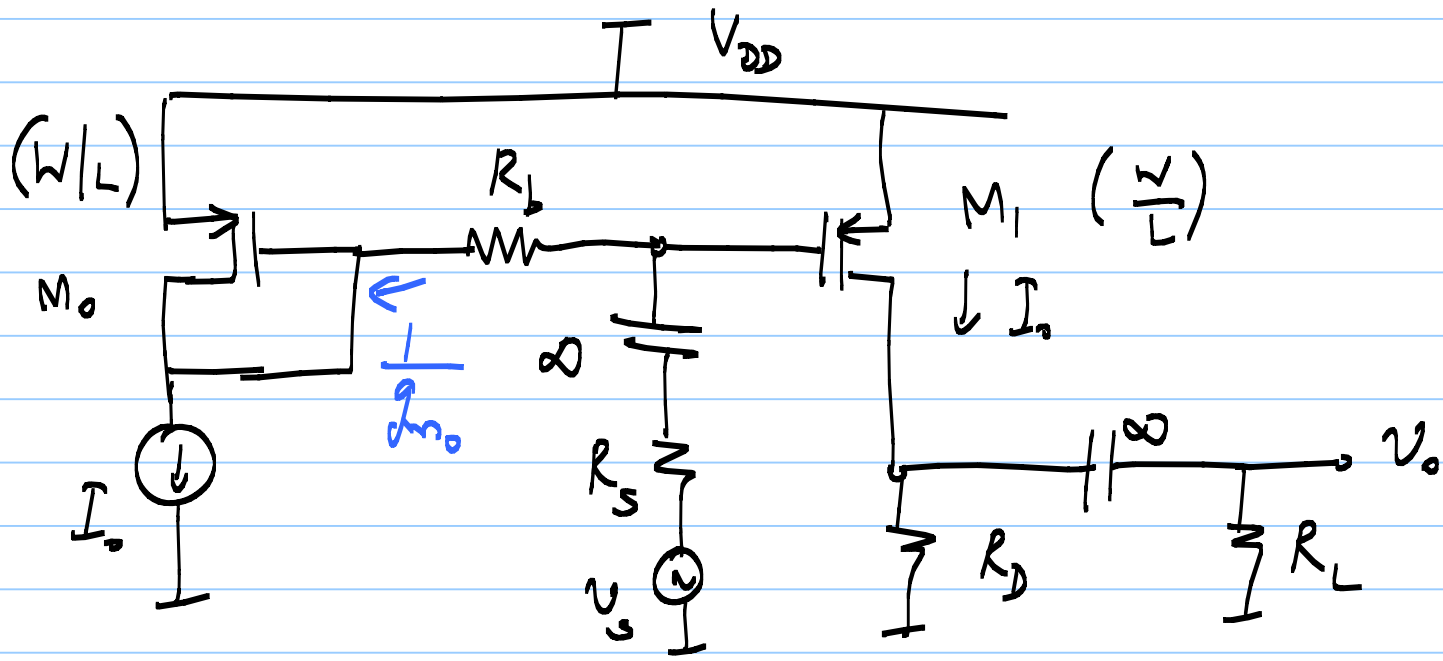


II

NMOS

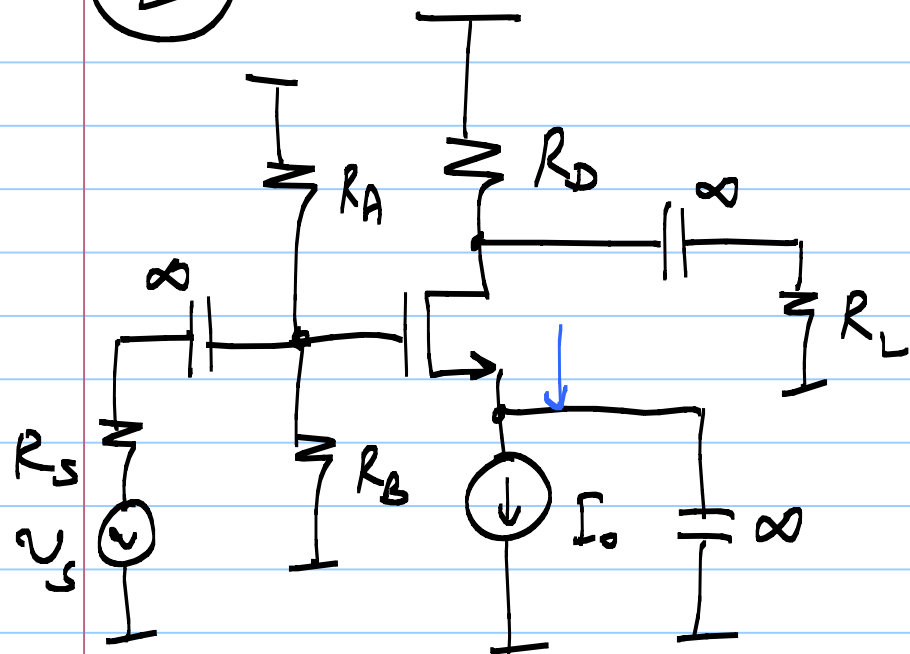

PMOS

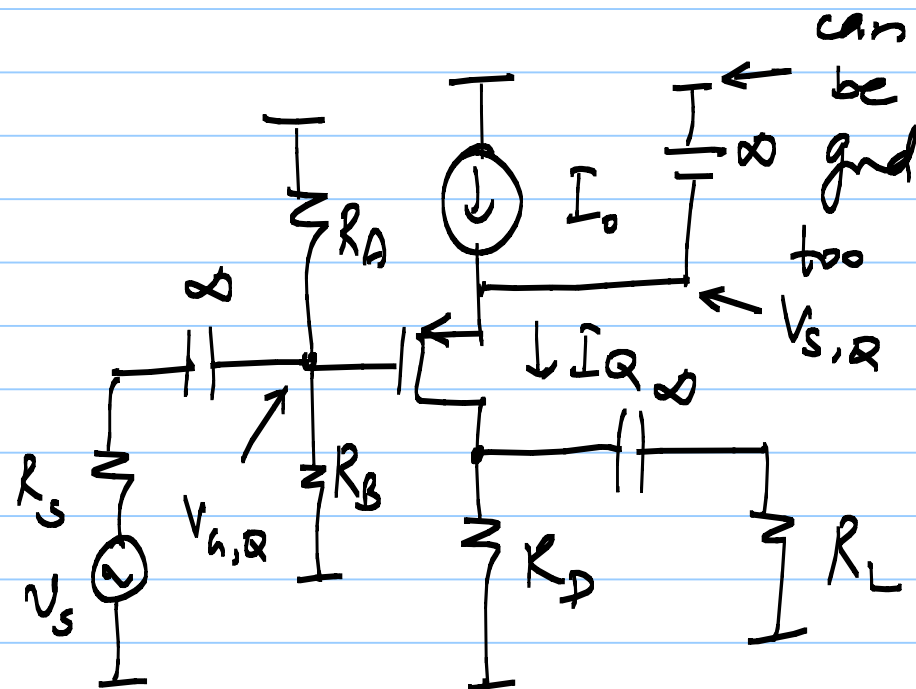

can be too V<sub>S,Q</sub> to be ground

$$I_Q = I_0$$

$$V_{G,Q} = \frac{R_B}{R_A + R_B} \cdot V_{DD}$$

$$V_{D,Q} = I_0 \cdot R_D$$

$$V_{S,Q} = V_{G,Q} + V_{SG,Q}$$

$$V_{SG,Q} = V_{Tp} + \sqrt{\frac{2I_0}{\mu_p C_{ox} \left(\frac{W}{L}\right)}}$$




HW12: SS analysis, swing limits

Case II & IV → HW13

SS Controlled Sources (SS eq. circuits are identical)

1) VCVS gain = 1 i.e.  $v_o = v_i$


PMOS Common Drain Amplifier

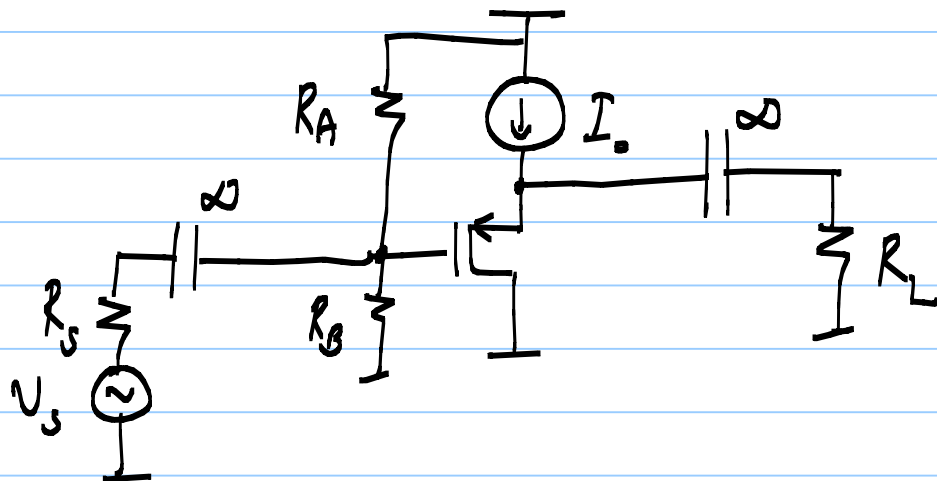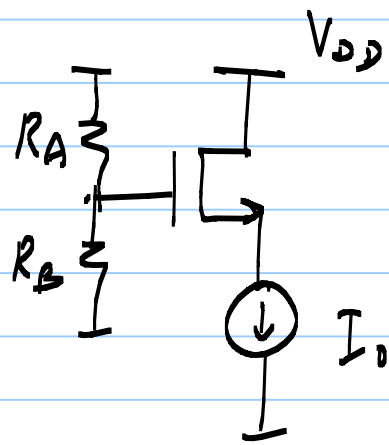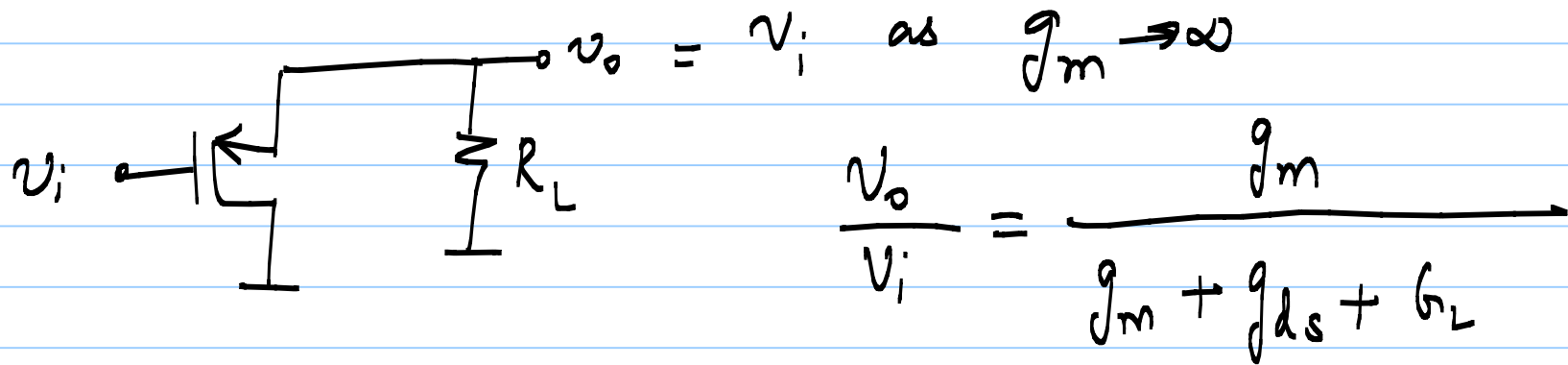

PMOS  
CDA

2) VCCS - TCA (Pmos)

$$i_o = \frac{v_i}{R}$$

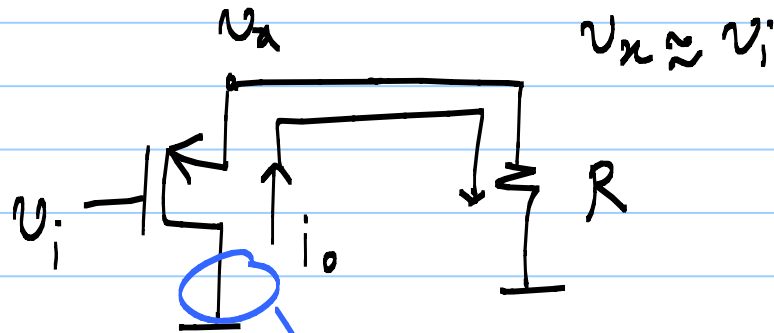

as  $g_m \rightarrow \infty$ ,  $v_d \approx v_i$

$$i_o = \frac{v_i}{R}$$

$R_L$  can be placed here