
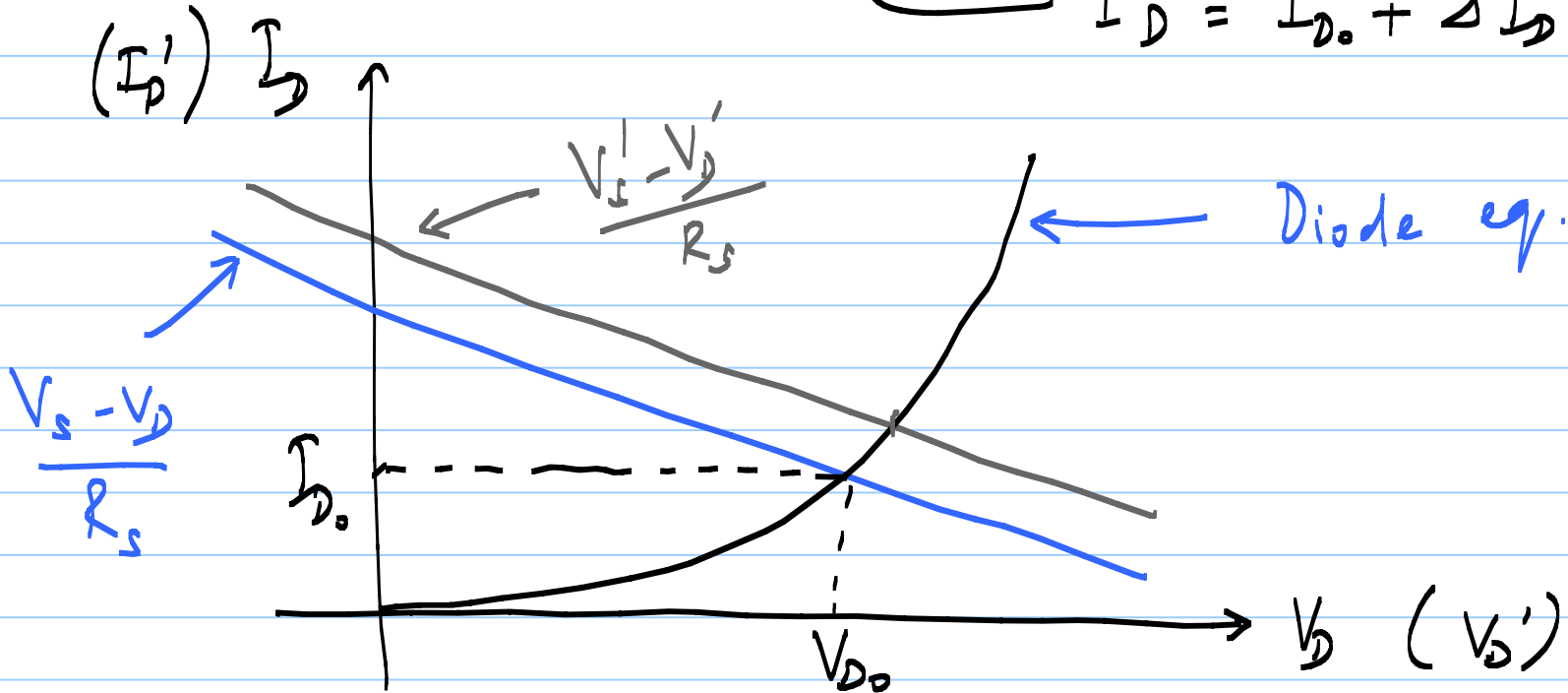


6/8/2020

Lecture 3

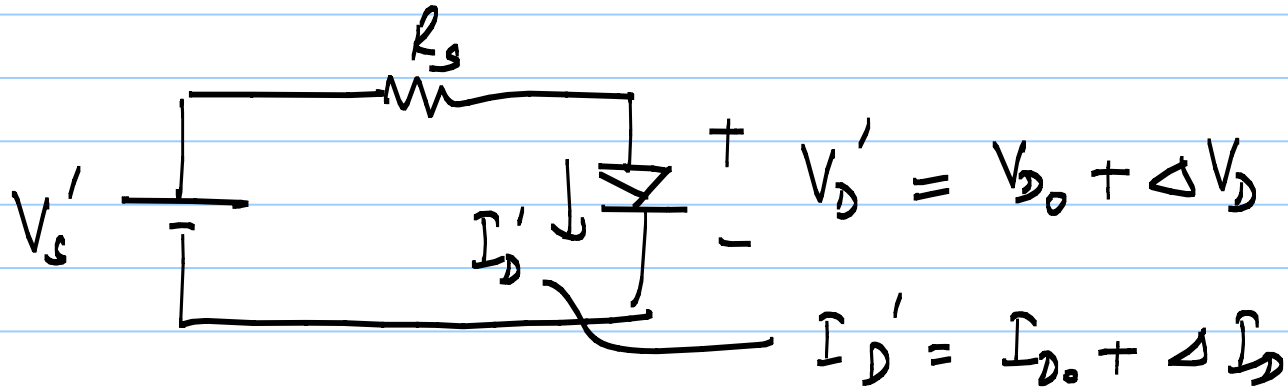* If $V_s' = V_s + \Delta V_s$ (increment), what is V_D' , I_D'



Orig. [~]

$$\frac{V_s - V_{D_0}}{R_s} = I_{D_0} = I_s \left[\exp\left(\frac{V_{D_0}}{V_t}\right) - 1 \right]$$

New

$$\frac{V_s' - V_{D_0}'}{R_s} = I_{D_0}' = I_s \left[\exp\left(\frac{V_{D_0}'}{V_t}\right) - 1 \right]$$

$$\frac{(V_s + \Delta V_s) - (V_{D_0} + \Delta V_{D_0})}{R_s} = I_{D_0} + \Delta I_{D_0}$$

$$= I_s \left[\exp\left(\frac{V_{D_0} + \Delta V_{D_0}}{V_t}\right) - 1 \right]$$

$$\frac{V_s - V_{D_0}}{R_s} + \frac{\Delta V_s - \Delta V_D}{R_s} = I_{D_0} + \Delta I_D$$

= ? \longrightarrow Taylor series
expansion around
 (V_{D_0}, I_{D_0})

for $y = f(x)$ around x_0

$$y = \sum_{n=0}^{\infty} \frac{f^{(n)}(x_0)}{n!} \cdot (x - x_0)^n$$

$$= f(x_0) + f'(x_0) \cdot (x - x_0)$$

oper. pt. \longrightarrow

$$+ \left(\frac{f''(x_0)}{2} \right) \cdot (x - x_0)^2 + \dots$$

$$I_s \left[\exp \left(\frac{V_{D0} + \Delta V_D}{V_T} \right) - 1 \right] = I_s \left[\exp \left(\frac{V_{D0}}{V_T} \right) - 1 \right]$$


$$+ \frac{I_s}{V_T} \exp \left(\frac{V_{D0}}{V_T} \right) \cdot (\Delta V_D) + \dots \rightarrow \Delta V_D^2, \Delta V_D^3, \dots$$

* For small increments (ΔV_D etc.), neglect $\Delta V_D^2, \Delta V_D^3, \dots$


$$\frac{V_s - V_{D0}}{R_s} + \frac{\Delta V_s - \Delta V_{D0}}{R_s} = \cancel{I_{D0}} + \Delta I_D = \cancel{I_s \left[\exp \left(\frac{V_{D0}}{V_T} \right) - 1 \right]} + \frac{I_s}{V_T} \exp \left(\frac{V_{D0}}{V_T} \right) \cdot \Delta V_D$$

$$\frac{\Delta V_s - \Delta V_D}{R_s} = \Delta I_D = \frac{I_s}{V_t} \exp\left(\frac{V_{D0}}{V_t}\right) \cdot \Delta V_D$$

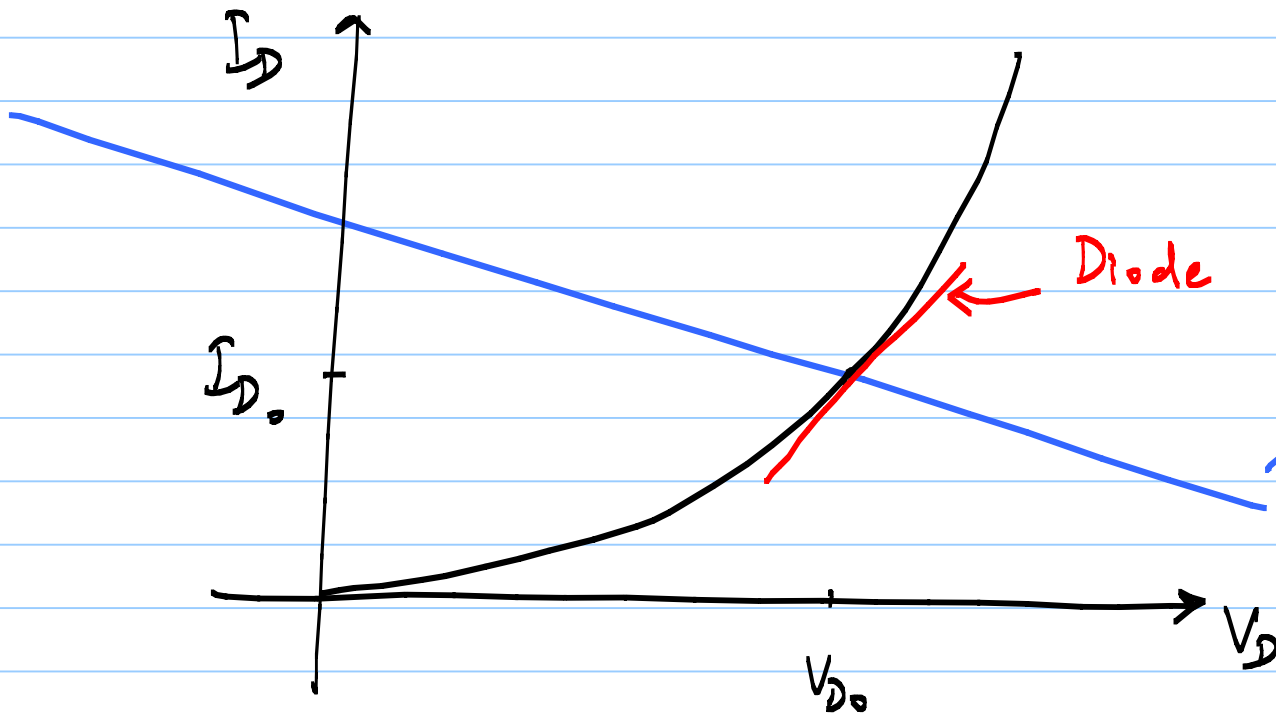Linear equations in $\Delta V_s, \Delta V_D, \Delta I_D$



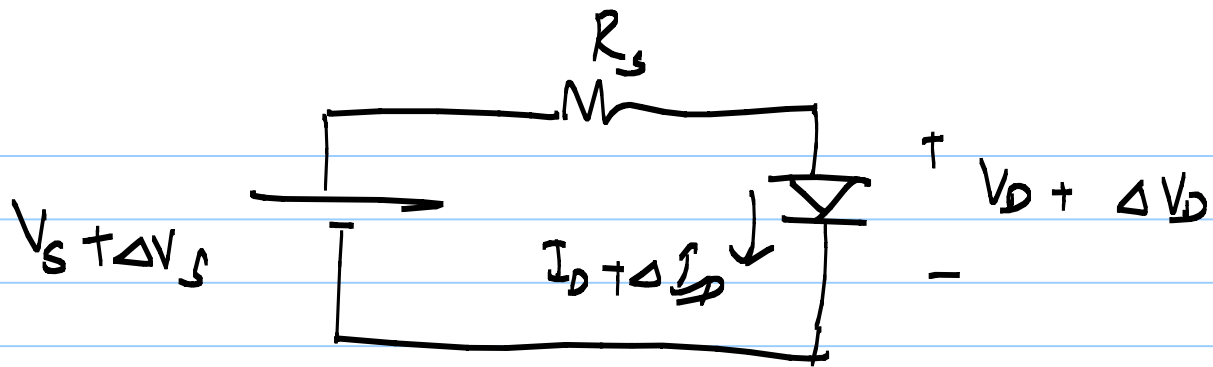Diode can be replaced by a linearized element for $\Delta V_D, \Delta I_D$



$$\Delta V_S = \Delta I_D \cdot R_s + \Delta V_D$$

$$\Delta I_D = \frac{I_S}{V_t} \exp\left(\frac{V_{D0}}{V_t}\right) \cdot \Delta V_D \approx \frac{I_{D0}}{V_t} \cdot \Delta V_D$$

$$\Delta V_D = \frac{V_t}{I_{D0}} \cdot \Delta I_D$$


"incremental resistance" of diode

$$\Delta V_S = \Delta I_D \cdot R_s + \Delta I_D \cdot \frac{V_t}{I_{D0}}$$


* Any $I = f(v)$ can be linearised around the op. pt.

* Assume $\Delta V_D, \Delta I_D$ etc are "small"

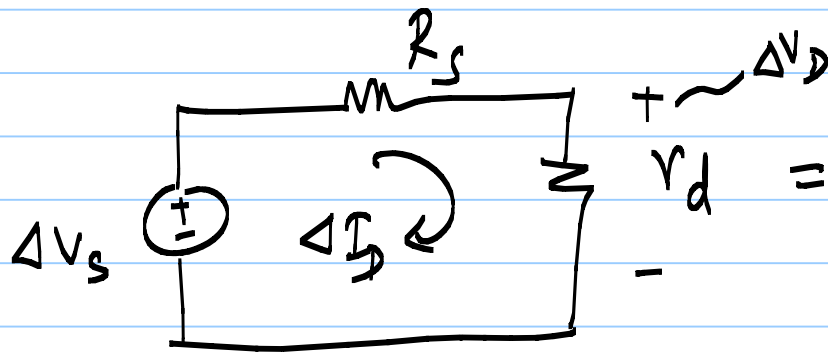(linear) Incremental eq. circuit for $\Delta I_D = \frac{\Delta V_S}{R_S + \frac{V_T}{I_{D_0}}}$


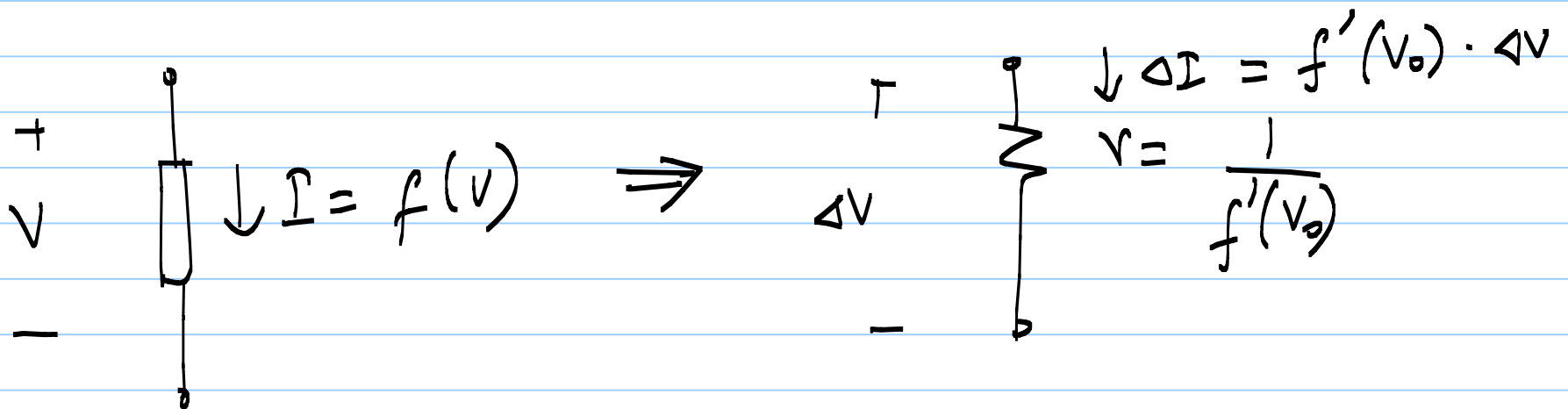
$$r_d = \frac{V_T}{I_{D_0}} = \text{inc. res. of diode @ } I_{D_0}$$



$I, V, \text{ etc.} \Rightarrow \text{DC}$

$I_0, V_0 \text{ etc} \Rightarrow \text{operating point,}$
 bias point


Quiescent point

$\Delta i, \Delta v \Rightarrow \text{incremental quantities}$

$i, v \Rightarrow \text{small-signal quantities}$


$V_D = V_{D0} + \Delta V_D \text{ etc.} \Rightarrow \text{total quantities}$

$$A \sin \omega t = v_s$$

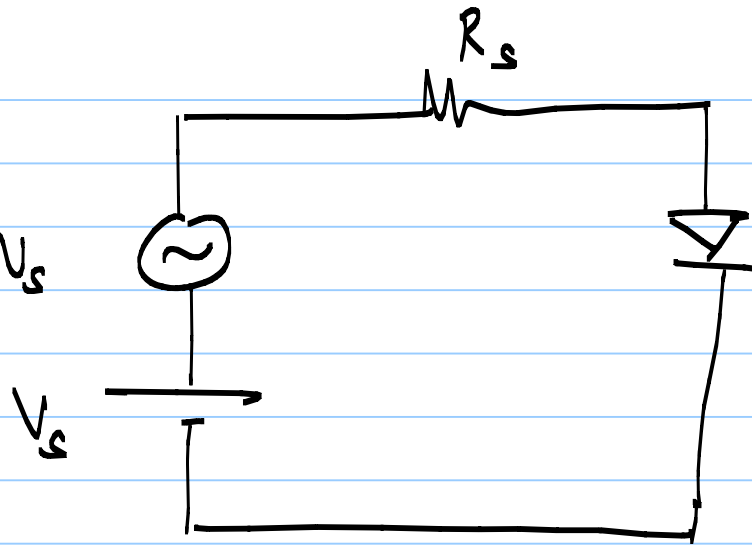

$\frac{1}{f}$ A is very
small \therefore

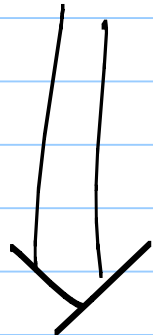@ every point of time,
instantaneous increments
are small enough that
linear approx. is valid



$$A \sin \omega t = v_s$$



$$r_d \rightarrow \frac{1}{f'(v_s)}$$

Small-signal
equivalent network

For op. pt. : you have to solve the
system of non-linear equations to determine
 I_{D0} , V_{D0} etc.