

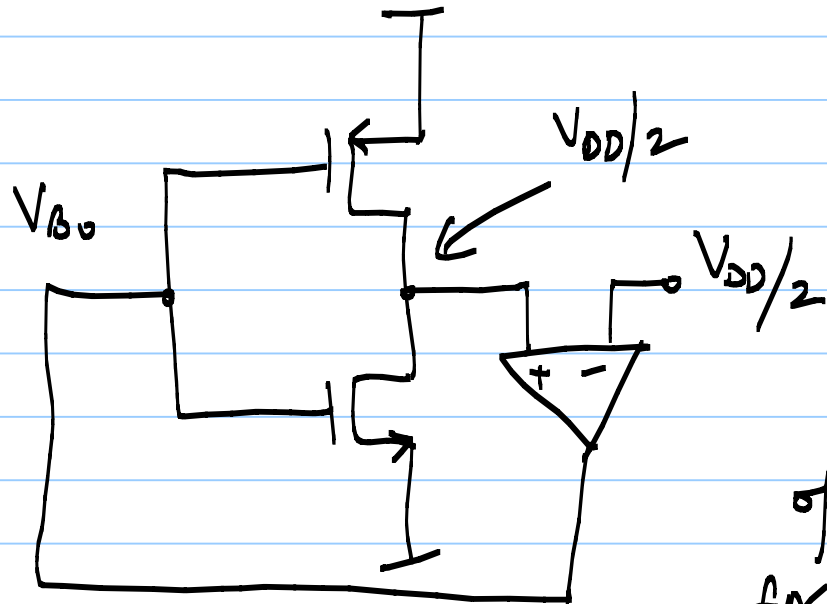
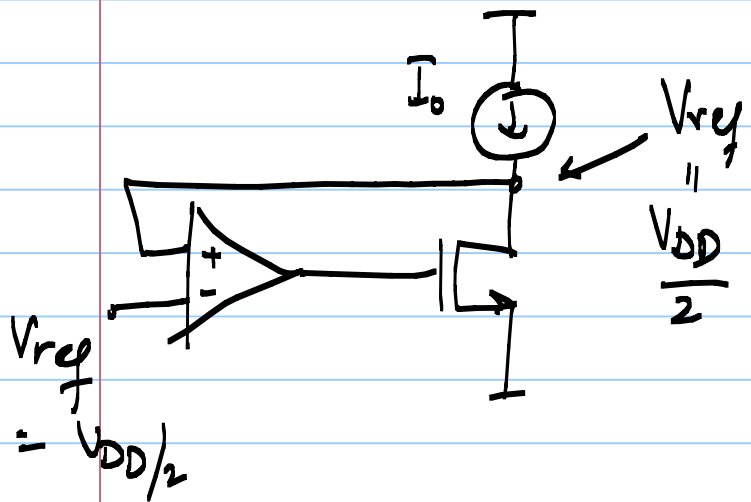
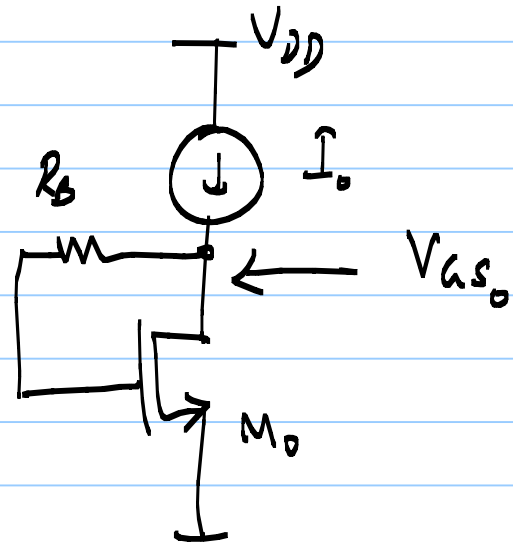
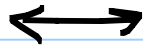


24/9/2020


Lecture 30

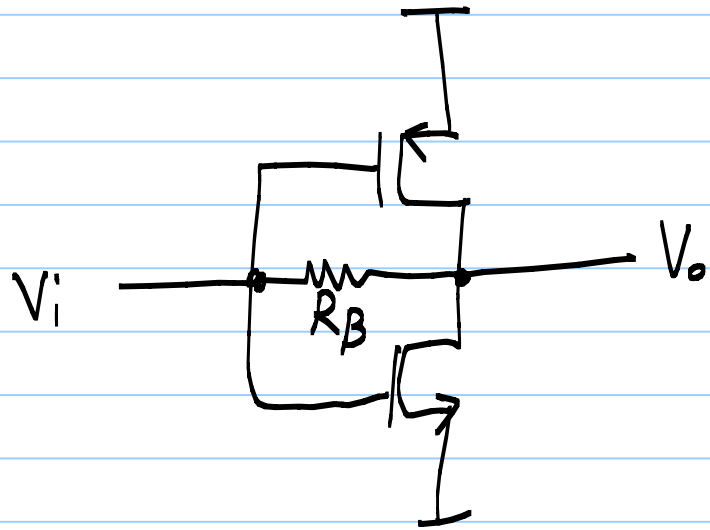

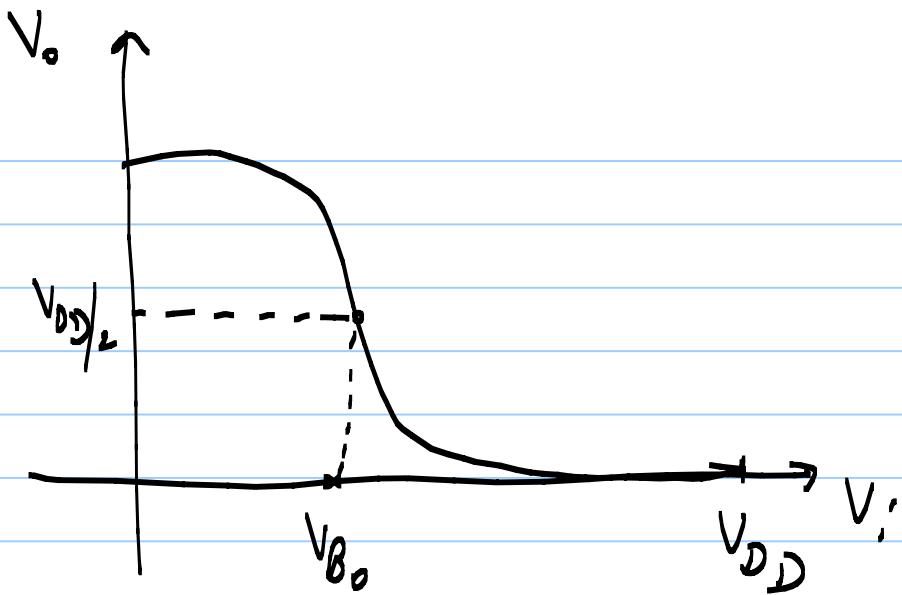
Modify the circuit to break opamp loop for AC.




Thevenin equivalent
 7 Bias

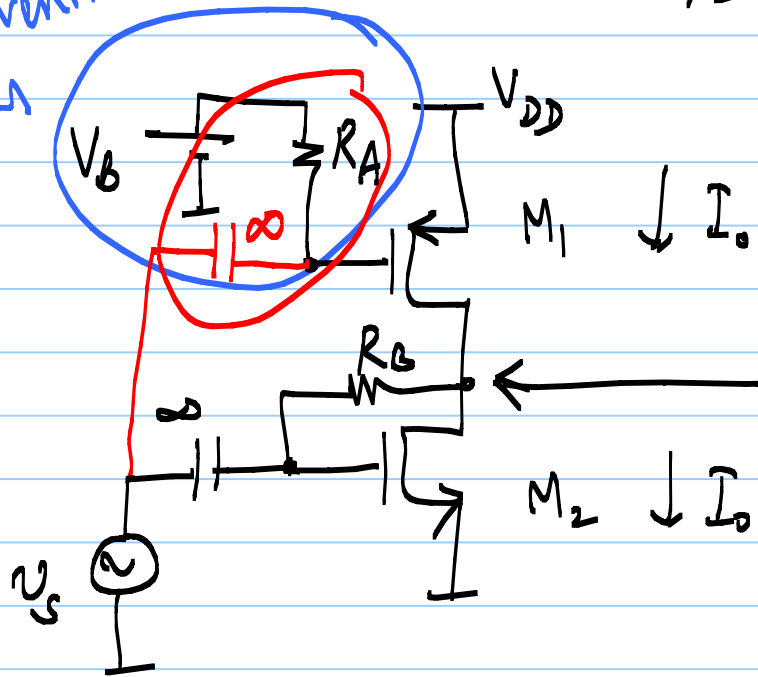

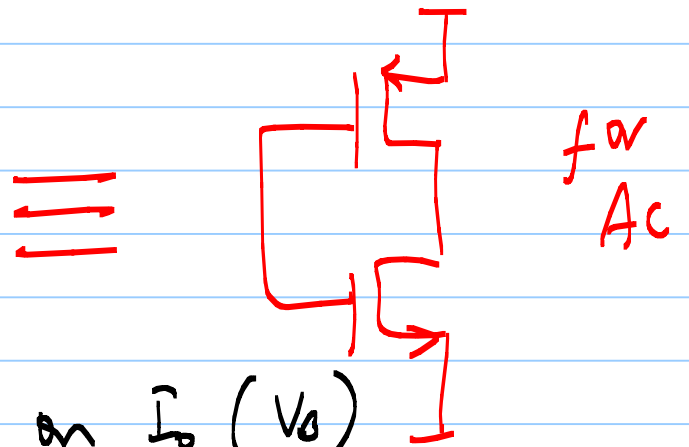V_{DC} adjusts itself based on $I_0 (V_o)$



Differential Amplifiers

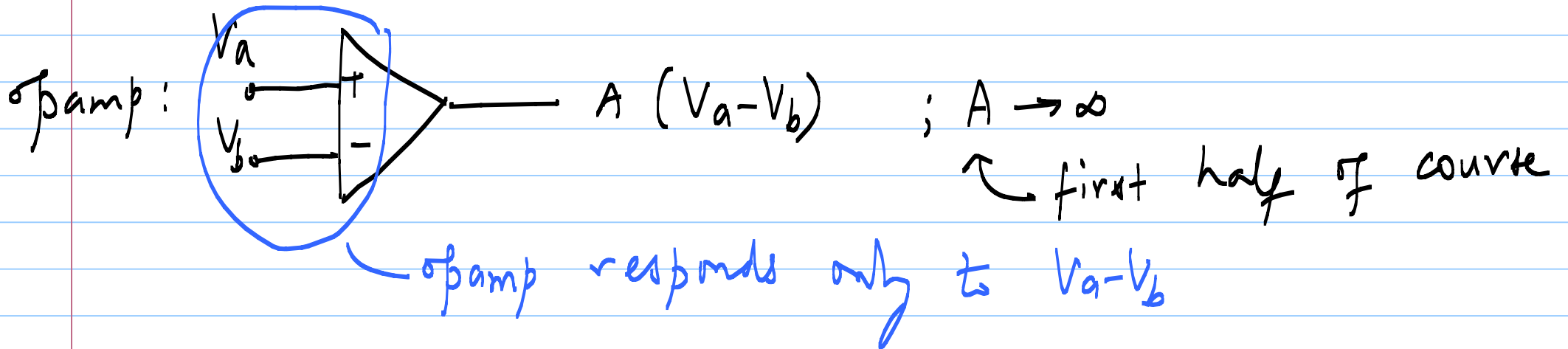

$$V_a = \left(\frac{V_a + V_b}{2} \right) + \left(\frac{V_a - V_b}{2} \right)$$

$$V_b = \left(\frac{V_a + V_b}{2} \right) - \left(\frac{V_a - V_b}{2} \right)$$

common-mode
voltage V_{cm}

differential mode
voltage V_{dm}

e.g. 1) $V_a = 1V$, $V_b = 1.1V$

$$V_{CM} = 1.05V \quad V_{DM} = -0.05V$$

$$V_a = V_{CM} + V_{DM} \quad * \text{ opamp should}$$
$$V_b = V_{CM} - V_{DM} \quad \text{amplify only } V_{DM}$$

2) $V_a = 1.1V$, $V_b = 1V$

$$V_{CM} = 1.05V, \quad V_{DM} = 0.05V$$


3) $V_a = 0.6V$, $V_b = 0.5V$

$$V_{CM} = 0.55V, \quad V_{DM} = 0.05V$$


* Assume $V_a = v_a$ & $V_b = v_b$

$$V_a = V_{CM} + \frac{\Delta V}{2} \quad V_b = V_{CM} - \frac{\Delta V}{2}$$


We know: $v \rightarrow kv$

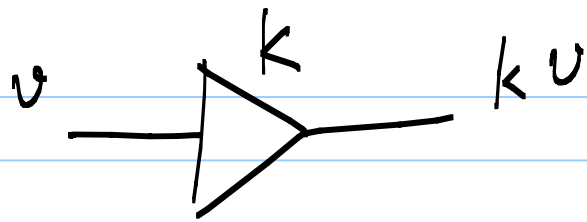

Circuit
①

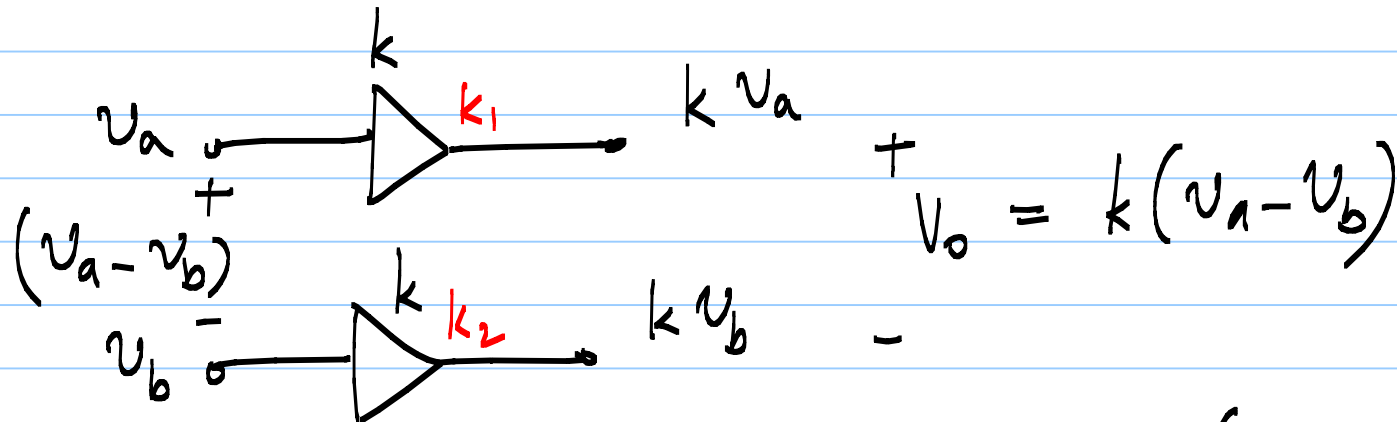

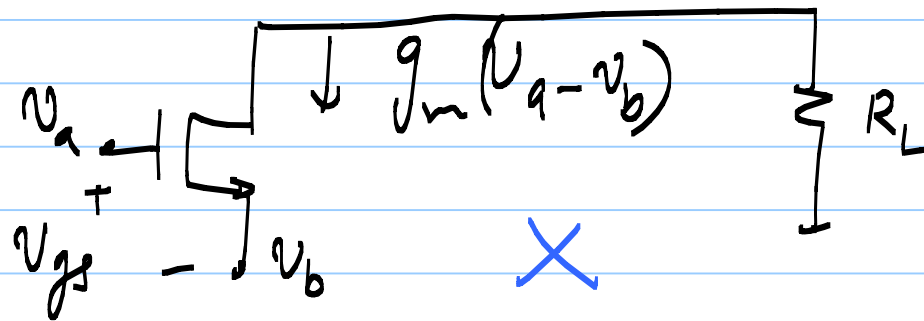
* We wanted single-ended output (ignore this for now)



For circuit ①, what are v_{icm} , v_{idm} , v_{ocm} , v_{odm} ?

Circuit (I)

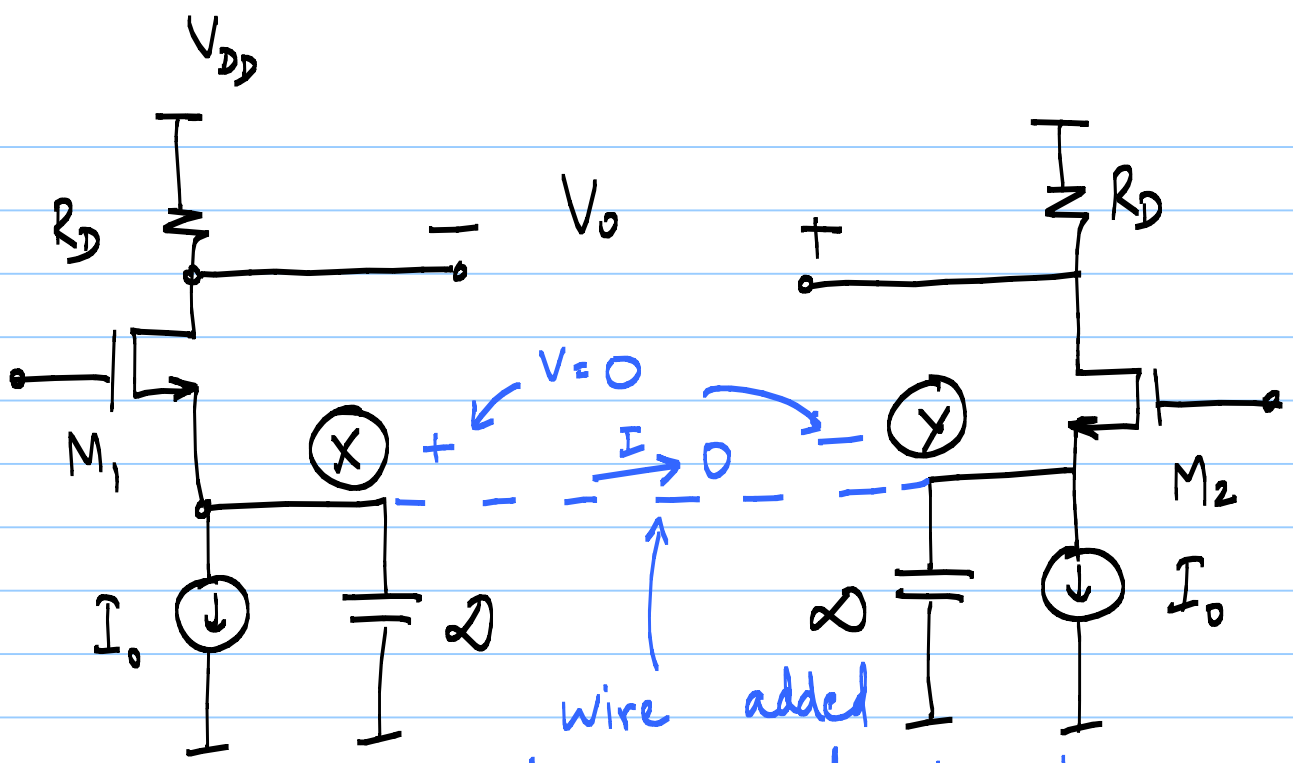DC
 $V_{CM} + \frac{\Delta V}{2}$
 increment



DC
 V_{CM}
 $-\frac{\Delta V}{2}$
 increment

$V=0$
 \rightarrow
 wire added
 to original circuit

$$V_x = V_{CM} - V_{GS1} ; V_y = V_{CM} - V_{GS2}$$

$$V_{GS1} = V_{GS2} \Rightarrow V_x = V_y$$