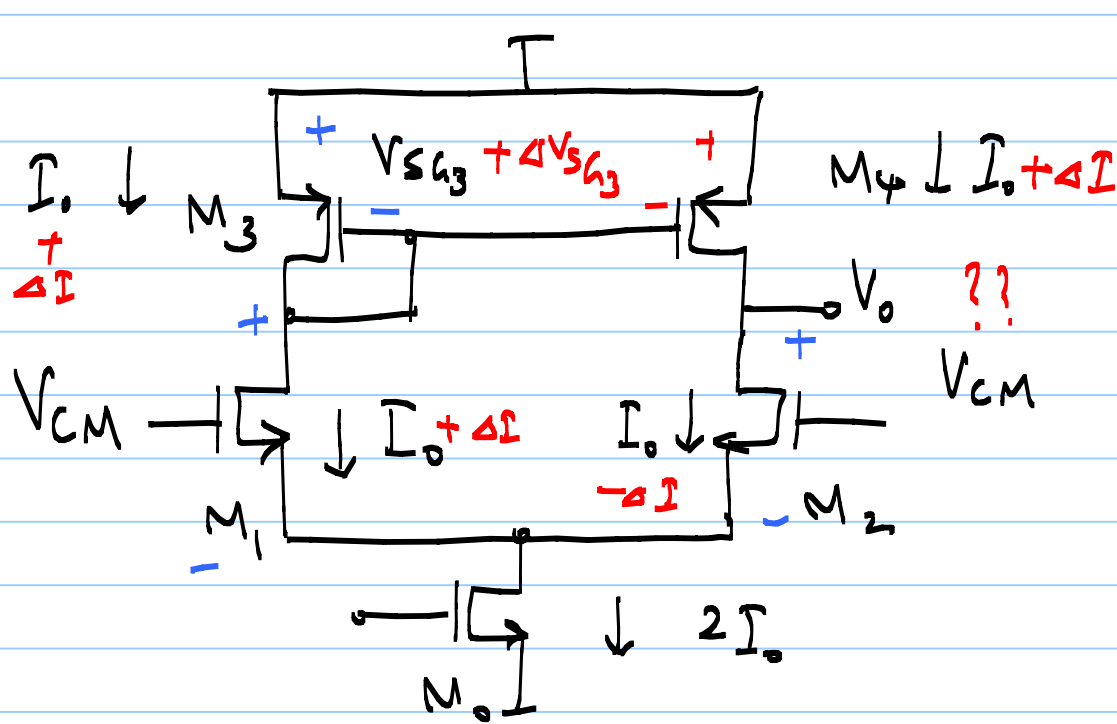


7/10/20

Lecture 34



$M_1 \equiv M_2$

$M_3 \equiv M_4$

$$V_{SG3} = V_{T3} + \sqrt{\frac{2I_0}{\mu_p C_{ox} \left(\frac{W}{L}\right)_3}}$$

$= V_{SG4}$

$V_{D1} = V_{DD} - V_{SG3} - \Delta V_{SG3} \quad ?? = 0$

$\Delta I = 0 ; V_{O_{cm}} = V_{DD} - V_{SG3}$



Case 2: λ 's are non-zero

$$I_{D1} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{GS1} - V_{Tn})^2 (1 + \lambda V_{DS1})$$



$$I_{D2} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_2 (V_{GS2} - V_{Tn})^2 (1 + \lambda V_{DS2})$$

DM SS analysis



$$\frac{v_o}{v_i} = ?$$

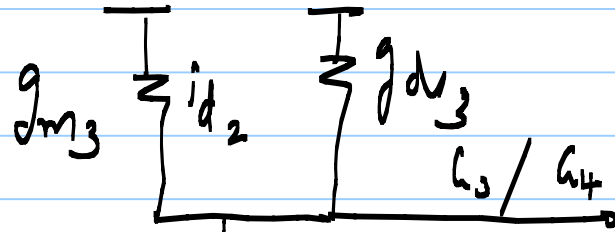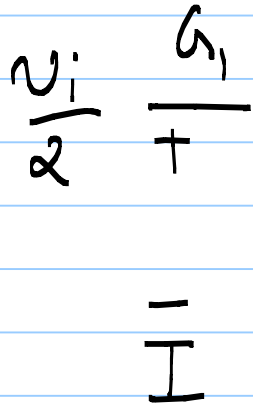

(A)

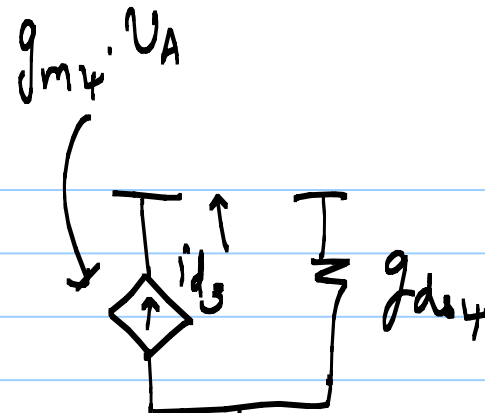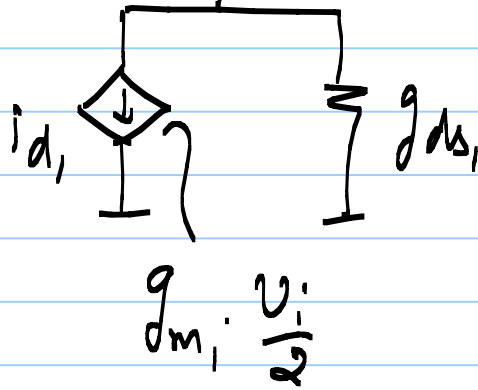

(B)

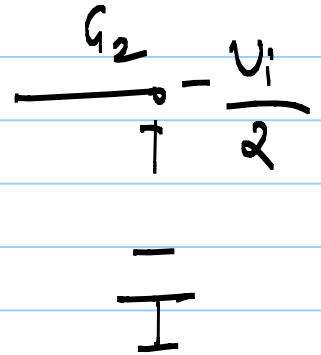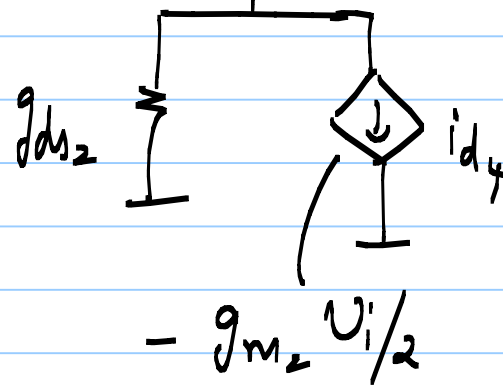

$$v_A = - \frac{g_{m1}}{g_{m3} + g_{ds1} + g_{ds3}} \cdot \frac{v_i}{2}$$

$$i_{d3} = g_{m4} \cdot v_A = - \frac{g_{m4}}{g_{m3} + g_{ds1} + g_{ds3}} \cdot g_{m1} \cdot \frac{v_i}{2}$$

$\approx -g_{m1} \frac{v_i}{2}$ if $g_{m3} \gg g_{ds1} \& g_{ds3}$



$$v_o = -\left(i_{d3} + i_{d4}\right) \cdot \frac{1}{g_{ds2} + g_{ds4}}$$

$$= -\left(-g_{m1} \frac{v_i}{2} - g_{m2} \frac{v_i}{2}\right) \cdot \frac{1}{g_{ds2} + g_{ds4}}$$

$$= \frac{g_{m1}}{g_{ds2} + g_{ds4}} \cdot v_i$$

$$\frac{v_o}{v_i} = \frac{g_{m1}}{g_{ds2} + g_{ds4}} = g_{m1} (r_{ds2} \parallel r_{ds4})$$

"Single-Stage Opamp"

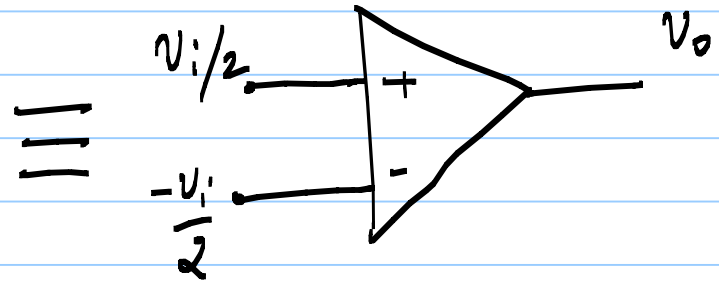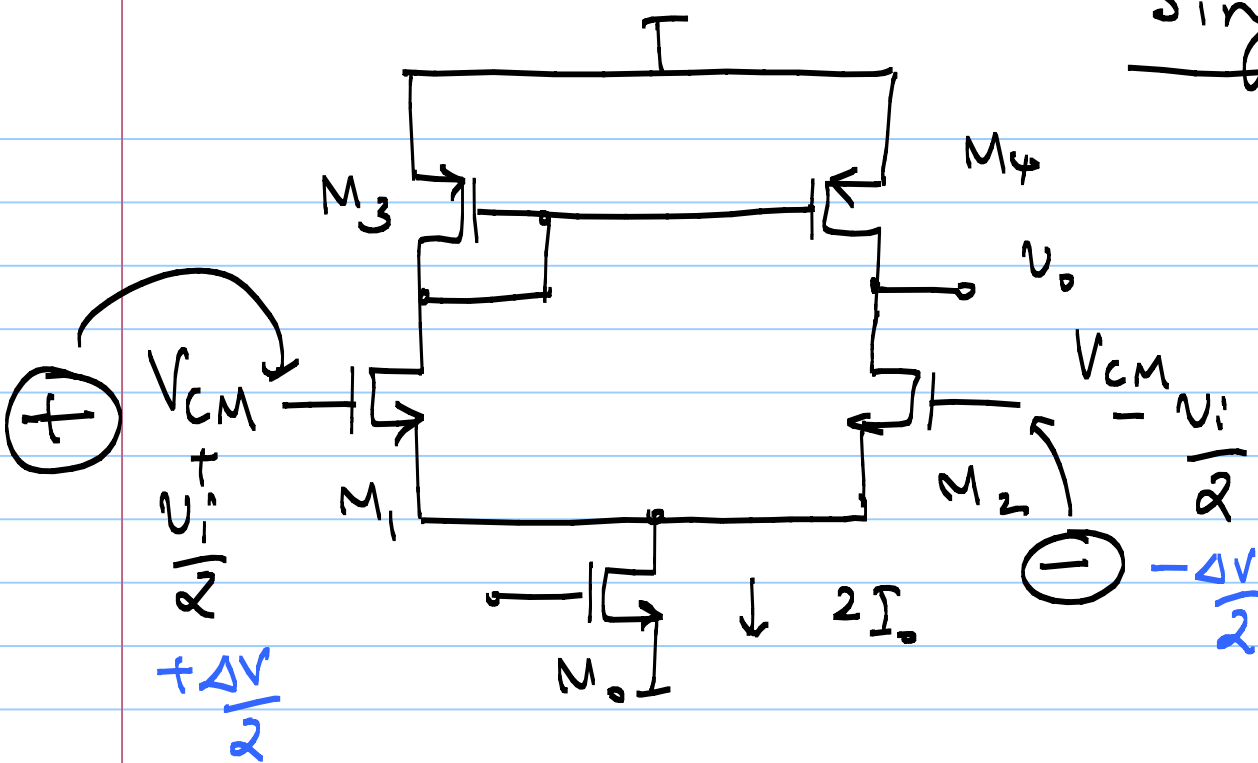


DM gain = $g_{m1} (r_{ds2} || r_{ds4})$



$r_{in} = \infty$

$r_{out} = r_{ds2} || r_{ds4}$
(large)

$G_m = g_{m1}$

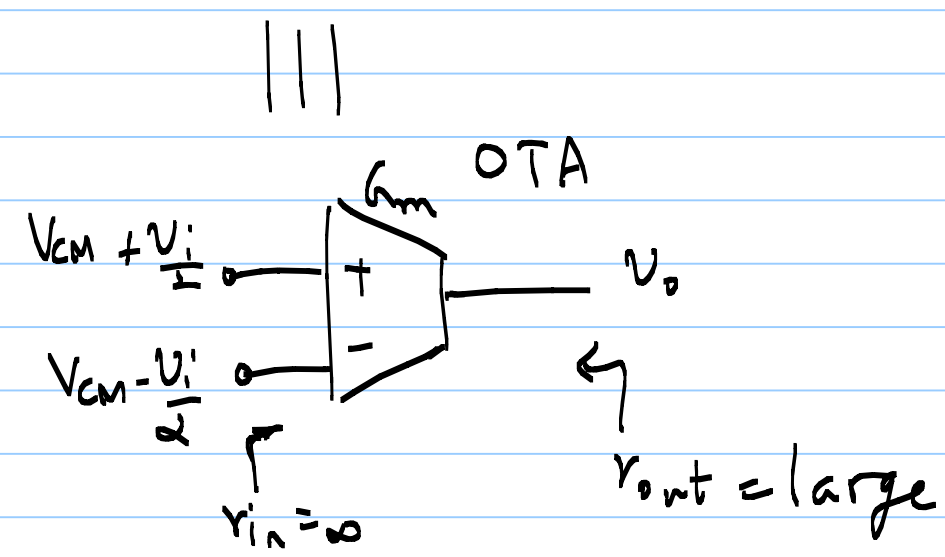

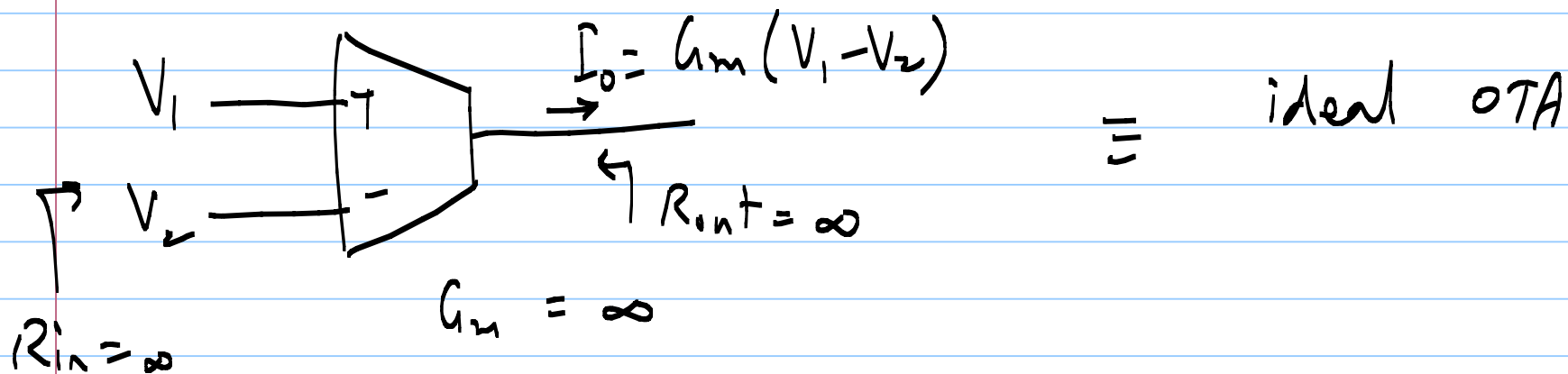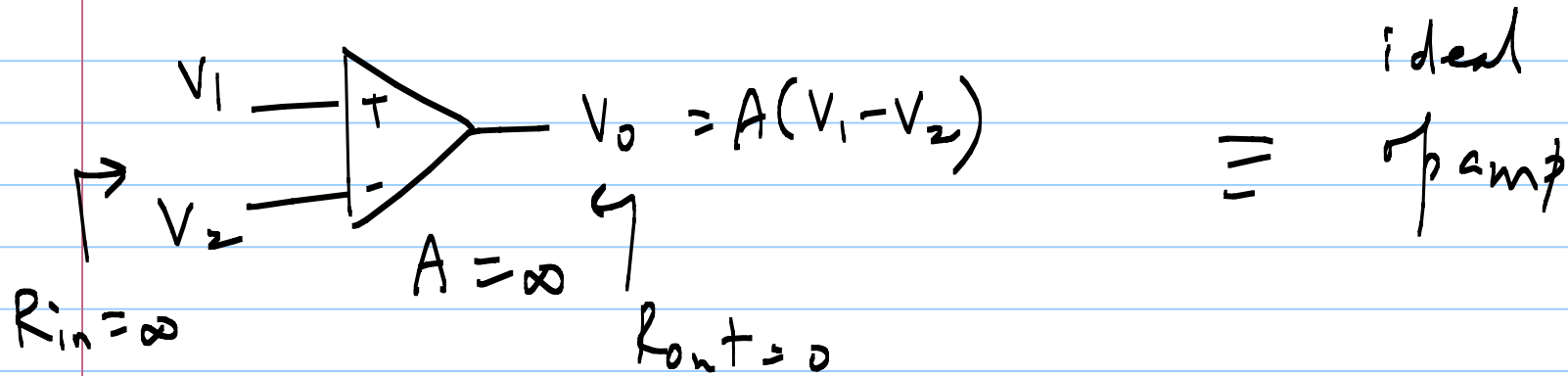OTA \equiv operational Transconductance Amplifier



$$\text{gain} = \frac{V_0}{V_1 - V_2} = g_m R_{out} = \text{large}$$