


15/10/2020

Lecture 39

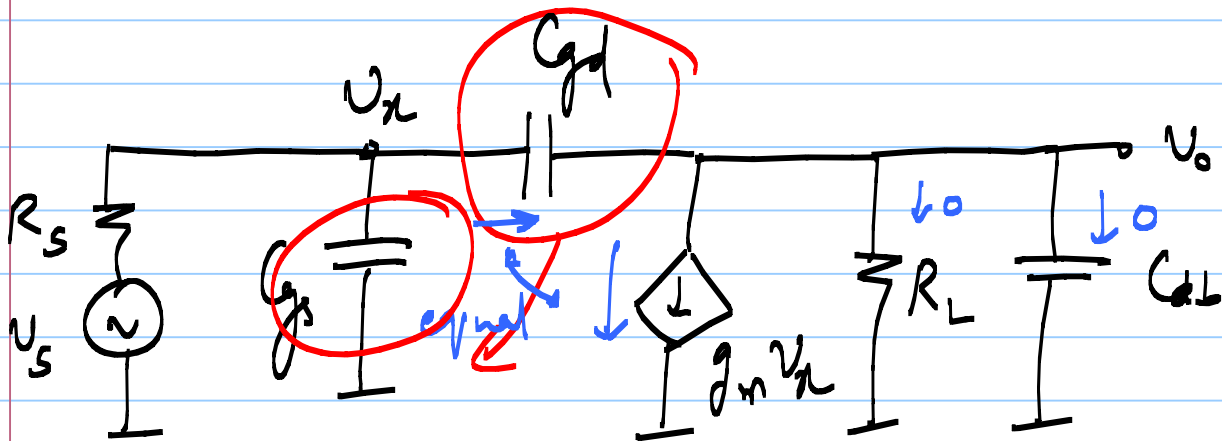2) CSA with C_{gd} considered:

$$\frac{V_o}{V_s}(s) = \left(\frac{-g_m}{g_L} \right) \frac{\left[1 - \frac{s C_{gd}}{g_m} \right]}{\left[\frac{s^2}{g_L g_s} (C_{gs} C_{gd} + C_{gs} C_{db} + C_{gd} C_{db}) \right.}$$

$$\left. + \frac{s}{g_L g_s} (g_L (C_{gs} + C_{gd}) + g_s (C_{gd} + C_{db}) + g_m C_{gd}) + 1 \right]$$



(a) zero freq.
 $\Rightarrow V_o = 0$

$$D(s) = \frac{s^2}{G_L G_S} \left[G_Y (C_{gd} + C_{cb}) \right]$$

(ignore C_{gd} C_{cb})

$$+ \frac{s}{G_L G_S} \left[G_L G_Y + G_S (C_{gd} + C_{cb}) + g_m C_{gd} \right]$$

(ignore C_{gd})


+

|

$$D(s) = \frac{s^2}{G_L G_S} [C_{gs} (C_{gd} + C_{db})] + \frac{s}{G_S} \left[C_{gs} + \frac{g_m}{G_L} C_{gd} + \frac{G_S}{G_L} (C_{gd} + C_{db}) \right] + 1$$

due to Miller Effect ignore

Miller Effect

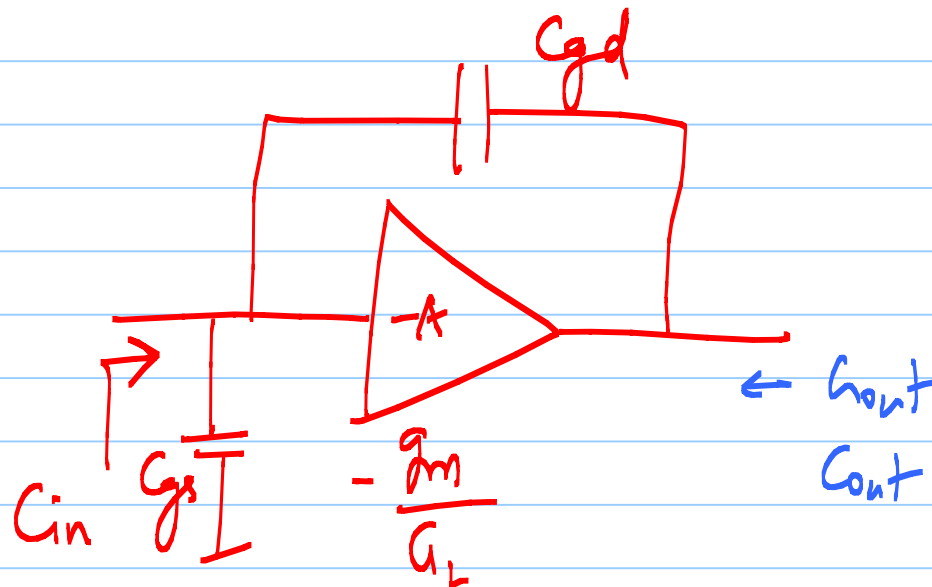

$$C_{in} \approx (1+A) C_{gd} + C_{gs} \approx \frac{g_m}{G_L} C_{gd} + C_{gs}$$

$$\begin{aligned}
 \frac{I_f}{I} D(s) &= \left(1 + \frac{s}{p_1}\right) \left(1 + \frac{s}{p_2}\right) \\
 &= \frac{s^2}{p_1 p_2} + s \left(\frac{1}{p_1} + \frac{1}{p_2}\right) + 1
 \end{aligned}$$

$$p_1 \gg p_2 \Rightarrow \frac{1}{p_2} \gg \frac{1}{p_1}$$

$$D(s) \approx \frac{s^2}{p_1 p_2} + \frac{s}{p_2} + 1$$

$$p_2 = \frac{G_s}{C_{gs} + C_{gd} \cdot \frac{g_m}{s_L}}$$

Compare this
with case without C_{gd}


$$p_{20} = \frac{G_s}{C_{gs}}$$


$$\begin{aligned}
 p_1 &= p_1 p_2 \cdot \frac{1}{p_2} \\
 &= \frac{g_L g_s}{C_{gs} (C_{gd} + C_{db})} \cdot \frac{C_{gs} + C_{gd} \cdot \frac{g_m}{g_L}}{g_s}
 \end{aligned}$$

$$p_1 = \frac{g_L (C_{gs} + C_{gd} \cdot \frac{g_m}{g_L})}{C_{gs} (C_{gd} + C_{db})}$$

Compare with case without C_{gd}


$$p_{10} = \frac{g_L}{C_{db}}$$

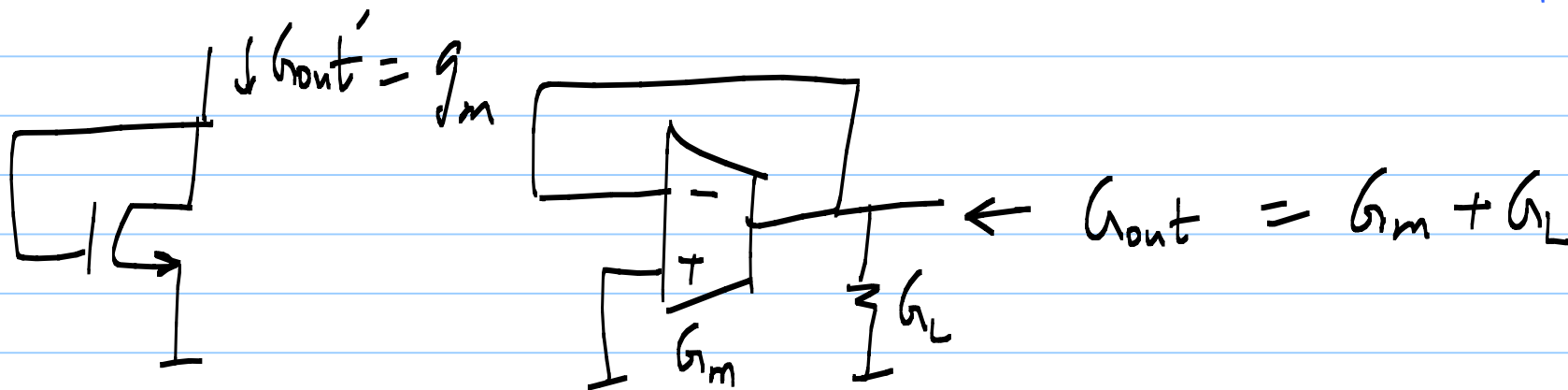

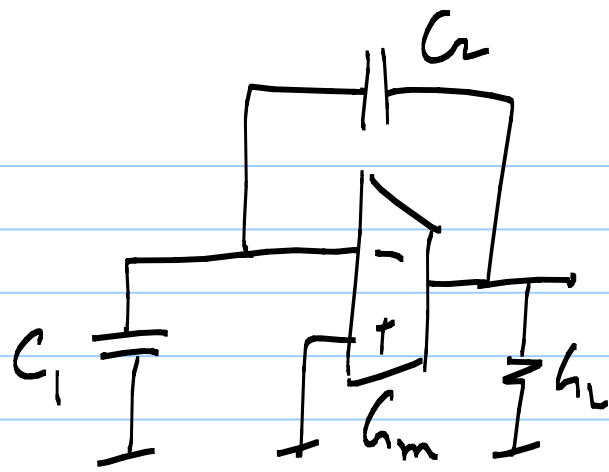

← $G_{out} = ?$

HW

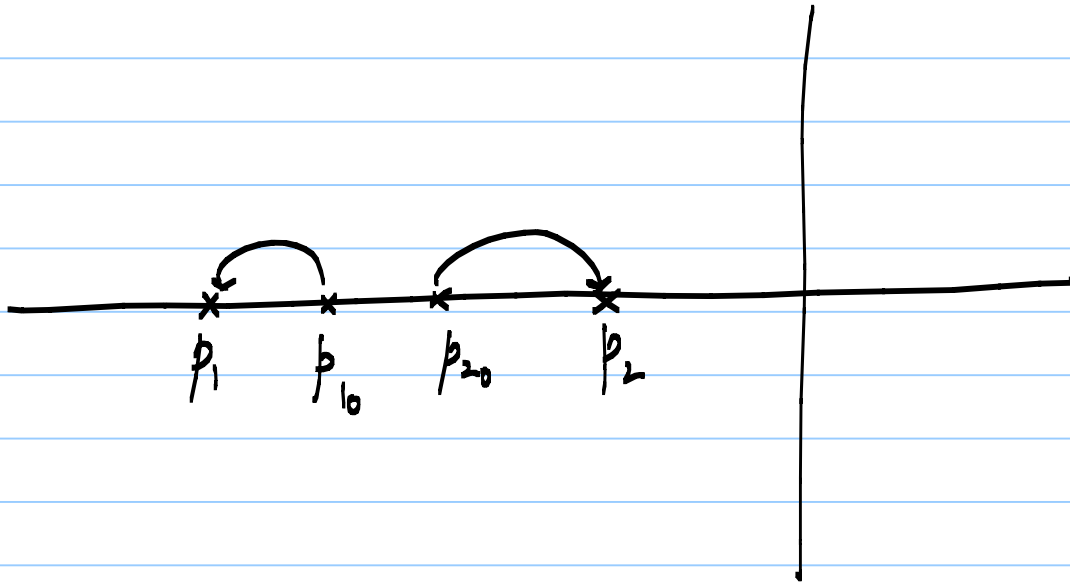


* Every node of an amplifier will have some parasitic cap.

→ made up of device cap. of transistors connected to that node

* pole associated with each mode


e.g.
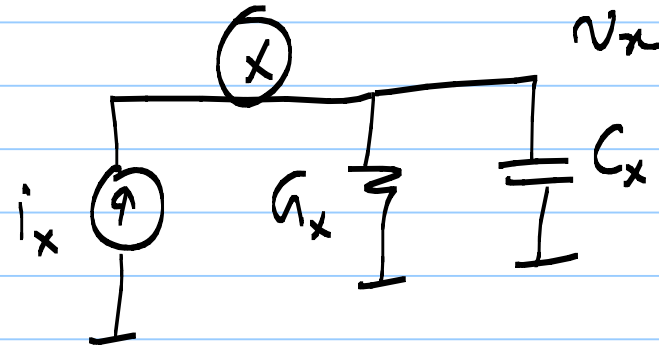
$$v_x = \frac{i_x}{Y_x} = \frac{i_x}{G_x + j\omega C_x}$$



pole @ $s_x = -\frac{1}{RC}$

v_x has no free response

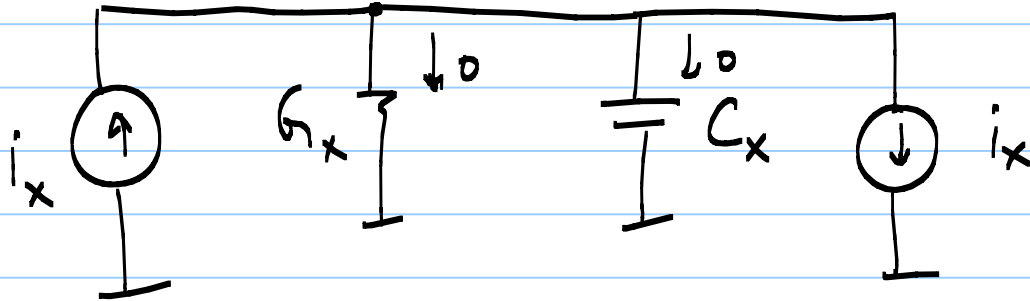

* More gain \rightarrow cascade amplifier stages
 \rightarrow more # of nodes \rightarrow more # of poles
(and maybe zeroes)

* More # of poles \rightarrow possibility of instability
when placed in feedback.