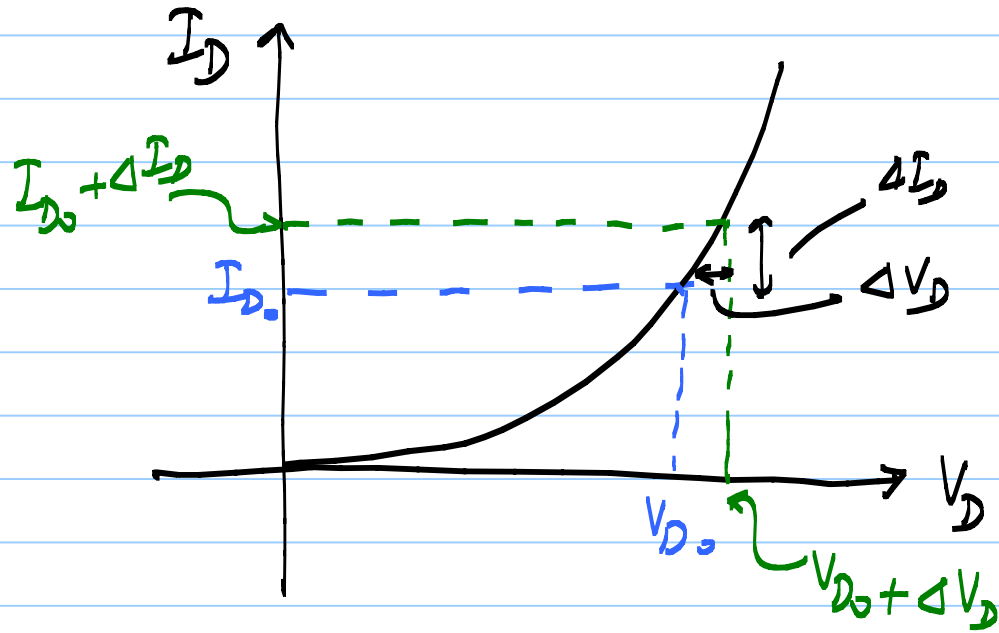


7/8/2020


Lecture 4



$$\frac{\Delta I_D}{\Delta V_D} = \left. \frac{dI_D}{dV_D} \right|_{(I_{D0}, V_{D0})}$$

= inc. conductance
(m)
dynamic " "
(u)
small-signal " "


Example

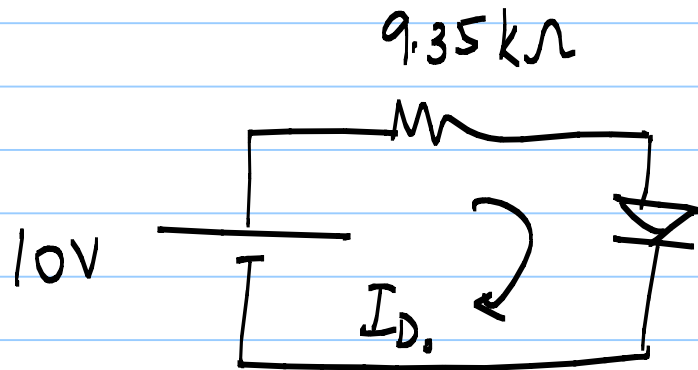

$$+ V_{D0} \approx 0.65 \text{ V}$$

$$I_{D0} = \frac{10 - 0.65}{9.35 \text{ k}\Omega} = 1 \text{ mA}$$

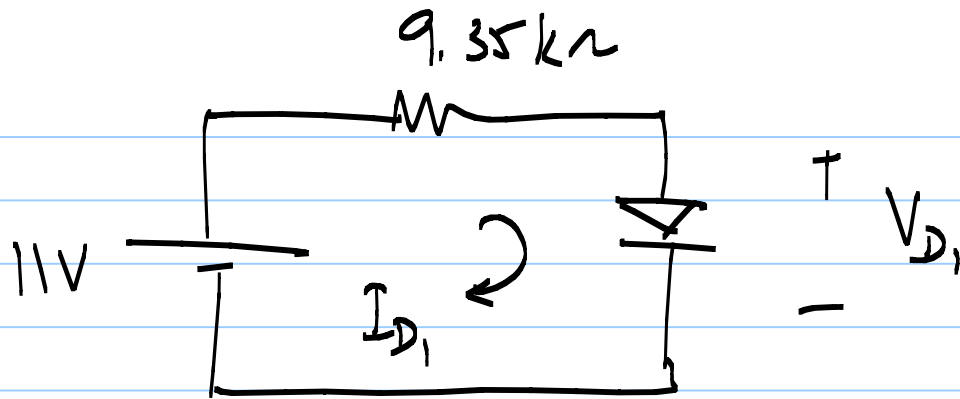Change $10 \text{ V} \rightarrow 11 \text{ V}$




$$\Delta V_s = 1\text{ V}$$

$$r_d = \frac{V_t}{I_{D0}} = \frac{25\text{ mV}}{1\text{ mA}}$$

$$= 25\ \Omega$$

Incremental Equivalent Circuit

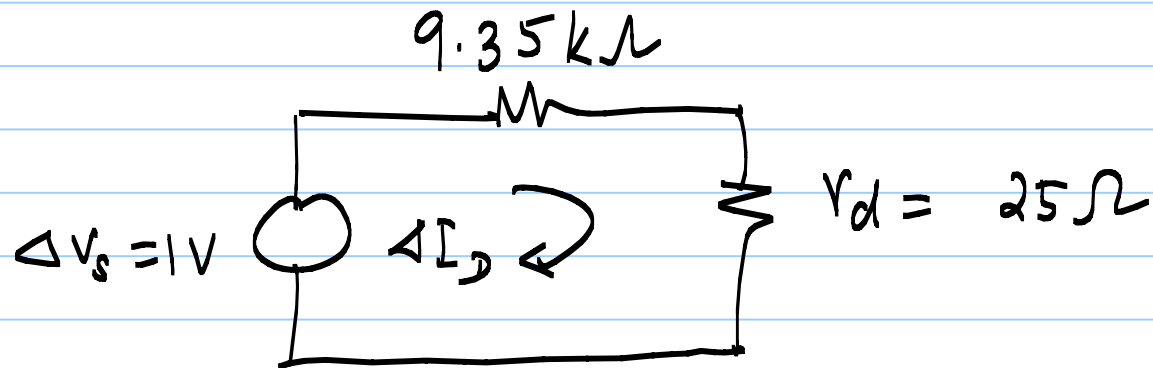

$$\Delta I_D = \frac{1\text{ V}}{9350 + 25} \approx 106\ \mu\text{A}$$

$$I_{D1} = I_{D0} + \Delta I_D = 1.106\text{ mA}$$

* If $V_s = 9\text{ V}$, $I_{D2} = ?$

$$\Delta V_S = -1V \Rightarrow \Delta I_D = -106 \mu A$$

$$\Rightarrow I_{D_2} = 0.894 \text{ mA}$$

$$* \quad I_f \quad V_S = 9.5V, \quad I_{D_3} = I_{D_0} - \frac{1}{2} (106 \mu A)$$

...

$$* \quad I_f \quad V_S = 10V + (1V)\sin \omega t$$

$$I_D = 1 \text{ mA} + (106 \mu A)\sin \omega t$$

Next: I_S linear approx. valid?

$$\Delta V_D = \Delta I_D \cdot r_d = 106 \mu A \times 25 \approx 2.7 \text{ mV}$$

$$f''(V_{D_0}) = ?$$

$$I_D = I_S \exp\left(\frac{V_D}{V_T}\right)$$

$$f''(V_{D0}) = \frac{I_s}{V_t^2} \exp\left(\frac{V_{D0}}{V_t}\right) \approx \frac{I_{D0}}{V_t^2}$$

Taylor Series 3rd term = $\frac{f''(V_{D0})}{2} (\Delta V_D)^2$


$$I_D = I_{D0} + \frac{I_{D0}}{V_t} (\Delta V_D) + \frac{I_{D0}}{2V_t^2} (\Delta V_D)^2 + \dots$$

$$= \frac{I_{D0}}{2V_t^2} \cdot (\Delta V_D)^2$$

compare these two

first error term is small if $\Delta V_D \ll 2V_t$ valid

\uparrow \uparrow
 $2 \cdot 7mV$ $50mV$

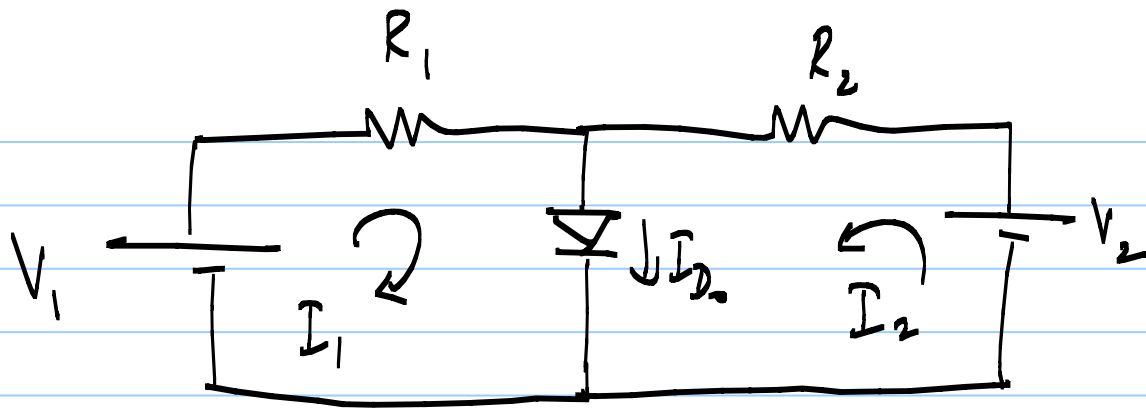

Assume
 $V_D = 0.65$
 if fwd. biased


Op. pt. V_{D0} NL eqn/s.

$$I_1 = \frac{V_1 - 0.65}{R_1} \quad \& \quad I_2 = \frac{V_2 - 0.65}{R_2}$$

$$I_{D0} = I_1 + I_2$$

$$V_1 \rightarrow V_1 + \Delta V_1 \quad \& \quad V_2 \rightarrow V_2 + \Delta V_2$$

Inc. picture :

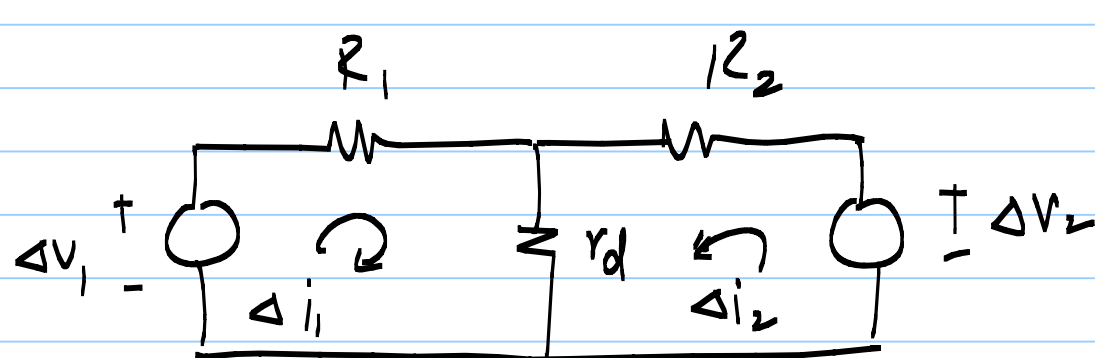

$$r_d = \frac{V_T}{I_{D0}}$$

$$\Delta i_d = \Delta i_1 + \Delta i_2$$

Incremental network

* All elements are linear

* No dc sources

* Inc. voltage across NL element

$$\Delta V_d = \Delta i_d \cdot r_d \quad \left\{ \Delta V_d = \frac{r_d}{r_d + 9.35k\Omega} \cdot \Delta V_s \right\}$$

* Total voltage across diode

$$= \text{Quiescent voltage} + \text{Incremental voltage}$$
$$\left\{ 0.65V + \Delta V_d \right\}$$

* Can extend to networks with multiple NL elements

→ replace each NL element with its

inc. resistance $r_i = \frac{1}{f'_i(V_{i0})}$