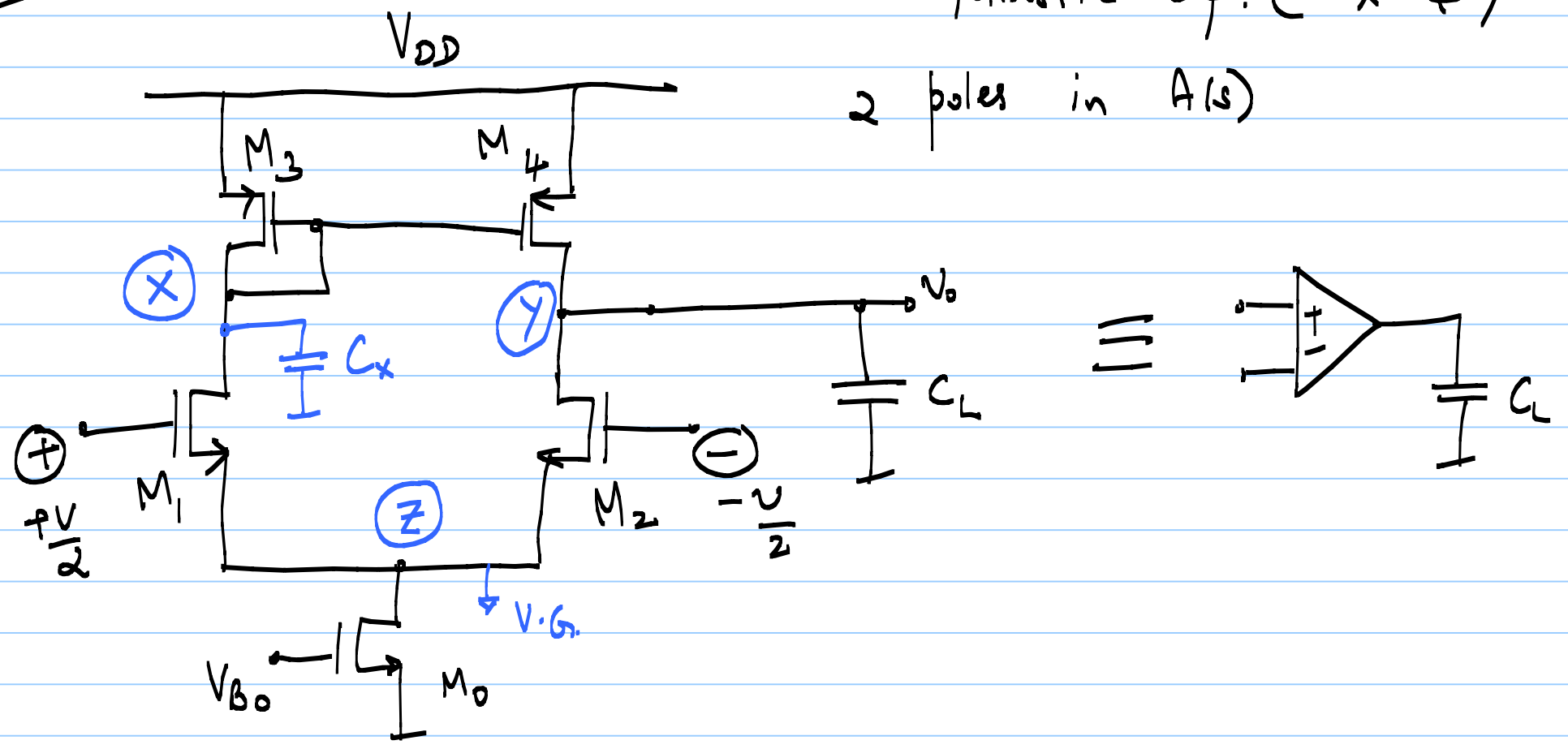



22/10/2020

# Lecture 43

parasitic cap. @ x & y

2 poles in  $A(s)$



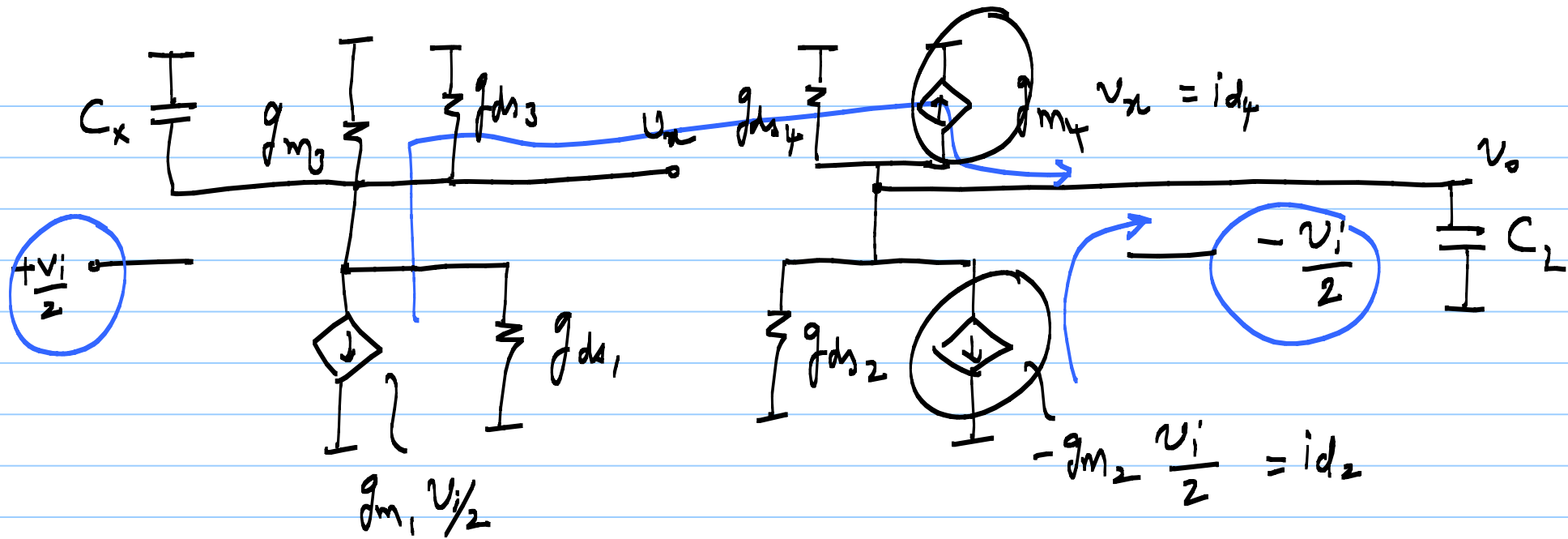

\* all  $g_m$ 's  $\gg$  all  $g_{ds}$ 's

$$v_x = - \frac{+g_{m1} v_i/2}{g_{m3} + g_{ds3} + g_{ds1} + sC_x} \approx \frac{-g_{m1} v_i/2}{g_{m3} + sC_x}$$

$$v_x \approx \frac{-g_{m1}}{g_{m3}} \cdot \frac{1}{1 + sC_x/g_{m3}} \cdot \frac{v_i}{2}$$

$$i_{d4} = g_{m4} \cdot v_x$$

$$= \frac{-g_{m1}}{1 + \frac{sC_x}{g_{m3}}} \cdot \frac{v_i}{2}$$

$$i_{d2} = -g_{m2} v_{i/2}$$

$$v_o = - \frac{(i_{d2} + i_{d4})}{g_{ds2} + g_{ds4} + sC_L}$$

$$v_o = - \frac{-g_{m2} v_{i/2} - \frac{g_{m1}}{1 + sC_x/g_{m3}} \cdot v_{i/2}}{g_{ds2} + g_{ds4} + sC_L}$$


$$= \frac{g_{m1} v_i}{g_{ds2} + g_{ds4}} \frac{\frac{1}{2} + \frac{1/2}{1 + sC_x/g_{m3}}}{1 + \frac{sC_L}{g_{ds2} + g_{ds4}}}$$

$$\frac{v_o}{v_i} = \frac{g_{m1}}{g_{ds2} + g_{ds4}} \cdot \frac{(1 + sC_x/2g_{m3})}{(1 + sC_x/g_{m3})(1 + sC_L/(g_{ds2} + g_{ds4}))}$$

$$* A_0 = \frac{g_{m1}}{g_{ds2} + g_{ds4}}$$

\* 2 poles  $\rightarrow$  @ (X), (Y)

\* 1 zero @  $2g_{m3}/C_x$


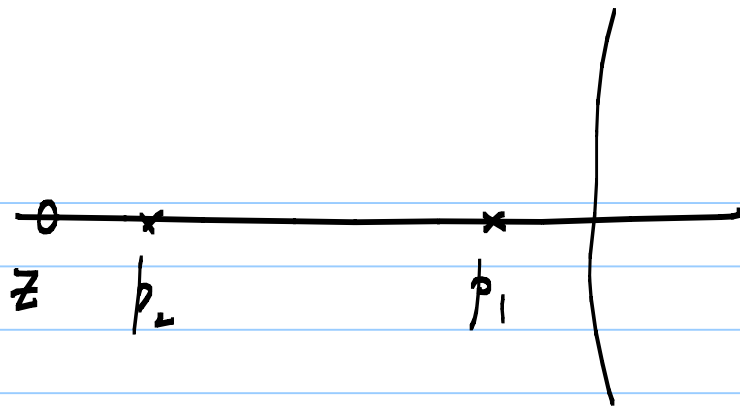


$$p_1 = \frac{g_{ds2} + g_{ds4}}{C_L}$$

$$p_2 = \frac{g_{m3}}{C_x}$$


$$z = 2p_2 = \frac{2g_{m3}}{C_x}$$

Ideal 1-stage opamp :

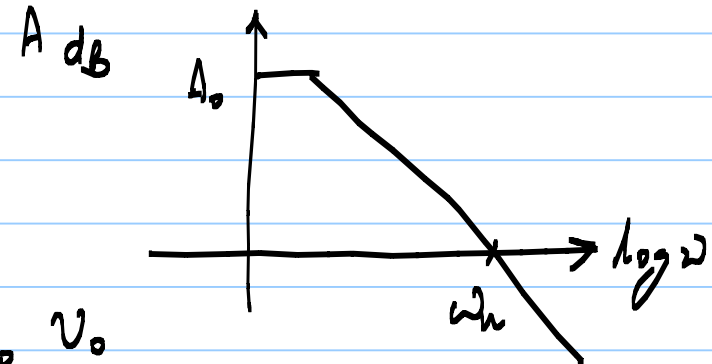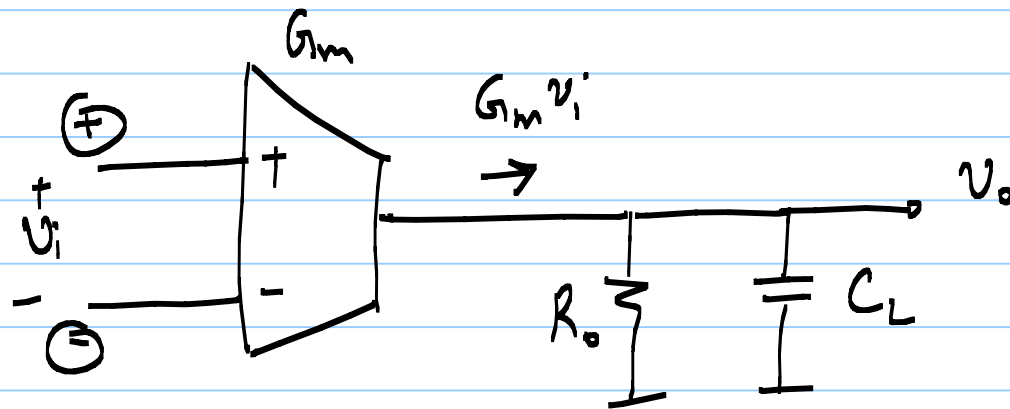


$$\omega_u = \frac{G_m}{C_L} = \frac{g_{m1}}{C_L}$$
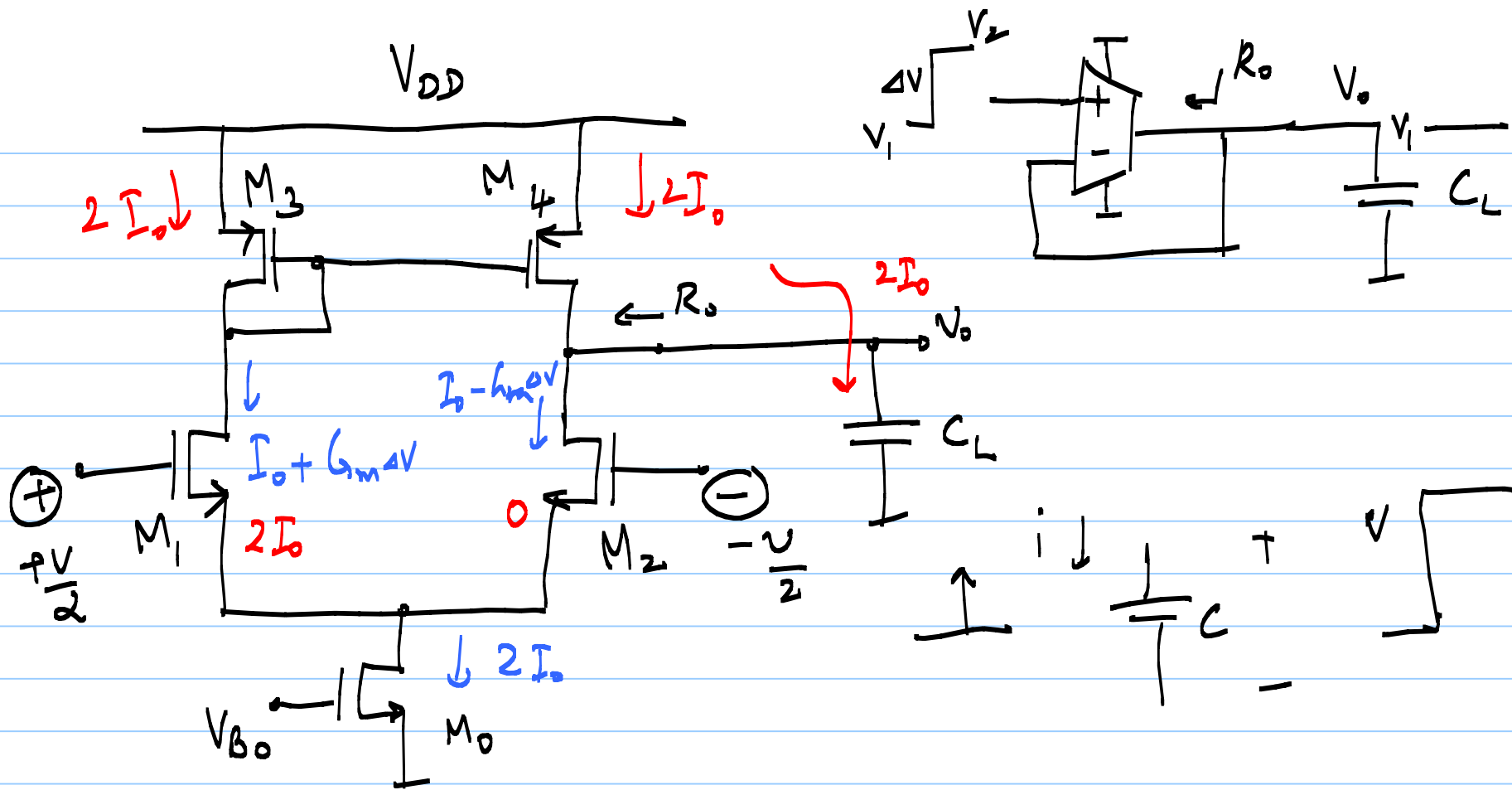
$$G_m = g_{m1} ; R_o = r_{ds2} \parallel r_{ds4} ; A_o = G_m R_o = g_{m1} (r_{ds2} \parallel r_{ds4})$$





@  $t = 0^+$  :

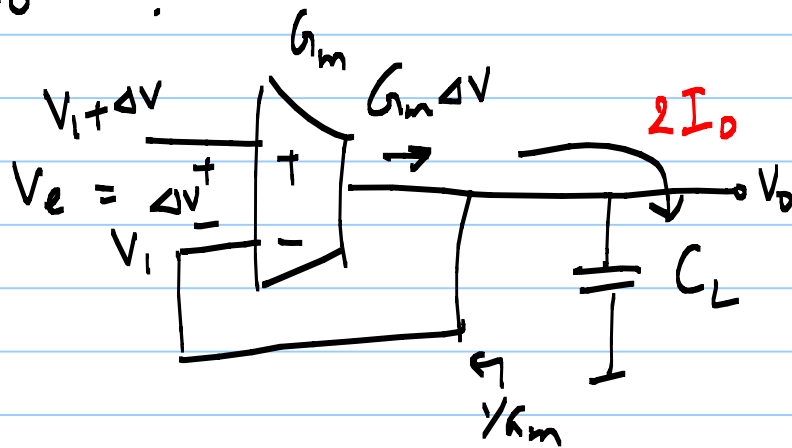


$V_e(t)$  approaches 0  
 as  $C_L$  charges towards  
 $V_1 + \Delta V$
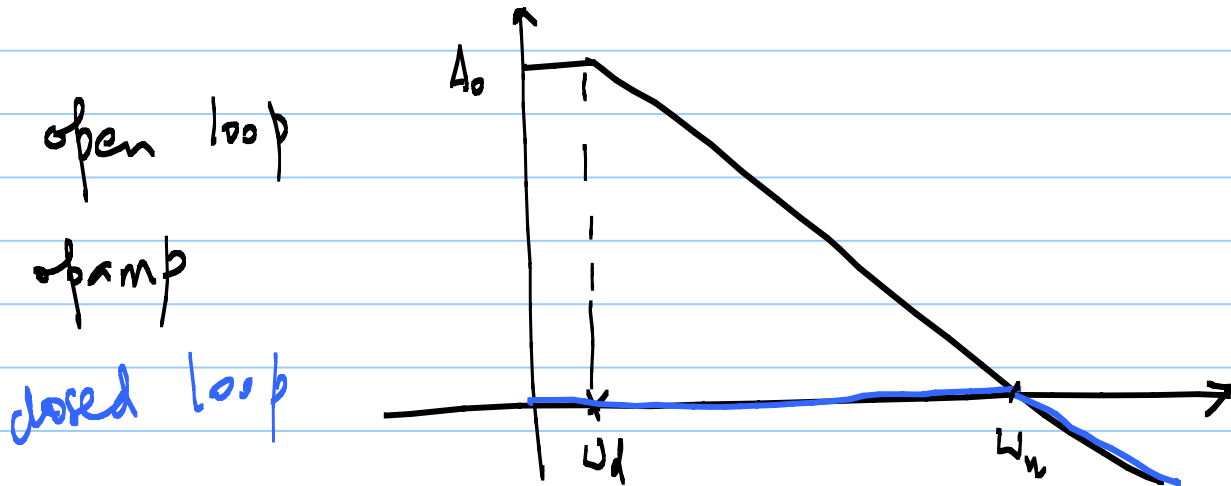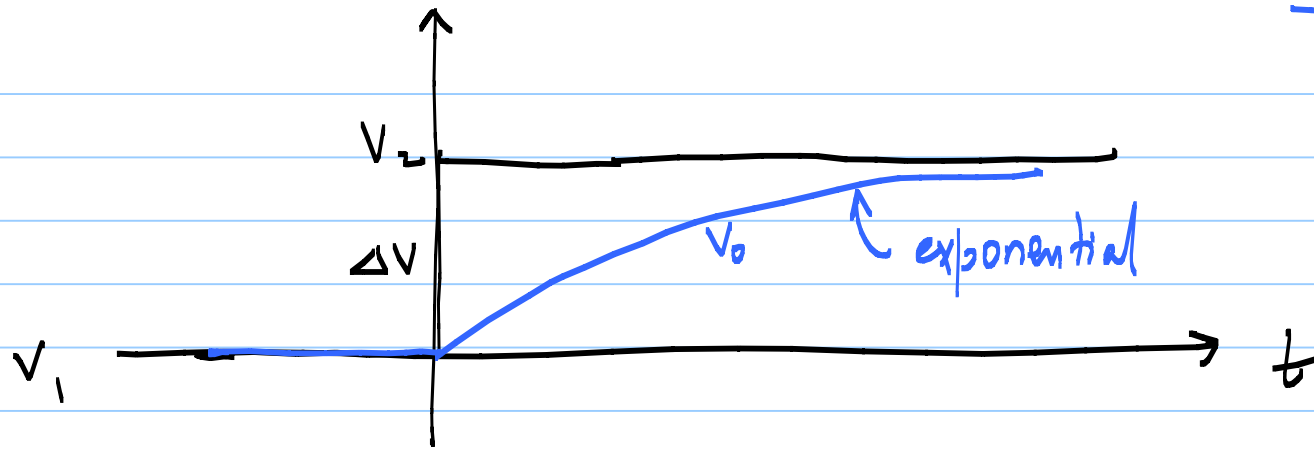
$$\tau = \frac{1}{\omega_u} = \frac{C_L}{G_m}$$





open loop  
opamp  
closed loop

Now start  $\uparrow \Delta V$

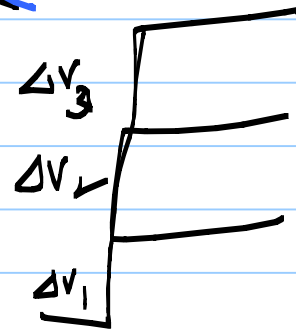

$$i_o \Big|_{t=0^+} = G_m \cdot \Delta V$$

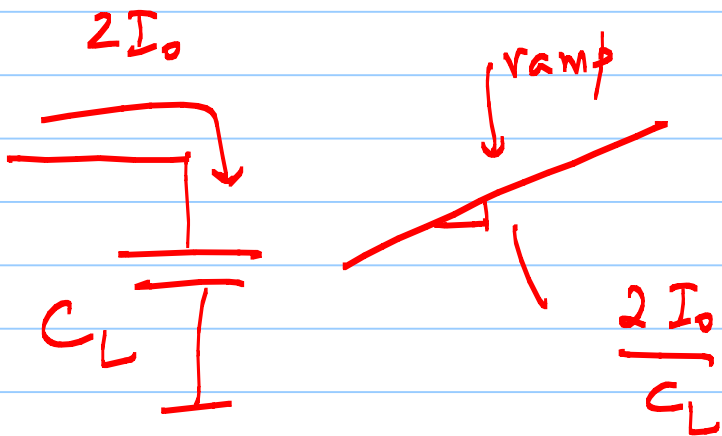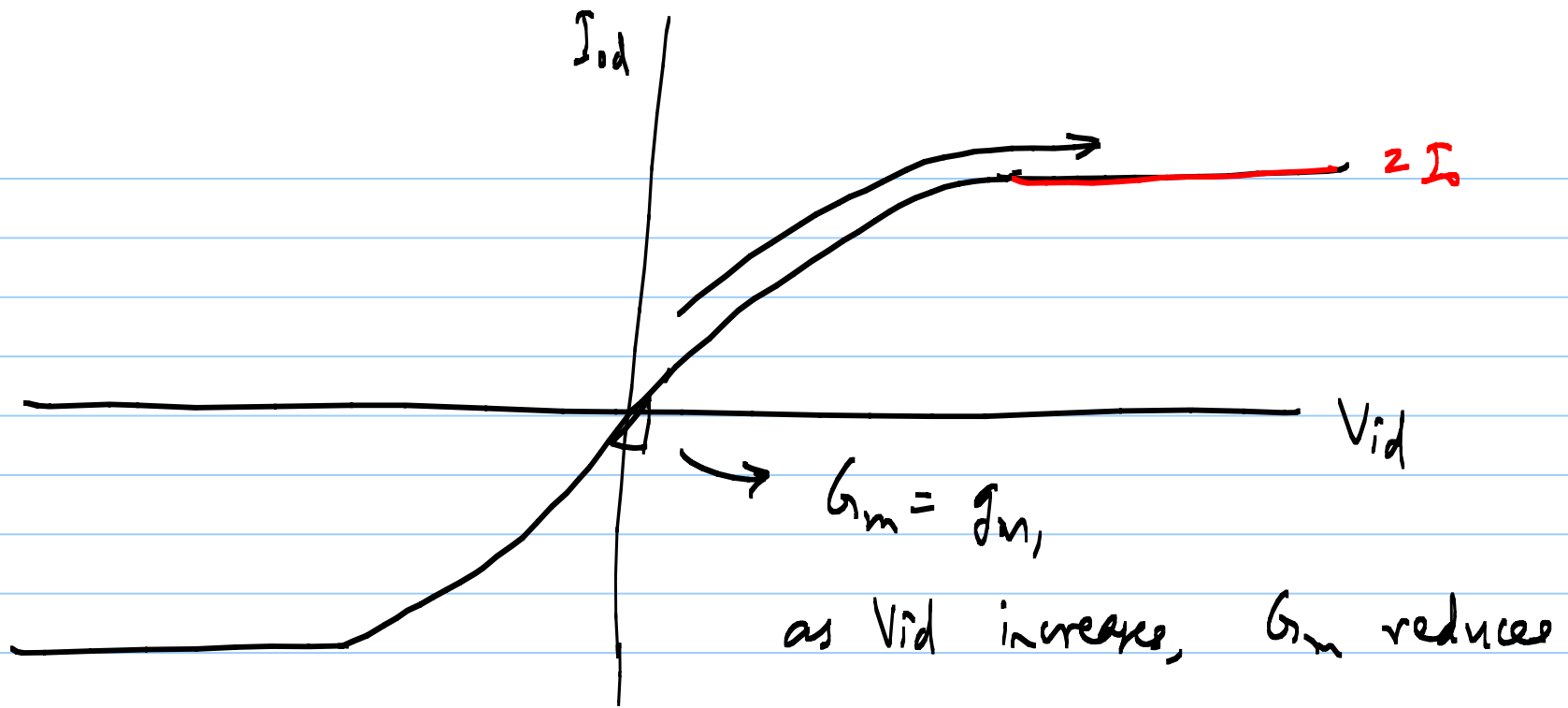

"slew"

$$\text{slew rate} = \frac{+ 2I_o}{- C_L}$$