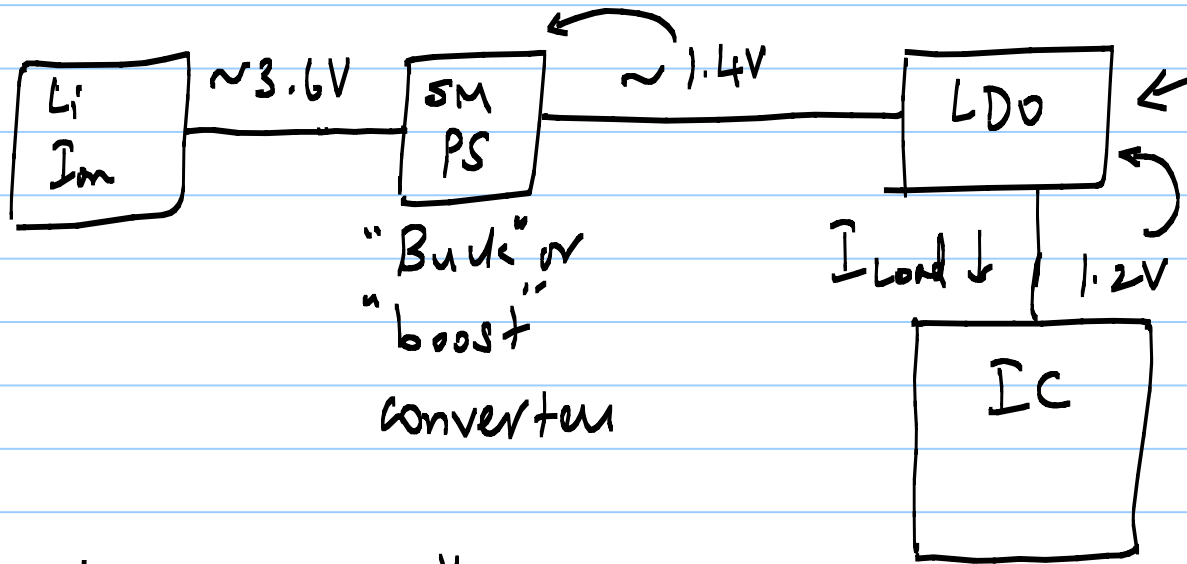



5/11/20



Lecture 50

One application of Bk reference - Low Dropout regulator



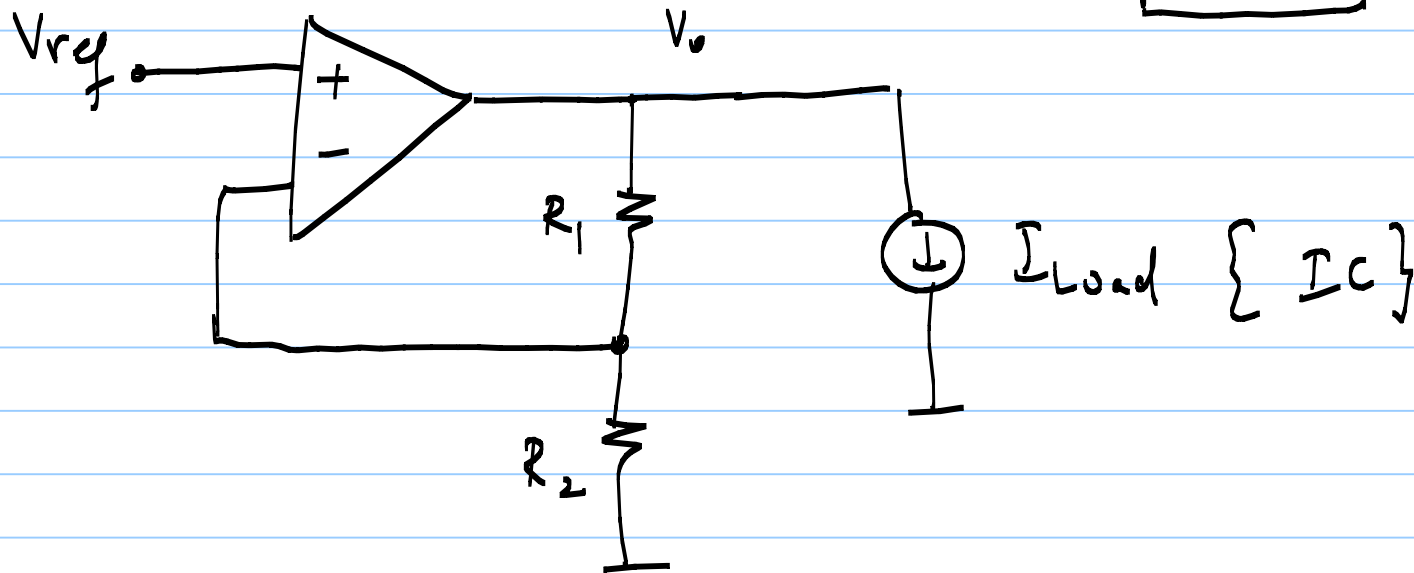← should be constant even if 3.6V battery voltage changes



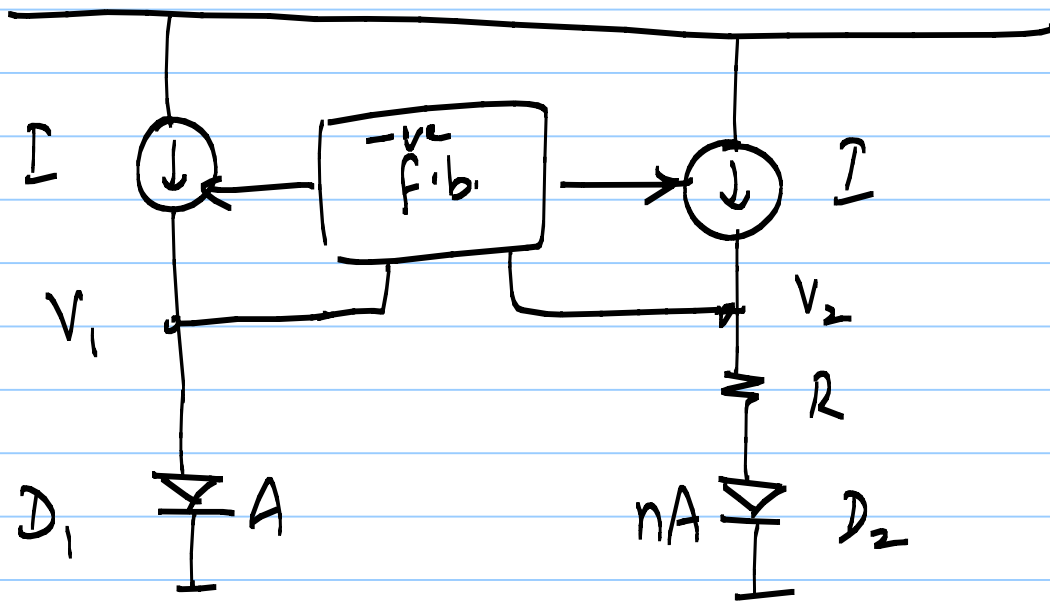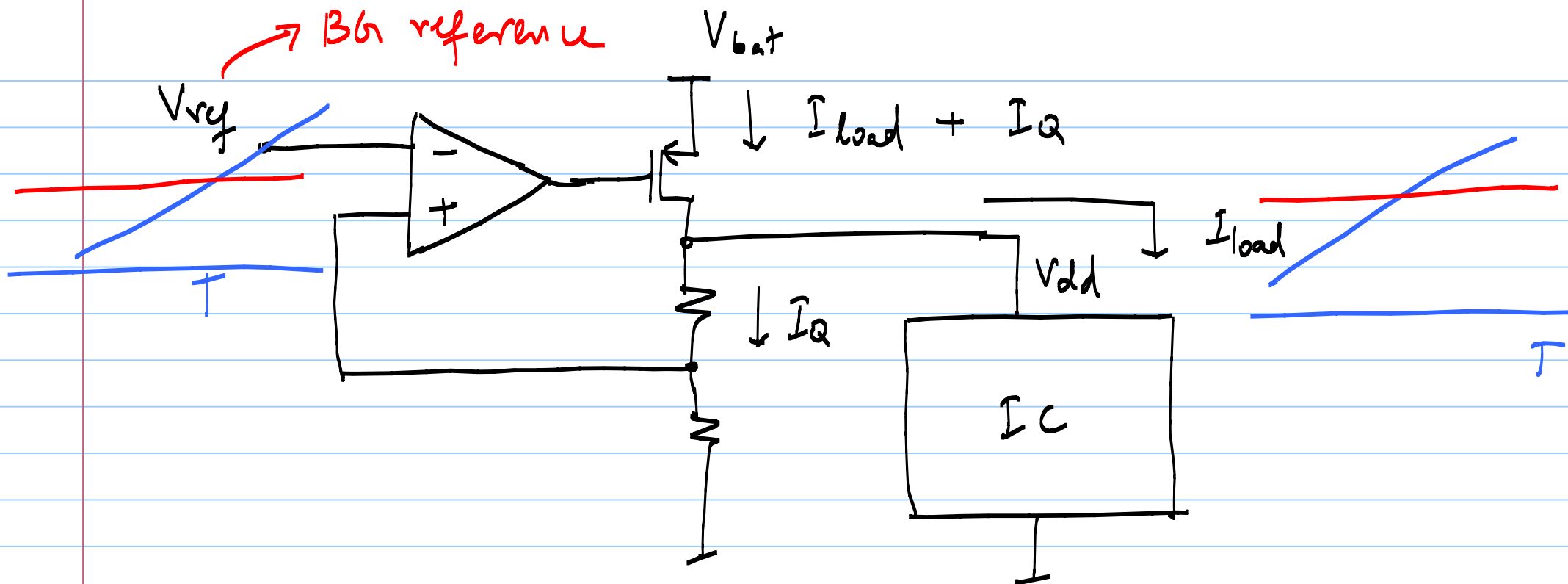

$$V_1 = V_2 = V_{ref} \sim 1.2V$$

$$V_1 = V_{BE1} \sim 1.2V$$


normally

$$V_{BE1} \sim 0.65V$$

$$V_{BE1} = V_T \ln \left(\frac{I_{C1}}{I_{S1}} \right) \approx \frac{0.65V}{0.026V} \approx 20. \times \times$$

\swarrow $0.65V$ \downarrow $26mV$

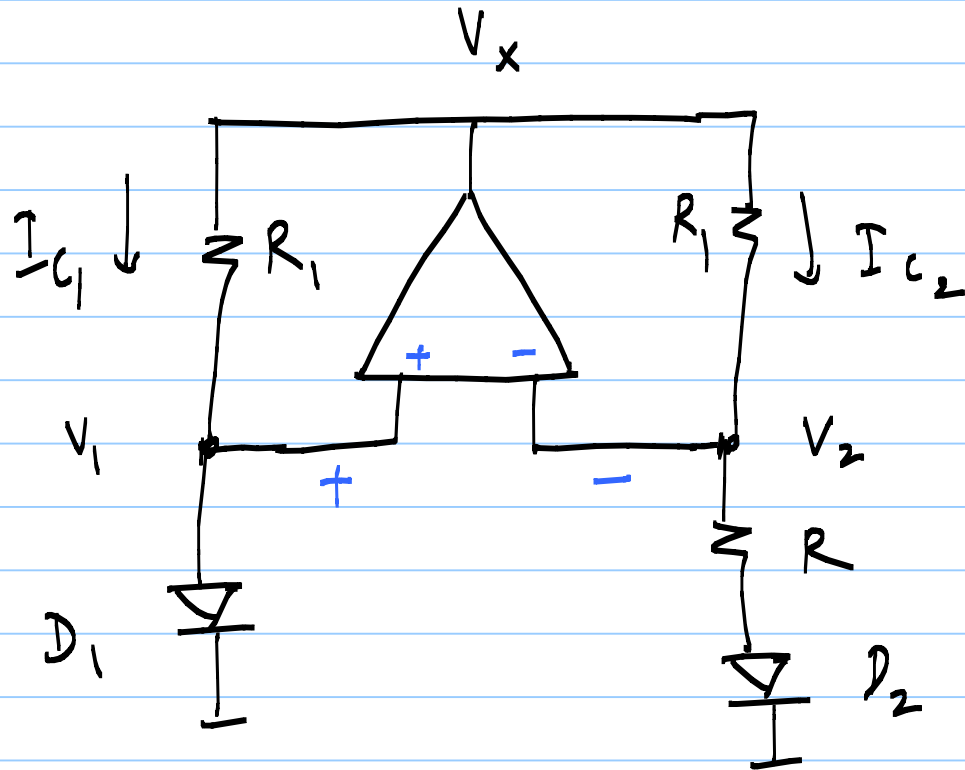I_{C1} large) $- V_{BE}$
 I_{S1} small) $\approx 1.2V$





$$I_{C1} = \frac{V_x - V_1}{R_1}$$

$$I_{C2} = \frac{V_x - V_2}{R_1} = I_{C1}$$

HW

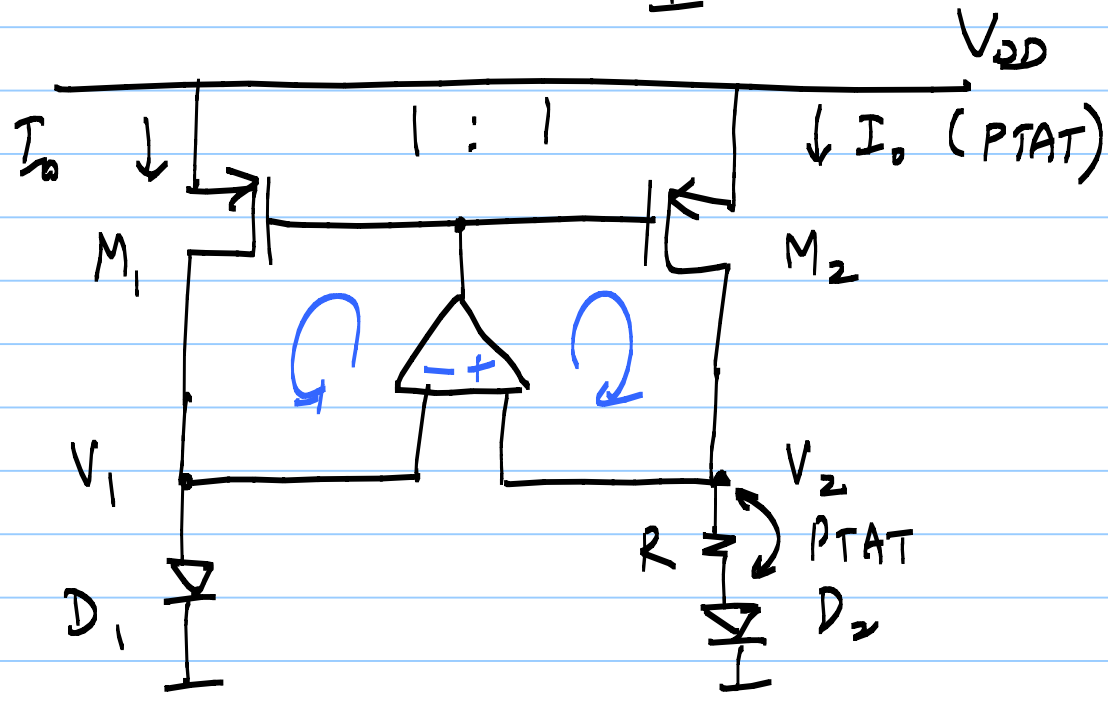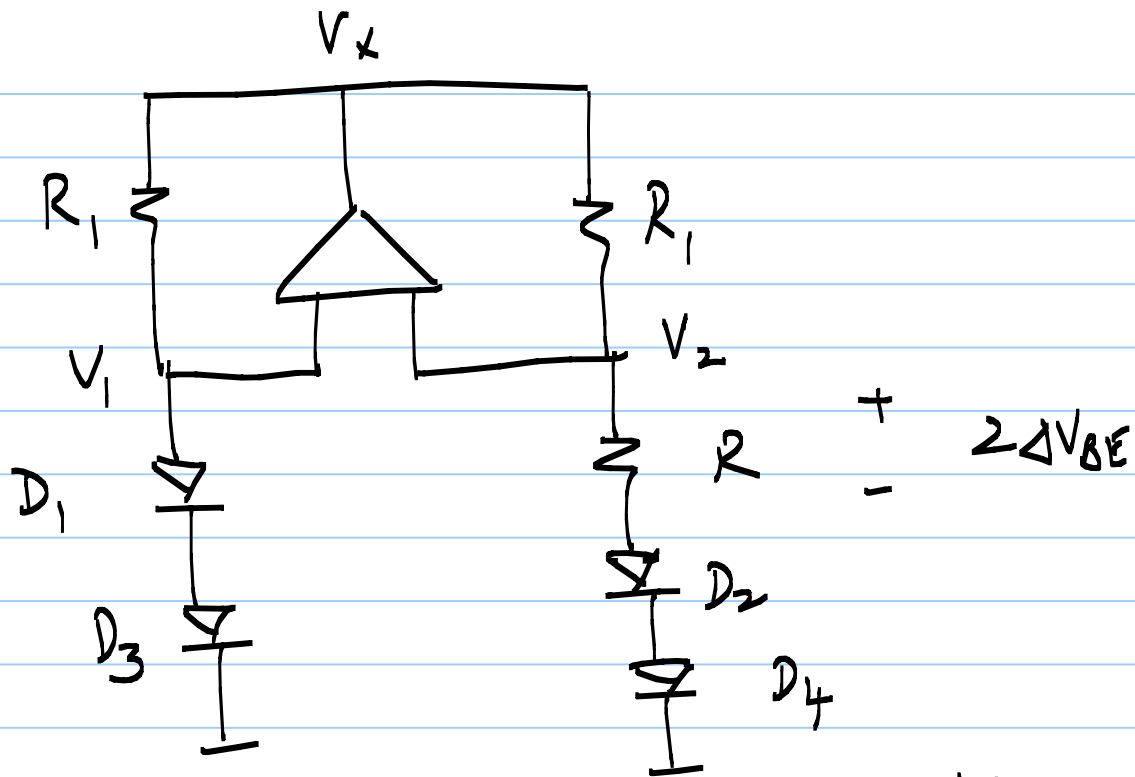* choose signs of opamp so that strength of -ve f.b. > strength of +ve f.b.





$$M_1 \equiv M_2$$

$$V_{SG1} = V_{SG2}$$

$$V_{SD1} = V_{SD2}$$

$$I_{D1} = I_{D2} = I_0$$

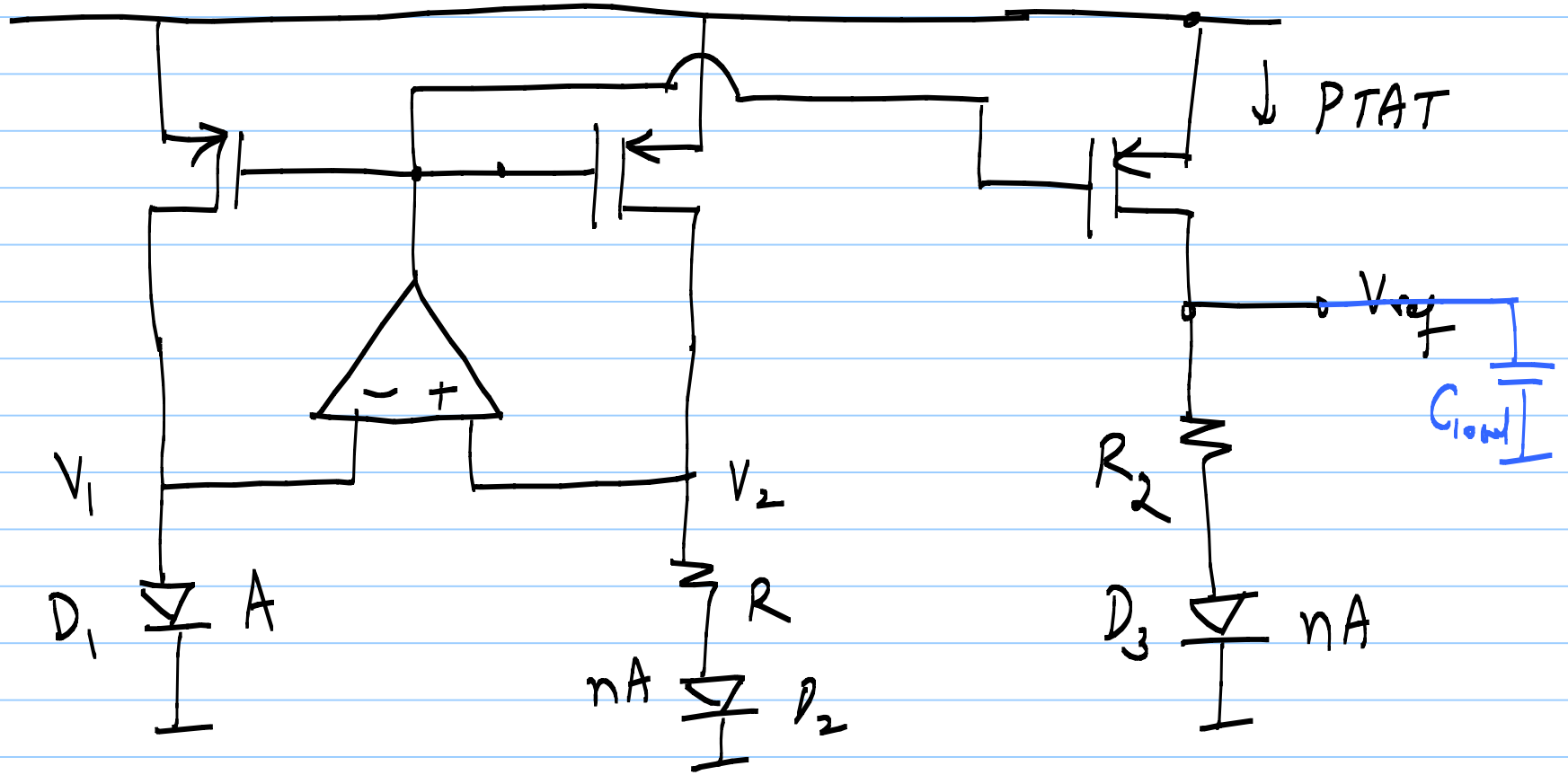

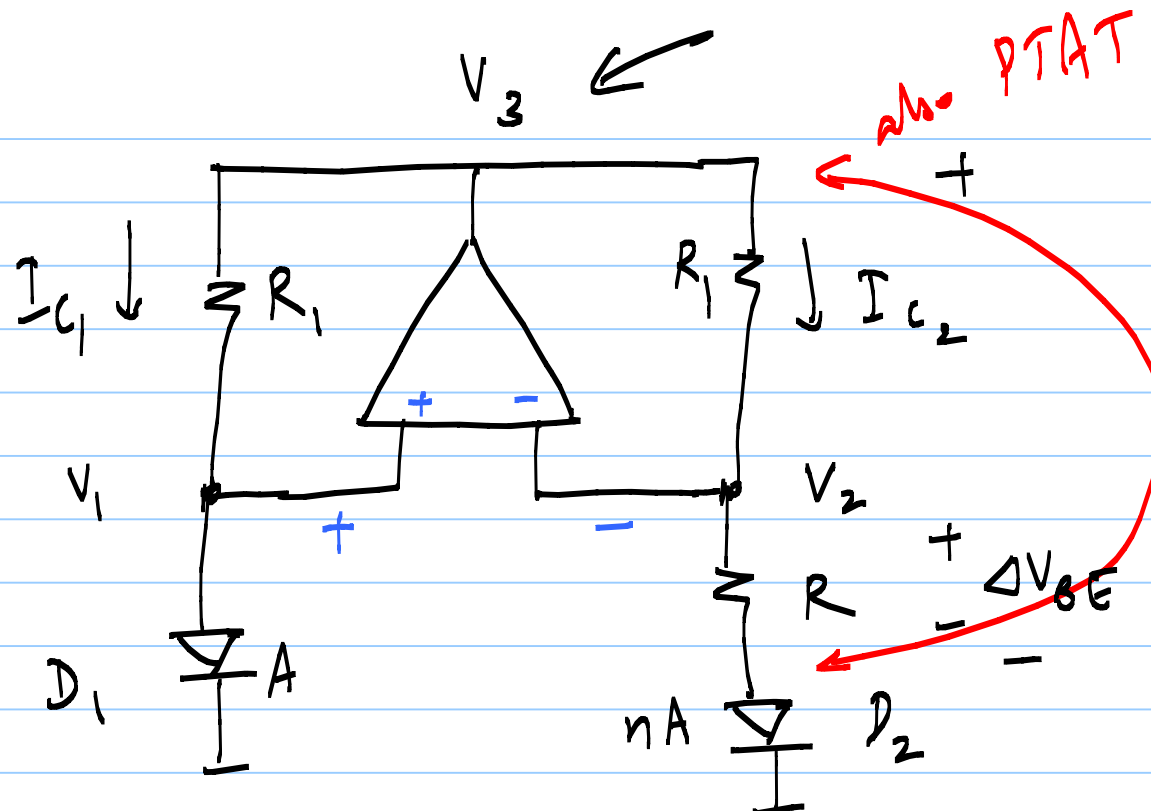

$$I_{C1} = I_{C2} = \frac{V_T \ln(n)}{R}$$

$$V_3 = V_2 + I_{C2} R_1$$

$$= \underbrace{V_{BE2} + I_{C2} R + I_{C2} R}_{} ,$$

earlier: set this T.C. = 0

Now: Set T.C. of $V_3 = 0$ i.e. $\left. \frac{\partial V_3}{\partial T} \right|_{300K} = 0$

$$V_3 = V_{BE2} + I_{C2} (R + R_1)$$

$$= V_{BE2} + \frac{V_T \ln(n)}{R} (R + R_1)$$

$$V_3 = V_{BE2} + \left[V_T \ln(n) \right] \left[1 + \frac{R_1}{R} \right]$$

$$\left. \frac{\partial V_3}{\partial T} \right|_{300K} = 0 \Rightarrow \left[1 + \frac{R_1}{R} \right] \ln(n) = 17.2$$

* choose $\frac{R_1}{R}$ so that n is small

* $V_3 = V_{ref}$ { Bk ref. voltage }

* V_{ref} depends on $\underbrace{\left(\frac{R_1}{R} \right)}_{\text{well controlled over "PVT" variations}}$