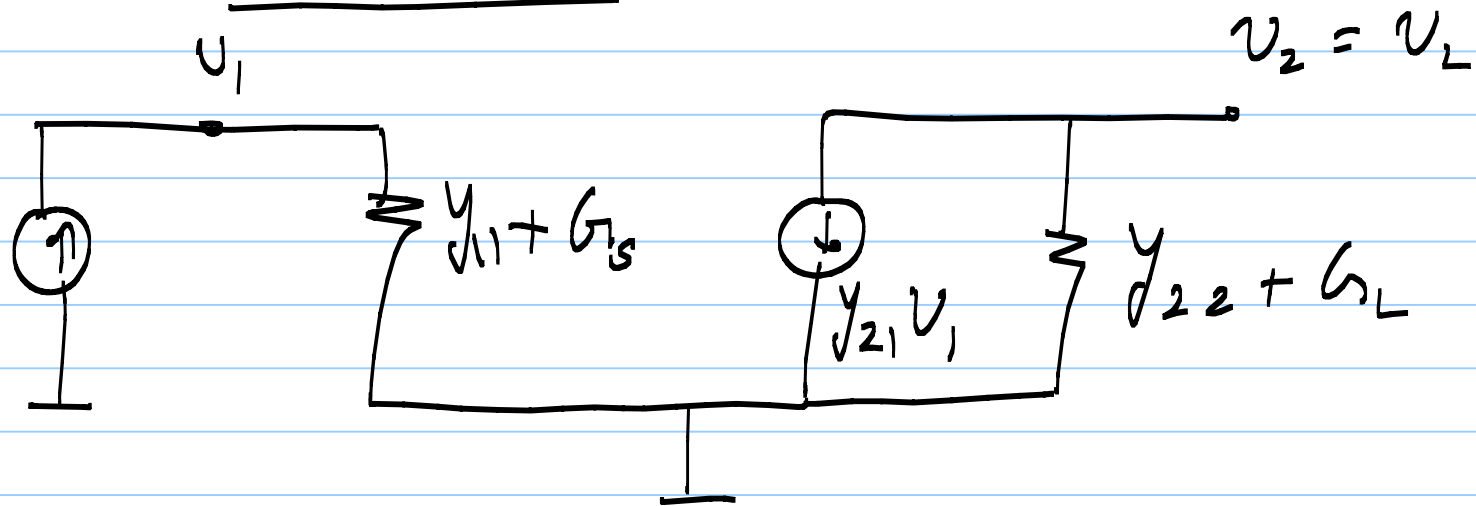


14/8/2020

Lecture 7



$$\text{Gain} = \frac{-y_{21}}{(y_{22} + G_L)} \cdot \left(\frac{G_s}{y_{11} + G_s} \right)$$

1) Gain independent of G_s : set $y_{11} = 0$
 $\Rightarrow i_1 = 0$

$$\frac{u_L}{u_s} = \frac{-y_{21}}{y_{22} + G_L}$$

2) Gain as large as possible:

y_{21} as large as possible

and

$y_{22} + G_L$ as small as possible

↳ set $y_{22} = 0$

$$\boxed{\frac{v_L}{v_s} = -\frac{y_{21}}{G_L}}$$

gain of amplifier
still dep. on G_L

We need a 2-port network with $inc[y]$:

$$[y] = \begin{bmatrix} 0 & 0 \\ \text{as large} & \\ \text{as possible} & 0 \end{bmatrix} = \begin{bmatrix} \partial f / \partial v_1 & \partial f / \partial v_2 \\ \partial g / \partial v_1 & \partial g / \partial v_2 \end{bmatrix}$$

$$I_1 = f(V_1, V_2) \quad ; \quad I_2 = g(V_1, V_2)$$


$$y_{11}, y_{12} = 0 \Rightarrow \frac{\partial f}{\partial V_1}, \frac{\partial f}{\partial V_2} = 0 \Rightarrow I_1 = I_0$$

constant current

$$y_{22} = 0, y_{21} = \text{large} \Rightarrow I_2 = g(V_1) \text{ only}$$

$$I_1 = I_0$$

$$I_2 = g(V_1)$$

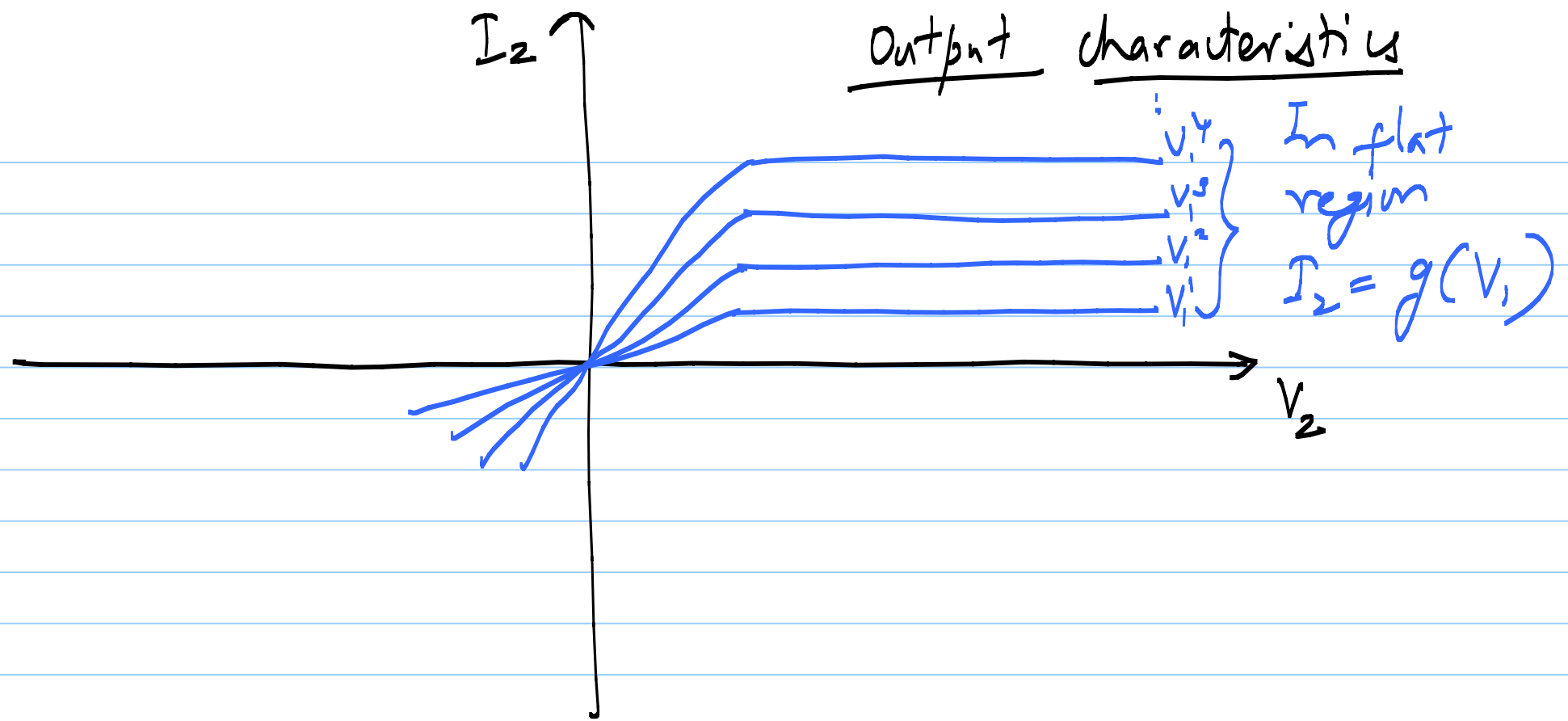


Special case: $I_1 = 0 \Rightarrow$ passivity: $V_1 I_1 + V_2 I_2 \geq 0$
 $\Rightarrow V_2 I_2 \geq 0$

All devices that exhibit "good" amplifier behaviour (high^{inc.} gain etc.) have such characteristics

MOSFET $\Rightarrow I_1 = 0$; BJT, JFET } $\Rightarrow I_1$ very small

MOSFET

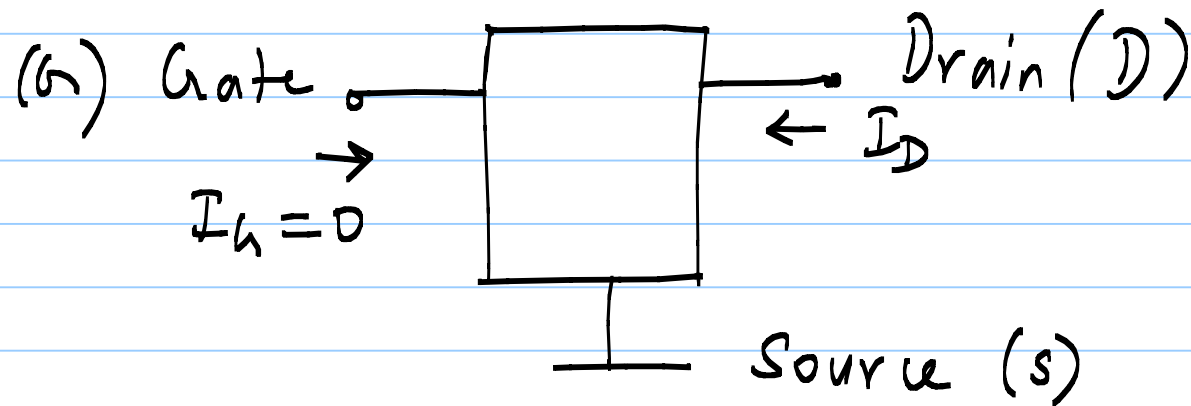

NMOSFET

$$I_D = 0 \quad \text{if} \quad V_{GS} < V_T$$

$$I_D = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right) (V_{GS} - V_T)^2 \quad \text{if} \quad V_{DS} \geq (V_{GS} - V_T)$$

"saturation"

$$I_D = \mu_n C_{ox} \left(\frac{W}{L}\right) \left[(V_{GS} - V_T) V_{DS} - \frac{V_{DS}^2}{2} \right] \quad \text{if} \quad V_{DS} \leq (V_{GS} - V_T)$$



"triode", "linear"

V_T = Threshold voltage

μ_n = mobility of electrons

C_{ox} = oxide cap. per unit area

W, L = geometric parameters of MOSFET

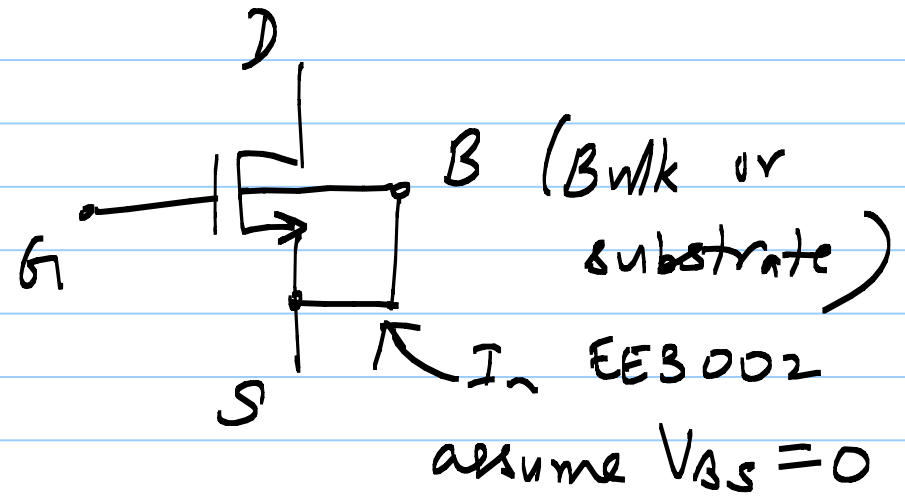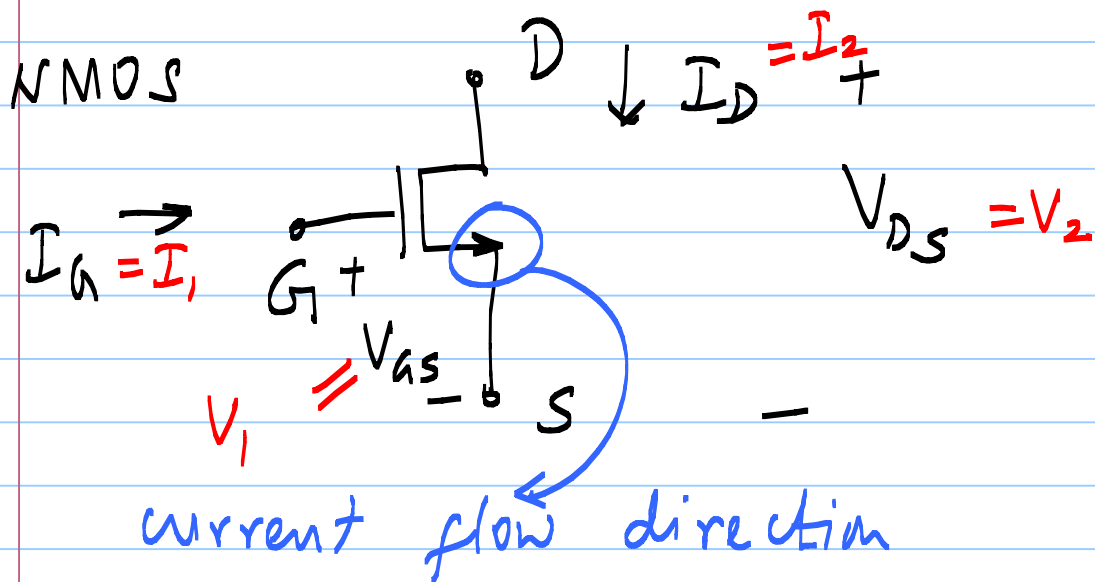

$$I_G = 0 \Rightarrow Y_{11} = Y_{12} = 0$$


In sat., I_D is independent of V_{DS}

Operate MOSFET in sat. for building a good amplifier

I_2 is indep. of $V_2 \Rightarrow y_{22} = 0$

$$y_{21} = \frac{\partial I_2}{\partial V_1} = \frac{\partial I_D}{\partial V_{as}} = \mu_n C_{ox} \left(\frac{W}{L} \right) (V_{as} - V_T)$$

for $V_{as} > V_T$ and and

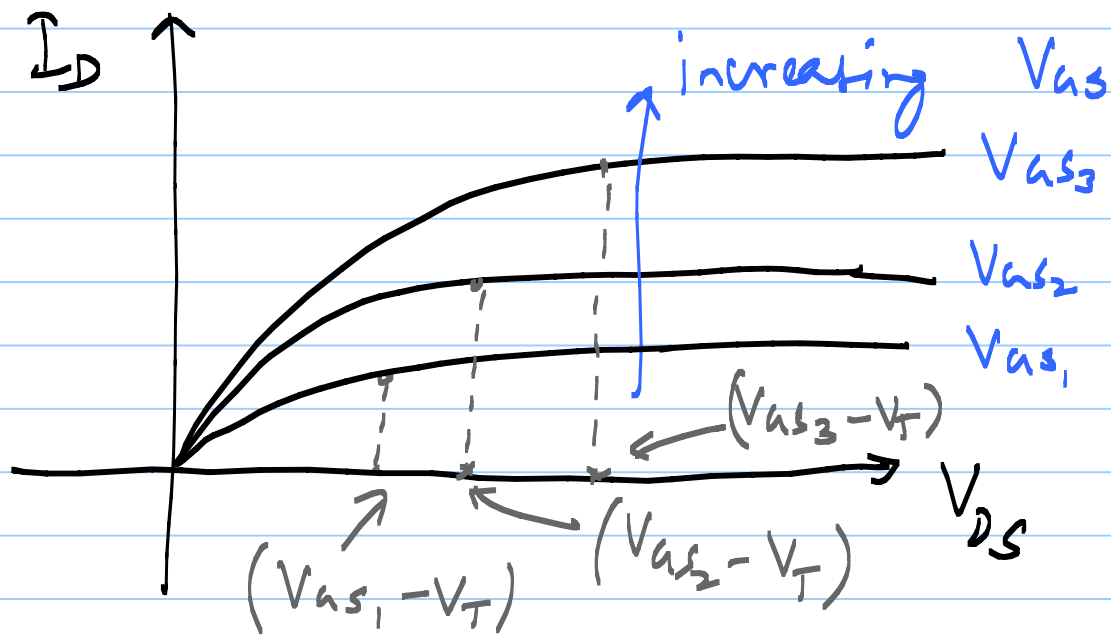

$$V_{DS} \geq (V_{as} - V_T)$$

$$I_{D1} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right) (V_{as1} - V_T)^2$$

