
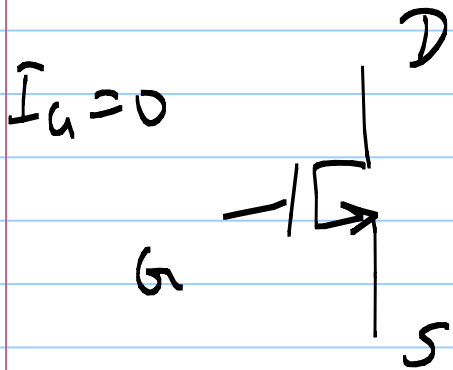


18/8/2020


Lecture 8

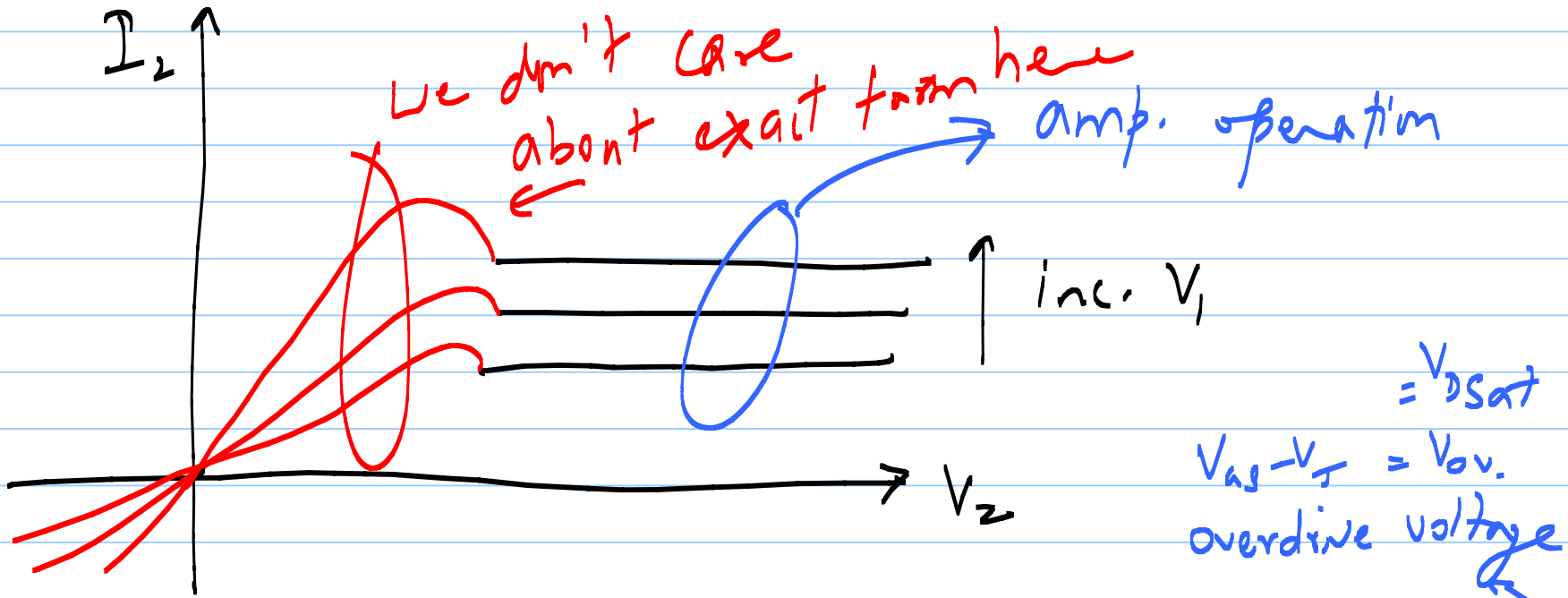

$$I_D = 0 \quad \text{if } V_{GS} < V_T \quad (\text{off})$$

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_T)^2 \quad \text{if } V_{DS} \geq \underline{V_{GS} - V_T} \quad (\text{sat.})$$
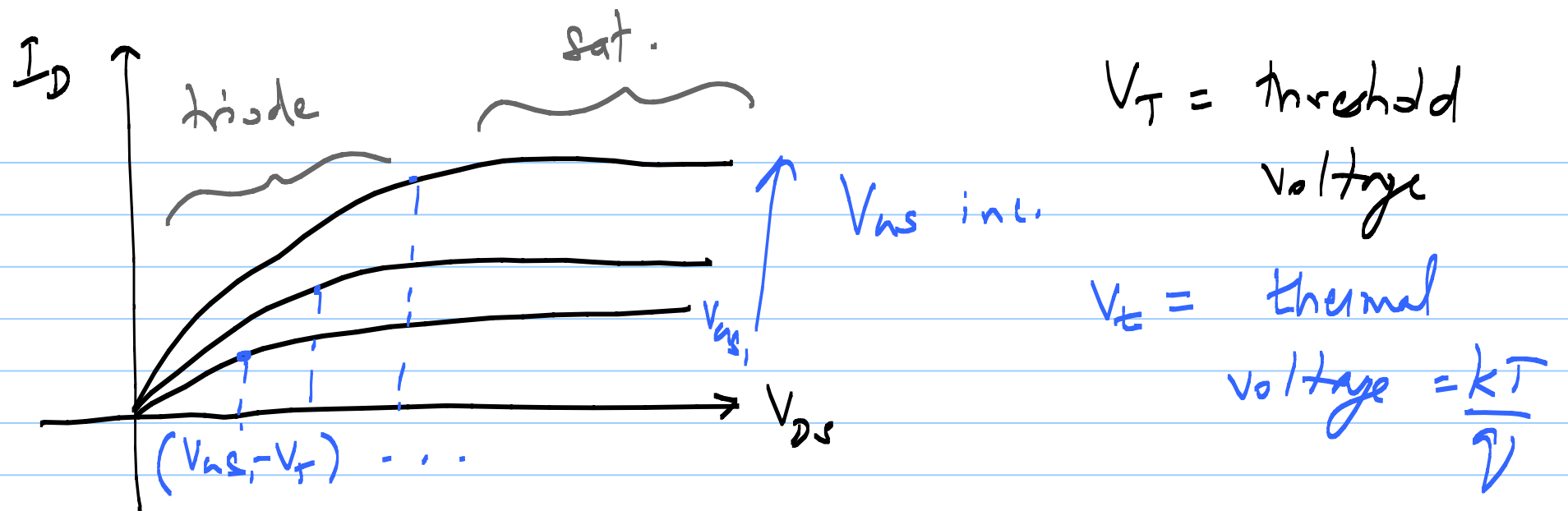
$$I_D = \mu_n C_{ox} \frac{W}{L} \left( (V_{GS} - V_T) V_{DS} - \frac{V_{DS}^2}{2} \right) \quad \text{if } V_{GS} > V_T \quad \text{and} \quad V_{DS} \leq V_{GS} - V_T$$



Amplifiers: Use sat. region

$$I_G = 0; \quad I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_T)^2$$

use this to derive op. pt.

$$y_{11} = \frac{\partial I_G}{\partial V_{GS}} = 0; \quad y_{12} = \frac{\partial I_G}{\partial V_{DS}} = 0;$$

$$y_{22} = \frac{\partial I_D}{\partial V_{DS}} = 0; \quad y_{21} = \frac{\partial I_D}{\partial V_{GS}}$$

$$y_{21} = \frac{\partial I_D}{\partial V_{GS}} = \mu_n C_{ox} \left( \frac{W}{L} \right) (V_{GS} - V_T) = g_m$$

transconductance  
of  
MOSFET

$$1) \quad g_m = \mu_n C_{ox} \left( \frac{W}{L} \right) (V_{GS} - V_T)$$

$$2) \quad g_m = 2 \times \frac{1}{2} \times \mu_n C_{ox} \left( \frac{W}{L} \right) (V_{GS} - V_T)^2 \times \frac{1}{(V_{GS} - V_T)}$$

$$= \frac{2 I_D}{V_{GS} - V_T}$$


$$3) \quad g_m^2 = 2 \times \frac{1}{2} \mu_n^2 C_{ox}^2 \left( \frac{W}{L} \right)^2 (V_{GS} - V_T)^2$$

$$= 2 \mu_n C_{ox} \left( \frac{W}{L} \right) I_D$$

$$g_m = \sqrt{2\mu_n C_{ox} \left(\frac{W}{L}\right) I_D}$$

$$[y] = \begin{bmatrix} 0 & 0 \\ g_m & 0 \end{bmatrix}$$

## MOSFET Amplifier

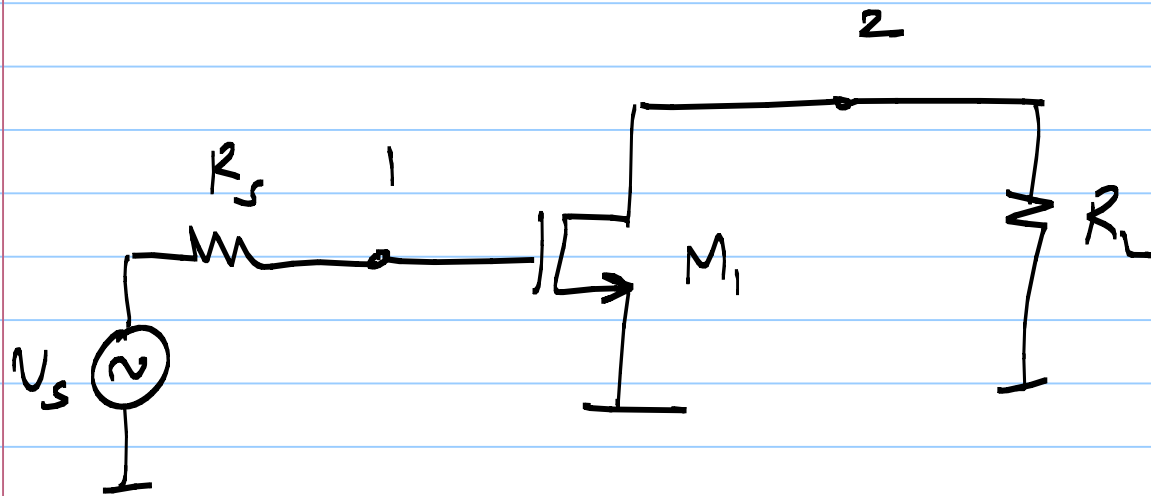

Small-signal  
picture

(op. pt. should be  
such that  $M_1$  is  
biased in sat.)

In triode region:

$$y_{11} = y_{12} = 0$$



$$y_{22} = \frac{\partial I_D}{\partial V_{DS}} = \frac{\partial}{\partial V_{DS}} \left[ \mu_n C_{ox} \left( \frac{W}{L} \right) \left\{ (V_{GS} - V_T) V_{DS} - \frac{V_{DS}^2}{2} \right\} \right]$$

$$= \mu_n C_{ox} \left( \frac{W}{L} \right) (V_{GS} - V_T - V_{DS}) \neq 0$$

$$y_{21} = \frac{\partial I_D}{\partial V_{GS}}$$

$$= \mu_n C_{ox} \left( \frac{W}{L} \right) \cdot V_{DS}$$

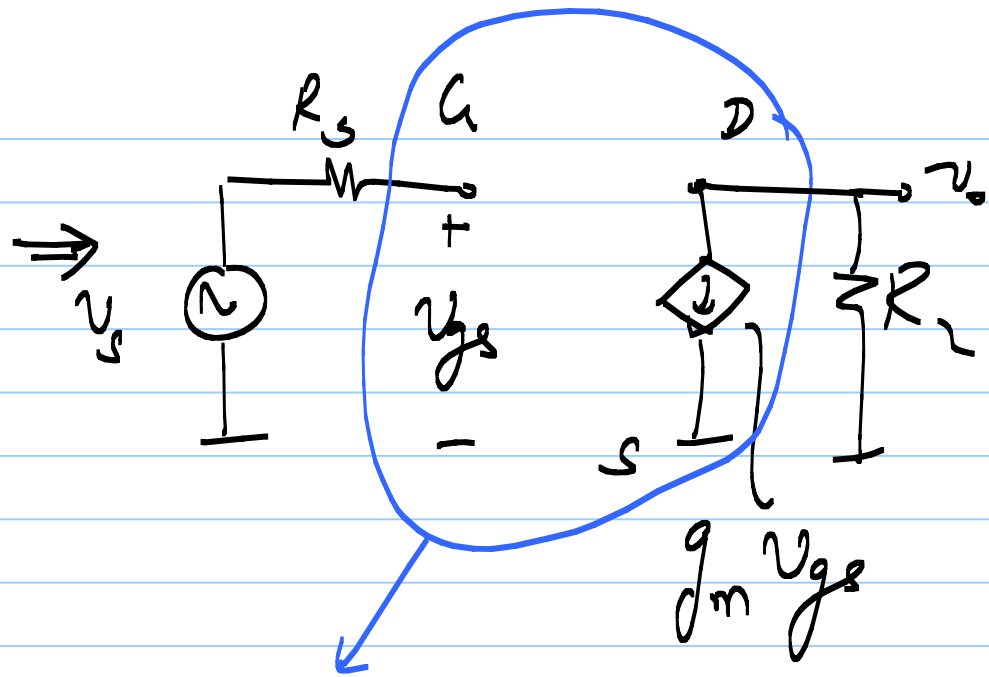
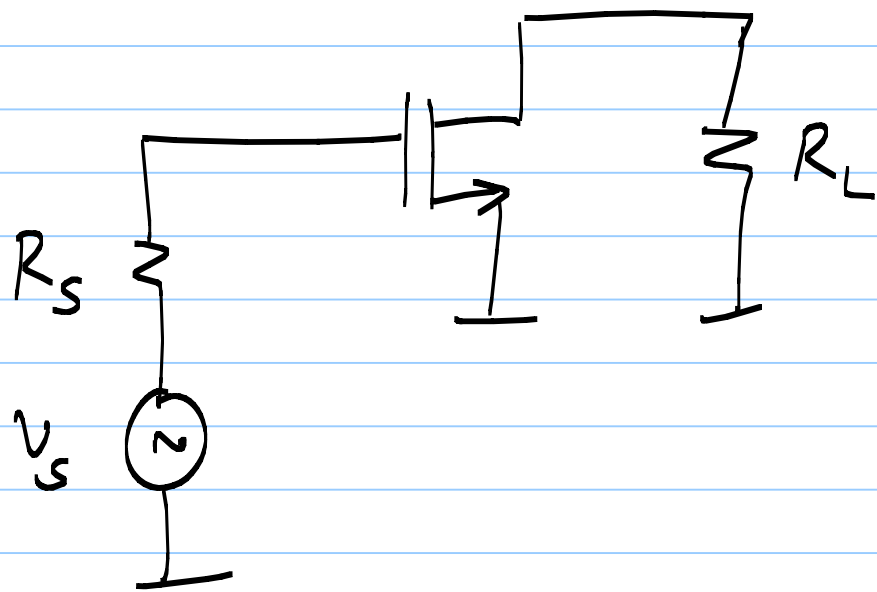
$$\left\{ V_{DS} < (V_{GS} - V_T) \right\}$$



SS model of MOSFET



$$\text{gain} = \frac{v_o}{v_s} = -g_m R_L$$

### MOSFET Biasing:

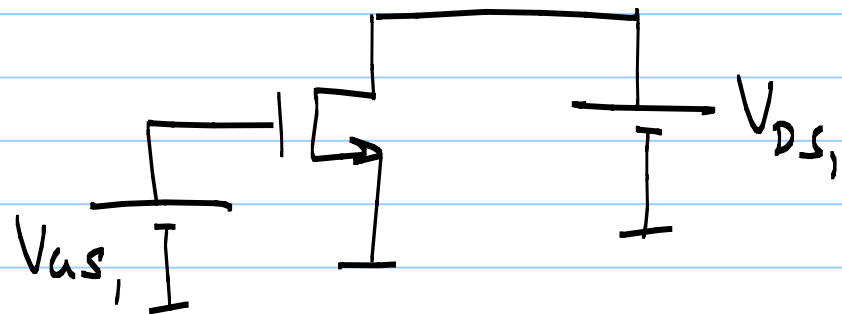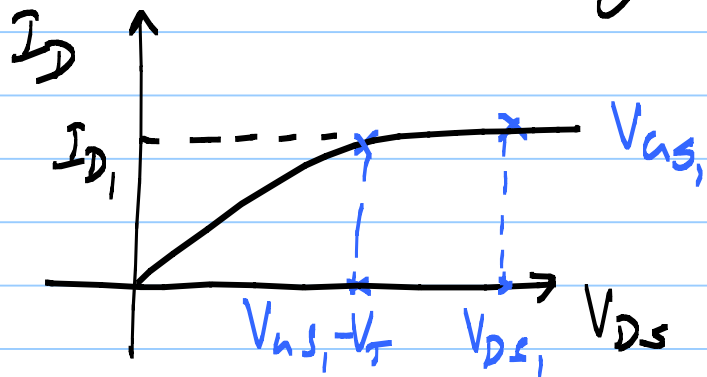

Add signal source & load to DC biased MOSFET:

$$-R_L + V_{R_L} = I_{D_1} \cdot R_L$$

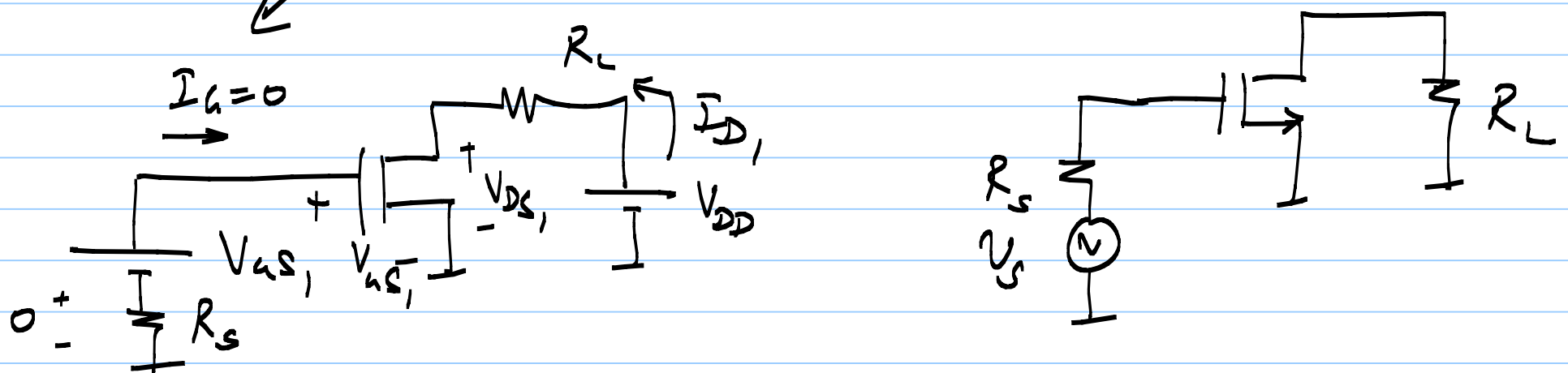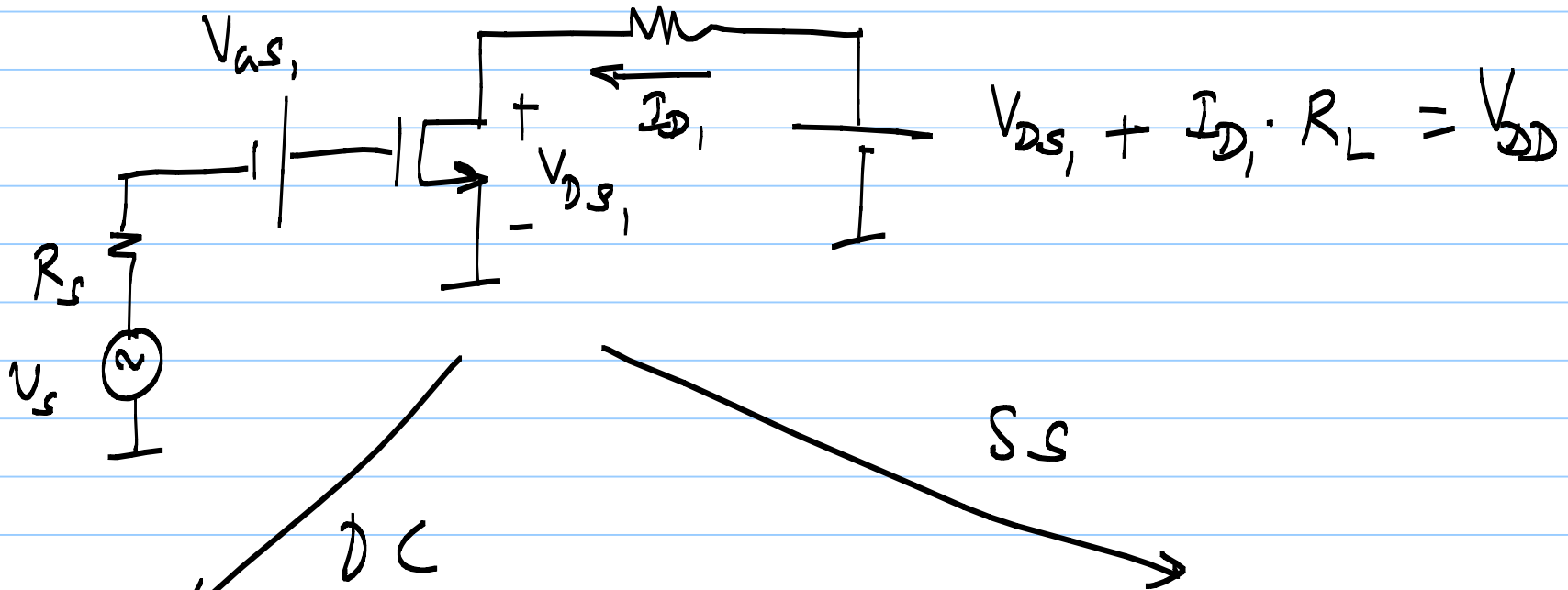


\* Avoid use of 2 batteries:

⇒ generate  $V_{GS}$  from  $V_{DD}$   
( $V_{DD} > V_{GS}$ )

largest voltage  
in the circuit

DC:

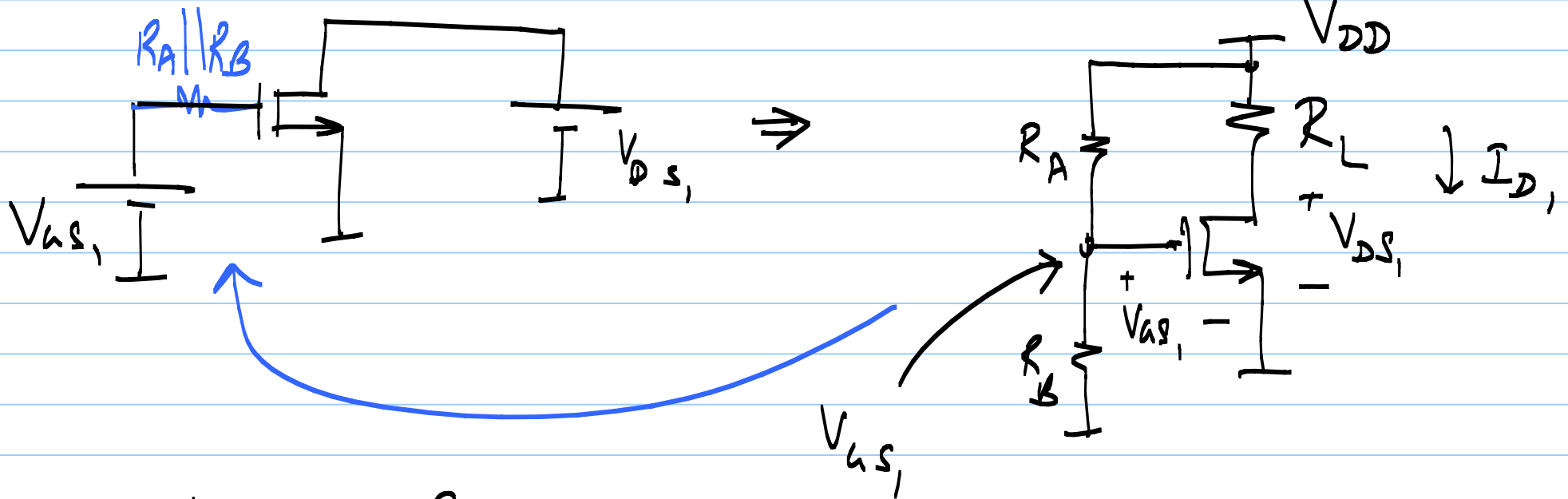

$$V_{GS} = \frac{R_B}{R_A + R_B} \cdot V_{DD}$$