

ADVANCED ELECTRICAL NETWORKS : PROBLEM SET 3

Problem 1

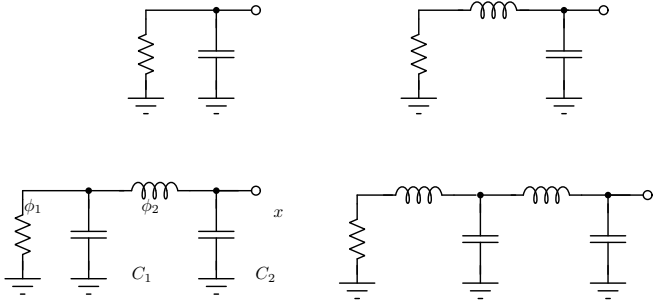


Figure 1: Networks for Problem 1.

Fig. 1 shows four passive impedances. For each of these networks, determine the mean square RMS noise at the terminal x (with respect to ground). Simulate and verify your answers using SPICE. Specifically, for each of the networks, plot

$$\int_0^f S_x(f') df' \quad (1)$$

as a function of f . Choose an appropriate scale for the x and y axes, using the component values below. Assume that $R = 1 \text{ K}\Omega$. All inductors are 1 nH and capacitors are 1 pF . You might want to run SPICE first, before doing the analysis.

Problem 2

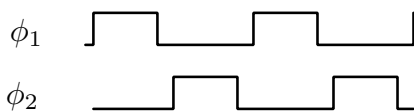
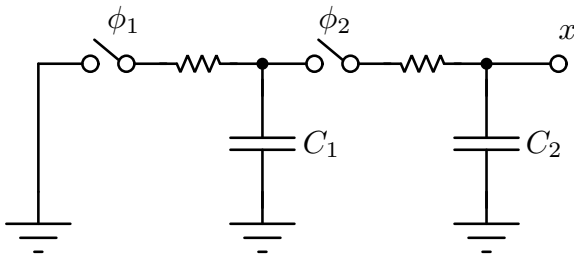


Figure 2: Network for Problem 2.

Fig. 2 shows a network, where the switches are periodically operated by the waveforms ϕ_1 and ϕ_2 , as shown. The switches are modeled as ideal ones in series with resistors of value r . All RC time constants are such that capacitor voltages completely settle in a clock phase. Determine the

mean square value of the noise the voltage at x , sampled at the falling edge of ϕ_2 .

Problem 3

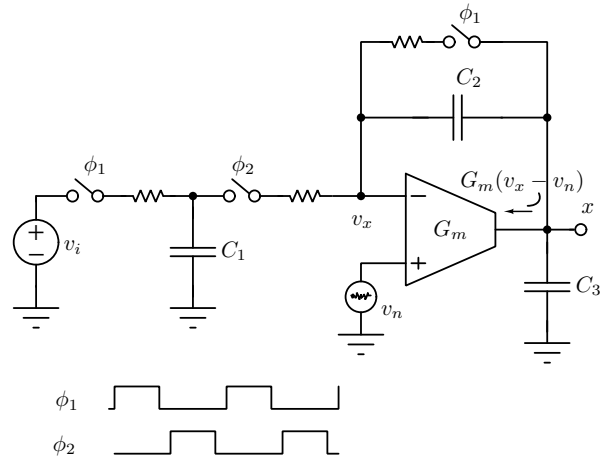


Figure 3: Network for Problem 3.

Fig. 3 shows a network, where the switches are periodically operated by the waveforms ϕ_1 and ϕ_2 , as shown. The switches are modeled as ideal ones in series with resistors of value r . v_i is a DC source. v_n represents the noise of the transconductor, and has a spectral density $4kT/G_m$. All time constants are such that capacitor voltages completely settle in a clock phase. The system output is the voltage at x , sampled at the falling edge of ϕ_2 .

1. For this part, assume that all noise sources are zero. Determine the output.
2. Determine the mean square value of the noise the voltage at x , sampled at the falling edge of ϕ_2 .

Problem 4

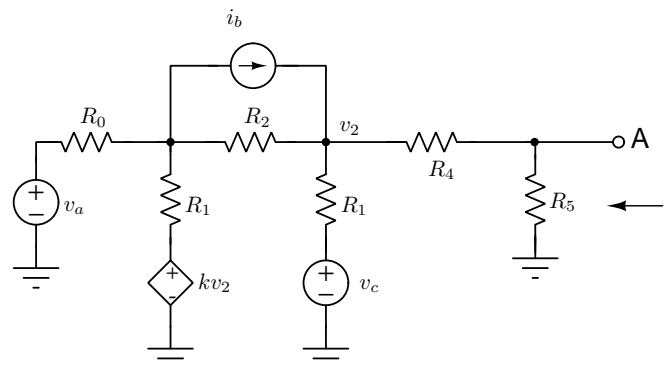


Figure 4: Networks for Problem 4.

Determine the Thevenin equivalent of the circuit of Fig. 4 looking between A and ground, in as efficient a way as possible.