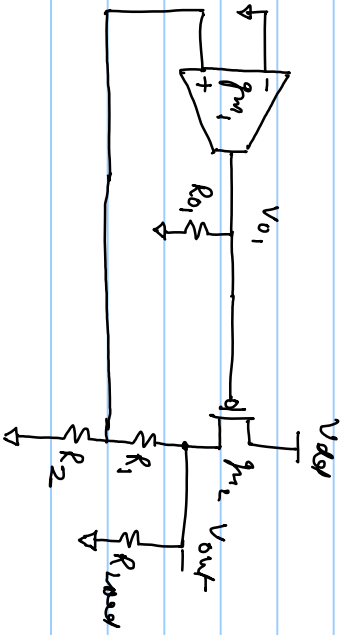


Line Regulation & Power Supply Rejection Ratio (PSRR)

$$\text{Line Regulation (d/c)} = \frac{\partial V_{out}}{\partial V_{dg}}$$



$$R_{out} = r_{o2} \parallel (R_1 + R_2) \parallel R_{load}$$

Assume $r_{o2} \gg (R_1 + R_2) \parallel R_{load}$

$$R_{out} = (R_1 + R_2) \parallel R_{load}$$

$$V_{o1} = \beta g_{m1} R_0 V_{out} \quad \text{--- (1)}$$

Apply KCL at V_{out}

$$\frac{V_{out}}{R_{out}} - (V_{dd} - V_{o1})g_{m2} = 0$$

$$\frac{V_{out}}{R_{out}} + \beta g_{m1} R_{o1} g_{m2} V_{out} = V_{dd} g_{m2}$$


$$V_{out} \left[\frac{1}{R_{out}} + \beta g_{m1} R_{o1} g_{m2} \right] = V_{dd} g_{m2}$$

$$\frac{V_{out}}{V_{dd}} = \frac{g_{m2} R_{out}}{1 + \beta g_{m1} R_{o1} g_{m2} R_{out}} = \frac{g_{m2} R_{out}}{\beta g_{m1} R_{o1} g_{m2} R_{out}}$$

$\gg 1$

$$\frac{V_{out}}{V_{dd}} = \frac{1}{\beta g_{m1} R_{o1}}$$

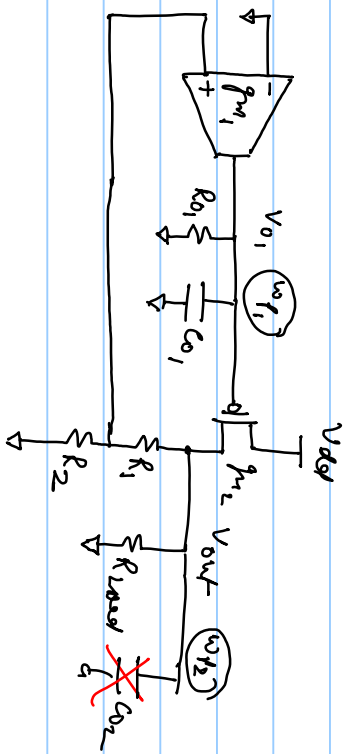$g_{m1} R_{o1} \rightarrow$ gain of error amplifier (1st stage)



for $\omega \leq \omega_{p1}$ & ω_{p1} is dominant
we can ignore ω_{p2}

$$V_{o1} = \frac{13 g_{m1} R_{o1}}{1 + R_{o1} C_{o1} s} V_{in} \quad \text{--- (1)}$$

apply KCL at V_{out}

$$\frac{V_{out}}{R_{out}} - (V_{out} - V_{o1}) g_{m2} = 0$$

$$\frac{V_{out}}{R_{out}} - V_{dd} g_{m2} + \frac{\beta g_{m1} R_{o1} g_{m2} V_{out}}{1 + R_{o1} c_{o1} s} = 0$$

$$V_{out} \left[\frac{1}{R_{out}} + \frac{\beta g_{m1} R_{o1} g_{m2}}{(1 + R_{o1} c_{o1} s)} \right] = V_{dd} g_{m2}$$

$$V_{out} \frac{1 + R_{o1} c_{o1} s + \beta g_{m1} R_{o1} R_{out} g_{m2}}{R_{out} (1 + R_{o1} c_{o1} s)} \stackrel{\gg 1}{=} V_{dd} g_{m2}$$

$$V_{out} \frac{(R_{o1} c_{o1} s + \beta g_{m1} R_{o1} R_{out} g_{m2})}{R_{out} (1 + R_{o1} c_{o1} s)} = V_{dd} g_{m2}$$

$$V_{out} \times \beta g_{m1} g_{m2} R_{o1} R_{out} \left(1 + \frac{R_{o1} c_{o1} s}{\beta g_{m1} R_{o1} g_{m2} R_{out}} \right) = V_{dd} g_{m2} (1 + R_{o1} c_{o1} s) R_{out}$$


$$\frac{V_{out}}{V_{dd}} = \frac{1}{\beta g_{m1} R_{o1}} \left[\frac{1 + R_{o1} c_{o1} s}{1 + \frac{R_{o1} c_{o1} s}{\beta g_{m1} R_{o1} g_{m2} R_{out}}} \right]$$

$$w_{p1} = \frac{1}{R_{o1} C_{o1}}$$



$$\& A_{o1} = g_{m1} R_{o1} \quad g_{m2} R_{o2}$$

$$L_{o1}(dc) = \beta A_{o1}$$


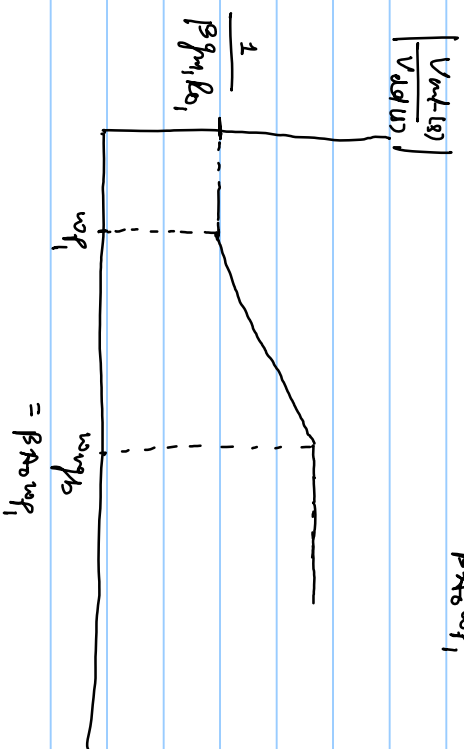
$$\frac{V_{out}(s)}{V_{in}(s)} = \frac{1}{\beta g_{m1} R_{o1}} \frac{1 + s/w_{p1}}{1 + s/w_{p2}}$$



Consider w_{p2} as well.

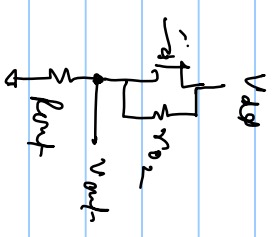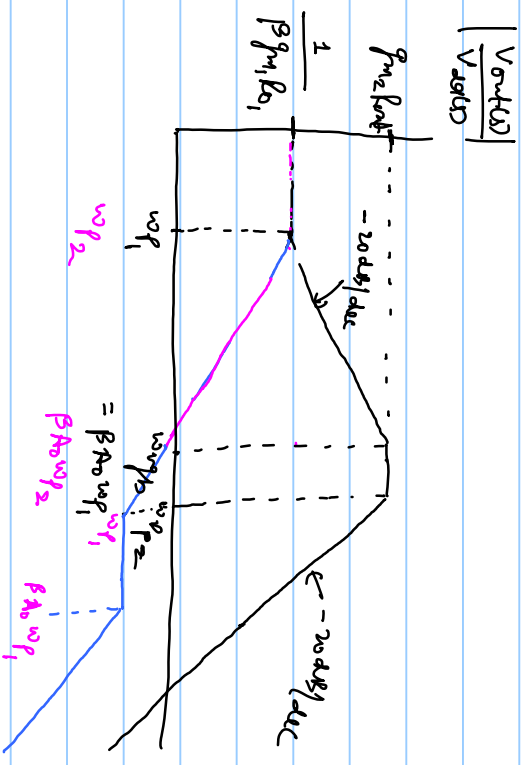

NMOS Regulator

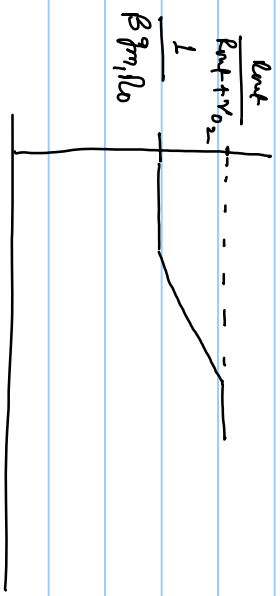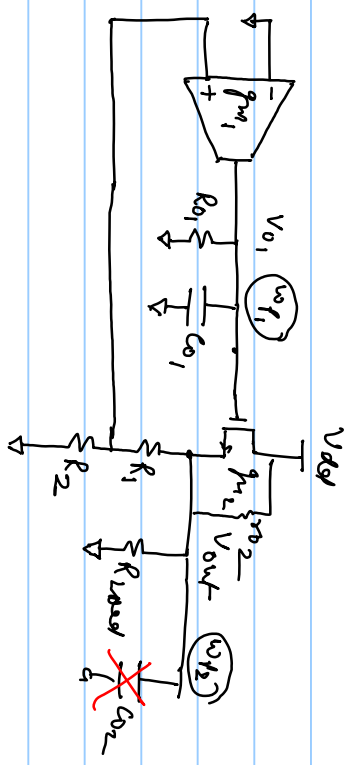

Low Transient & PSRR in NMOS regulator is improved compared to PMOS.

