

⇒ Integral or type-1 compensation slows down the loop due to lower wngl.

⇒ Poor transient response.

⇒ Only suitable for low bandwidth system.

(fixed load ON/OFF system)

For example: Battery charger → battery is charged with a constant current.
② LED light → requires constant current

Type-II compensation

also called PI (P → Proportional, I → Integral)

Integral → $\frac{k_i}{s}$


Proportional → k_p


$$H_{\text{comp-II}} = k_p + \frac{k_i}{s} \quad \text{type-I (H}_{\text{comp-I}})$$

$$= \frac{k_p s + k_i}{s} = \frac{k_i}{s} \left(1 + \frac{k_p}{k_i} s \right)$$

$$= \frac{k_i}{s} \left(1 + \beta / \omega_z \right)$$

$$\omega_z = \frac{k_i}{k_p}$$

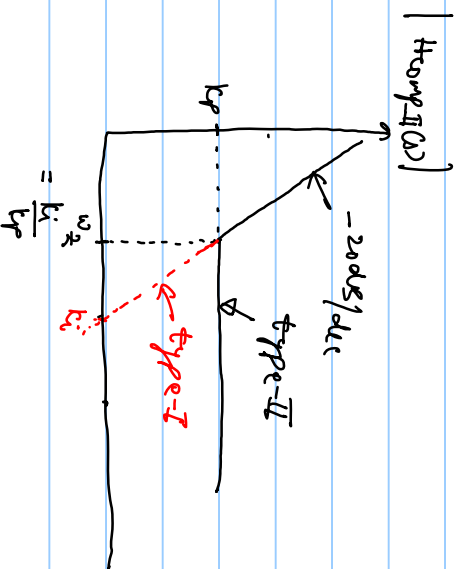


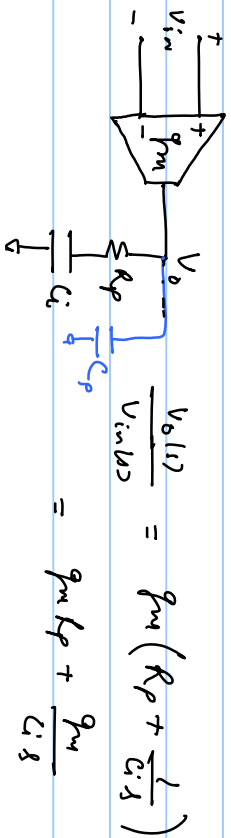


$\left[\text{H}_{\text{comp-II}}(s) \right]$

$$k_p = g_m R_p$$

$$k_i = \frac{g_m}{C_i}$$
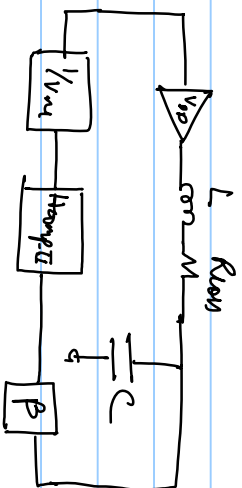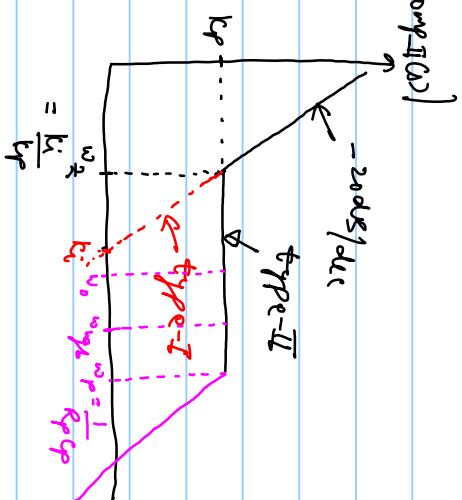
$$\omega_x = \frac{g_m}{C_i} \times \frac{1}{g_m R_p} = \frac{1}{R_p C_i}$$



$$H_{LCL}(s) = \beta \frac{V_d(s)}{V_{in}} \text{H}_{\text{comp-II}}(s) \text{H}_{LC}(s)$$

$$= \beta \frac{V_{od}}{V_{in}} \frac{k_i}{s} (1 + k_p s) \left(\frac{1/LC}{s^2 + \frac{R_{ov}}{L}s + 1/LC} \right)$$

$$\omega_0 = \frac{1}{R_{ov}} \sqrt{\frac{L}{C}}$$


$$\frac{\omega_0}{\omega_0} = \frac{1/\sqrt{Cq}}{\frac{1}{R_{ov}} \sqrt{L/q}} = \frac{R_{ov}}{L}$$

$L(s)$ has 3-poles and 1-zero.

So system is unstable.

We need one more zero.

Add ESR with output cap C .

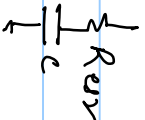

$$H_L(s) = \frac{1}{LC} (1 + R_{ov}Cs) \frac{1}{s^2 + \frac{R_{ov} + R_{ov} + R_{ov}}{L}s + 1/LC}$$

$$\omega_{\text{res}} = \frac{1}{R_{\text{eff}} C} \quad \text{should appear before resonance } \left(\frac{1}{\sqrt{LC}} \right)$$

$$L = 3.3 \mu\text{H}, \quad C = 10 \mu\text{F}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{3.3 \times 10^{-6} \times 10^{-5}}} = \frac{10^6}{\sqrt{33}} = 0.174 \text{ M rad/sec}$$

$$\frac{1}{R_{\text{eff}} C} = 0.174 \times 10^6 \text{ rad/sec}$$

$$R_{\text{eff}} = \frac{1}{C \times 0.174 \times 10^6} = 0.577 \Omega$$

$$\omega_{\text{z}} = \frac{1}{2} \omega_0 = \frac{1}{2} \sqrt{\frac{1}{LC}} \approx 0.09 \text{ M rad/sec}$$

$$\frac{1}{R_{\text{eff}} C} = 0.9 \text{ M rad/sec}$$

$$\text{output } p_m = 1 \text{ mW/V}$$

Gain of wgb without compensation

$$G_{0-wgb} = K_{uo} \left(\frac{\omega_0}{\omega_{wgb}} \right)^2$$

$$K_{uo} = \frac{V_{dip}}{V_{ue}} \beta$$

After compensation. gain at $\omega_{wgb} = 1$

$$G_{0-wgb} \times \rho_{m,lp} \left(\frac{\omega_{wgb}}{\omega_{z,erp}} \right) = 1$$

$$K_{uo} \left(\frac{\omega_0}{\omega_{wgb}} \right)^2 \times \rho_{m,lp} \left(\frac{\omega_{wgb}}{\omega_{z,erp}} \right) = 1$$

$$\omega_{z,erp} = \omega_0$$

$$\Rightarrow K_{uo} \left(\frac{\omega_0}{\omega_{wgb}} \right)^2 \times \rho_{m,lp} \left(\frac{\omega_{wgb}}{\omega_0} \right) = 1$$

$$K_{uo} \frac{\omega_0}{\omega_{wgb}} \times \rho_{m,lp} = 1$$

$$\rho_{lp} = \frac{\omega_{wgb}}{\omega_0 K_{uo} \rho_{m,lp}}$$

$$\omega_{\text{avg}} = \frac{2\pi F_{\text{avg}}}{10}$$

$$\omega_{\text{avg}} = 0.09 \text{ Mrad/ber} = \frac{1}{\text{epci}}$$

$$c_i = \frac{1}{\text{ep} \omega_{\text{avg}}}$$