


Feed Forward Line Compensation

$$L_G \propto \frac{V_{in}}{V_m} \text{ for opamp-RC compensator}$$

$$L_G \propto \beta \frac{V_{in}}{V_m} \text{ for gm-C compensator.}$$

$V_{in} \rightarrow$ line voltage



Phase

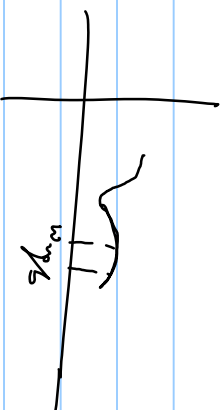

if $V_m \propto V_{in}$

then
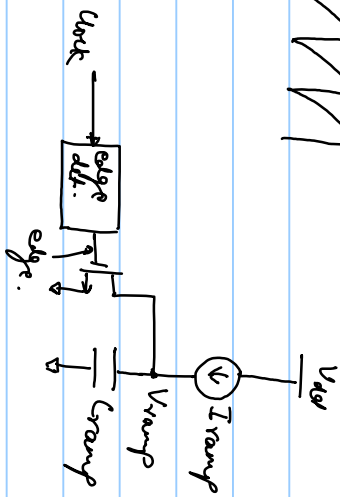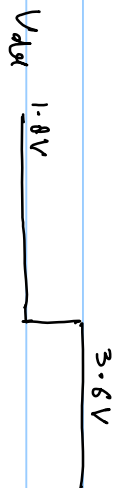
$$L_G \propto \beta \text{ for gm-C compensator.}$$




$$V_0 = D \cdot V_{in}$$

$$V_{in} = 1.8V, V_0 = 0.9V$$

$$D = 0.5$$

for $V_{in} = 3.6$,

$$D = 0.25$$

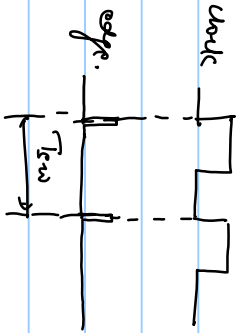

$$V_m = \frac{I_{ramp} \times T_{clk}}{C}$$



$$I_{ramp} = \frac{V_m}{R}$$

$$V_m = \frac{V_{in} \times T_{clk}}{R \cdot C}$$

$T_{clk}, R \& C \rightarrow$ constant

$$V_m \propto V_{in}$$

Improves line transient as well.

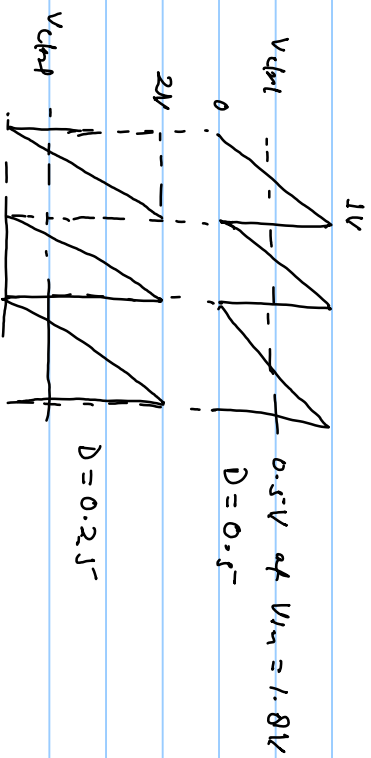
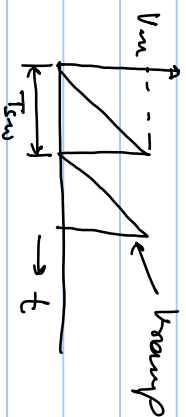




For $G_m - C$ compensation

$$L_d \approx \frac{V_{in}}{V_{in}} \beta = \frac{V_{in}}{V_{in}} \times \frac{V_{ref}}{V_o} = \frac{V_{ref}}{V_{in}} \left(\frac{1}{D} \right)$$


if V_{ref} & V_{in} are constant


then $L_d \propto \frac{1}{D}$

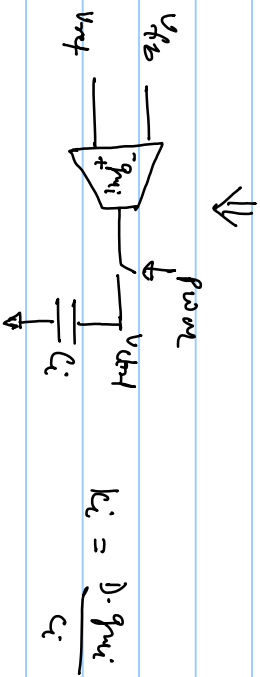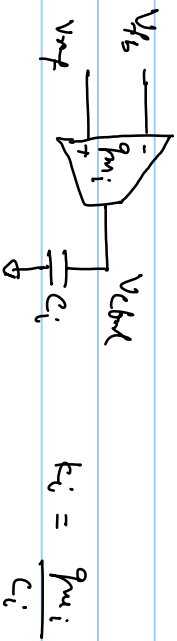

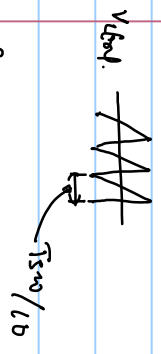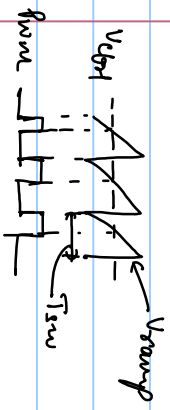

form of low frequency with same D.

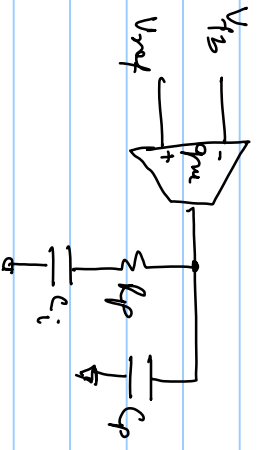

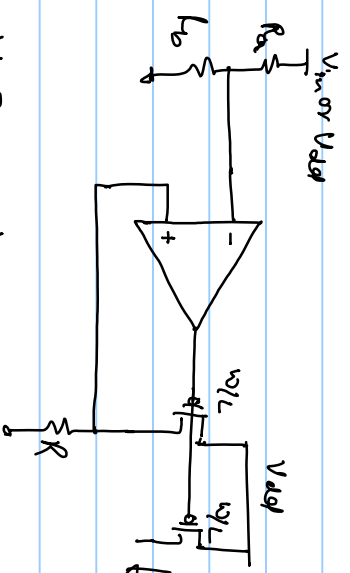

V-I converter.

$$V_{out} = \frac{V_{in}}{R} \times \left(\frac{R_2}{R_1 + R_2} \right)$$