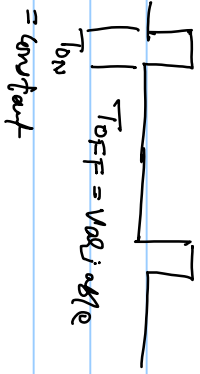



Constant-ON time control


$$V_o = D \cdot V_{dd}$$




$$D = \frac{T_{ON}}{T_{ON} + T_{OFF}} = \frac{T_{ON}}{T_{SW}}$$


$T_{SW} \rightarrow$  Varying.

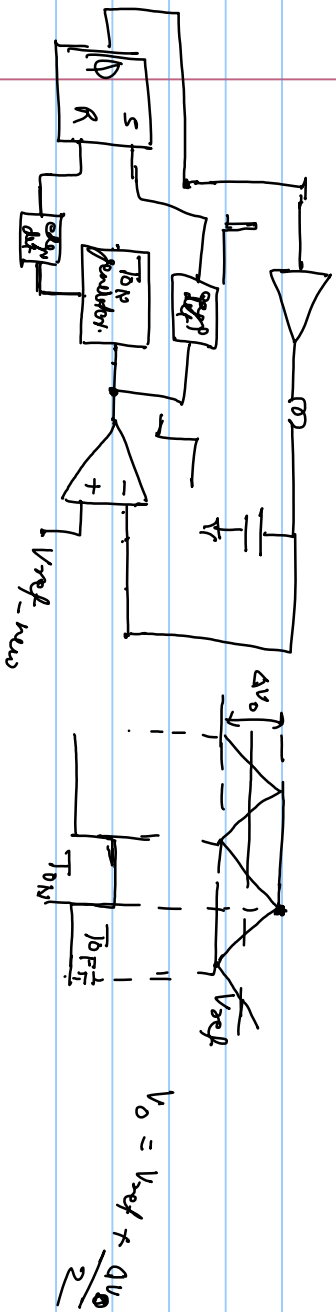

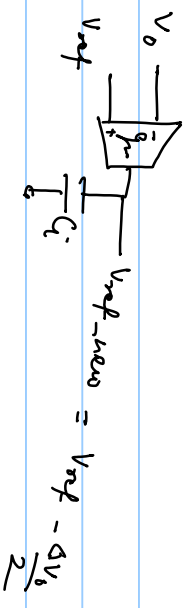

Digital TON generator.

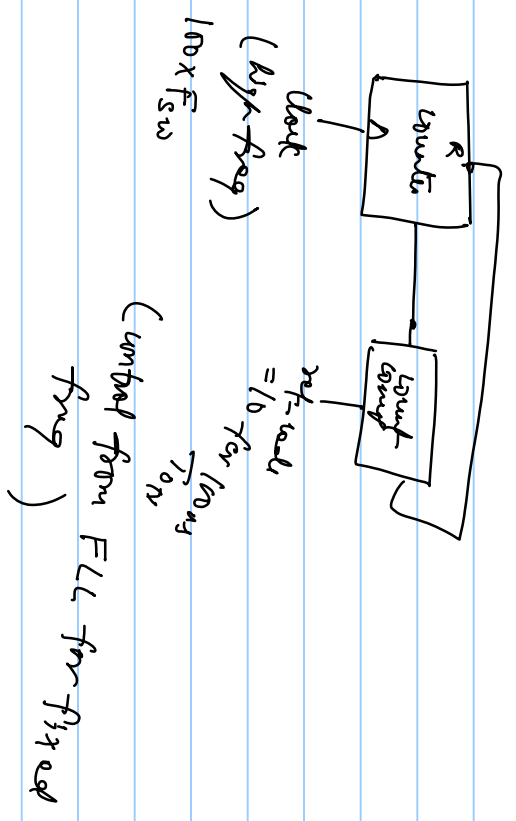

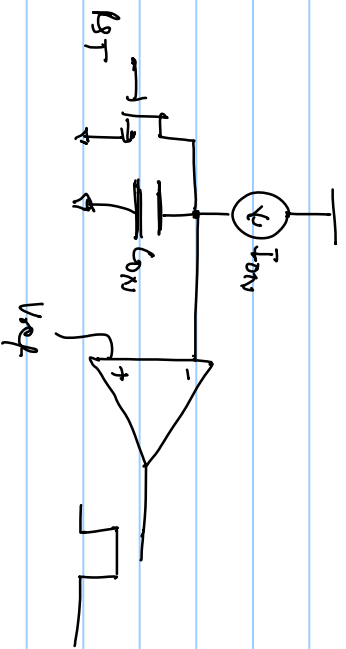


$$I = C \frac{dV}{dt}$$

$$dt = T_{ON}, \quad qV = V_{ref}$$

$$T_{ON} = \frac{C_{ON}}{I_{GT}} \times V_{ref}$$

For Fixed freq. FLL can be used to control  $T_{ON}$  or  $V_{ref}$ .

### Boost Converter

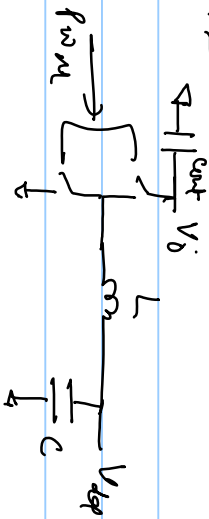

$$V_0 = D \cdot V_{out}$$

$$V_0 \leq V_{in}$$

$$V_0 \geq V_{in}$$

$$V_0 = \frac{V_{in}}{D}$$


$$V_0 \propto \frac{1}{D}$$

to get

$$V_0 \propto D$$

$$V_0 \propto \frac{1}{1-D}$$

$$V_o = V_{dd} / (1-D)$$

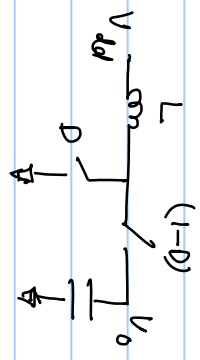

During ON Time voltage across inductor  
 Volt-second


$$V_{dd} \times T_{on}$$

During OFF time

$$(V_{dd} - V_o) \times T_{off}$$

$$V_{dd} \times T_{on} + (V_{dd} - V_o) \times T_{off} = 0$$
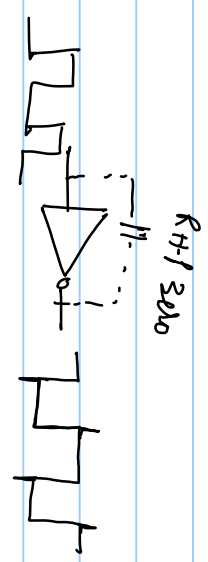
$$V_{dd} \times D \times T_{sw} + (V_{dd} - V_o) \times (1-D) \times T_{sw} = 0$$



$$D \cdot V_{old} = V_0(1-D) - V_{old}(1-D)$$

$$D \cdot V_{old} = V_0(1-D) - V_{old} + D \cdot V_{old}$$

$$V_0 = \frac{V_{old}}{1-D}$$

For ideal conversion


$$P_{out} = P_{in}$$

$$V_{out} \cdot I_{out} = V_{old} \cdot I_{old}$$


$$\frac{V_{old}}{1-D} \cdot I_{out} = V_{old} \cdot I_{old}$$

$\Rightarrow$

$$I_{old} = \frac{I_{out}}{1-D}$$

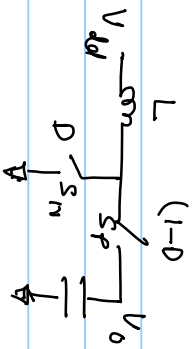

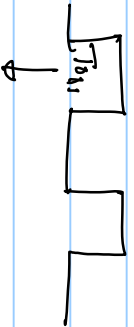R.H.P zero due to discontinuity in  $S_f$  switch



inductor is charging

but  $V_o$  is discharging  $\rightarrow$  cause R.H.P zero.

$$V_o^2 = \frac{(1-D)^2 R_{load}}{L}$$

$$L = 1 \mu H, \quad R_{load} = 5 \Omega$$

$$D = 0.5 \quad (V_{dd} = 2.5V, V_o = 2.5V)$$

$$v_2 = \frac{(0.5)^2 \cdot 5}{1.41} = 1.25 \text{ m/s} / \text{sec}$$

$$f_2 = \frac{1.25 \text{ m}}{2\pi} = 250 \text{ kHz}$$