
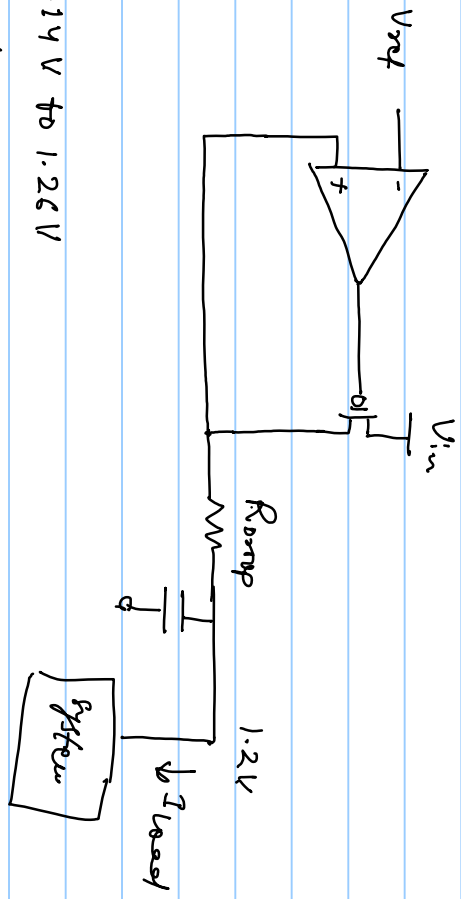



Drop Compensation

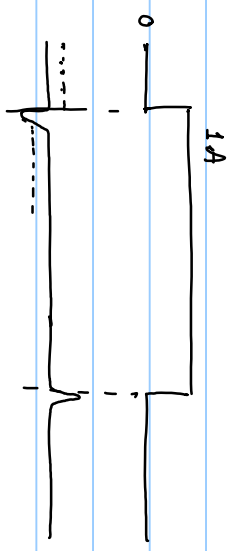

$V_{out} = 1.14V$ to $1.26V$

$I_{load} = 0$ to $1A$




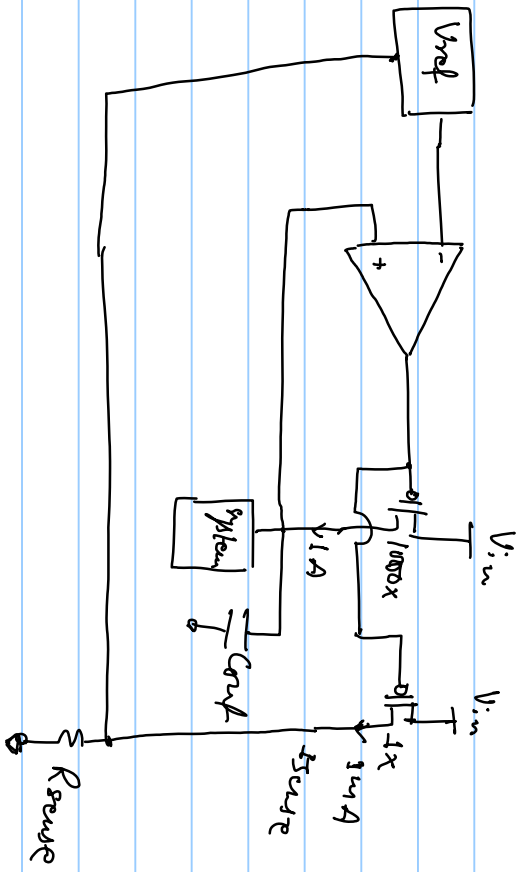

Current Regulator

Applications

1. Battery charger

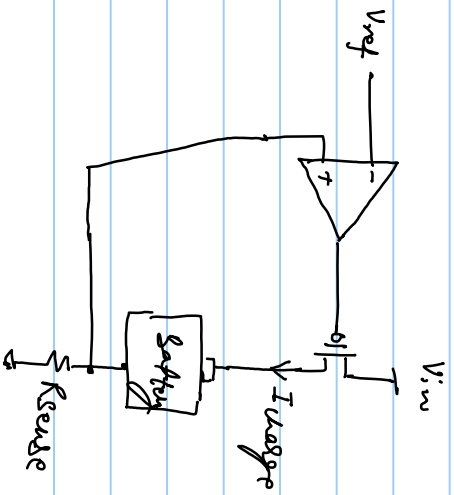


$$I_{charge} = \frac{V_{ref}}{R_{sense}}$$

$$R_1 = R_2$$

$$V_{ref} = 1V$$

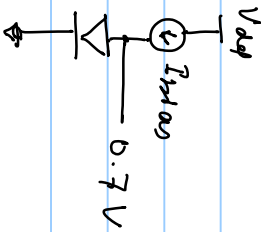if V_{DD} is not constant then
 V_{ref} is not constant.




V_{be} is not constant across temperature.

We need reference to be constant across temperature.


Bandgap Voltage Reference

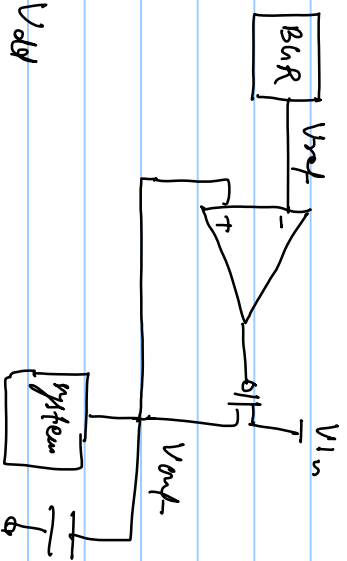used to provide constant voltage reference across Process, Voltage & Temperature.




$$V_{ref} = \frac{R_2}{R_1 + R_2} \cdot V_{dd}$$
$$V_{dd} = 2V$$
$$V_{ref} = 1V$$

2. LED driver

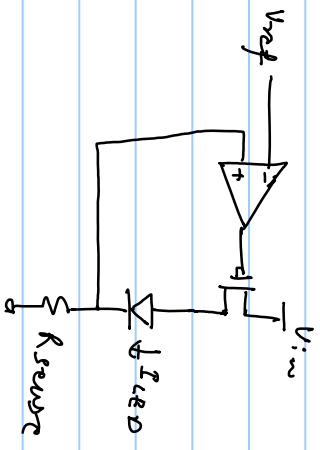

$$I_{LED} = \frac{V_{ref}}{R_{sense}}$$

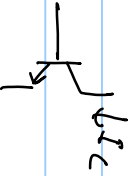

$$I_C = I_S e^{V_{BE}/V_T}$$

$$V_{BE} = V_T \ln \frac{I_C}{I_S}$$


$$V_T = kT/q$$

$$\frac{\partial V_T}{\partial T} = \frac{k}{q} \cdot k = 1.38 \times 10^{-23} \text{ J/K}$$
$$q = 1.61 \times 10^{-19} \text{ C}$$

$$\frac{\partial V_T}{\partial T} = 86 \text{ mV/K}$$

$$V_T \text{ at room temp.} = 86 \text{ mV} \times 300$$
$$\approx 26 \text{ mV}$$

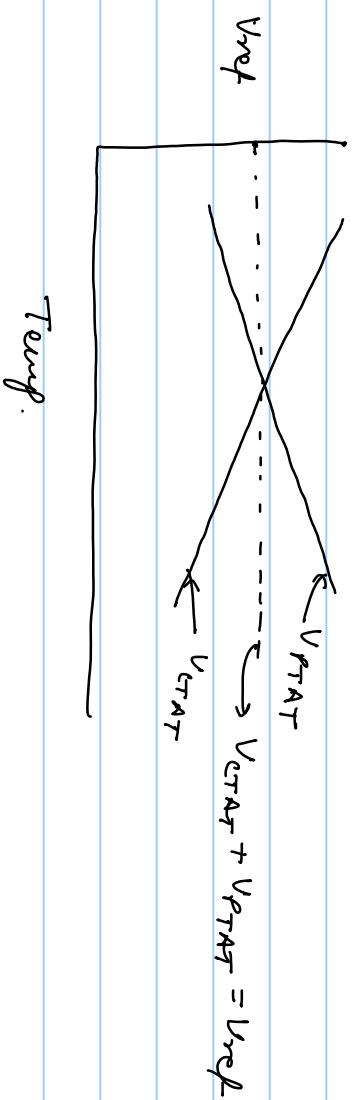$V_T \rightarrow$ proportional to temperature




$$\frac{\partial V_{rel}}{\partial T} = 0 = \frac{\partial V_{PTAT}}{\partial T} + \frac{\partial V_{GTAT}}{\partial T} = 0$$


$$\Rightarrow \frac{\partial V_{PTAT}}{\partial T} = - \frac{\partial V_{GTAT}}{\partial T}$$

$$V_{be} = V_T \ln \frac{I_C}{I_S}$$
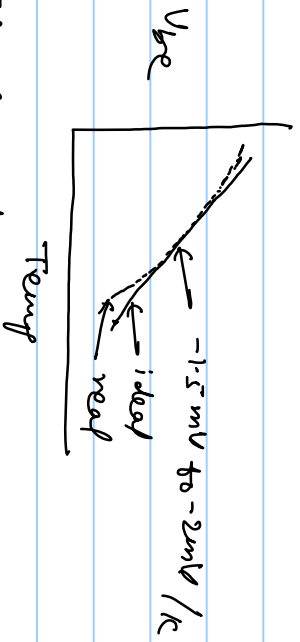
$$\frac{I_C}{I_S} \rightarrow -ve \text{ temp. coeff}$$



PTAT Generation

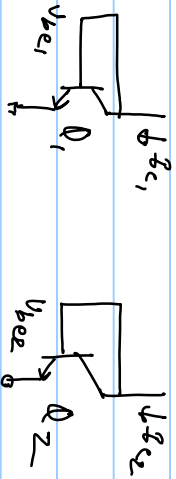

$$V_{be1} = V_T \ln \frac{I_{C1}}{I_{S1}}, \quad V_{RC2} = V_T \ln \frac{I_{C2}}{I_{S2}}$$

$$V_{be1} - V_{be2} = V_T \left[\ln \frac{I_{c1}}{I_{s1}} \times \frac{I_{s2}}{I_{c2}} \right]$$

$$\Delta V_{be} = V_T \left[\ln \frac{I_{c1}}{I_{s1}} \times \frac{I_{s2}}{I_{c2}} \right]$$

Case-1
 $I_{c1} \neq I_{c2}$

$$I_{s1} = I_{s2} \Rightarrow Q_1 = Q_2 \text{ (same size)}$$

$$\Delta V_{be} = V_T \ln \left(\frac{I_{c1}}{I_{c2}} \right)$$

$$I_{c1} = m I_{c2}$$

$$\Delta V_{be} = V_T \ln(m)$$

Case-2
 $I_{c1} = I_{c2}$

$$Q_1 \neq Q_2$$

$$Q_2 = m Q_1 \Rightarrow \Delta V_{be} = V_T \ln(m)$$