



## Problem 2 : Bandpass Filter Design

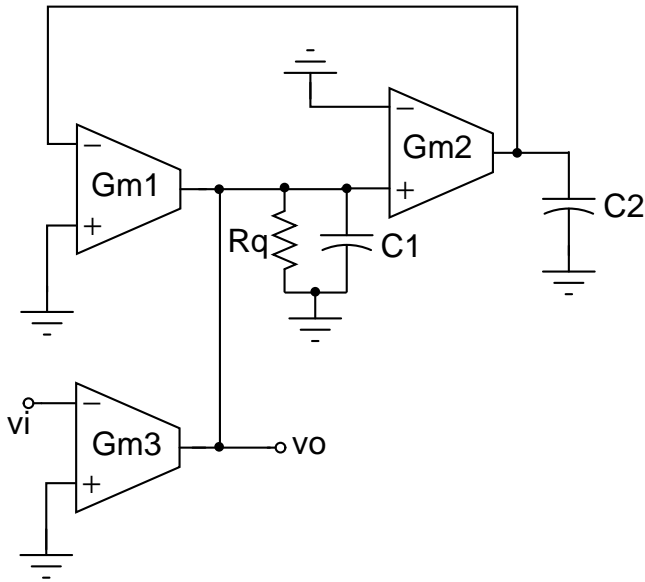


Figure 2: Second order bandpass filter.

Consider the second order bandpass filter shown in Figure 2. Find the component values of a filter that maximizes dynamic range under the following constraints

- $\omega_p = 2\pi \cdot 10^6 \text{ rad s}^{-1}$ ,  $Q_p = 20$ .
- The filter gain at  $\omega_p$  should be 1.
- The input range of the transconductors is  $-0.5$  to  $0.5$  volts.
- The absolute value of the filter input never exceeds  $0.5$  V.
- $C1 + C2 \leq 20 \text{ pF}$ .

Assume that all transconductors have an input voltage noise spectral density given by  $\overline{v_n^2} = (4kT/G_M)$ . Simulate the filter in SPICE and plot the output noise spectral density of the filter. What is the RMS output noise ?

Repeat the entire exercise for a filter with a  $Q_p = 40$ , and all other constraints unchanged. What is the RMS output noise now ?